

---

## Introduction to Frequency-Selective Circuits

---

### Assessment Problems

AP 14.1

$$f_c = 8 \text{ kHz}, \quad \omega_c = 2\pi f_c = 16\pi \text{ krad/s}$$

$$\omega_c = \frac{1}{RC}; \quad R = 10 \text{ k}\Omega;$$

$$\therefore C = \frac{1}{\omega_c R} = \frac{1}{(16\pi \times 10^3)(10^4)} = 1.99 \text{ nF}$$

AP 14.2 [a]  $\omega_c = 2\pi f_c = 2\pi(2000) = 4\pi \text{ krad/s}$

$$L = \frac{R}{\omega_c} = \frac{5000}{4000\pi} = 0.40 \text{ H}$$

$$[b] H(j\omega) = \frac{\omega_c}{\omega_c + j\omega} = \frac{4000\pi}{4000\pi + j\omega}$$

$$\text{When } \omega = 2\pi f = 2\pi(50,000) = 100,000\pi \text{ rad/s}$$

$$H(j100,000\pi) = \frac{4000\pi}{4000\pi + j100,000\pi} = \frac{1}{1 + j25} = 0.04 \angle 87.71^\circ$$

$$\therefore |H(j100,000\pi)| = 0.04$$

$$[c] \therefore \theta(100,000\pi) = -87.71^\circ$$

AP 14.3

$$\omega_c = \frac{R}{L} = \frac{5000}{3.5 \times 10^{-3}} = 1.43 \text{ Mrad/s}$$

AP 14.4 [a]  $\omega_c = \frac{1}{RC} = \frac{10^6}{R} = \frac{10^6}{100} = 10 \text{ krad/s}$

[b]  $\omega_c = \frac{10^6}{5000} = 200 \text{ rad/s}$

[c]  $\omega_c = \frac{10^6}{3 \times 10^4} = 33.33 \text{ rad/s}$

AP 14.5 Let  $Z$  represent the parallel combination of  $(1/SC)$  and  $R_L$ . Then

$$Z = \frac{R_L}{(R_L C s + 1)}$$

$$\begin{aligned} \text{Thus } H(s) &= \frac{Z}{R + Z} = \frac{R_L}{R(R_L C s + 1) + R_L} \\ &= \frac{(1/RC)}{s + \frac{R+R_L}{R_L} \left(\frac{1}{RC}\right)} = \frac{(1/RC)}{s + \frac{1}{K} \left(\frac{1}{RC}\right)} \end{aligned}$$

where  $K = \frac{R_L}{R + R_L}$

AP 14.6

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = \frac{1}{(24\pi \times 10^3)^2 (0.1 \times 10^{-6})} = 1.76 \text{ mH}$$

$$Q = \frac{\omega_o}{\beta} = \frac{\omega_o}{R/L} \quad \text{so} \quad R = \frac{\omega_o L}{Q} = \frac{(24\pi \times 10^3)(1.76 \times 10^{-3})}{6} = 22.10 \Omega$$

AP 14.7

$$\omega_o = 2\pi(2000) = 4000\pi \text{ rad/s};$$

$$\beta = 2\pi(500) = 1000\pi \text{ rad/s}; \quad R = 250 \Omega$$

$$\beta = \frac{1}{RC} \quad \text{so} \quad C = \frac{1}{\beta R} = \frac{1}{(1000\pi)(250)} = 1.27 \mu\text{F}$$

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = \frac{10^6}{(4000\pi)^2 (1.27)} = 4.97 \text{ mH}$$

AP 14.8

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = \frac{1}{(10^4\pi)^2 (0.2 \times 10^{-6})} = 5.07 \text{ mH}$$

$$\beta = \frac{1}{RC} \quad \text{so} \quad R = \frac{1}{\beta C} = \frac{1}{400\pi(0.2 \times 10^{-6})} = 3.98 \text{ k}\Omega$$

AP 14.9

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = \frac{1}{(400\pi)^2(0.2 \times 10^{-6})} = 31.66 \text{ mH}$$

$$Q = \frac{f_o}{\beta} = \frac{5 \times 10^3}{200} = 25 = \omega_o RC$$

$$\therefore R = \frac{Q}{\omega_o C} = \frac{25}{(400\pi)(0.2 \times 10^{-6})} = 9.95 \text{ k}\Omega$$

AP 14.10

$$\omega_o = 8000\pi \text{ rad/s}$$

$$C = 500 \text{ nF}$$

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = 3.17 \text{ mH}$$

$$Q = \frac{\omega_o}{\beta} = \frac{\omega_o L}{R} = \frac{1}{\omega_o CR}$$

$$\therefore R = \frac{1}{\omega_o C Q} = \frac{1}{(8000\pi)(500)(5 \times 10^{-9})} = 15.92 \text{ }\Omega$$

AP 14.11

$$\omega_o = 2\pi f_o = 2\pi(20,000) = 40\pi \text{ krad/s}; \quad R = 100 \text{ }\Omega; \quad Q = 5$$

$$Q = \frac{\omega_o}{\beta} = \frac{\omega_o}{(R/L)} \quad \text{so} \quad L = \frac{QR}{\omega_o} = \frac{5(100)}{(40\pi \times 10^3)} = 3.98 \text{ mH}$$

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad C = \frac{1}{\omega_o^2 L} = \frac{1}{(40\pi \times 10^3)^2(3.98 \times 10^{-3})} = 15.92 \text{ nF}$$

## Problems

$$\text{P 14.1 [a]} \quad \omega_c = \frac{R}{L} = \frac{1.5 \times 10^3}{0.25} = 6000 \text{ rad/s}$$

$$\therefore f_c = \frac{6000}{2\pi} = 954.93 \text{ Hz}$$

$$\text{[b]} \quad H(s) = \frac{R/L}{s + R/L} = \frac{6000}{s + 6000}$$

$$H(j\omega) = \frac{6000}{6000 + j\omega}$$

$$H(j\omega_c) = \frac{6000}{6000 + j6000} = 0.7071 \angle -45^\circ$$

$$H(j0.3\omega_c) = \frac{6000}{6000 + j1800} = 0.9578 \angle -16.70^\circ$$

$$H(j3\omega_c) = \frac{6000}{6000 + j18,000} = 0.3162 \angle -71.57^\circ$$

$$\text{[c]} \quad v_o(\omega_c) = 35.36 \cos(6000t - 45^\circ) \text{ V}$$

$$v_o(0.3\omega_c) = 47.89 \cos(1800t - 16.70^\circ) \text{ V}$$

$$v_o(3\omega_c) = 15.81 \cos(18,000t - 71.57^\circ) \text{ V}$$

$$\text{P 14.2 [a]} \quad \frac{R}{L} = 5000\pi \text{ rad/s}$$

$$R = (0.025)(5000)(\pi) = 392.70 \Omega$$

$$\text{[b]} \quad R_e = 392.70 \parallel 750 = 257.74 \Omega$$

$$\omega_{\text{loaded}} = \frac{R_e}{L} = 10,309.78 \text{ rad/s}$$

$$\therefore f_{\text{loaded}} = 1640.85 \text{ Hz}$$

$$\text{P 14.3 [a]} \quad H(s) = \frac{V_o}{V_i} = \frac{R}{sL + R + R_l} = \frac{(R/L)}{s + (R + R_l)/L}$$

$$\text{[b]} \quad H(j\omega) = \frac{(R/L)}{\left(\frac{R+R_l}{L}\right) + j\omega}$$

$$|H(j\omega)| = \frac{(R/L)}{\sqrt{\left(\frac{R+R_l}{L}\right)^2 + \omega^2}}$$

$$|H(j\omega)|_{\text{max}} \text{ occurs when } \omega = 0$$

$$[\text{c}] \quad |H(j\omega)|_{\max} = \frac{R}{R + R_l}$$

$$[\text{d}] \quad |H(j\omega_c)| = \frac{R}{\sqrt{2}(R + R_l)} = \frac{R/L}{\sqrt{\left(\frac{R+R_l}{L}\right)^2 + \omega_c^2}}$$

$$\therefore \omega_c^2 = \left(\frac{R + R_l}{L}\right)^2; \quad \therefore \omega_c = (R + R_l)/L$$

$$[\text{e}] \quad \omega_c = \frac{1575}{0.25} = 6300 \text{ rad/s}$$

$$H(j\omega) = \frac{6000}{6300 + j\omega}$$

$$H(j0) = 0.9524$$

$$H(j6300) = \frac{0.9524}{\sqrt{2}} \angle -45^\circ = 0.6734 \angle -45^\circ$$

$$H(j1890) = \frac{6000}{6300 + j1890} = 0.9122 \angle -16.70^\circ$$

$$H(j18,900) = \frac{6000}{6300 + j18,900} = 0.3012 \angle -71.57^\circ$$

$$\text{P 14.4} \quad [\text{a}] \quad \omega_c = \frac{10^9}{80 \times 10^3} = 12,500 \text{ rad/s}$$

$$f_c = 1989.44 \text{ Hz}$$

$$[\text{b}] \quad H(j\omega) = \frac{12,500}{12,500 + j\omega}$$

$$\therefore H(j\omega_c) = 0.7071 \angle -45^\circ$$

$$H(j0.2\omega_c) = \frac{12,500}{12,500 + j2500} = 0.9806 \angle -11.31^\circ$$

$$H(j8\omega_c) = \frac{12,500}{12,500 + j100,000} = 0.1240 \angle -82.87^\circ$$

$$[\text{c}] \quad v_o(\omega_c) = 339.41 \cos(12,500t - 45^\circ) \text{ mV}$$

$$v_o(0.2\omega_c) = 470.68 \cos(2500t - 11.31^\circ) \text{ mV}$$

$$v_o(8\omega_c) = 59.54 \cos(100,000t - 82.87^\circ) \text{ mV}$$

P 14.5 [a] Let  $Z = \frac{R_L(1/SC)}{R_L + 1/SC} = \frac{R_L}{R_LCs + 1}$

$$\begin{aligned}\text{Then } H(s) &= \frac{Z}{Z + R} \\ &= \frac{R_L}{RR_LCs + R + R_L} \\ &= \frac{(1/RC)}{s + \left(\frac{R + R_L}{RR_LC}\right)}\end{aligned}$$

[b]  $|H(j\omega)| = \frac{(1/RC)}{\sqrt{\omega^2 + [(R + R_L)/RR_LC]^2}}$

$|H(j\omega)|$  is maximum at  $\omega = 0$

[c]  $|H(j\omega)|_{\max} = \frac{R_L}{R + R_L}$

[d]  $|H(j\omega_c)| = \frac{R_L}{\sqrt{2}(R + R_L)} = \frac{(1/RC)}{\sqrt{\omega_c^2 + [(R + R_L)/RR_LC]^2}}$

$$\therefore \omega_c = \frac{R + R_L}{RR_LC} = \frac{1}{RC} (1 + (R/R_L))$$

[e]  $\omega_c = 12,500 \left(1 + \frac{20}{300}\right) = 13,333.33 \text{ rad/s}$

$$H(j0) = \frac{300}{320} = 0.9375$$

$$H(j\omega_c) = \frac{12,500}{13,333.33 + j13,333.33} = 0.6629 / -45^\circ$$

$$H(j0.2\omega_c) = \frac{12,500}{13,333.33 + j2666.67} = 0.9193 / -11.31^\circ$$

$$H(j8\omega_c) = \frac{12,500}{13,333.33 + j106,666.67} = 0.1163 / -82.87^\circ$$

P 14.6 [a]  $f_c = \frac{160}{2\pi} \times 10^3 = 25.46 \text{ kHz}$

[b]  $\frac{1}{RC} = 160 \times 10^3$

$$R = \frac{1}{(160 \times 10^3)(25 \times 10^{-9})} = 250 \Omega$$

$$[c] \quad \omega_c = \frac{1}{RC} \left( 1 + \frac{R}{R_L} \right)$$

$$\therefore \frac{R}{R_L} = 0.08 \quad \therefore R_L = 12.5R = 3125 \Omega$$


$$[d] \quad H(j0) = \frac{R_L}{R + R_L} = \frac{3125}{3375} = 0.9259$$

$$H(j0) = 0.9259$$

P 14.7 [a]  $\omega_c = 2\pi(500) = 3141.59 \text{ rad/s}$

$$[b] \quad \omega_c = \frac{1}{RC} \quad \text{so} \quad R = \frac{1}{\omega_c C} = \frac{1}{(3141.59)(50 \times 10^{-9})} = 6366 \Omega$$

[c]

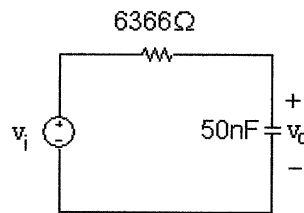

$$[d] \quad H(s) = \frac{V_o}{V_i} = \frac{1/sC}{R + 1/sC} = \frac{1/RC}{s + 1/RC} = \frac{3141.59}{s + 3141.59}$$

$$[e] \quad H(s) = \frac{V_o}{V_i} = \frac{(1/sC) \parallel R_L}{R + (1/sC) \parallel R_L} = \frac{1/RC}{s + \left( \frac{R + R_L}{R_L} \right) 1/RC} = \frac{3141.59}{s + 2(3141.59)}$$

$$[f] \quad \omega_c = 2(3141.59) = 6283.19 \text{ rad/s}$$

$$[g] \quad H(0) = 1/2$$

P 14.8 [a]  $Z_L = j\omega L = j0L = 0$  so it is a short circuit

$$\text{At } \omega = 0, \quad V_o = V_i$$

[b]  $Z_L = j\omega L = j\infty L = \infty$  so it is an open circuit

$$\text{At } \omega = \infty, \quad V_o = 0$$

[c] This is a low pass filter, with a gain of 1 at low frequencies and a gain of 0 at high frequencies.

$$[d] \quad H(s) = \frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{R/L}{s + R/L}$$

$$[e] \quad \omega_c = \frac{R}{L} = \frac{1000}{0.02} = 50 \text{ krad/s}$$

P 14.9 [a]  $H(s) = \frac{V_o}{V_i} = \frac{R \parallel R_L}{R \parallel R_L + sL} = \frac{\frac{R}{L} \left( \frac{R_L}{R + R_L} \right)}{s + \frac{R}{L} \left( \frac{R_L}{R + R_L} \right)}$

[b]  $\omega_{c(UL)} = \frac{R}{L}$ ;  $\omega_{c(L)} = \frac{R}{L} \left( \frac{R_L}{R + R_L} \right)$  so the cutoff frequencies are different

$H(0)_{(UL)} = 1$ ;  $H(0)_{(L)} = 1$  so the passband gains are the same

[c]  $\omega_{c(UL)} = 50,000$  rad/s

$\omega_{c(L)} = 50,000 - 0.1(50,000) = 45,000$  rad/s

$45,000 = \frac{1000}{0.02} \left( \frac{R_L}{1000 + R_L} \right)$  so  $\frac{R_L}{1000 + R_L} = 0.9$

$\therefore 0.1R_L = 900$  so  $R_L \geq 9 \text{ k}\Omega$

P 14.10 [a]  $\frac{1}{RC} = \frac{10^9}{(40 \times 10^3)(2.5)} = 10 \text{ krad/s}$

$f_c = \frac{5000}{\pi} = 1591.55 \text{ Hz}$

[b]  $H(j\omega) = \frac{j\omega}{10,000 + j\omega}$

$H(j\omega_c) = \frac{j10,000}{10,000 + j10,000} = 0.7071/\underline{45^\circ}$

$H(j0.1\omega_c) = \frac{j1000}{10,000 + j1000} = 0.0995/\underline{84.29^\circ}$

$H(j10\omega_c) = \frac{j100,000}{10,000 + j100,000} = 0.9950/\underline{5.71^\circ}$

[c]  $v_o(\omega_c) = 565.69 \cos(10,000t + 45^\circ) \text{ mV}$

$v_o(0.1\omega_c) = 79.60 \cos(1000t + 84.29^\circ) \text{ mV}$

$v_o(10\omega_c) = 796.03 \cos(100,000t + 5.71^\circ) \text{ mV}$

P 14.11 [a]  $H(s) = \frac{V_o}{V_i} = \frac{R}{R + R_c + (1/sC)}$

$$= \frac{R}{R + R_c} \cdot \frac{s}{[s + (1/(R + R_c)C)]}$$

[b]  $H(j\omega) = \frac{R}{R + R_c} \cdot \frac{j\omega}{j\omega + (1/(R + R_c)C)}$

$|H(j\omega)| = \frac{R}{R + R_c} \cdot \frac{\omega}{\sqrt{\omega^2 + \frac{1}{(R + R_c)^2 C^2}}}$

The magnitude will be maximum when  $\omega = \infty$



$$[c] |H(j\omega)|_{\max} = \frac{R}{R + R_c}$$

$$[d] |H(j\omega_c)| = \frac{R\omega_c}{(R + R_c)\sqrt{\omega_c^2 + [1/(R + R_c)C]^2}}$$

$$\therefore |H(j\omega)| = \frac{R}{\sqrt{2}(R + R_c)} \quad \text{when}$$

$$\therefore \omega_c^2 = \frac{1}{(R + R_c)^2 C^2}$$

$$\text{or } \omega_c = \frac{1}{(R + R_c)C}$$

$$[e] \omega_c = \frac{1}{(R + R_c)C} = \frac{10^9}{(50 \times 10^3)(2.5)} = 8000 \text{ rad/s}$$

$$H(j\omega_c) = \left(\frac{40}{50}\right) \frac{j8000}{8000 + j8000} = 0.5657/\underline{45^\circ}$$

$$H(j0.1\omega_c) = \frac{(0.8)j800}{8000 + j800} = 0.0796/\underline{84.29^\circ}$$

$$H(j10\omega_c) = \frac{(0.8)j80,000}{8000 + j80,000} = 0.7960/\underline{5.71^\circ}$$

$$P 14.12 [a] \frac{1}{RC} = 2\pi(800) = 1600\pi \text{ rad/s}$$

$$\therefore R = \frac{10^9}{(1600\pi)(20)} = 9.95 \text{ k}\Omega$$

$$[b] R_e = 9.95 \parallel 68 = 8.68 \text{ k}\Omega$$

$$\omega_c = \frac{10^9}{(8.68)(10^3)(20)} = 5761.84 \text{ rad/s}$$

$$f_c = \frac{5761.84}{2\pi} = 917.03 \text{ Hz}$$

$$P 14.13 [a] R = \omega_c L = (160 \times 10^3)(25 \times 10^{-3}) = 4000 \Omega = 4 \text{ k}\Omega$$

$$[b] \frac{R}{L} \cdot \frac{R_L}{R + R_L} = 150,000$$


$$\therefore \frac{R_L}{R + R_L} = \frac{150,000}{160,000} = 0.9375$$

$$\therefore 0.0625R_L = (0.9375)(4000); \quad \therefore R_L = 60 \text{ k}\Omega$$

P 14.14 [a]  $\omega_c = 2\pi(300) = 1884.96 \text{ rad/s}$

[b]  $\omega_c = \frac{1}{RC}$  so  $R = \frac{1}{\omega_c C} = \frac{1}{(1884.96)(100 \times 10^{-9})} = 5305 \Omega$

[c]

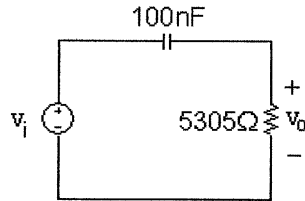

[d]  $H(s) = \frac{V_o}{V_i} = \frac{R}{R + 1/sC} = \frac{s}{s + 1/RC} = \frac{s}{s + 1884.96}$

[e]  $H(s) = \frac{V_o}{V_i} = \frac{R \parallel R_L}{R \parallel R_L + (1/sC)} = \frac{s}{s + \left(\frac{R + R_L}{R_L}\right) 1/RC} = \frac{s}{s + 2(1884.96)}$

[f]  $\omega_c = 2(1884.96) = 3769.91 \text{ rad/s}$

[g]  $H(\infty) = 1$

P 14.15 [a] For  $\omega = 0$ , the inductor behaves as a short circuit, so  $V_o = 0$ .

For  $\omega = \infty$ , the inductor behaves as an open circuit, so  $V_o = V_i$ .

Thus, the circuit is a high pass filter.

[b]  $H(s) = \frac{sL}{R + sL} = \frac{s}{s + R/L} = \frac{s}{s + 20,000}$

[c]  $\omega_c = \frac{R}{L} = 20,000 \text{ rad/s}$

[d]  $|H(jR/L)| = \left| \frac{jR/L}{jR/L + R/L} \right| = \left| \frac{j}{j + 1} \right| = \frac{1}{\sqrt{2}}$

P 14.16 [a]  $H(s) = \frac{V_o}{V_i} = \frac{R_L \parallel sL}{R + R_L \parallel sL} = \frac{s \left( \frac{R_L}{R + R_L} \right)}{s + \frac{R}{L} \left( \frac{R_L}{R + R_L} \right)}$

$$= \frac{\frac{1}{2}s}{s + \frac{1}{2}(20,000)}$$

[b]  $\omega_c = \frac{R}{L} \left( \frac{R_L}{R + R_L} \right) = \frac{1}{2}(20,000) = 10,000 \text{ rad/s}$

[c]  $\omega_{c(L)} = \frac{1}{2}\omega_{c(UL)}$

[d] The gain in the passband is also reduced by a factor of 1/2 for the loaded filter.

P 14.17 By definition  $Q = \omega_o/\beta$  therefore  $\beta = \omega_o/Q$ . Substituting this expression into Eqs. 14.34 and 14.35 yields

$$\omega_{c1} = -\frac{\omega_o}{2Q} + \sqrt{\left(\frac{\omega_o}{2Q}\right)^2 + \omega_o^2}$$

$$\omega_{c2} = \frac{\omega_o}{2Q} + \sqrt{\left(\frac{\omega_o}{2Q}\right)^2 + \omega_o^2}$$

Now factor  $\omega_o$  out to get

$$\omega_{c1} = \omega_o \left[ -\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]$$

$$\omega_{c2} = \omega_o \left[ \frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]$$

P 14.18  $\omega_o = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{(180)(200)} = 189.74 \text{ krad/s}$

$$f_o = \frac{\omega_o}{2\pi} = 30.20 \text{ kHz}$$

$$\beta = 200 - 180 = 20 \text{ krad/s} = 3.18 \text{ kHz}$$

$$Q = \frac{\omega_o}{\beta} = \frac{189.74}{20} = 9.49 = \frac{30.20}{3.18}$$

P 14.19  $\beta = \frac{\omega_o}{Q} = \frac{80}{8} = 10 \text{ krad/s} = \frac{5}{\pi} = 1.59 \text{ kHz}$

$$\omega_{c2} = 80 \left[ \frac{1}{16} + \sqrt{1 + \left(\frac{1}{16}\right)^2} \right] = 85.16 \text{ krad/s}$$

$$f_{c2} = \frac{85.16}{2\pi} = 13.55 \text{ kHz}$$

$$\omega_{c1} = 80 \left[ -\frac{1}{16} + \sqrt{1 + \left(\frac{1}{16}\right)^2} \right] = 75.16 \text{ krad/s}$$

$$f_{c1} = \frac{75.16}{2\pi} = 11.96 \text{ kHz}$$

$$\text{P 14.20 [a]} \quad L = \frac{1}{[2\pi(20,000)]^2(20 \times 10^{-9})} = 3.17 \text{ mH}$$

$$R = \frac{\omega_o L}{Q} = \frac{40\pi \times 10^3(3.17 \times 10^{-3})}{5} = 79.58 \Omega$$

$$\text{[b]} \quad f_{c1} = 20 \left[ -\frac{1}{10} + \sqrt{1 + \frac{1}{100}} \right] = 18.10 \text{ kHz}$$

$$\text{[c]} \quad f_{c2} = 20 \left[ \frac{1}{10} + \sqrt{1 + \frac{1}{100}} \right] = 22.10 \text{ kHz}$$

$$\text{[d]} \quad \beta = f_{c2} - f_{c1} = 4 \text{ kHz}$$

or

$$\beta = \frac{f_o}{Q} = \frac{20}{5} = 4 \text{ kHz}$$

$$\text{P 14.21 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{(10^6)(10^9)}{(40)(25)} = 10^{12}$$

$$\omega_o = 10^6 \text{ rad/s} = 1 \text{ Mrad/s}$$

$$\text{[b]} \quad f_o = \frac{500}{\pi} \text{ kHz} = 159.15 \text{ kHz}$$

$$\text{[c]} \quad Q = \omega_o RC = (10^6)(300)(25 \times 10^{-9}) = 7.5$$

$$\text{[d]} \quad \omega_{c1} = 10^6 \left[ -\frac{1}{15} + \sqrt{1 + \frac{1}{225}} \right] = 935.55 \text{ krad/s}$$

$$\text{[e]} \quad \therefore f_{c1} = 148.90 \text{ kHz}$$

$$\text{[f]} \quad \omega_{c2} = 10^6 \left[ \frac{1}{15} + \sqrt{1 + \frac{1}{225}} \right] = 1068.89 \text{ krad/s}$$

$$\text{[g]} \quad \therefore f_{c2} = 170.12 \text{ kHz}$$

$$\text{[h]} \quad \beta = \frac{\omega_o}{Q} = 133.33 \text{ krad/s or } 21.22 \text{ kHz}$$

$$\text{P 14.22 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{L(25)} = 25 \times 10^8$$

$$\therefore L = \frac{10^9}{625 \times 10^8} = 16 \text{ mH}; \quad R = \frac{10 \times 10^9}{(50 \times 10^3)(25)} = 8 \text{ k}\Omega$$

$$\text{[b]} \quad \omega_{c2} = 50 \left[ \frac{1}{20} + \sqrt{1 + \frac{1}{400}} \right] = 52.56 \text{ krad/s}$$

$$\therefore f_{c2} = 8.37 \text{ kHz}$$

$$\omega_{c1} = 50 \left[ -\frac{1}{20} + \sqrt{1 + \frac{1}{400}} \right] = 47.56 \text{ krad/s}$$

$$\therefore f_{c1} = 7.57 \text{ kHz}$$

$$[c] \beta = \frac{\omega_o}{Q} = 5000 \text{ rad/s} = 795.77 \text{ Hz}$$

$$\text{Check: } \beta = f_{c2} - f_{c1} = 795.77 \text{ Hz}$$

$$\text{P 14.23 [a]} \omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^{12})}{(312.5)(1.25)} = 2.56 \times 10^{12}$$

$$\omega_o = 1.6 \times 10^6 \text{ rad/s}$$

$$f_o = \frac{800}{\pi} = 254.65 \text{ kHz}$$

$$[b] Q = \frac{\omega_o L}{R + R_i} = \frac{(1.6 \times 10^6)(312.5 \times 10^{-3})}{(50 + 12.5)10^3} = 8$$

$$[c] f_{c1} = \frac{800}{\pi} \left[ -\frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 239.23 \text{ kHz}$$

$$[d] f_{c2} = \frac{800}{\pi} \left[ \frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 271.06 \text{ kHz}$$

$$[e] \beta = f_{c2} - f_{c1} = 31.83 \text{ kHz}$$

or

$$\beta = \frac{\omega_o}{Q} = 200 \text{ krad/s} = \frac{100}{\pi} \text{ kHz} = 31.83 \text{ kHz}$$

$$\text{P 14.24 [a]} H(s) = \frac{(R/L)s}{s^2 + \frac{(R+R_i)}{L}s + \frac{1}{LC}}$$

For the numerical values in Problem 14.23 we have

$$H(s) = \frac{16 \times 10^4 s}{s^2 + 2 \times 10^5 s + 2.56 \times 10^{12}}$$

$$\therefore H(j\omega) = \frac{j16 \times 10^4 \omega}{(2.56 \times 10^{12} - \omega^2) + j2 \times 10^5 \omega}$$

$$H(j\omega_o) = \frac{j16 \times 10^4 (1.6 \times 10^6)}{j2 \times 10^5 (1.6 \times 10^6)} = 0.8 \angle 0^\circ$$

$$\therefore v_o(t) = 640 \cos \omega t \text{ mV}$$

$$[\text{b}] \quad \omega_{c1} = 1.6 \times 10^6 \left[ -\frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 1.5 \times 10^6 \text{ rad/s}$$

$$H(j\omega_{c1}) = \frac{j16 \times 10^4(1.5 \times 10^6)}{2.56 \times 10^{12} - 1.5^2 \times 10^{12} + j2 \times 10^5(1.5 \times 10^6)}$$

$$= 0.57/\underline{45^\circ}$$

$$\therefore v_o(t) = 452.55 \cos(1.5 \times 10^6 t + 45^\circ) \text{ mV}$$

$$[\text{c}] \quad \omega_{c2} = 1.6 \times 10^6 \left[ \frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 1.7 \times 10^6 \text{ rad/s}$$

$$H(j\omega_{c2}) = \frac{j16 \times 10^4(1.7 \times 10^6)}{2.56 \times 10^{12} - 1.7^2 \times 10^{12} + j2 \times 10^5(1.7 \times 10^6)}$$


$$= 0.57/\underline{45^\circ}$$

$$\therefore v_o(t) = 452.55 \cos(1.7 \times 10^6 t - 45^\circ) \text{ mV}$$

P 14.25 [a]  $\omega_o = \sqrt{1/LC}$  so  $L = \frac{1}{\omega_o^2 C} = \frac{(20,000)^2}{(50 \times 10^{-9})} = 50 \text{ mH}$

$$Q = \frac{\omega_o}{\beta} \quad \text{so} \quad \beta = \frac{\omega_o}{Q} = \frac{20,000}{5} = 4000 \text{ rad/s}$$
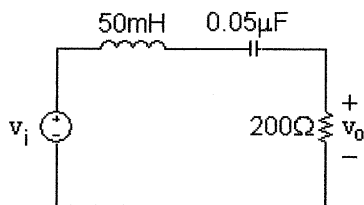
$$\beta = \frac{R}{L} \quad \text{so} \quad R = L\beta = (50 \times 10^{-3})(4000) = 200 \Omega$$



$$[\text{b}] \quad \omega_{c1,2} = \pm \frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2} = \pm \frac{4000}{2} + \sqrt{\left(\frac{4000}{2}\right)^2 + 20,000^2} = \pm 2000 + 20,099.75$$

$$\omega_{c1} = 18,099.75 \text{ rad/s} \quad \omega_{c2} = 22,099.75 \text{ rad/s}$$

P 14.26  $H(j\omega) = \frac{j\omega(4000)}{20,000^2 - \omega^2 + j\omega(4000)}$

$$[\text{a}] \quad H(j20,000) = \frac{j20,000(4000)}{20,000^2 - 20,000^2 + j(20,000)(4000)} = 1$$

$$V_o = (1)V_i \quad \therefore v_o(t) = 200 \cos 20,000t \text{ mV}$$

$$[b] \quad H(j18,099.75) = \frac{j18,099.75(4000)}{20,000^2 - 18,099.75^2 + j(18,099.75)(4000)} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle 45^\circ V_i \quad \therefore \quad v_o(t) = 141.42 \cos(18,099.75t + 45^\circ) \text{ mV}$$

$$[c] \quad H(j22,099.75) = \frac{j22,099.75(4000)}{20,000^2 - 22,099.75^2 + j(22,099.75)(4000)} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle -45^\circ V_i \quad \therefore \quad v_o(t) = 141.42 \cos(22,099.75t - 45^\circ) \text{ mV}$$

$$[d] \quad H(j2000) = \frac{j2000(4000)}{20,000^2 - 2000^2 + j(2000)(4000)} = 0.02 \angle 88.8^\circ$$

$$V_o = 0.02 \angle 88.8^\circ V_i \quad \therefore \quad v_o(t) = 4 \cos(2000t + 88.8^\circ) \text{ mV}$$

$$[e] \quad H(j200,000) = \frac{j200,000(4000)}{20,000^2 - 200,000^2 + j(200,000)(4000)} = 0.02 \angle -88.8^\circ$$

$$V_o = 0.02 \angle -88.8^\circ V_i \quad \therefore \quad v_o(t) = 4 \cos(200,000t - 88.8^\circ) \text{ mV}$$

$$P \ 14.27 \quad H(s) = 1 - \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)} = \frac{s^2 + (1/LC)}{s^2 + (R/L)s + (1/LC)}$$

$$H(j\omega) = \frac{20,000^2 - \omega^2}{20,000^2 - \omega^2 + j\omega(4000)}$$

$$[a] \quad H(j20,000) = \frac{20,000^2 - 20,000^2}{20,000^2 - 20,000^2 + j(20,000)(4000)} = 0$$

$$V_o = (0)V_i \quad \therefore \quad v_o(t) = 0 \text{ mV}$$

$$[b] \quad H(j18,099.75) = \frac{20,000^2 - 18,099.75^2}{20,000^2 - 18,099.75^2 + j(18,099.75)(4000)} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle -45^\circ V_i \quad \therefore \quad v_o(t) = 141.42 \cos(18,099.75t - 45^\circ) \text{ mV}$$

$$[c] \quad H(j22,099.75) = \frac{20,000^2 - 22,099.75^2}{20,000^2 - 22,099.75^2 + j(22,099.75)(4000)} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle 45^\circ V_i \quad \therefore \quad v_o(t) = 141.42 \cos(22,099.75t + 45^\circ) \text{ mV}$$


$$[d] \quad H(j2000) = \frac{20,000^2 - 2000^2}{20,000^2 - 2000^2 + j(2000)(4000)} = 0.9998 \angle -1.16^\circ$$

$$V_o = 0.9998 \angle -1.16^\circ V_i \quad \therefore \quad v_o(t) = 199.96 \cos(2000t - 1.16^\circ) \text{ mV}$$

$$[e] \quad H(j200,000) = \frac{20,000^2 - 200,000^2}{20,000^2 - 200,000^2 + j(200,000)(4000)} = 0.9998/\underline{1.16^\circ}$$

$$V_o = 0.9998/\underline{1.16^\circ} V_i \quad \therefore v_o(t) = 199.96 \cos(200,000t + 1.16^\circ) \text{ mV}$$

P 14.28 [a]

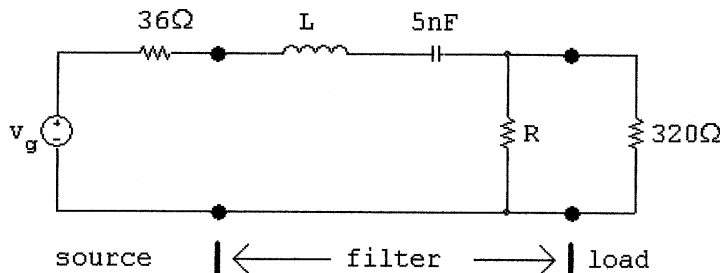

$$[b] \quad L = \frac{1}{\omega_o^2 C} = \frac{10^9}{(625 \times 10^8)5} = 3.2 \times 10^{-3} = 3.2 \text{ mH}$$

$$R = \frac{\omega_o L}{Q} = \frac{800}{10} = 80 \Omega$$

$$[c] \quad R_e = 80 \parallel 320 = 64 \Omega$$

$$R_e + R_i = 64 + 36 = 100 \Omega$$

$$Q_{\text{system}} = \frac{\omega_o L}{R_e + R_i} = \frac{800}{100} = 8$$

$$[d] \quad \beta_{\text{system}} = \frac{\omega_o}{Q_{\text{system}}} = \frac{250 \times 10^3}{8} = 31.25 \text{ krad/s}$$

$$\beta_{\text{system}}(\text{kHz}) = \frac{31.25}{2\pi} = 4.97 \text{ kHz} = 4973.59 \text{ Hz}$$

P 14.29 [a]  $\frac{V_o}{V_i} = \frac{Z}{Z + R}$  where  $Z = \frac{1}{Y}$

$$\text{and } Y = sC + \frac{1}{sL} + \frac{1}{R_L} = \frac{LCR_L s^2 + sL + R_L}{R_L L s}$$

$$H(s) = \frac{R_L L s}{R_L R L C s^2 + (R + R_L) L s + R R_L}$$

$$= \frac{(1/RC)s}{s^2 + \left[ \left( \frac{R+R_L}{R_L} \right) \left( \frac{1}{RC} \right) \right] s + \frac{1}{LC}}$$

$$= \frac{\left( \frac{R_L}{R+R_L} \right) \left( \frac{R+R_L}{R_L} \right) \left( \frac{1}{RC} \right) s}{s^2 + \left[ \left( \frac{R+R_L}{R_L} \right) \left( \frac{1}{RC} \right) \right] s + \frac{1}{LC}}$$

$$= \frac{K \beta s}{s^2 + \beta s + \omega_o^2}, \quad K = \frac{R_L}{R + R_L}$$



$$[\text{b}] \quad \beta = \left( \frac{R + R_L}{R_L} \right) \frac{1}{RC}$$

$$[\text{c}] \quad \beta_u = \frac{1}{RC}$$

$$\therefore \beta_L = \left( \frac{R + R_L}{R_L} \right) \beta_u = \left( 1 + \frac{R}{R_L} \right) \beta_u$$

$$[\text{d}] \quad Q = \frac{\omega_o}{\beta} = \frac{\omega_o RC}{\left( \frac{R + R_L}{R_L} \right)}$$

$$[\text{e}] \quad Q_u = \omega_o RC$$

$$\therefore Q_L = \left( \frac{R_L}{R + R_L} \right) Q_u = \frac{1}{[1 + (R/R_L)]} Q_u$$

$$[\text{f}] \quad H(j\omega) = \frac{Kj\omega\beta}{\omega_o^2 - \omega^2 + j\omega\beta}$$

$$H(j\omega_o) = K$$

Let  $\omega_c$  represent a corner frequency. Then

$$|H(j\omega_c)| = \frac{K}{\sqrt{2}} = \frac{K\omega_c\beta}{\sqrt{(\omega_o^2 - \omega_c^2)^2 + \omega_c^2\beta^2}}$$

$$\therefore \frac{1}{\sqrt{2}} = \frac{\omega_c\beta}{\sqrt{(\omega_o^2 - \omega_c^2)^2 + \omega_c^2\beta^2}}$$

Squaring both sides leads to

$$(\omega_o^2 - \omega_c^2)^2 = \omega_c^2\beta^2 \text{ or } (\omega_o^2 - \omega_c^2) = \pm\omega_c\beta$$

$$\therefore \omega_c^2 \pm \omega_c\beta - \omega_o^2 = 0$$

or

$$\omega_c = \mp \frac{\beta}{2} \pm \sqrt{\frac{\beta^2}{4} + \omega_o^2}$$

The two positive roots are

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2} \quad \text{and} \quad \omega_{c2} = \frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2}$$

where

$$\beta = \left( 1 + \frac{R}{R_L} \right) \frac{1}{RC} \text{ and } \omega_o^2 = \frac{1}{LC}$$

$$\text{P 14.30 } [\text{a}] \quad \omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^{12})}{(10)(4)} = 25 \times 10^{12}$$

$$\omega_o = 5 \text{ Mrad/s}$$

$$[\text{b}] \quad \beta = \frac{R + R_L}{R_L} \cdot \frac{1}{RC} = \left( \frac{6.25}{5.0} \right) \left( \frac{10^{12}}{5 \times 10^6} \right) = 250 \text{ krad/s}$$

$$[\text{c}] \quad Q = \frac{\omega_o}{\beta} = \frac{5}{0.25} = 20$$

$$[\text{d}] \quad H(j\omega_o) = \frac{R_L}{R + R_L} = 0.8 \angle 0^\circ$$


$$\therefore v_o(t) = 600 \cos(5 \times 10^6 t) \text{ mV}$$

$$[\text{e}] \quad \beta = \left( 1 + \frac{R}{R_L} \right) \frac{1}{RC} = \left( 1 + \frac{1.25}{R_L} \right) (200 \times 10^3) \text{ rad/s}$$

$$\omega_o = 5 \times 10^6 \text{ rad/s}$$

$$Q = \frac{\omega_o}{\beta} = \frac{25}{1 + (1.25/R_L)} \quad \text{where } R_L \text{ is in megohms}$$

[f]

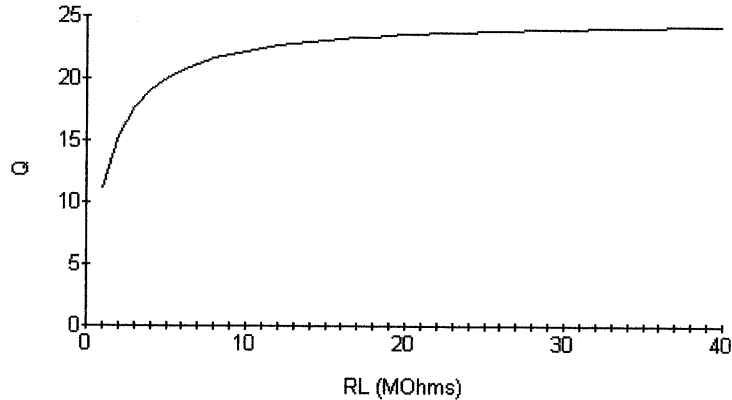

$$\text{P 14.31} \quad \omega_o^2 = \frac{1}{LC} = \frac{(10^6)(10^{12})}{(400)(4)} = 625 \times 10^{12}$$

$$\omega_o = 25 \text{ Mrad/s}$$

$$Q_u = \omega_o RC = (25 \times 10^6)(100 \times 10^3)(4 \times 10^{-12}) = 10$$

$$\therefore \left( \frac{R_L}{R + R_L} \right) 10 = 9; \quad \therefore R_L = 9R = 900 \text{ k}\Omega$$

P 14.32 [a] In analyzing the circuit qualitatively we visualize  $v_i$  is a sinusoidal voltage and we seek the steady-state nature of the output voltage  $v_o$ .

At zero frequency the inductor provides a direct connection between the input and the output, hence  $v_o = v_i$  when  $\omega = 0$ .

At infinite frequency the capacitor provides the direct connection, hence  $v_o = v_i$  when  $\omega = \infty$ .

At the resonant frequency of the parallel combination of  $L$  and  $C$  the impedance of the combination is infinite and hence the output voltage will be zero when  $\omega = \omega_o$ .

At frequencies on either side of  $\omega_o$  the amplitude of the output voltage will be nonzero but less than the amplitude of the input voltage.

Thus the circuit behaves like a band-reject filter.

[b] Let  $Z$  represent the impedance of the parallel branches  $L$  and  $C$ , thus

$$Z = \frac{sL(1/sC)}{sL + 1/sC} = \frac{sL}{s^2LC + 1}$$

Then

$$\begin{aligned} H(s) &= \frac{V_o}{V_i} = \frac{R}{Z + R} = \frac{R(s^2LC + 1)}{sL + R(s^2LC + 1)} \\ &= \frac{[s^2 + (1/LC)]}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)} \end{aligned}$$

$$H(s) = \frac{s^2 + \omega_o^2}{s^2 + \beta s + \omega_o^2}$$

[c] From part (b) we have

$$H(j\omega) = \frac{\omega_o^2 - \omega^2}{\omega_o^2 - \omega^2 + j\omega\beta}$$

It follows that  $H(j\omega) = 0$  when  $\omega = \omega_o$

$$\therefore \omega_o = \frac{1}{\sqrt{LC}}$$

$$[d] |H(j\omega)| = \frac{\omega_o^2 - \omega^2}{\sqrt{(\omega_o^2 - \omega^2)^2 + \omega^2\beta^2}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}} \text{ when } \omega^2\beta^2 = (\omega_o^2 - \omega^2)^2$$

or  $\pm \omega\beta = \omega_o^2 - \omega^2$ , thus

$$\omega^2 \pm \beta\omega - \omega_o^2 = 0$$

The two positive roots of this quadratic are

$$\omega_{c1} = \frac{-\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}$$

Also note that since  $\beta = \omega_o/Q$

$$\omega_{c1} = \omega_o \left[ \frac{-1}{2Q} + \sqrt{1 + \left( \frac{1}{2Q} \right)^2} \right]$$

$$\omega_{c2} = \omega_o \left[ \frac{1}{2Q} + \sqrt{1 + \left( \frac{1}{2Q} \right)^2} \right]$$

[e] It follows from the equations derived in part (d) that

$$\beta = \omega_{c2} - \omega_{c1} = 1/RC$$

[f] By definition  $Q = \omega_o/\beta = \omega_o RC$

P 14.33 [a]  $\omega_o^2 = \frac{1}{LC} = \frac{(10^6)(10^{12})}{(625)(25)} = 64 \times 10^{12}$

$$\therefore \omega_o = 8 \text{ Mrad/s}$$

[b]  $f_o = \frac{\omega_o}{2\pi} = 1.27 \text{ MHz}$

[c]  $Q = \omega_o RC = (8 \times 10^6)(80 \times 10^3)(25 \times 10^{-12}) = 16$

[d]  $\omega_{c1} = 8 \times 10^6 \left[ -\frac{1}{32} + \sqrt{1 + \frac{1}{1024}} \right] = 7.75 \text{ Mrad/s}$

[e]  $f_{c1} = \frac{\omega_{c1}}{2\pi} = 1.234 \text{ MHz}$

[f]  $\omega_{c2} = 8 \times 10^6 \left[ \frac{1}{32} + \sqrt{1 + \frac{1}{1024}} \right] = 8.25 \text{ Mrad/s}$

[g]  $f_{c2} = \frac{\omega_{c2}}{2\pi} = 1.31 \text{ MHz}$

[h]  $\beta = f_{c2} - f_{c1} = 79.58 \text{ kHz}$

or

$$\beta = \frac{\omega_o}{2\pi Q} = \frac{500 \times 10^3}{2\pi} = 79.58 \text{ kHz}$$

P 14.34 [a]  $\omega_o = 2\pi f_o = 100\pi \text{ krad/s}$

$$L = \frac{1}{\omega_o^2 C} = \frac{10^6}{10^4 \pi \times 10^6 (0.1)} = 101.32 \mu\text{H}$$

$$R = \frac{Q}{\omega_o C} = \frac{8 \times 10^6}{(100\pi)(0.1 \times 10^3)} = 254.65 \Omega$$

$$[b] f_{c2} = 50k \left[ \frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 53.22 \text{ kHz}$$

$$f_{c1} = 50k \left[ -\frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 46.97 \text{ kHz}$$

$$[c] \beta = f_{c2} - f_{c1} = 6.25 \text{ kHz}$$

or

$$\beta = \frac{f_o}{Q} = \frac{50k}{8} = 6.25 \text{ kHz}$$

$$P 14.35 [a] R_e = 254.65 \parallel 932 = 200 \Omega$$

$$Q = \omega_o R_e C = 100\pi \times 10^3 (200)(0.1)10^{-6} = 2\pi = 6.28$$

$$[b] \beta = \frac{f_o}{Q} = \frac{50}{2\pi} = 7.96 \text{ kHz}$$


$$[c] f_{c2} = 50 \left[ \frac{1}{4\pi} + \sqrt{1 + \frac{1}{16\pi^2}} \right] = 54.14 \text{ kHz}$$

$$[d] f_{c1} = 50 \left[ -\frac{1}{4\pi} + \sqrt{1 + \frac{1}{16\pi^2}} \right] = 46.18 \text{ kHz}$$

$$P 14.36 [a] \omega_o = \sqrt{1/LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = \frac{1}{(4000)^2 (80 \times 10^{-9})} = 781.25 \text{ mH}$$

$$Q = \frac{\omega_o}{\beta} \quad \text{so} \quad \beta = \frac{\omega_o}{Q} = \frac{4000}{2/3} = 6000 \text{ rad/s}$$
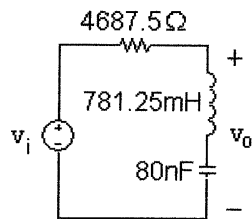
$$\beta = \frac{R}{L} \quad \text{so} \quad R = L\beta = (781.25 \times 10^{-3})(6000) = 4687.5 \Omega$$



$$[b] \omega_{c1,2} = \pm \frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2} = \pm \frac{6000}{2} + \sqrt{\left(\frac{6000}{2}\right)^2 + 4000^2} = \pm 3000 + 5000$$

$$\omega_{c1} = 2000 \text{ rad/s} \quad \omega_{c2} = 8000 \text{ rad/s}$$

$$P 14.37 \quad H(j\omega) = \frac{\omega_o^2 - \omega^2}{\omega_o^2 - \omega^2 + j\omega\beta} = \frac{4000^2 - \omega^2}{4000^2 - \omega^2 + j\omega(6000)}$$

$$[a] H(j4000) = \frac{4000^2 - 4000^2}{4000^2 - 4000^2 + j(4000)(6000)} = 0$$

$$V_o = (0)V_i \quad \therefore v_o(t) = 0 \text{ mV}$$

$$[b] H(j2000) = \frac{4000^2 - 2000^2}{4000^2 - 2000^2 + j(2000)(6000)} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle -45^\circ V_i \quad \therefore v_o(t) = 88.39 \cos(2000t - 45^\circ) \text{ mV}$$

$$[c] H(j8000) = \frac{4000^2 - 8000^2}{4000^2 - 8000^2 + j(8000)(6000)} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle 45^\circ V_i \quad \therefore v_o(t) = 88.39 \cos(8000t + 45^\circ) \text{ mV}$$

$$[d] H(j400) = \frac{4000^2 - 400^2}{4000^2 - 400^2 + j(400)(6000)} = 0.989 \angle -8.62^\circ$$

$$V_o = 0.989 \angle -8.62^\circ V_i \quad \therefore v_o(t) = 123.6 \cos(400t - 8.62^\circ) \text{ mV}$$

$$[e] H(j40,000) = \frac{4000^2 - 40,000^2}{4000^2 - 40,000^2 + j(40,000)(6000)} = 0.989 \angle 8.62^\circ$$

$$V_o = 0.989 \angle 8.62^\circ V_i \quad \therefore v_o(t) = 123.6 \cos(40,000t + 8.62^\circ) \text{ mV}$$

$$P 14.38 \quad H(j\omega) = \frac{j\omega\beta}{\omega_o^2 - \omega^2 + j\omega\beta} = \frac{j\omega(6000)}{4000^2 - \omega^2 + j\omega(6000)}$$

$$[a] H(j4000) = \frac{j(4000)(6000)}{4000^2 - 4000^2 + j(4000)(6000)} = 1$$

$$V_o = (1)V_i \quad \therefore v_o(t) = 125 \cos 4000t \text{ mV}$$

$$[b] H(j2000) = \frac{j(2000)(6000)}{4000^2 - 2000^2 + j(2000)(6000)} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle 45^\circ V_i \quad \therefore v_o(t) = 88.39 \cos(2000t + 45^\circ) \text{ mV}$$

$$[c] H(j8000) = \frac{j(8000)(6000)}{4000^2 - 8000^2 + j(8000)(6000)} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \angle -45^\circ V_i \quad \therefore v_o(t) = 88.39 \cos(8000t - 45^\circ) \text{ mV}$$

$$[d] H(j400) = \frac{j(400)(6000)}{4000^2 - 400^2 + j(400)(6000)} = 0.15 \angle 81.4^\circ$$

$$V_o = 0.15 \angle 81.4^\circ V_i \quad \therefore v_o(t) = 18.73 \cos(400t + 81.4^\circ) \text{ mV}$$

$$[e] \quad H(j40,000) = \frac{j(40,000)(6000)}{4000^2 - 40,000^2 + j(40,000)(6000)} = 0.15 / -81.4^\circ$$

$$V_o = 0.15 / -81.4^\circ V_i \quad \therefore \quad v_o(t) = 18.73 \cos(40,000t - 81.4^\circ) \text{ mV}$$

P 14.39 [a] Let  $Z = \frac{R_L(sL + (1/sC))}{R_L + sL + (1/sC)}$

$$Z = \frac{R_L(s^2LC + 1)}{s^2LC + R_LCs + 1}$$

$$\text{Then } H(s) = \frac{V_o}{V_i} = \frac{s^2R_LCL + R_L}{(R + R_L)LCs^2 + RR_LCs + R + R_L}$$

Therefore

$$\begin{aligned} H(s) &= \left( \frac{R_L}{R + R_L} \right) \cdot \frac{[s^2 + (1/LC)]}{\left[ s^2 + \left( \frac{RR_L}{R + R_L} \right) \frac{s}{L} + \frac{1}{LC} \right]} \\ &= \frac{K(s^2 + \omega_o^2)}{s^2 + \beta s + \omega_o^2} \end{aligned}$$

$$\text{where } K = \frac{R_L}{R + R_L}; \quad \omega_o^2 = \frac{1}{LC}; \quad \beta = \left( \frac{RR_L}{R + R_L} \right) \frac{1}{L}$$

$$[b] \quad \omega_o = \frac{1}{\sqrt{LC}}$$

$$[c] \quad \beta = \left( \frac{RR_L}{R + R_L} \right) \frac{1}{L}$$

$$[d] \quad Q = \frac{\omega_o}{\beta} = \frac{\omega_o L}{[RR_L/(R + R_L)]}$$

$$[e] \quad H(j\omega) = \frac{K(\omega_o^2 - \omega^2)}{(\omega_o^2 - \omega^2) + j\beta\omega}$$

$$H(j\omega_o) = 0$$

$$[f] \quad H(j0) = \frac{K\omega_o^2}{\omega_o^2} = K$$

$$[g] \quad H(j\omega) = \frac{K[(\omega_o/\omega)^2 - 1]}{\left\{ [(\omega_o/\omega)^2 - 1] + j\beta/\omega \right\}}$$

$$H(j\infty) = \frac{-K}{-1} = K$$

$$[h] \quad H(j\omega) = \frac{K(\omega_o^2 - \omega^2)}{(\omega_o^2 - \omega^2) + j\beta\omega}$$

$$H(j0) = H(j\infty) = K$$

Let  $\omega_c$  represent a corner frequency. Then

$$|H(j\omega_c)| = \frac{K}{\sqrt{2}}$$

$$\therefore \frac{K}{\sqrt{2}} = \frac{K(\omega_o^2 - \omega_c^2)}{\sqrt{(\omega_o^2 - \omega_c^2)^2 + \omega_c^2 \beta^2}}$$

Squaring both sides leads to

$$(\omega_o^2 - \omega_c^2)^2 = \omega_c^2 \beta^2 \text{ or } (\omega_o^2 - \omega_c^2) = \pm \omega_c \beta$$

$$\therefore \omega_c^2 \pm \omega_c \beta - \omega_o^2 = 0$$

or

$$\omega_c = \mp \frac{\beta}{2} \pm \sqrt{\frac{\beta^2}{4} + \omega_o^2}$$

The two positive roots are

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2} \quad \text{and} \quad \omega_{c2} = \frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2}$$

where

$$\beta = \frac{RR_L}{R + R_L} \cdot \frac{1}{L} \text{ and } \omega_o^2 = \frac{1}{LC}$$

$$\text{P 14.40 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(400 \times 10^{-3})(250 \times 10^{-12})} = 10^{10}$$

$$\omega_o = 10^5 = 100 \text{ krad/s} = 15.9 \text{ kHz}$$

$$\beta = \frac{RR_L}{R + R_L} \cdot \frac{1}{L} = \frac{(5000)(20,000)}{25,000} \cdot \frac{1}{0.4} = 10^4 \text{ rad/s} = 1.59 \text{ kHz}$$

$$Q = \frac{\omega_o}{\beta} = \frac{10^5}{10^4} = 10$$

$$\text{[b]} \quad H(j0) = \frac{R_L}{R + R_L} = \frac{20,000}{25,000} = 0.8$$

$$H(j\infty) = \frac{R_L}{R + R_L} = 0.8$$

$$\text{[c]} \quad f_{c2} = \frac{10^5}{2\pi} \left[ \frac{1}{20} + \sqrt{1 + \frac{1}{400}} \right] = 16.73 \text{ kHz}$$

$$f_{c1} = \frac{10^5}{2\pi} \left[ -\frac{1}{20} + \sqrt{1 + \frac{1}{400}} \right] = 15.14 \text{ kHz}$$

$$\text{Check:} \quad \beta = f_{c2} - f_{c1} = 1.59 \text{ kHz.}$$




$$[d] \quad Q = \frac{\omega_o}{\beta} = \frac{10^5}{\frac{RR_L}{R+R_L} \cdot \frac{1}{L}}$$

$$= \frac{40(R+R_L)}{RR_L} = 8 \left( 1 + \frac{5}{R_L} \right)$$

where  $R_L$  is in kilohms.

[e]

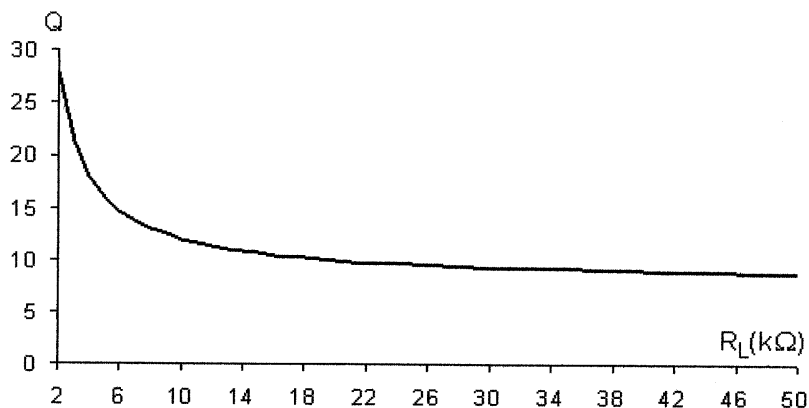

P 14.41 [a]  $\omega_o^2 = \frac{1}{LC} = 10^{12}$

$$\therefore L = \frac{1}{(10^{12})(400 \times 10^{-12})} = 2.5 \text{ mH}$$

$$\frac{R_L}{R+R_L} = 0.96; \quad \therefore 0.04R_L = 0.96R$$

$$\therefore R_L = 24R \quad \therefore R = \frac{36,000}{24} = 1.5 \text{ k}\Omega$$

[b]  $\beta = \left( \frac{R_L}{R+R_L} \right) R \cdot \frac{1}{L} = 576 \times 10^3$

$$Q = \frac{\omega_o}{\beta} = \frac{10^6}{576 \times 10^3} = 1.74$$

P 14.42 [a]  $|H(j\omega)| = \frac{4 \times 10^6}{\sqrt{(4 \times 10^6 - \omega^2)^2 + (500\omega)^2}} = 1$

$$\therefore 16 \times 10^{12} = (4 \times 10^6 - \omega^2)^2 + (500\omega)^2$$

$$= -8 \times 10^6 \omega^2 + \omega^4 + 25 \times 10^4 \omega^2$$

$$\therefore \omega^2 = 8 \times 10^6 - 25 \times 10^4 \quad \text{so} \quad \omega = 2783.88 \text{ rad/s}$$

[b] From the equation for  $|H(j\omega)|$  in part (a), the frequency for which the magnitude is maximum is the frequency for which the denominator is minimum. This is the frequency at which

$$(4 \times 10^6 - \omega^2)^2 = 0 \quad \text{so} \quad \omega = \sqrt{4 \times 10^6} = 2000 \text{ rad/s}$$

$$[c] |H(j2000)| = \frac{4 \times 10^6}{\sqrt{(4 \times 10^6 - 2000^2)^2 + [500(2000)]^2}} = 4$$

P 14.43 [a] Use the cutoff frequencies to calculate the bandwidth:

$$\omega_{c1} = 2\pi(697) = 4379.38 \text{ rad/s} \quad \omega_{c2} = 2\pi(941) = 5912.48 \text{ rad/s}$$

$$\text{Thus } \beta = \omega_{c2} - \omega_{c1} = 1533.10 \text{ rad/s}$$

Calculate inductance using Eq. (14.32) and capacitance using Eq. (14.31):

$$L = \frac{R}{\beta} = \frac{600}{1533.10} = 0.39 \text{ H}$$

$$C = \frac{1}{L\omega_{c1}\omega_{c2}} = \frac{1}{(0.39)(4379.38)(5912.48)} = 0.10 \mu\text{F}$$

[b] At the outermost two frequencies in the low-frequency group (687 Hz and 941 Hz) the amplitudes are

$$|V_{697\text{Hz}}| = |V_{941\text{Hz}}| = \frac{|V_{\text{peak}}|}{\sqrt{2}} = 0.707|V_{\text{peak}}|$$

because these are cutoff frequencies. We calculate the amplitudes at the other two low frequencies using Eq. (14.32):

$$|V| = (|V_{\text{peak}}|)(|H(j\omega)|) = |V_{\text{peak}}| \frac{\omega\beta}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\omega\beta)^2}}$$

Therefore

$$\begin{aligned} |V_{770\text{Hz}}| &= |V_{\text{peak}}| = \frac{(4838.05)(1533.10)}{\sqrt{(5088.52^2 - 4838.05^2)^2 + [(4838.05)(1533.10)]^2}} \\ &= 0.948|V_{\text{peak}}| \end{aligned}$$

and

$$\begin{aligned} |V_{852\text{Hz}}| &= |V_{\text{peak}}| = \frac{(5353.27)(1533.10)}{\sqrt{(5088.52^2 - 5353.27^2)^2 + [(5353.27)(1533.10)]^2}} \\ &= 0.948|V_{\text{peak}}| \end{aligned}$$

It is not a coincidence that these two magnitudes are the same. The frequencies in both bands of the DTMF system were carefully chosen to produce this type of predictable behavior with linear filters. In other words, the frequencies were chosen to be equally far apart with respect to the response produced by a linear filter. Most musical scales consist of tones designed with this same property – note intervals are selected to place the notes equally far apart. That is why the DTMF tones remind

us of musical notes! Unlike musical scales, DTMF frequencies were selected to be harmonically unrelated, to lower the risk of misidentifying a tone's frequency if the circuit elements are not perfectly linear.

- [c] The high-band frequency closest to the low-frequency band is 1209 Hz. The amplitude of a tone with this frequency is

$$\begin{aligned} |V_{1209\text{Hz}}| &= |V_{\text{peak}}| = \frac{(7596.37)(1533.10)}{\sqrt{(5088.52^2 - 7596.37^2)^2 + [(7596.37)(1533.10)]^2}} \\ &= 0.344|V_{\text{peak}}| \end{aligned}$$

This is less than one half the amplitude of the signals with the low-band cutoff frequencies, ensuring adequate separation of the bands.

P 14.44 The cutoff frequencies and bandwidth are

$$\omega_{c_1} = 2\pi(1209) = 7596 \text{ rad/s}$$

$$\omega_{c_2} = 2\pi(1633) = 10.26 \text{ krad/s}$$

$$\beta = \omega_{c_2} - \omega_{c_1} = 2664 \text{ rad/s}$$

Telephone circuits always have  $R = 600 \Omega$ . Therefore, the filters inductance and capacitance values are

$$L = \frac{R}{\beta} = \frac{600}{2664} = 0.225 \text{ H}$$

$$C = \frac{1}{\omega_{c_1}\omega_{c_2}L} = 0.057 \mu\text{F}$$

At the highest of the low-band frequencies, 941 Hz, the amplitude is

$$|V_\omega| = |V_{\text{peak}}| \frac{\omega\beta}{\sqrt{(\omega_o^2 - \omega^2)^2 + \omega^2\beta^2}}$$

where  $\omega_o = \sqrt{\omega_{c_1}\omega_{c_2}}$ . Thus,

$$\begin{aligned} |V_\omega| &= \frac{|V_{\text{peak}}|(5912)(2664)}{\sqrt{[(8828)^2 - (5912)^2]^2 + [(5912)(2664)]^2}} \\ &= 0.344 |V_{\text{peak}}| \end{aligned}$$

Again it is not coincidental that this result is the same as the response of the low-band filter to the lowest of the high-band frequencies.

P 14.45 From Problem 14.43 the response to the largest of the DTMF low-band tones is  $0.948|V_{\text{peak}}|$ . The response to the 20 Hz tone is

$$\begin{aligned}|V_{20\text{Hz}}| &= \frac{|V_{\text{peak}}|(125.6)(1533)}{[(5089^2 - 125.6^2)^2 + [(125.6)(1533)]^2]^{1/2}} \\ &= 0.00744|V_{\text{peak}}|\end{aligned}$$

$$\therefore \frac{|V_{20\text{Hz}}|}{|V_{770\text{Hz}}|} = \frac{|V_{20\text{Hz}}|}{|V_{852\text{Hz}}|} = \frac{0.00744|V_{\text{peak}}|}{0.948|V_{\text{peak}}|} = 0.5$$

$$\therefore |V_{20\text{Hz}}| = 63.7|V_{770\text{Hz}}|$$

Thus, the 20Hz signal can be 63.7 times as large as the DTMF tones.