

# The Laplace Transform in Circuit Analysis

## Assessment Problems

$$\text{AP 13.1 [a]} \quad Y = \frac{1}{R} + \frac{1}{sL} + sC = \frac{C[s^2 + (1/RC)s + (1/LC)]}{s}$$

$$\frac{1}{RC} = \frac{10^6}{(500)(0.025)} = 80,000; \quad \frac{1}{LC} = 25 \times 10^8$$

$$\text{Therefore } Y = \frac{25 \times 10^{-9}(s^2 + 80,000s + 25 \times 10^8)}{s}$$

$$\text{[b]} \quad z_{1,2} = -40,000 \pm \sqrt{16 \times 10^8 - 25 \times 10^8} = -40,000 \pm j30,000 \text{ rad/s}$$

$$-z_1 = -40,000 - j30,000 \text{ rad/s}$$

$$-z_2 = -40,000 + j30,000 \text{ rad/s}$$

$$p_1 = 0 \text{ rad/s}$$

$$\text{AP 13.2 [a]} \quad Z = 2000 + \frac{1}{Y} = 2000 + \frac{4 \times 10^7 s}{s^2 + 80,000s + 25 \times 10^8}$$

$$= \frac{2000(s^2 + 10^5 s + 25 \times 10^8)}{s^2 + 80,000s + 25 \times 10^8} = \frac{2000(s + 50,000)^2}{s^2 + 80,000s + 25 \times 10^8}$$


$$\text{[b]} \quad -z_1 = -z_2 = -50,000 \text{ rad/s}$$

$$-p_1 = -40,000 - j30,000 \text{ rad/s}$$

$$-p_2 = -40,000 + j30,000 \text{ rad/s}$$

AP 13.3 [a] At  $t = 0^-$ ,  $0.2v_1 = (0.8)v_2$ ;  $v_1 = 4v_2$ ;  $v_1 + v_2 = 100$  V

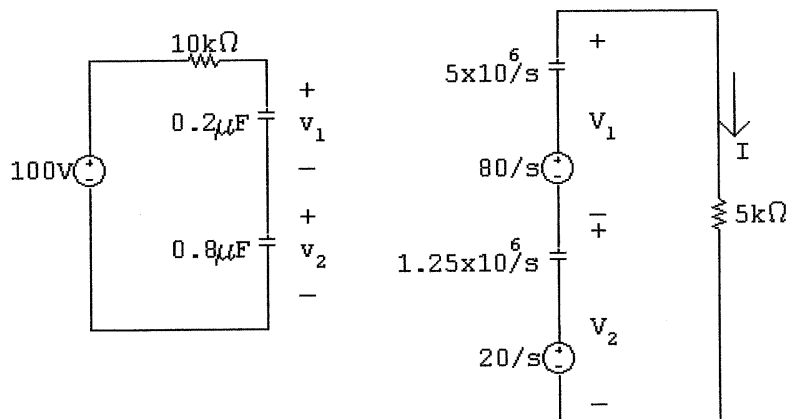Therefore  $v_1(0^-) = 80\text{V} = v_1(0^+)$ ;  $v_2(0^-) = 20\text{V} = v_2(0^+)$



$$I = \frac{(80/s) + (20/s)}{5000 + [(5 \times 10^6)/s] + (1.25 \times 10^6/s)} = \frac{20 \times 10^{-3}}{s + 1250}$$


$$V_1 = \frac{80}{s} - \frac{5 \times 10^6}{s} \left( \frac{20 \times 10^{-3}}{s + 1250} \right) = \frac{80}{s + 1250}$$

$$V_2 = \frac{20}{s} - \frac{1.25 \times 10^6}{s} \left( \frac{20 \times 10^{-3}}{s + 1250} \right) = \frac{20}{s + 1250}$$

[b]  $i = 20e^{-1250t}u(t)$  mA;  $v_1 = 80e^{-1250t}u(t)$  V

$v_2 = 20e^{-1250t}u(t)$  V

AP 13.4 [a]

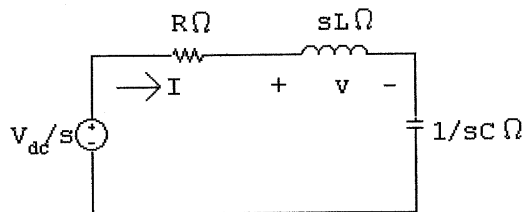

$$I = \frac{V_{dc}/s}{R + sL + (1/sC)} = \frac{V_{dc}/L}{s^2 + (R/L)s + (1/LC)}$$

$$\frac{V_{dc}}{L} = 40; \quad \frac{R}{L} = 1.2; \quad \frac{1}{LC} = 1.0$$

$$I = \frac{40}{(s + 0.6 - j0.8)(s + 0.6 + j0.8)} = \frac{K_1}{s + 0.6 - j0.8} + \frac{K_1^*}{s + 0.6 + j0.8}$$

$$K_1 = \frac{40}{j1.6} = -j25 = 25/\underline{-90^\circ}; \quad K_1^* = 25/\underline{90^\circ}$$

[b]  $i = 50e^{-0.6t} \cos(0.8t - 90^\circ) = [50e^{-0.6t} \sin 0.8t]u(t)$  A


[c] 
$$V = sLI = \frac{160s}{(s + 0.6 - j0.8)(s + 0.6 + j0.8)}$$

$$= \frac{K_1}{s + 0.6 - j0.8} + \frac{K_1^*}{s + 0.6 + j0.8}$$

$$K_1 = \frac{160(-0.6 + j0.8)}{j1.6} = 100 \angle 36.87^\circ$$

[d]  $v(t) = [200e^{-0.6t} \cos(0.8t + 36.87^\circ)]u(t)$  V

AP 13.5 [a]

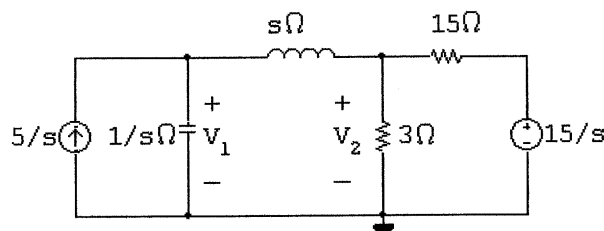

The two node voltage equations are

$$\frac{V_1 - V_2}{s} + V_1 s = \frac{5}{s} \quad \text{and} \quad \frac{V_2}{3} + \frac{V_2 - V_1}{s} + \frac{V_2 - (15/s)}{15} = 0$$

Solving for  $V_1$  and  $V_2$  yields

$$V_1 = \frac{5(s+3)}{s(s^2 + 2.5s + 1)}, \quad V_2 = \frac{2.5(s^2 + 6)}{s(s^2 + 2.5s + 1)}$$

[b] The partial fraction expansions of  $V_1$  and  $V_2$  are

$$V_1 = \frac{15}{s} - \frac{50/3}{s + 0.5} + \frac{5/3}{s + 2} \quad \text{and} \quad V_2 = \frac{15}{s} - \frac{125/6}{s + 0.5} + \frac{25/3}{s + 2}$$

It follows that

$$v_1(t) = \left[ 15 - \frac{50}{3}e^{-0.5t} + \frac{5}{3}e^{-2t} \right] u(t) \text{ V} \quad \text{and}$$


$$v_2(t) = \left[ 15 - \frac{125}{6}e^{-0.5t} + \frac{25}{3}e^{-2t} \right] u(t) \text{ V}$$

[c]  $v_1(0^+) = 15 - \frac{50}{3} + \frac{5}{3} = 0$

$$v_2(0^+) = 15 - \frac{125}{6} + \frac{25}{3} = 2.5 \text{ V}$$

[d]  $v_1(\infty) = 15 \text{ V}; \quad v_2(\infty) = 15 \text{ V}$


AP 13.6 [a]

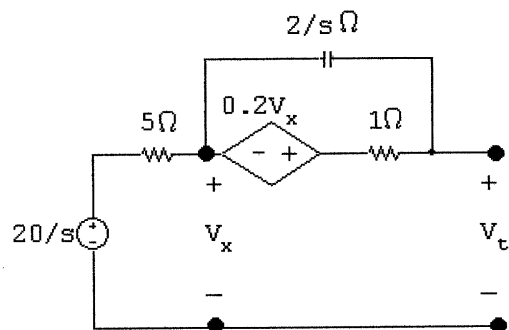

With no load across terminals  $a - b$   $V_x = 20/s$ :

$$\frac{1}{2} \left[ \frac{20}{s} - V_{Th} \right] s + \left[ 1.2 \left( \frac{20}{s} \right) - V_{Th} \right] = 0$$
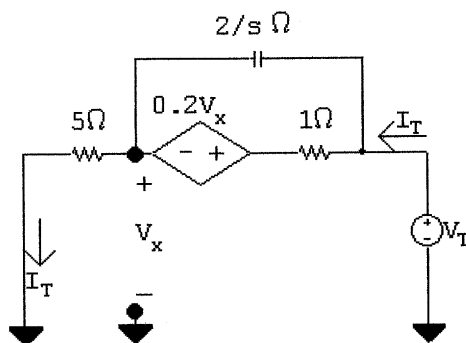
$$\text{therefore } V_{Th} = \frac{20(s + 2.4)}{s(s + 2)}$$



$$V_x = 5I_T \quad \text{and} \quad Z_{Th} = \frac{V_T}{I_T}$$


Solving for  $I_T$  gives

$$I_T = \frac{(V_T - 5I_T)s}{2} + V_T - 6I_T$$

Therefore

$$14I_T = V_T s + 5sI_T + 2V_T; \quad \text{therefore } Z_{Th} = \frac{5(s + 2.8)}{s + 2}$$

[b]

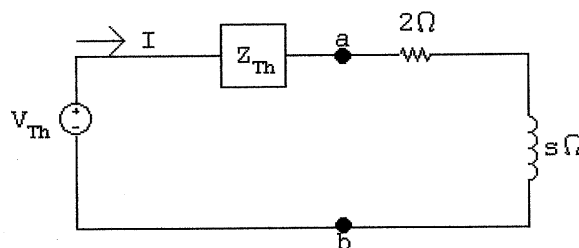

$$I = \frac{V_{Th}}{Z_{Th} + 2 + s} = \frac{20(s + 2.4)}{s(s + 3)(s + 6)}$$

AP 13.7 [a]  $i_2 = 1.25e^{-t} - 1.25e^{-3t}$ ; therefore  $\frac{di_2}{dt} = -1.25e^{-t} + 3.75e^{-3t}$

Therefore  $\frac{di_2}{dt} = 0$  when

$$1.25e^{-t} = 3.75e^{-3t} \quad \text{or} \quad e^{2t} = 3, \quad t = 0.5(\ln 3) = 549.31 \text{ ms}$$

$$i_2(\text{max}) = 1.25[e^{-0.549} - e^{-3(0.549)}] = 481.13 \text{ mA}$$

[b] From Eqs. 13.68 and 13.69, we have

$$\Delta = 12(s^2 + 4s + 3) = 12(s+1)(s+3) \quad \text{and} \quad N_1 = 60(s+2)$$

$$\text{Therefore} \quad I_1 = \frac{N_1}{\Delta} = \frac{5(s+2)}{(s+1)(s+3)}$$

A partial fraction expansion leads to the expression

$$I_1 = \frac{2.5}{s+1} + \frac{2.5}{s+3}$$

Therefore we get

$$i_1 = 2.5[e^{-t} + e^{-3t}]u(t) \text{ A}$$

[c]  $\frac{di_1}{dt} = -2.5[e^{-t} + 3e^{-3t}]$ ;  $\frac{di_1(0.54931)}{dt} = -2.89 \text{ A/s}$


[d] When  $i_2$  is at its peak value,

$$\frac{di_2}{dt} = 0$$

$$\text{Therefore} \quad L_2 \left( \frac{di_2}{dt} \right) = 0 \quad \text{and} \quad i_2 = - \left( \frac{M}{12} \right) \left( \frac{di_1}{dt} \right)$$

[e]  $i_2(\text{max}) = \frac{-2(-2.89)}{12} = 481.13 \text{ mA} \quad (\text{checks})$

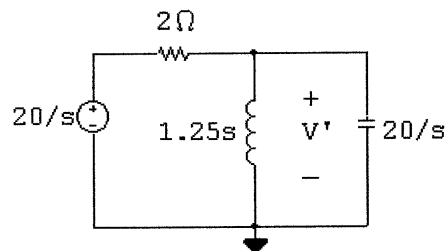AP 13.8 [a] The  $s$ -domain circuit with the voltage source acting alone is




$$\frac{V' - (20/s)}{2} + \frac{V'}{1.25s} + \frac{V's}{20} = 0$$

$$V' = \frac{200}{(s+2)(s+8)} = \frac{100/3}{s+2} - \frac{100/3}{s+8}$$

$$v' = \frac{100}{3}[e^{-2t} - e^{-8t}]u(t) \text{ V}$$

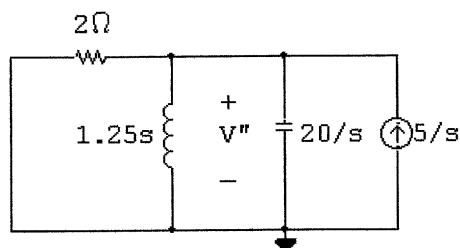[b] With the current source acting alone,



$$\frac{V''}{2} + \frac{V''}{1.25s} + \frac{V''s}{20} = \frac{5}{s}$$

$$V'' = \frac{100}{(s+2)(s+8)} = \frac{50/3}{s+2} - \frac{50/3}{s+8}$$

$$v'' = \frac{50}{3}[e^{-2t} - e^{-8t}]u(t) \text{ V}$$

[c]  $v = v' + v'' = [50e^{-2t} - 50e^{-8t}]u(t) \text{ V}$

AP 13.9 [a]  $\frac{V_o}{s+2} + \frac{V_o s}{10} = I_g$ ; therefore  $\frac{V_o}{I_g} = H(s) = \frac{10(s+2)}{s^2 + 2s + 10}$

[b]  $-z_1 = -2 \text{ rad/s}$ ;  $-p_1 = -1 + j3 \text{ rad/s}$ ;  $-p_2 = -1 - j3 \text{ rad/s}$

AP 13.10 [a]

$$V_o = \frac{10(s+2)}{s^2 + 2s + 10} \cdot \frac{1}{s} = \frac{K_o}{s} + \frac{K_1}{s+1-j3} + \frac{K_1^*}{s+1+j3}$$

$$K_o = 2; \quad K_1 = 5/3 \angle -126.87^\circ; \quad K_1^* = 5/3 \angle 126.87^\circ$$

$$v_o = [2 + (10/3)e^{-t} \cos(3t - 126.87^\circ)]u(t) \text{ V}$$

[b]  $V_o = \frac{10(s+2)}{s^2 + 2s + 10} \cdot 1 = \frac{K_2}{s+1-j3} + \frac{K_2^*}{s+1+j3}$

$$K_2 = 5.27 \angle -18.43^\circ; \quad K_2^* = 5.27 \angle 18.43^\circ$$

$$v_o = [10.54e^{-t} \cos(3t - 18.43^\circ)]u(t) \text{ V}$$

AP 13.11 [a]

$$H(s) = \mathcal{L}\{h(t)\} = \mathcal{L}\{v_o(t)\}$$

$$\begin{aligned} v_o(t) &= 10,000 \cos \theta e^{-70t} \cos 240t - 10,000 \sin \theta e^{-70t} \sin 240t \\ &= 9600e^{-70t} \cos 240t - 2800e^{-70t} \sin 240t \end{aligned}$$

$$\begin{aligned} \text{Therefore } H(s) &= \frac{9600(s+70)}{(s+70)^2 + (240)^2} - \frac{2800(240)}{(s+70)^2 + (240)^2} \\ &= \frac{9600s}{s^2 + 140s + 62,500} \end{aligned}$$

$$\begin{aligned} \text{[b] } V_o(s) &= H(s) \cdot \frac{1}{s} = \frac{9600}{s^2 + 140s + 62,500} \\ &= \frac{K_1}{s + 70 - j240} + \frac{K_1^*}{s + 70 + j240} \end{aligned}$$

$$K_1 = \frac{9600}{j480} = -j20 = 20 \angle -90^\circ$$

Therefore

$$v_o(t) = [40e^{-70t} \cos(240t - 90^\circ)]u(t) \text{ V} = [40e^{-70t} \sin 240t]u(t) \text{ V}$$

AP 13.12 From Assessment Problem 13.9:

$$H(s) = \frac{10(s+2)}{s^2 + 2s + 10}$$

$$\text{Therefore } H(j4) = \frac{10(2+j4)}{10 - 16 + j8} = 4.47 \angle -63.43^\circ$$

Thus,

$$v_o = (10)(4.47) \cos(4t - 63.43^\circ) = 44.7 \cos(4t - 63.43^\circ) \text{ V}$$

AP 13.13 [a]

$$\text{Let } R_1 = 10 \text{ k}\Omega, \quad R_2 = 50 \text{ k}\Omega, \quad C = 400 \text{ pF}, \quad R_2C = 2 \times 10^{-5}$$

$$\text{then } V_1 = V_2 = \frac{V_g R_2}{R_2 + (1/sC)}$$

$$\text{Also } \frac{V_1 - V_g}{R_1} + \frac{V_1 - V_o}{R_1} = 0$$

$$\text{therefore } V_o = 2V_1 - V_g$$

$$\text{Now solving for } V_o/V_g, \text{ we get } H(s) = \frac{R_2Cs - 1}{R_2Cs + 1}$$

It follows that  $H(j50,000) = \frac{j-1}{j+1} = j1 = 1\angle 90^\circ$

Therefore  $v_o = 10 \cos(50,000t + 90^\circ) \text{ V}$

[b] Replacing  $R_2$  by  $R_x$  gives us  $H(s) = \frac{R_x C s - 1}{R_x C s + 1}$

Therefore

$$H(j50,000) = \frac{j20 \times 10^{-6} R_x - 1}{j20 \times 10^{-6} R_x + 1} = \frac{R_x + j50,000}{R_x - j50,000}$$

Thus,

$$\frac{50,000}{R_x} = \tan 60^\circ = 1.7321, \quad R_x = 28,867.51 \, \Omega$$



## Problems

$$\text{P 13.1} \quad I_{scab} = I_N = \frac{-LI_0}{sL} = \frac{-I_0}{s}; \quad Z_N = sL$$

Therefore, the Norton equivalent is the same as the circuit in Fig. 13.4.

$$\text{P 13.2} \quad i = \frac{1}{L} \int_{0^-}^t v d\tau + I_0; \quad \text{therefore} \quad I = \left(\frac{1}{L}\right) \left(\frac{V}{s}\right) + \frac{I_0}{s} = \frac{V}{sL} + \frac{I_0}{s}$$

$$\text{P 13.3} \quad V_{Th} = V_{ab} = CV_o \left(\frac{1}{sC}\right) = \frac{V_o}{s}; \quad Z_{Th} = \frac{1}{sC}$$

$$\begin{aligned} \text{P 13.4} \quad [\text{a}] \quad Z &= R + sL + \frac{1}{sC} = \frac{L[s^2 + (R/L)s + (1/LC)]}{s} \\ &= \frac{5[s^2 + 2000s + 10^7]}{s} \end{aligned}$$

$$[\text{b}] \quad s_{1,2} = -1000 \pm \sqrt{10^6 - 10^7} = -1000 \pm j3000 \text{ rad/s}$$


Zeros at  $-1000 + j3000 \text{ rad/s}$  and  $-1000 - j3000 \text{ rad/s}$   
Pole at 0.

$$\begin{aligned} \text{P 13.5} \quad [\text{a}] \quad Y &= \frac{1}{R} + \frac{1}{sL} + sC = \frac{C[s^2 + (1/RC)s + (1/LC)]}{s} \\ Z &= \frac{1}{Y} = \frac{s/C}{s^2 + (1/RC)s + (1/LC)} = \frac{25 \times 10^6 s}{s^2 + 5000s + 4 \times 10^6} \end{aligned}$$

$$[\text{b}] \quad \text{zero at } z_1 = 0$$

poles at  $-p_1 = -1000 \text{ rad/s}$  and  $-p_2 = -4000 \text{ rad/s}$

$$\text{P 13.6} \quad [\text{a}]$$

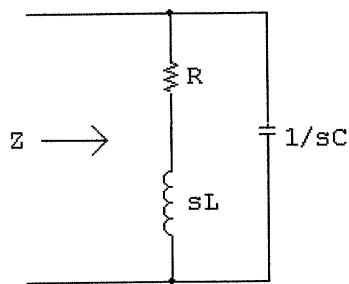

$$Z = \frac{(R + sL)(1/sC)}{R + sL + (1/sC)} = \frac{(1/C)(s + R/L)}{s^2 + (R/L)s + (1/LC)}$$

$$\frac{R}{L} = \frac{1000}{0.5} = 2000; \quad \frac{1}{LC} = \frac{10^6}{0.2} = 5 \times 10^6$$

$$Z = \frac{2.5 \times 10^6 (s + 2000)}{s^2 + 2000s + 5 \times 10^6}$$


$$[b] \quad s_{1,2} = -1000 \pm \sqrt{10^6 - 5 \times 10^6} = -1000 \pm j2000$$

$$Z = \frac{2.5 \times 10^6 (s + 2000)}{(s + 1000 - j2000)(s + 1000 + j2000)}$$

$$-z_1 = -2000 \text{ rad/s}; \quad -p_1 = -1000 + j2000 \text{ rad/s}$$

$$-p_2 = -1000 - j2000 \text{ rad/s}$$

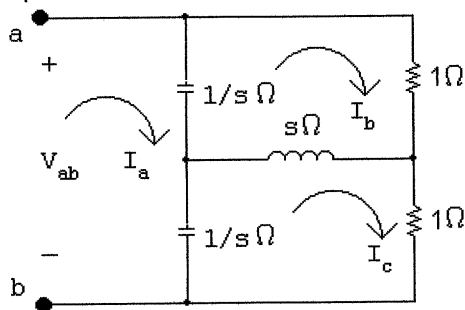P 13.7 Transform the Y-connection of the two resistors and the inductor into the equivalent delta-connection:



where

$$Z_a = \frac{(s)(1) + (1)(s) + (1)(1)}{s} = \frac{2s + 1}{s}$$

$$Z_b = Z_c = \frac{(s)(1) + (1)(s) + (1)(1)}{1} = 2s + 1$$

Then

$$Z_{ab} = Z_a \parallel [(1/s \parallel Z_c) + (1/s \parallel Z_b)] = Z_a \parallel 2(1/s \parallel Z_b)$$

$$1/s \parallel Z_b = \frac{\frac{1}{s}(2s + 1)}{\frac{1}{s} + 2s + 1} = \frac{2s + 1}{2s^2 + s + 1}$$

$$\begin{aligned} Z_{ab} &= \left( \frac{2s + 1}{s} \right) \parallel \frac{2(2s + 1)}{2s^2 + s + 1} \\ &= \frac{2(2s + 1)^2}{(2s + 1)(2s^2 + s + 1) + 2s(2s + 1)} = \frac{2}{s + 1} \end{aligned}$$

No zeros; one pole at  $-1 \text{ rad/s}$ .


$$\text{P 13.8} \quad Z_1 = 0.5s + \frac{2(50/s)}{(2 + 50/s)} = \frac{s^2 + 25s + 100}{2s + 50}$$

$$Y_{ab} = \frac{1}{25} + \frac{2s + 50}{s^2 + 25s + 100} = \frac{s^2 + 75s + 1350}{25(s^2 + 25s + 100)}$$

$$Z_{ab} = \frac{25(s^2 + 25s + 100)}{s^2 + 75s + 1350} = \frac{25(s + 5)(s + 20)}{(s + 30)(s + 45)}$$

Zeros at  $-5$  rad/s and  $-20$  rad/s; poles at  $-30$  rad/s and  $-45$  rad/s.

P 13.9 [a] For  $t > 0$ :

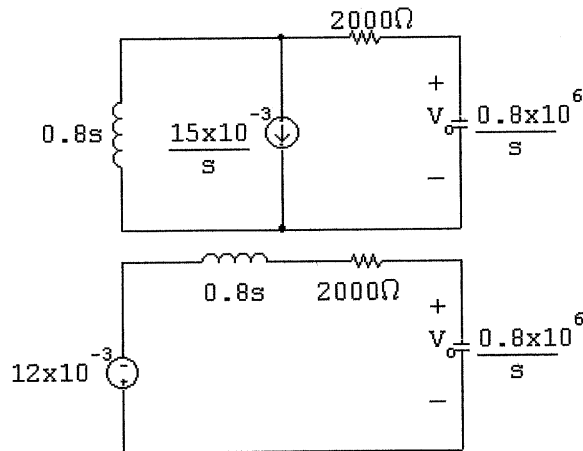

$$\begin{aligned} \text{[b]} \quad V_o &= \frac{-12 \times 10^{-3}(0.8/s) \times 10^6}{0.8s + 2000 + (0.8 \times 10^6)/s} \\ &= \frac{-9600}{0.8s^2 + 2000s + 0.8 \times 10^6} \\ &= \frac{-12,000}{s^2 + 2500s + 10^6} \end{aligned}$$


$$\text{[c]} \quad V_o = \frac{-12,000}{(s + 500)(s + 2000)} = \frac{K_1}{s + 500} + \frac{K_2}{s + 2000}$$

$$K_1 = -8; \quad K_2 = 8$$

$$V_o = \frac{-8}{s + 500} + \frac{8}{s + 2000}$$

$$v_o(t) = (-8e^{-500t} + 8e^{-2000t})u(t) \text{ V}$$

P 13.10 [a] For  $t < 0$ :

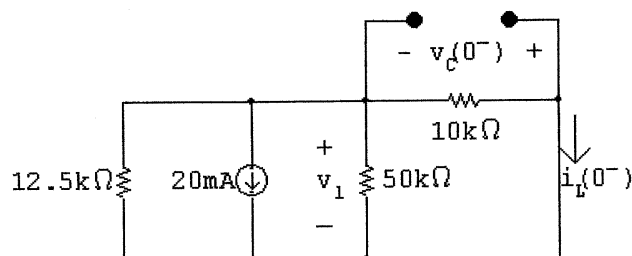


$$\frac{1}{R_e} = \frac{1}{12.5} + \frac{1}{50} + \frac{1}{10} = \frac{1}{5}; \quad R_e = 5 \text{ k}\Omega$$

$$v_1 = -20(5) = -100 \text{ V}$$


$$i_L(0^-) = \frac{-100}{10} \times 10^{-3} = -10 \text{ mA}$$

$$v_C(0^-) = -v_1 = 100 \text{ V}$$

For  $t = 0^+$ :

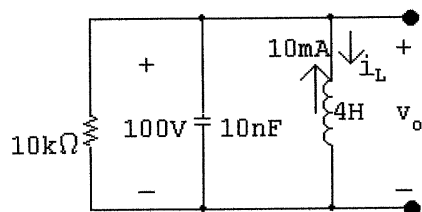

$s$ -domain circuit:

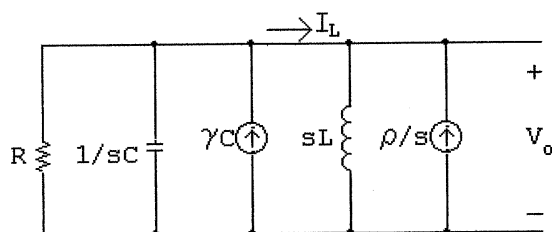

where

$$R = 10 \text{ k}\Omega; \quad C = 10 \text{ nF}; \quad \gamma = 100 \text{ V};$$

$$L = 4 \text{ H}; \quad \text{and} \quad \rho = 10 \text{ mA}$$

[b]  $\frac{V_o}{R} + V_o s C - \gamma C + \frac{V_o}{s L} - \frac{\rho}{s} = 0$

$$\therefore V_o = \frac{\gamma[s + (\rho/\gamma C)]}{s^2 + (1/RC)s + (1/LC)}$$

$$\frac{\rho}{\gamma C} = \frac{10 \times 10^{-3}}{(100)(10)10^{-9}} = 10^4$$

$$\frac{1}{RC} = \frac{10^9}{10^5} = 10^4$$

$$\frac{1}{LC} = \frac{10^9}{40} = 25 \times 10^6$$

$$V_o = \frac{100(s + 10^4)}{s^2 + 10^4s + 25 \times 10^6}$$

$$[c] \quad I_L = \frac{V_o}{sL} - \frac{\rho}{s} = \frac{V_o}{4s} - \frac{10 \times 10^{-3}}{s}$$

$$I_L = \frac{25(s + 10^4)}{s(s^2 + 10^4s + 25 \times 10^6)} - \frac{10^{-2}}{s} = \frac{-0.01(s + 7500)}{(s + 5000)^2}$$

$$[d] \quad V_o = \frac{100(s + 10^4)}{s^2 + 10^4s + 25 \times 10^6}$$

$$= \frac{100(s + 10^4)}{(s + 5000)^2} = \frac{K_1}{(s + 5000)^2} + \frac{K_2}{s + 5000}$$

$$K_1 = 100(5000) = 5 \times 10^5$$

$$K_2 = \frac{d}{ds} [100(s + 10,000)]_{s=-5000} = 100$$

$$V_o = \frac{5 \times 10^5}{(s + 5000)^2} + \frac{100}{s + 5000}$$

$$v_o = [5 \times 10^5 t e^{-5000t} + 100 e^{-5000t}] u(t) \text{ V}$$

$$[e] \quad I_L = \frac{-0.01(s + 7500)}{(s + 5000)^2}$$


$$= \frac{K_1}{(s + 5000)^2} + \frac{K_2}{(s + 5000)}$$

$$K_1 = -0.01(2500) = -25$$

$$K_2 = \frac{d}{ds} [-0.01(s + 7500)]_{s=-5000} = -0.01$$


$$I_L = \left[ \frac{-25,000}{(s + 5000)^2} - \frac{10}{s + 5000} \right] \times 10^{-3}$$

$$i_L = -[25,000t + 10] e^{-5000t} u(t) \text{ mA}$$

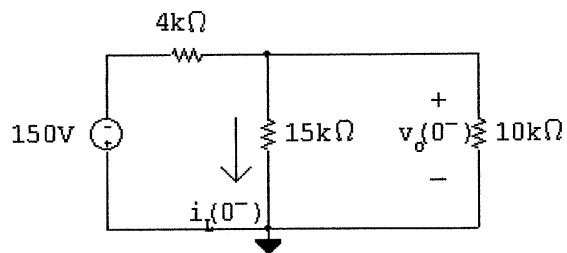P 13.11 For  $t < 0$ :

$$\frac{v_o(0^-) + 150}{4000} + \frac{v_o(0^-)}{15,000} + \frac{v_o(0^-)}{10,000} = 0$$

$$\therefore v_o(0^-) = -90 \text{ V}; \quad \therefore i_L(0^-) = -6 \text{ mA}$$

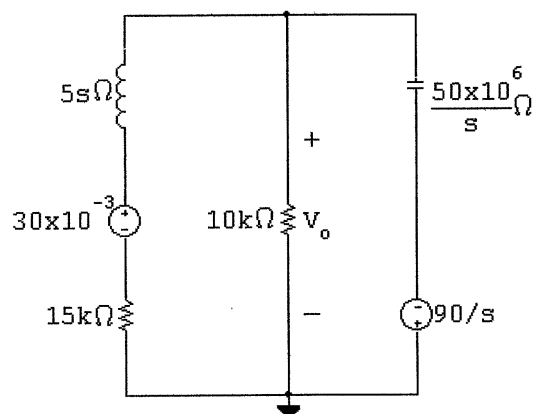For  $t > 0$ :

$$\frac{V_o - 30 \times 10^{-3}}{5s + 15,000} + \frac{V_o}{10^4} + \frac{(V_o + 90/s)s}{50 \times 10^6} = 0$$


$$V_o = \frac{30(1000 - 3s)}{s^2 + 8000s + 25 \times 10^6}$$

$$= \frac{30(1000 - 3s)}{(s + 4000 - j3000)(s + 4000 + j3000)}$$

$$K_1 = \frac{30(1000 + 12,000 - j9000)}{j6000} = 79.06 / -124.70^\circ \text{ V}$$


$$v_o(t) = 158.11e^{-4000t} \cos(3000t - 124.70^\circ)u(t) \text{ V}$$

$$\text{Check: } v_o(0) = 158.11 \cos(-124.70^\circ) = -90 \text{ V}$$

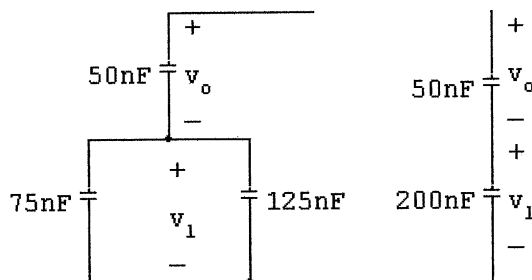P 13.12 [a] For  $t > 0$ :

$$v_1 = 75 - v_o; \quad 50v_o = 200(75 - v_o);$$
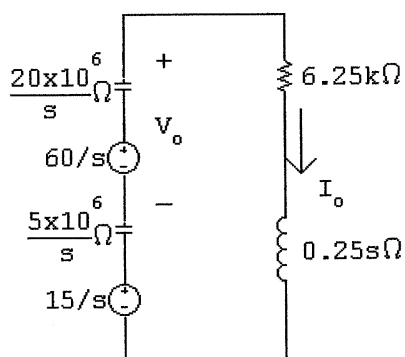
$$\therefore v_o = 60 \text{ V}; \quad v_1 = 15 \text{ V}$$




$$\begin{aligned} \text{[b]} \quad I_o &= \frac{75/s}{(25 \times 10^6/s) + 6250 + 0.25s} = \frac{300}{s^2 + 25,000s + 10^8} \\ &= \frac{300}{(s + 5000)(s + 20,000)} = \frac{20 \times 10^{-3}}{s + 5000} - \frac{20 \times 10^{-3}}{s + 20,000} \end{aligned}$$

$$i_o(t) = (20e^{-5000t} - 20e^{-20,000t})u(t) \text{ mA}$$

$$\begin{aligned} \text{[c]} \quad V_o &= \frac{60}{s} - \frac{20 \times 10^6}{s} \cdot \frac{300}{(s + 5000)(s + 20,000)} \\ &= \frac{60}{s} - \left[ \frac{60}{s} - \frac{80}{s + 5000} + \frac{20}{s + 20,000} \right] \\ &= \frac{80}{s + 5000} + \frac{-20}{s + 20,000} \end{aligned}$$

$$v_o(t) = (80e^{-5000t} - 20e^{-20,000t})u(t) \text{ V}$$

P 13.13 [a] For  $t < 0$ :

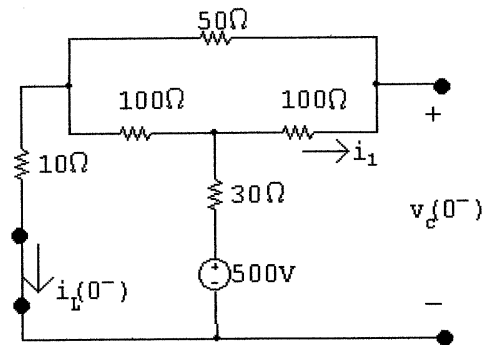


$$i_L(0^-) = \frac{500}{30 + 60 + 10} = 5 \text{ A}$$

$$i_1 = \frac{5(100)}{250} = 2 \text{ A}$$

$$v_C(0^-) = 500 - 5(30) - 2(100) = 500 - 350 = 150 \text{ V}$$

For  $t > 0$ :

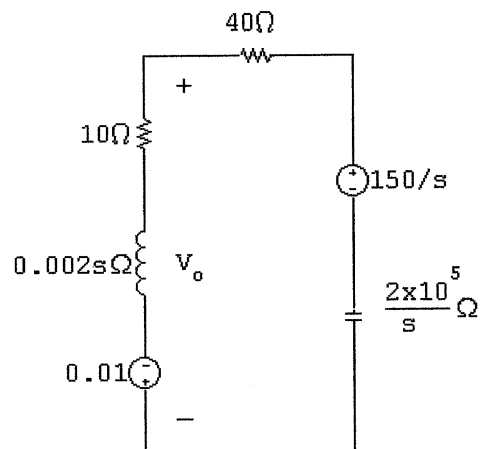

$$[b] \frac{V_o + 0.01}{10 + 0.002s} + \frac{V_o - 150/s}{40 + 2 \times 10^5/s} = 0$$

$$V_o \left[ \frac{1}{10 + 0.002s} + \frac{s}{40s + 2 \times 10^5} \right] = \frac{150}{40s + 2 \times 10^5} - \frac{0.01}{10 + 0.002s}$$

$$V_o = \frac{-50(s + 5000)}{s^2 + 25,000s + 10^8} = \frac{-50(s + 5000)}{(s + 5000)(s + 20,000)}$$


$$V_o = \frac{-50}{s + 20,000}$$

$$[c] v_o(t) = -50e^{-20,000t}u(t) \text{ V}$$



P 13.14 [a]  $i_L(0^-) = i_L(0^+) = 5 \text{ A}$ , down

$$v_C(0^-) = v_C(0^+) = 0$$

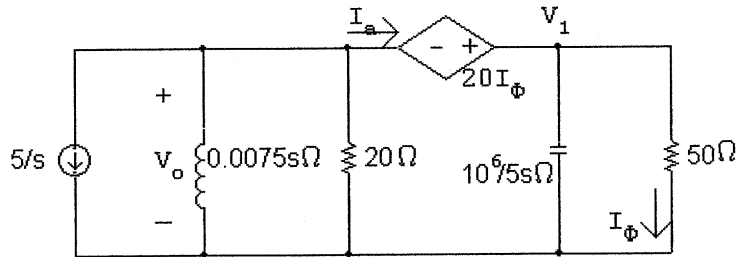

$$\frac{V_o}{20} + \frac{V_o}{0.0075s} + I_a = \frac{-5}{s}$$

$$I_a = \frac{V_1(5s)}{10^6} + \frac{V_1}{50} = \left( \frac{250s + 10^6}{50 \times 10^6} \right) V_1$$

$$V_o + 20I_\phi = V_1; \quad V_o + 20\frac{V_1}{50} = V_1; \quad \therefore 0.6V_1 = V_o$$

$$\therefore \frac{V_o}{20} + \frac{V_o}{0.0075s} + \frac{250s + 10^6}{30 \times 10^6} V_o = \frac{-5}{s}$$

$$\therefore (s^2 + 10,000s + 16 \times 10^6)V_o = -6 \times 10^5$$

$$V_o = \frac{-6 \times 10^5}{s^2 + 10,000s + 16 \times 10^6}$$


$$[b] V_o = \frac{-6 \times 10^5}{(s + 2000)(s + 8000)} = \frac{K_1}{(s + 8000)} + \frac{K_2}{(s + 2000)}$$

$$K_1 = \frac{-6 \times 10^5}{-6000} = 100$$

$$K_2 = \frac{-6 \times 10^5}{6000} = -100$$

$$v_o(t) = [100e^{-8000t} - 100e^{-2000t}]u(t) \text{ V}$$

P 13.15 [a]

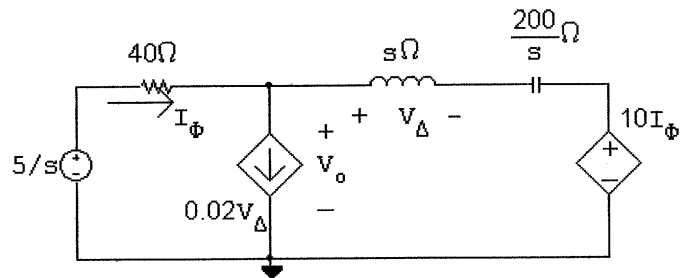

$$\frac{V_o - 5/s}{40} + 0.02V_\Delta + \frac{V_o - 10I_\phi}{s + (200/s)} = 0$$

$$V_{\Delta} = \left[ \frac{V_o - 10I_{\phi}}{s + (200/s)} \right] s; \quad I_{\phi} = \frac{(5/s) - V_o}{40}$$

Solving for  $V_o$  yields:

$$V_o = \frac{3s^2 + 25s + 500}{s(s^2 + 25s + 100)} = \frac{3s^2 + 25s + 500}{s(s+5)(s+20)}$$

$$V_o = \frac{K_1}{s} + \frac{K_2}{s+5} + \frac{K_3}{s+20}$$

$$K_1 = \left. \frac{3s^2 + 25s + 500}{(s+5)(s+20)} \right|_{s=0} = 5$$


$$K_2 = \left. \frac{3s^2 + 25s + 500}{s(s+20)} \right|_{s=-5} = -6$$

$$K_3 = \left. \frac{3s^2 + 25s + 500}{s(s+5)} \right|_{s=-20} = 4$$

$$\therefore V_o = \frac{5}{s} + \frac{-6}{s+5} + \frac{4}{s+20}$$

$$\therefore v_o(t) = [5 - 6e^{-5t} + 4e^{-20t}]u(t) \text{ V}$$

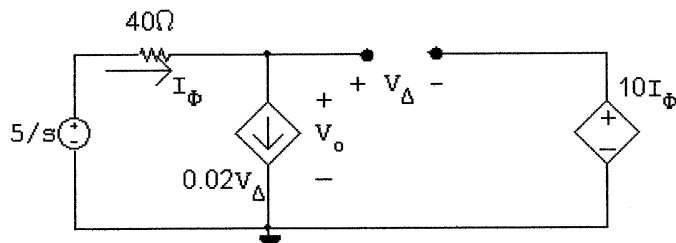[b] At  $t = 0^+$   $v_o = 5 - 6 + 4 = 3 \text{ V}$



$$v_o = v_{\Delta} + 10i_{\phi}$$

$$i_{\phi} = \frac{5 - v_o}{40}$$

$$\therefore v_o = v_{\Delta} + 10 \frac{(5 - v_o)}{40} = v_{\Delta} + 1.25 - 0.25v_o$$


$$\therefore 1.25v_o - 1.25 = v_{\Delta}$$

$$\frac{v_o - 5}{40} + 0.02v_{\Delta} = 0$$

$$v_o = 5 + 0.8v_{\Delta} = 0$$

$$v_o - 5 + v_o - 1 = 0 \quad \text{so} \quad v_o = 3 \text{ V (checks)}$$


At  $t = \infty$ , the circuit is

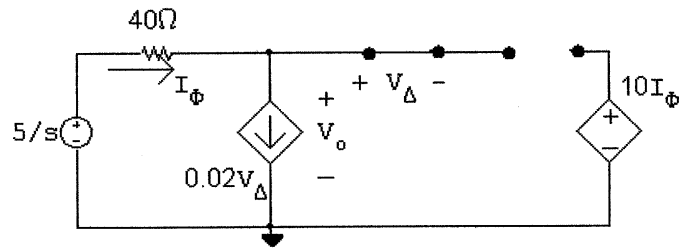

From the equation for  $v_o(t)$ ,  $v_o(\infty) = 5$  V. From the circuit,

$$v_{\Delta} = 0, \quad i_{\phi} = 0 \quad \therefore v_o = 5 \text{ V (checks)}$$


P 13.16 [a] For  $t < 0$ :

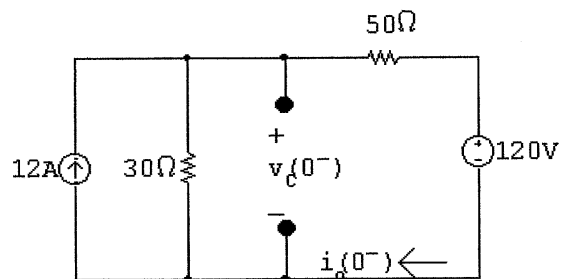

$$-12 + \frac{v_C(0^-)}{30} + \frac{v_C(0^-) - 120}{50} = 0$$

$$8v_C(0^-) = 2160; \quad \therefore v_C(0^-) = 270 \text{ V}$$

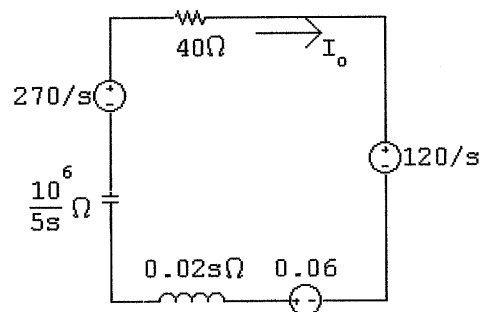
$$i_o(0^-) = \frac{270 - 120}{50} = 3 \text{ A}$$



$$\begin{aligned}
 \text{[b]} \quad I_o &= \frac{(270/s) + 0.06 - (120/s)}{40 + 0.02s + (10^6/5s)} \\
 &= \frac{3(s + 2500)}{s^2 + 2000s + 10^7} \\
 &= \frac{3(s + 2500)}{(s + 1000 - j3000)(s + 1000 + j3000)} \\
 K_1 &= \frac{3(1500 + j3000)}{j6000} = 0.75\sqrt{5}/-26.57^\circ
 \end{aligned}$$

$$\text{[c]} \quad i_o(t) = 3.35e^{-1000t} \cos(3000t - 26.57^\circ)u(t) \text{ A}$$

P 13.17

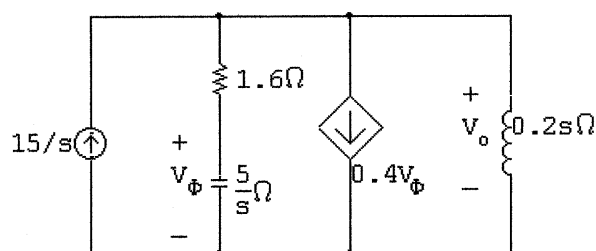

$$\frac{15}{s} = \frac{V_o}{1.6 + 5/s} + 0.4V_\phi + \frac{V_o}{0.2s}$$

$$V_\phi = \frac{5/s}{1.6 + 5/s} V_o = \frac{5V_o}{1.6s + 5}$$

$$\begin{aligned}
 \therefore \frac{15}{s} &= \frac{V_o s}{1.6s + 5} + \frac{2V_o}{1.6s + 5} + \frac{5V_o}{s} \\
 &= V_o \left[ \frac{s(s + 2) + 5(1.6s + 5)}{s(1.6s + 5)} \right]
 \end{aligned}$$

$$15(1.6s + 5) = V_o(s^2 + 10s + 25)$$

$$\therefore V_o = \frac{15(1.6s + 5)}{(s + 5)^2} = \frac{K_1}{(s + 5)^2} + \frac{K_2}{s + 5}$$

$$K_1 = 15(-8 + 5) = -45; \quad K_2 = 24$$


$$V_o = \frac{-45}{(s + 5)^2} + \frac{24}{s + 5}$$

$$v_o(t) = [-45te^{-5t} + 24e^{-5t}]u(t) \text{ V}$$



P 13.18  $v_C(0^-) = v_C(0^+) = 0$

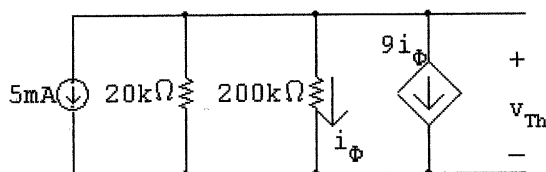
Find the Thévenin equivalent with respect to the capacitor:



$$\frac{v_{Th}}{20,000} + \frac{v_{Th}}{200,000} + \frac{9v_{Th}}{200,000} = -0.005$$

$$\therefore v_{Th} = -50 \text{ V}$$

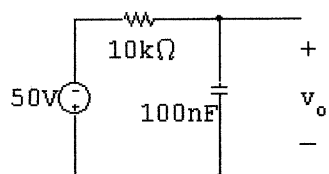
$$i_{sc} = -5 \text{ mA}; \quad \therefore R_{Th} = 10 \text{ k}\Omega$$



$$\begin{aligned} V_o &= \frac{-50/s}{10,000 + (10^7/s)} \cdot \frac{10^7}{s} \\ &= \frac{-50 \times 10^3}{s(s + 1000)} = \frac{-50}{s} + \frac{50}{s + 1000} \end{aligned}$$

$$v_o(t) = [-50 + 50e^{-1000t}]u(t) \text{ V}$$

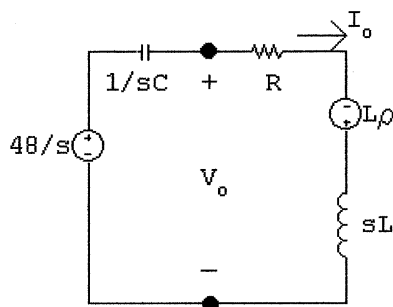P 13.19 [a]  $i_o(0^-) = \frac{48}{4} \times 10^{-3} = 12 \text{ mA} = \rho$



$$\frac{V_o - 48/s}{(1/sC)} + \frac{V_o + \rho L}{R + sL} = 0$$

$$\therefore V_o = \frac{48(s + R/L) - \rho/C}{s^2 + (R/L)s + (1/LC)}$$

When the numerical values are substituted we get

$$V_o = \frac{48(s + 4875)}{(s + 4000 - j3000)(s + 4000 + j3000)}$$

$$K_1 = \frac{48(875 + j3000)}{j6000} = 25 \angle -16.26^\circ$$

$$v_o(t) = 50e^{-4000t} \cos(3000t - 16.26^\circ)u(t) \text{ V}$$

Check:  $v_o(0^+) = 50 \cos(-16.26^\circ) = 48 \text{ V}$ , which agrees with the fact that the initial capacitor voltage is zero.


$$[b] I_o = \frac{48/s + \rho L}{R + sL + (1/sC)} = \frac{\rho[s + (48/\rho L)]}{s^2 + (R/L)s + (1/LC)}$$

$$I_o = \frac{12 \times 10^{-3}(s + 8000)}{(s + 4000 - j3000)(s + 4000 + j3000)}$$

$$K_1 = \frac{12 \times 10^{-3}(4000 + j3000)}{j6000} = 10 \times 10^{-3} \angle -53.13^\circ$$

$$i_o(t) = 20e^{-4000t} \cos(3000t - 53.13^\circ)u(t) \text{ mA}$$

P 13.20

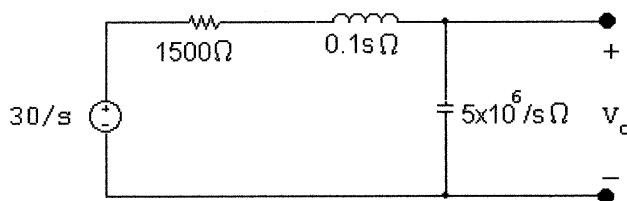

$$\begin{aligned} V_o &= \frac{(30/s)(5 \times 10^6/s)}{1500 + 0.1s + (5 \times 10^6/s)} \\ &= \frac{1500 \times 10^6}{s(s^2 + 15,000s + 50 \times 10^6)} \\ &= \frac{1500 \times 10^6}{s(s + 5000)(s + 10,000)} \\ &= \frac{K_1}{s} + \frac{K_2}{s + 5000} + \frac{K_3}{s + 10,000} \end{aligned}$$

$$K_1 = \frac{1500 \times 10^6}{(5000)(10,000)} = 30$$

$$K_2 = \frac{1500 \times 10^6}{(-5000)(5000)} = -60$$

$$K_3 = \frac{1500 \times 10^6}{(-5000)(-10,000)} = 30$$


$$V_o = \frac{30}{s} - \frac{60}{s + 5000} + \frac{30}{s + 10,000}$$

$$v_o(t) = [30 - 60e^{-5000t} + 30e^{-10,000t}]u(t) \text{ V}$$

P 13.21 Since we already have the solution for  $v_o(t)$  when the initial voltage is zero, we will use superposition to determine the contribution of the initial voltage of  $-20 \text{ V}$ .

$V_{o1}$  = output when  $\gamma = 0$

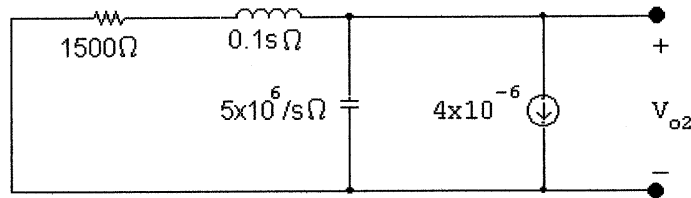$V_{o2}$  = output when  $\gamma = -20 \text{ V}$



$$4 \times 10^{-6} + \frac{V_{o2}s}{5 \times 10^6} + \frac{V_{o2}}{1500 + 0.1s} = 0$$

$$\begin{aligned} \therefore V_{o2} &= \frac{-20(s + 15,000)}{s^2 + 15,000s + 50 \times 10^6} \\ &= \frac{K_1}{s + 5000} + \frac{K_2}{s + 10,000} \end{aligned}$$

$$K_1 = \frac{-20(10,000)}{5000} = -40$$

$$K_2 = \frac{-20(5000)}{-5000} = 20$$

$$V_{o2} = \frac{-40}{s + 5000} + \frac{20}{s + 10,000}$$



From the solution to Problem 13.20 we have


$$V_{o1} = \frac{30}{s} - \frac{60}{s+5000} + \frac{30}{s+10,000}$$

$$V_o = V_{o1} + V_{o2}$$

$$\therefore V_o = \frac{30}{s} - \frac{100}{s+5000} + \frac{50}{s+10,000}$$

$$v_o(t) = [30 - 100e^{-5000t} + 50e^{-10,000t}]u(t) \text{ V}$$

P 13.22 [a]

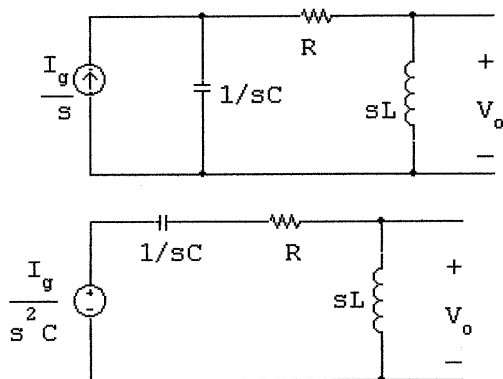

$$V_o = \frac{(I_g/s^2 C)(sL)}{R + sL + (1/sC)} = \frac{I_g/C}{s^2 + (R/L)s + (1/LC)}$$

$$\frac{I_g}{C} = \frac{9.6 \times 10^{-3}}{3.2 \times 10^{-9}} = 3000 \times 10^3 = 3 \times 10^6$$

$$\frac{R}{L} = \frac{7000}{0.5} = 14,000; \quad \frac{1}{LC} = \frac{2}{3.2} \times 10^9 = 625 \times 10^6$$

$$V_o = \frac{3 \times 10^6}{s^2 + 14,000s + 625 \times 10^6}$$

$$[b] \quad sV_o = \frac{3 \times 10^6 s}{s^2 + 14,000s + 625 \times 10^6}$$

$$\lim_{s \rightarrow 0} sV_o = 0; \quad \therefore v_o(\infty) = 0$$

$$\lim_{s \rightarrow \infty} sV_o = 0; \quad \therefore v_o(0^+) = 0$$

$$[c] \quad s_{1,2} = -7000 \pm \sqrt{49 \times 10^6 - 625 \times 10^6} = -7000 \pm j24,000 \text{ rad/s}$$

$$V_o = \frac{3,000,000}{(s + 7000 - j24,000)(s + 7000 + j24,000)}$$

$$K_1 = \frac{3 \times 10^6}{j48,000} = -j62.5 = 62.5 \angle -90^\circ$$

$$v_o = 125e^{-7000t} \cos(24,000t - 90^\circ) = [125e^{-7000t} \sin 24,000t]u(t) \text{ V}$$

$$\text{P 13.23} \quad I_C = \frac{I_g}{s} - \frac{V_o}{sL}$$

$$\begin{aligned} &= \frac{9.6 \times 10^{-3}}{s} - \frac{2}{s} \left[ \frac{3 \times 10^6}{(s + 7000 - j24,000)(s + 7000 + j24,000)} \right] \\ &= \frac{9.6 \times 10^{-3}}{s} - \frac{6 \times 10^6}{s(s + 7000 - j24,000)(s + 7000 + j24,000)} \\ &= \frac{9.6 \times 10^{-3}}{s} - \frac{K_1}{s} - \frac{K_2}{s + 7000 - j24,000} - \frac{K_2^*}{s + 7000 + j24,000} \end{aligned}$$

$$K_1 = \frac{6 \times 10^6}{625 \times 10^6} = 9.6 \times 10^{-3}$$

$$\begin{aligned} K_2 &= \frac{6 \times 10^6}{(-7000 + j24,000)(j48,000)} \\ &= \frac{6}{(-7 + j24)(j48)} = 5 \times 10^{-3} \angle 163.74^\circ \end{aligned}$$

$$\begin{aligned} \therefore I_C &= \frac{9.6 \times 10^{-3}}{s} - \frac{9.6 \times 10^{-3}}{s} - [\text{conjugate terms}] \\ &= \left[ \frac{-5 \angle 163.74^\circ}{s + 7000 - j24,000} + \text{conjugate} \right] \times 10^{-3} \\ &= \left[ \frac{5 \angle -16.26^\circ}{s + 7000 - j24,000} + \text{conjugate} \right] \times 10^{-3} \end{aligned}$$


$$i_C = 10e^{-7000t} \cos(24,000t - 16.26^\circ)u(t) \text{ mA}$$

Check:

$$i_C(0^+) = 10 \cos(-16.26^\circ) = 9.6 \text{ mA} \quad (\text{ok})$$


$$i_C(\infty) = 0 \quad (\text{ok})$$

P 13.24 [a]

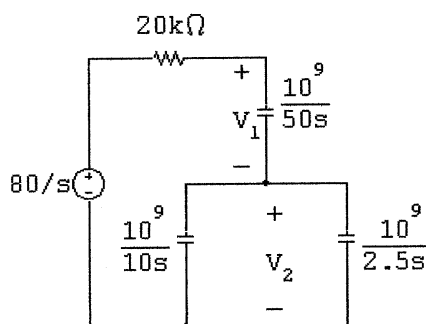

$$Y_e = \frac{10s}{10^9} + \frac{2.5s}{10^9} = \frac{12.5s}{10^9}$$
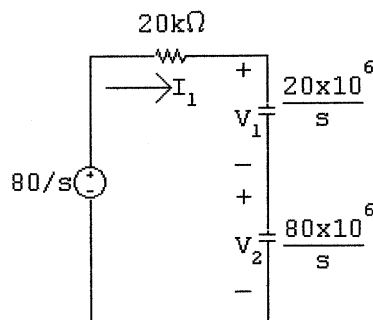
$$Z_e = \frac{10^9}{12.5s} = \frac{80 \times 10^6}{s}$$



$$[b] \quad I_1 = \frac{80/s}{20,000 + (100 \times 10^6/s)} = \frac{4 \times 10^{-3}}{s + 5000}$$

$$V_1 = \frac{4 \times 10^{-3}}{s + 5000} \cdot \frac{20 \times 10^6}{s} = \frac{80,000}{s(s + 5000)}$$

$$V_2 = \frac{4 \times 10^{-3}}{s + 5000} \cdot \frac{80 \times 10^6}{s} = \frac{320,000}{s(s + 5000)}$$

$$[c] \quad i_1(t) = 4e^{-5000t}u(t) \text{ mA}$$

$$V_1 = \frac{16}{s} - \frac{16}{s + 5000}; \quad v_1(t) = (16 - 16e^{-5000t})u(t) \text{ V}$$

$$V_2 = \frac{64}{s} - \frac{64}{s + 5000}; \quad v_2(t) = (64 - 64e^{-5000t})u(t) \text{ V}$$

$$[d] \quad i_1(0^+) = 4 \text{ mA}$$

$$i_1(0^+) = \frac{80}{20} \times 10^{-3} = 4 \text{ mA (checks)}$$

$$v_1(0^+) = 0; \quad v_2(0^+) = 0 \text{ (checks)}$$


$$v_1(\infty) = 16 \text{ V}; \quad v_2(\infty) = 64 \text{ V (checks)}$$

$$v_1(\infty) + v_2(\infty) = 80 \text{ V (checks)}$$

$$(50 \times 10^{-9})v_1(\infty) = 800 \text{ nC}$$

$$(12.5 \times 10^{-9})v_2(\infty) = 800 \text{ nC (checks)}$$

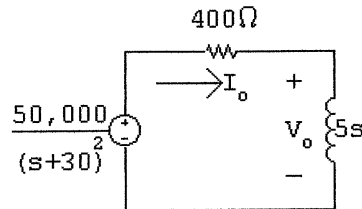P 13.25 [a]  $V_g = \frac{50,000}{(s+30)^2}$



$$I_o = \frac{50,000}{(s+30)^2(5s+400)} = \frac{10,000}{(s+30)^2(s+80)}$$

$$V_o = 5sI_o = \frac{50,000s}{(s+30)^2(s+80)}$$

[b]  $I_o = \frac{K_1}{(s+30)^2} + \frac{K_2}{s+30} + \frac{K_3}{s+80}$

$$K_1 = \frac{10,000}{50} = 200$$

$$K_2 = \frac{d}{ds} \left[ \frac{10,000}{s+80} \right]_{s=-30} = -4$$

$$K_3 = \frac{10,000}{(-50)^2} = 4$$

$$I_o = \frac{200}{(s+30)^2} - \frac{4}{s+30} + \frac{4}{s+80}$$

$$i_o(t) = [200te^{-30t} - 4e^{-30t} + 4e^{-80t}]u(t) \text{ A}$$

$$V_o = \frac{K_1}{(s+30)^2} + \frac{K_2}{s+30} + \frac{K_3}{s+80}$$


$$K_1 = \frac{50,000(-30)}{50} = -30,000$$

$$K_2 = \frac{d}{ds} \left[ \frac{50,000s}{s+80} \right]_{s=-30} = 1600$$

$$K_3 = \frac{50,000(-80)}{(-50)^2} = -1600$$

$$v_o(t) = [-30,000te^{-30t} + 1600e^{-30t} - 1600e^{-80t}]u(t) \text{ V}$$

P 13.26 [a]

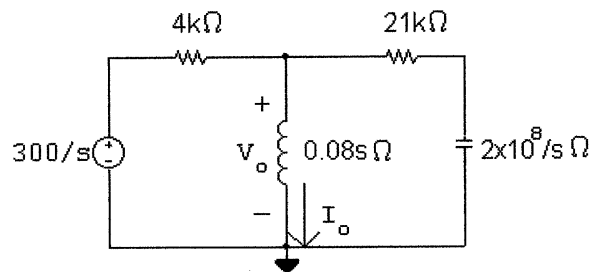

$$\frac{V_o - 300/s}{4000} + \frac{12.5V_o}{s} + \frac{V_o s}{21,000s + 2 \times 10^8} = 0$$

$$\therefore V_o = \frac{12(21s + 20 \times 10^4)}{(s + 10,000)(s + 40,000)} = \frac{K_1}{s + 10,000} + \frac{K_2}{s + 40,000}$$

$$K_1 = -4; \quad K_2 = 256$$

$$V_o = \frac{-4}{s + 10,000} + \frac{256}{s + 40,000}$$


$$v_o(t) = (256e^{-40,000t} - 4e^{-10,000t})u(t) \text{ V}$$

$$[b] \quad I_o = \frac{V_o}{0.08s} = \frac{12.5V_o}{s}$$

$$I_o = \frac{150(21s + 20 \times 10^4)}{s(s + 10,000)(s + 40,000)} = \frac{K_1}{s} + \frac{K_2}{s + 10,000} + \frac{K_3}{s + 40,000}$$

$$K_1 = 75 \times 10^{-3}; \quad K_2 = 5 \times 10^{-3}; \quad K_3 = -80 \times 10^{-3}$$


$$i_o(t) = (75 + 5e^{-10,000t} - 80e^{-40,000t})u(t) \text{ mA}$$

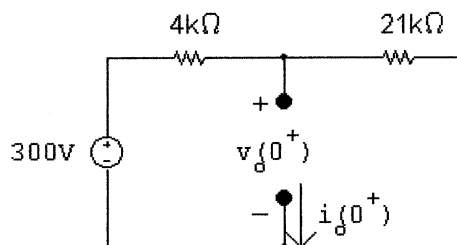[c] At  $t = 0^+$  the circuit is

$$\therefore v_o(0^+) = \frac{300}{25}(21) = 252 \text{ V}; \quad i_o(0^+) = 0$$

Both values agree with our solutions for  $v_o$  and  $i_o$ .


At  $t = \infty$  the circuit is

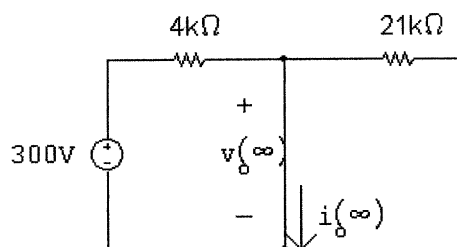

$$\therefore v_o(\infty) = 0; \quad i_o(\infty) = 75 \text{ mA}$$

Both values agree with our solutions for  $v_o$  and  $i_o$ .

P 13.27 [a]

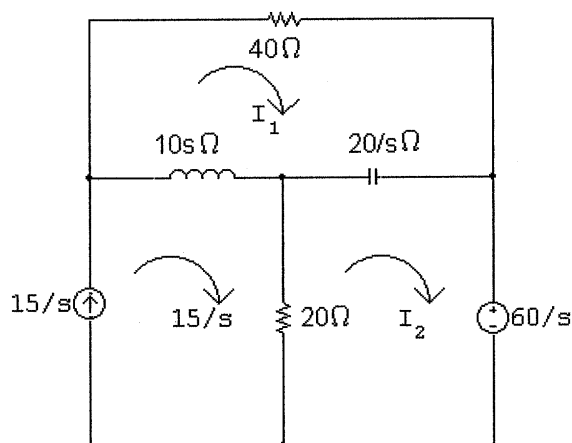

$$40I_1 + \frac{20}{s}(I_1 - I_2) + 10s(I_1 - 15/s) = 0$$

$$20(I_2 - 15/s) + \frac{20}{s}(I_2 - I_1) + \frac{60}{s} = 0$$

or

$$(s^2 + 4s + 2)I_1 - 2I_2 = 15s$$

$$-I_1 + (s + 1)I_2 = 12$$

$$\Delta = \begin{vmatrix} (s^2 + 4s + 2) & -2 \\ -1 & (s + 1) \end{vmatrix} = s(s + 2)(s + 3)$$

$$N_1 = \begin{vmatrix} 15s & -2 \\ 12 & (s + 1) \end{vmatrix} = 15s^2 + 15s + 24$$

$$I_1 = \frac{N_1}{\Delta} = \frac{15s^2 + 15s + 24}{s(s+2)(s+3)}$$

$$N_2 = \begin{vmatrix} (s^2 + 4s + 2) & 15s \\ -1 & 12 \end{vmatrix} = 12s^2 + 63s + 24$$

$$I_2 = \frac{N_2}{\Delta} = \frac{12s^2 + 63s + 24}{s(s+2)(s+3)}$$

$$[b] \quad sI_1 = \frac{15s^2 + 15s + 24}{(s+2)(s+3)}$$

$$\lim_{s \rightarrow \infty} sI_1 = 15 \quad \therefore i_1(0^+) = 15 \text{ A}$$

$$\lim_{s \rightarrow 0} sI_1 = 4 \quad \therefore i_1(\infty) = 4 \text{ A}$$

$$sI_2 = \frac{12s^2 + 63s + 24}{(s+2)(s+3)}$$

$$\lim_{s \rightarrow \infty} sI_2 = 12 \quad \therefore i_2(0^+) = 12 \text{ A}$$

$$\lim_{s \rightarrow 0} sI_2 = 4 \quad \therefore i_2(\infty) = 4 \text{ A}$$


$$[c] \quad I_1 = \frac{4}{s} - \frac{27}{s+2} + \frac{38}{s+3}$$

$$i_1(t) = (4 - 27e^{-2t} + 38e^{-3t})u(t) \text{ A}$$

$$I_2 = \frac{4}{s} + \frac{27}{s+2} - \frac{19}{s+3}$$

$$i_2(t) = (4 + 27e^{-2t} - 19e^{-3t})u(t) \text{ A}$$

P 13.28 [a]

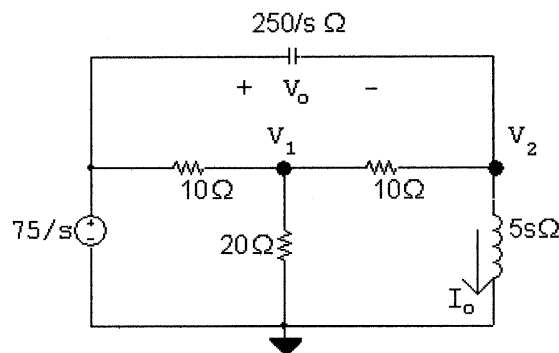

$$\frac{V_1 - 75/s}{10} + \frac{V_1}{20} + \frac{V_1 - V_2}{10} = 0$$

$$\frac{V_2}{5s} + \frac{V_2 - V_1}{10} + \frac{(V_2 - 75/s)s}{250} = 0$$

Thus,

$$5V_1 - 2V_2 = \frac{150}{s}$$

$$-25sV_1 + (s^2 + 25s + 50)V_2 = 75s$$

$$\Delta = \begin{vmatrix} 5 & -2 \\ -25s & s^2 + 25s + 50 \end{vmatrix} = 5(s+5)(s+10)$$

$$N_2 = \begin{vmatrix} 5 & 150/s \\ -25s & 75s \end{vmatrix} = 375(s+10)$$

$$V_2 = \frac{N_2}{\Delta} = \frac{375(s+10)}{5(s+5)(s+10)} = \frac{75}{s+5}$$


$$V_o = \frac{75}{s} - \frac{75}{s+5} = \frac{375}{s(s+5)}$$

$$I_o = \frac{V_2}{5s} = \frac{15}{s(s+5)} = \frac{3}{s} - \frac{3}{s+5}$$

[b]  $v_o(t) = (75 - 75e^{-5t})u(t)$  V

$i_o(t) = (3 - 3e^{-5t})u(t)$  A


[c] At  $t = 0^+$  the circuit is

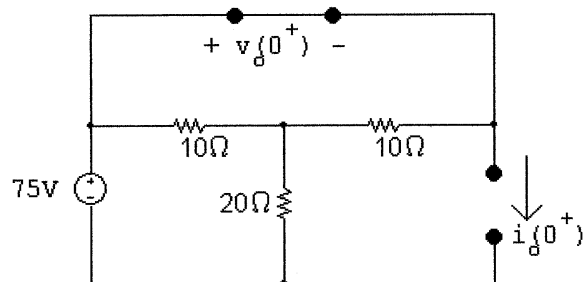

$v_o(0^+) = 0; \quad i_o(0^+) = 0 \quad \text{Checks}$




At  $t = \infty$  the circuit is

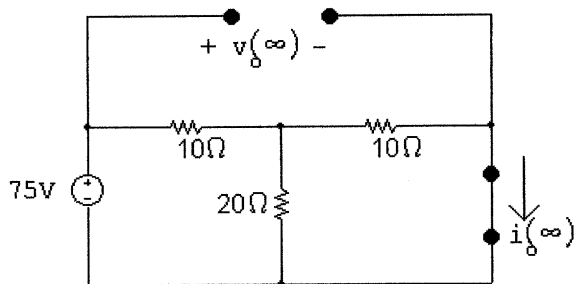

$$v_o(\infty) = 75 \text{ V}; \quad i_o(\infty) = \frac{75}{10 + (200/30)} \cdot \frac{20}{30} = 3 \text{ A} \quad \text{Checks}$$

P 13.29 [a]

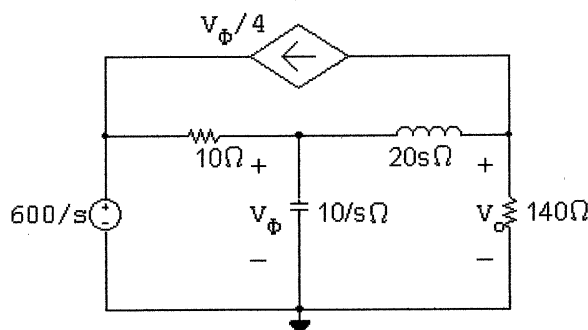

$$\frac{V_\phi}{10/s} + \frac{V_\phi - (600/s)}{10} + \frac{V_\phi - V_o}{20s} = 0$$

$$\frac{V_o}{140} + \frac{V_o - V_\phi}{20s} + \frac{V_\phi}{4} = 0$$

Simplifying,

$$(2s^2 + 2s + 1)V_\phi - V_o = 1200$$

$$(35s - 7)V_\phi + (s + 7)V_o = 0$$

$$\Delta = \begin{vmatrix} 2s^2 + 2s + 1 & -1 \\ 35s - 7 & s + 7 \end{vmatrix} = 2s(s^2 + 8s + 25)$$


$$N_2 = \begin{vmatrix} 2s^2 + 2s + 1 & 1200 \\ 35s - 7 & 0 \end{vmatrix} = -42,000s + 8400$$

$$V_o = \frac{N_2}{\Delta} = \frac{-21,000s + 4200}{s(s^2 + 8s + 25)} = \frac{-4200(5s - 1)}{s(s^2 + 8s + 25)}$$


[b]  $v_o(0^+) = \lim_{s \rightarrow \infty} sV_o = 0$

$$v_o(\infty) = \lim_{s \rightarrow 0} sV_o = \frac{4200}{25} = 168$$

[c] At  $t = 0^+$  the circuit is

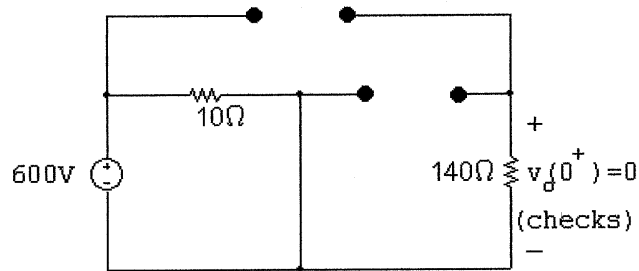

At  $t = \infty$  the circuit is

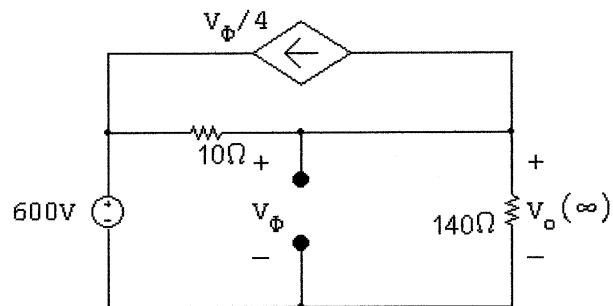

$$\frac{V_\phi - 600}{10} + \frac{V_\phi}{140} + \frac{V_\phi}{4} = 0$$

$$\therefore V_\phi = 168 \text{ V} = V_o(\infty) \quad (\text{checks})$$

$$[d] V_o = \frac{N_2}{\Delta} = \frac{-21,000s + 4200}{s(s^2 + 8s + 25)} = \frac{K_1}{s} + \frac{K_2}{s + 4 - j3} + \frac{K_2^*}{s + 4 + j3}$$


$$K_1 = \frac{4200}{25} = 168$$

$$K_2 = \frac{-21,000(-4 + j3) + 4200}{(-4 + j3)(j6)} = -84 + j3612 = 3612.98 \angle 91.33^\circ$$

$$v_o(t) = [168 + 7225.95e^{-4t} \cos(3t + 91.33^\circ)]u(t) \text{ V}$$

$$\text{Check: } v_o(0^+) = 0 \text{ V; } v_o(\infty) = 168 \text{ V}$$

P 13.30 [a]

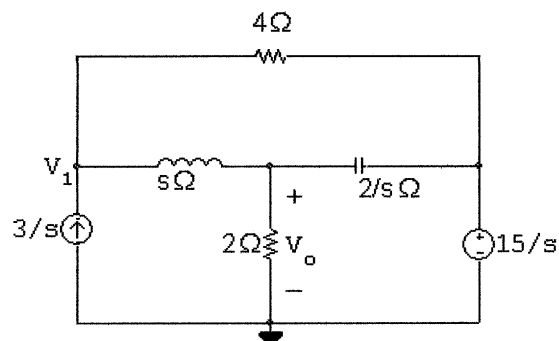

$$\frac{-3}{s} + \frac{V_1 - V_o}{s} + \frac{V_1 - (15/s)}{4} = 0$$

$$\frac{V_o}{2} + \frac{V_o - V_1}{s} + \frac{V_o - (15/s)}{2/s} = 0$$

Simplifying,

$$(s + 4)V_1 - 4V_o = 27$$

$$(s^2 + s + 2)V_o - 2V_1 = 15s$$

$$\Delta = \begin{vmatrix} s+4 & -4 \\ -2 & s^2+s+2 \end{vmatrix} = s(s+2)(s+3)$$

$$N_2 = \begin{vmatrix} s+4 & 27 \\ -2 & 15s \end{vmatrix} = 15s^2 + 60s + 54$$

$$V_o = \frac{N_2}{\Delta} = \frac{15s^2 + 60s + 54}{s(s+2)(s+3)} = \frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+3}$$


$$K_1 = \frac{54}{(2)(3)} = 9; \quad K_2 = \frac{60 - 120 + 54}{(-2)(1)} = 3$$

$$K_3 = \frac{135 - 180 + 54}{(-3)(-1)} = 3$$


$$\therefore V_o = \frac{9}{s} + \frac{3}{s+2} + \frac{3}{s+3}$$

[b]  $v_o(t) = (9 + 3e^{-2t} + 3e^{-3t})u(t)$  V

[c] At  $t = 0^+$ :

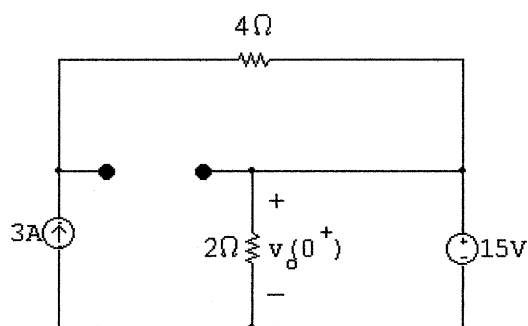


$$v_o(0^+) = 15 \text{ V (checks)}$$

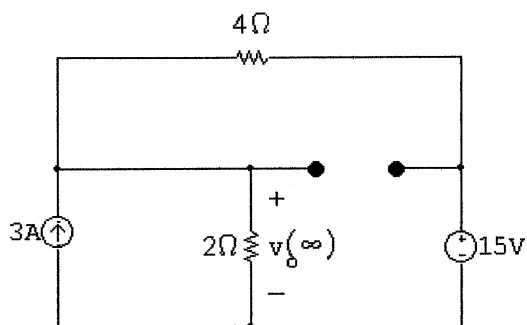At  $t = \infty$ :

$$\frac{v_o(\infty)}{2} - 3 + \frac{v_o(\infty) - 15}{4} = 0$$

$$\therefore 3v_o(\infty) = 27; \quad \therefore v_o(\infty) = 9 \text{ V (checks)}$$

P 13.31 [a]

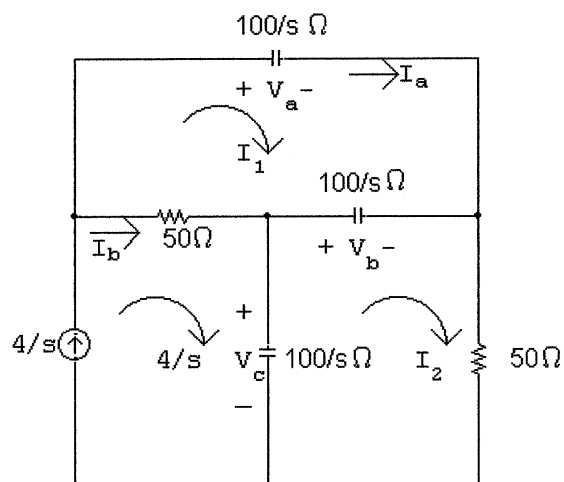

$$\frac{100}{s}I_1 + \frac{100}{s}(I_1 - I_2) + 50(I_1 - 4/s) = 0$$

$$\frac{100}{s}(I_2 - 4/s) + \frac{100}{s}(I_2 - I_1) + 50I_2 = 0$$

Simplifying,

$$(s + 4)I_1 - 2I_2 = 4$$

$$-2I_1 + (s + 4)I_2 = \frac{8}{s}$$

$$\Delta = \begin{vmatrix} (s + 4) & -2 \\ -2 & (s + 4) \end{vmatrix} = s^2 + 8s + 12 = (s + 2)(s + 6)$$

$$N_1 = \begin{vmatrix} 4 & -2 \\ 8/s & (s+4) \end{vmatrix} = \frac{4s^2 + 16s + 16}{s} = \frac{4(s+2)^2}{s}$$

$$I_1 = \frac{N_1}{\Delta} = \frac{4(s+2)^2}{s(s+2)(s+6)} = \frac{4(s+2)}{s(s+6)} = \frac{4/3}{s} + \frac{8/3}{s+6}$$

$$N_2 = \begin{vmatrix} (s+4) & 4 \\ -2 & 8/s \end{vmatrix} = \frac{16s + 32}{s} = \frac{16(s+2)}{s}$$

$$I_2 = \frac{N_2}{\Delta} = \frac{16(s+2)}{s(s+2)(s+6)} = \frac{16}{s(s+6)} = \frac{8/3}{s} - \frac{8/3}{s+6}$$

$$I_a = I_1 = \frac{4/3}{s} + \frac{8/3}{s+6}$$

$$I_b = \frac{4}{s} - I_1 = \frac{8/3}{s} - \frac{8/3}{s+6}$$

$$[b] \quad i_a(t) = (4/3)(1 + 2e^{-6t})u(t) \text{ A}$$

$$i_b(t) = (8/3)(1 - e^{-6t})u(t) \text{ A}$$

$$[c] \quad V_a = \frac{100}{s} I_a = \frac{100}{s} \left( \frac{4/3}{s} + \frac{8/3}{s+6} \right) \\ = \frac{400/3}{s^2} + \frac{800/3}{s(s+6)} = \frac{400/3}{s^2} + \frac{400/9}{s} - \frac{400/9}{s+6}$$

$$V_b = \frac{100}{s} (I_2 - I_1) = \frac{100}{s} \left( \frac{4/3}{s} - \frac{16/3}{s+6} \right) \\ = \frac{400/3}{s^2} - \frac{1600/3}{s(s+6)} = \frac{400/3}{s^2} - \frac{800/9}{s} + \frac{800/9}{s+6}$$

$$V_c = \frac{100}{s} (4/s - I_2) = \frac{100}{s} \left( \frac{4/3}{s} + \frac{8/3}{s+6} \right) \\ = \frac{400/3}{s^2} + \frac{800/3}{s(s+6)} = \frac{400/3}{s^2} + \frac{400/9}{s} - \frac{400/9}{s+6}$$

$$[d] \quad v_a(t) = (400/9)(3t + 1 - e^{-6t})u(t) \text{ V}$$

$$v_b(t) = (400/9)(3t - 2 + 2e^{-6t})u(t) \text{ V}$$

$$v_c(t) = (400/9)(3t + 1 - e^{-6t})u(t) \text{ V}$$

[e] Calculating the time when a capacitor's voltage drop first reaches 1000 V:

For  $v_a(t)$  or  $v_c(t)$  :

$$1000 \left( \frac{9}{400} \right) = 3t + 1 - e^{-6t} = 22.5$$

$$3t - e^{-6t} = 21.5$$

$$t = 7.17 \text{ s}$$

For  $v_b(t)$  :


$$3t - 2 + 2e^{-6t} = 22.5$$

$$3t + 2e^{-6t} = 24.5$$

$$t = 8.17 \text{ s}$$

Thus, the capacitors whose voltage drops are designated  $v_a$  and  $v_c$  will break down first, at a time of 7.17 s.

P 13.32 [a]

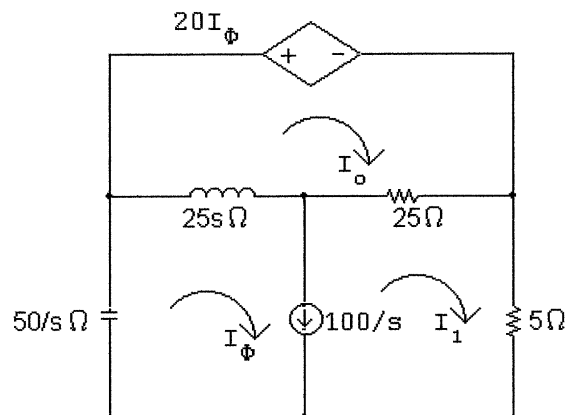

$$20I_\phi + 25s(I_o - I_\phi) + 25(I_o - I_1) = 0$$

$$25s(I_\phi - I_o) + \frac{50}{s}I_\phi + 5I_1 + 25(I_1 - I_o) = 0$$

$$I_\phi - I_1 = \frac{100}{s}; \quad \therefore I_1 = I_\phi - \frac{100}{s}$$

Simplifying,

$$(-5s - 1)I_\phi + (5s + 5)I_o = -500/s$$

$$(5s^2 + 6s + 10)I_\phi + (-5s^2 - 5s)I_o = 600$$

$$\Delta = \begin{vmatrix} -5s - 1 & 5s + 5 \\ 5s^2 + 6s + 10 & -5s^2 - 5s \end{vmatrix} = -25(s^2 + 3s + 2)$$


$$N_2 = \begin{vmatrix} -5s - 1 & -500/s \\ 5s^2 + 6s + 10 & 600 \end{vmatrix} = -\frac{500}{s}(s^2 - 4.8s - 10)$$

$$I_o = \frac{N_2}{\Delta} = \frac{20s^2 - 96s - 200}{s(s+1)(s+2)}$$

[b]  $i_o(0^+) = \lim_{s \rightarrow \infty} sI_o = 20 \text{ A}$

$$i_o(\infty) = \lim_{s \rightarrow 0} sI_o = \frac{-200}{2} = -100 \text{ A}$$

[c] At  $t = 0^+$  the circuit is

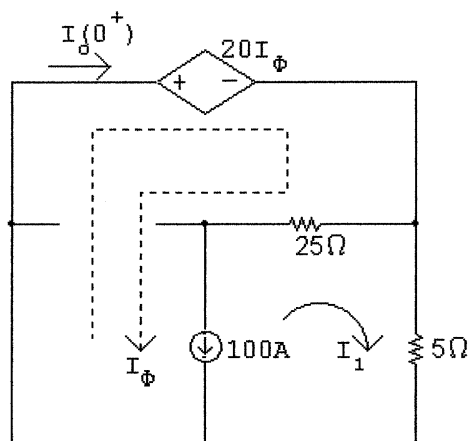


$$20I_\phi + 5I_1 = 0; \quad I_\phi - I_1 = 100$$

$$\therefore 20I_\phi + 5(I_\phi - 100) = 0; \quad 25I_\phi = 500$$

$$\therefore I_\phi = I_o(0^+) = 20 \text{ A (checks)}$$

At  $t = \infty$  the circuit is

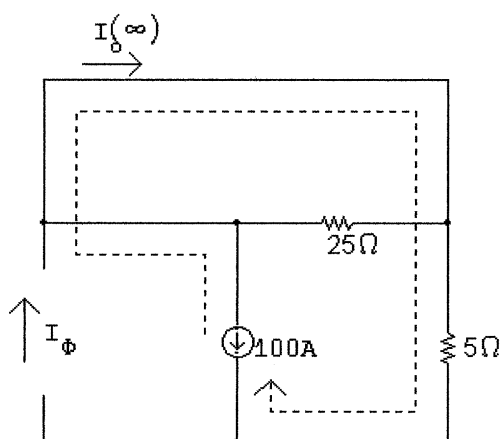

$$I_o(\infty) = -100 \text{ A (checks)}$$

$$[\text{d}] \quad I_o = \frac{20s^2 - 96s - 200}{s(s+1)(s+2)} = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+2}$$

$$K_1 = \frac{-200}{(1)(2)} = -100; \quad K_2 = \frac{20 + 96 - 200}{(-1)(1)} = 84$$

$$K_3 = \frac{80 + 192 - 200}{(-2)(-1)} = 36$$

$$I_o = \frac{-100}{s} + \frac{84}{s+1} + \frac{36}{s+2}$$

$$i_o(t) = (-100 + 84e^{-t} + 36e^{-2t})u(t) \text{ A}$$

$$i_o(\infty) = -100 \text{ A (checks)}$$

$$i_o(0^+) = -100 + 84 + 36 = 20 \text{ A (checks)}$$

P 13.33  $v_C = 12 \times 10^5 te^{-5000t} \text{ V}$ ,  $C = 5 \mu\text{F}$ ; therefore

$$i_C = C \left( \frac{dv_C}{dt} \right) = 6e^{-5000t}(1 - 5000t) \text{ A}$$

$$i_C > 0 \quad \text{when} \quad 1 > 5000t \quad \text{or} \quad i_C \geq 0 \quad \text{when} \quad 0 \leq t \leq 200 \mu\text{s}$$


$$\text{and} \quad i_C < 0 \quad \text{when} \quad t > 200 \mu\text{s}$$

$$i_C = 0 \quad \text{when} \quad 1 - 5000t = 0, \quad \text{or} \quad t = 200 \mu\text{s}$$

$$\frac{dv_C}{dt} = 12 \times 10^5 e^{-5000t} [1 - 5000t]$$

$$\therefore i_C = 0 \quad \text{when} \quad \frac{dv_C}{dt} = 0$$

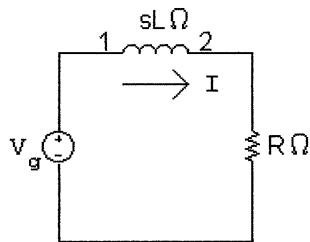P 13.34 [a] The  $s$ -domain equivalent circuit is



$$I = \frac{V_g}{R + sL} = \frac{V_g/L}{s + (R/L)}, \quad V_g = \frac{V_m(\omega \cos \phi + s \sin \phi)}{s^2 + \omega^2}$$



$$I = \frac{K_0}{s + R/L} + \frac{K_1}{s - j\omega} + \frac{K_1^*}{s + j\omega}$$

$$K_0 = \frac{V_m(\omega L \cos \phi - R \sin \phi)}{R^2 + \omega^2 L^2}, \quad K_1 = \frac{V_m/\phi - 90 - \theta(\omega)}{2\sqrt{R^2 + \omega^2 L^2}}$$

where  $\tan \theta(\omega) = \omega L/R$ . Therefore, we have

$$i(t) = \frac{V_m(\omega L \cos \phi - R \sin \phi)}{R^2 + \omega^2 L^2} e^{-(R/L)t} + \frac{V_m \sin[\omega t + \phi - \theta(\omega)]}{\sqrt{R^2 + \omega^2 L^2}}$$

$$[b] \quad i_{ss}(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin[\omega t + \phi - \theta(\omega)]$$

$$[c] \quad i_{tr} = \frac{V_m(\omega L \cos \phi - R \sin \phi)}{R^2 + \omega^2 L^2} e^{-(R/L)t}$$

$$[d] \quad \mathbf{I} = \frac{\mathbf{V}_g}{R + j\omega L}, \quad \mathbf{V}_g = V_m/\underline{\phi}$$


$$\text{Therefore } \mathbf{I} = \frac{V_m/\underline{\phi}}{\sqrt{R^2 + \omega^2 L^2} \angle \theta(\omega)} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle \phi - \theta(\omega)$$

$$\text{Therefore } i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin[\omega t + \phi - \theta(\omega)]$$

[e] The transient component vanishes when


$$\omega L \cos \phi = R \sin \phi \quad \text{or} \quad \tan \phi = \frac{\omega L}{R} \quad \text{or} \quad \phi = \theta(\omega)$$

P 13.35

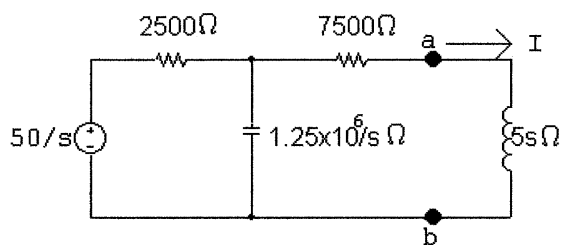

$$V_{Th} = \frac{50/s}{2500 + (1.25 \times 10^6/s)} \cdot \frac{1.25 \times 10^6}{s} = \frac{25,000}{s(s + 500)}$$
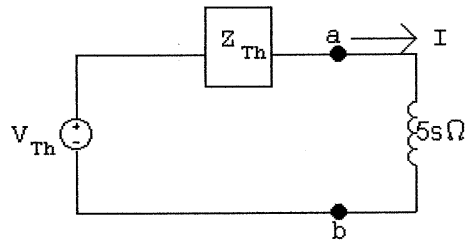
$$Z_{Th} = 7500 + \frac{2500(1.25 \times 10^6/s)}{2500 + (1.25 \times 10^6/s)} = \frac{7500s + 5 \times 10^6}{s + 500}$$



$$\begin{aligned}
 I &= \frac{25,000/s(s+500)}{5s + \frac{7500s + 5 \times 10^6}{s+500}} \\
 &= \frac{5000}{s(s^2 + 2000s + 10^6)} = \frac{5000}{s(s+1000)^2} \\
 &= \frac{K_1}{s} + \frac{K_2}{(s+1000)^2} + \frac{K_3}{s+1000}
 \end{aligned}$$


$$K_1 = \frac{5000}{10^6} = 5 \times 10^{-3}$$

$$K_2 = \frac{5000}{-1000} = -5000 \times 10^{-3}$$

$$K_3 = \frac{d}{ds} \left( \frac{5000}{s} \right)_{s=-1000} = -5 \times 10^{-3}$$

$$i(t) = [5 - 5000te^{-1000t} - 5e^{-1000t}]u(t) \text{ mA}$$

P 13.36 [a]

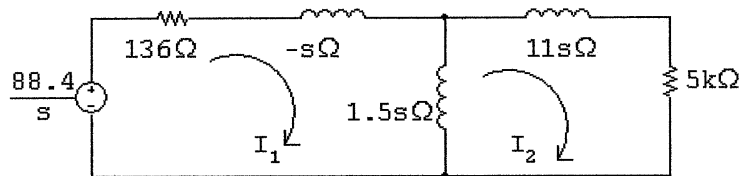

$$\frac{88.4}{s} = 136I_1 - sI_1 + 1.5s(I_1 - I_2)$$

$$0 = 1.5s(I_2 - I_1) + 11sI_2 + 5000I_2$$

Simplifying,

$$\frac{88.4}{s} = (0.5s + 136)I_1 - 1.5sI_2$$

$$0 = -1.5sI_1 + (12.5s + 5000)I_2$$

$$\Delta = \begin{vmatrix} 0.5s + 136 & -1.5s \\ -1.5s & 12.5s + 5000 \end{vmatrix} = 4(s + 200)(s + 850)$$

$$N_1 = \begin{vmatrix} 88.4/s & -1.5s \\ 0 & 12.5s + 5000 \end{vmatrix} = \frac{1105(s + 400)}{s}$$

$$I_1 = \frac{N_1}{\Delta} = \frac{276.25(s + 400)}{s(s + 200)(s + 850)}$$

$$[b] \quad sI_1 = \frac{276.25(s + 400)}{(s + 200)(s + 850)}$$

$$\lim_{s \rightarrow 0} sI_1 = i_1(\infty) = 650 \text{ mA}$$

$$\lim_{s \rightarrow \infty} sI_1 = i_1(0) = 0$$

$$[c] \quad I_1 = \frac{K_1}{s} + \frac{K_2}{s + 200} + \frac{K_3}{s + 850}$$

$$K_1 = 650 \times 10^{-3}; \quad K_2 = -425 \times 10^{-3}; \quad K_3 = -225 \times 10^{-3}$$

$$i_1(t) = (650 - 425e^{-200t} - 225e^{-850t})u(t) \text{ mA}$$


P 13.37 [a] From the solution to Problem 13.36 we have

$$N_2 = \begin{vmatrix} 0.5s + 136 & 88.4/s \\ -1.5s & 0 \end{vmatrix} = 132.6$$

$$\begin{aligned} \therefore I_2 &= \frac{132.6}{4(s + 200)(s + 850)} = \frac{33.15}{(s + 200)(s + 850)} \\ &= \frac{51 \times 10^{-3}}{s + 200} - \frac{51 \times 10^{-3}}{s + 850} \end{aligned}$$

$$i_2(t) = (51e^{-200t} - 51e^{-850t})u(t) \text{ mA}$$

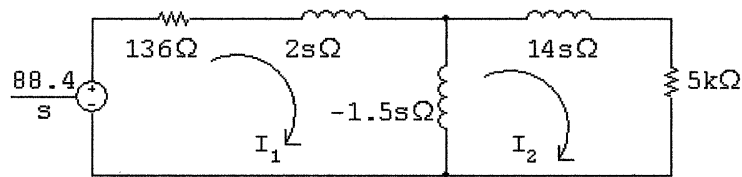[b] Reversing the dot on the 12.5 H coil will reverse the sign of  $M$ , thus the circuit becomes



The two simultaneous equations are

$$\frac{88.4}{s} = (136 + 0.5s)I_1 + 1.5sI_2$$

$$0 = 1.5sI_1 + (12.5s + 5000)I_2$$


When these equations are compared to those derived in Problem 13.39 we see the only difference is the algebraic sign of the  $1.5s$  term. Thus reversing the dot will have no effect on  $I_1$  and will reverse the sign of  $I_2$ . Hence,

$$i_2(t) = (-51e^{-200t} + 51e^{-850t})u(t) \text{ mA}$$

P 13.38 [a]  $w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + Mi_1i_2$

$$w = \left[ \frac{1}{2}(40)(9) + \frac{1}{2}(90)(4) + 30(6) \right] \times 10^{-3} = 540 \text{ mJ}$$

[b] The  $s$ -domain circuit:

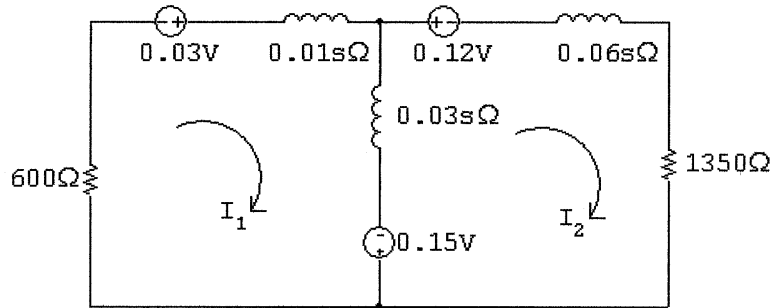

$$(600 + 0.04s)I_1 - 0.03sI_2 = 0.18$$

$$-0.03sI_1 + (0.09s + 1350)I_2 = -0.27$$

$$\Delta = \begin{vmatrix} 0.04(s + 15,000) & -0.03s \\ -0.03s & 0.09(s + 15,000) \end{vmatrix}$$

$$= 27 \times 10^{-4}(s + 10,000)(s + 30,000)$$

$$N_1 = \begin{vmatrix} 0.18 & -0.03s \\ -0.27 & 0.09(s + 15,000) \end{vmatrix} = 81 \times 10^{-4}(s + 30,000)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{3}{s + 10,000}$$

$$N_2 = \begin{vmatrix} 0.04(s + 15,000) & 0.18 \\ -0.03s & -0.27 \end{vmatrix} = -54 \times 10^{-4}(s + 30,000)$$

$$I_2 = \frac{N_2}{\Delta} = \frac{-2}{s + 10,000}$$

[c]  $i_1(t) = 3e^{-10,000t}u(t) \text{ A}; \quad i_2(t) = -2e^{-10,000t}u(t) \text{ A}$

$$[d] \quad p_{600\Omega} = (600)(9e^{-20,000t}) = 5400e^{-20,000t} \text{ W}$$

$$p_{1350\Omega} = (1350)(4e^{-20,000t}) = 5400e^{-20,000t} \text{ W}$$

$$w_{600} = \frac{5400}{20} \times 10^{-3} = 270 \text{ mJ}$$


$$w_{1350} = \frac{5400}{20} \times 10^{-3} = 270 \text{ mJ}$$

$$w_T = 540 \text{ mJ}$$

[e] With the dot reversed,

$$w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 - Mi_1i_2 = 180 + 180 - 180 = 180 \text{ mJ}$$

The  $s$ -domain equivalent circuit is

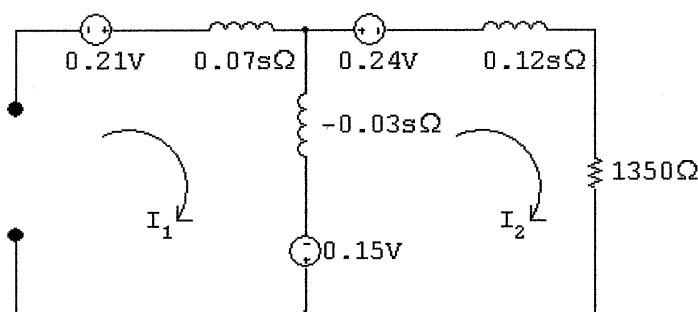

Solving for  $I_1$  and  $I_2$  yields

$$I_1 = \frac{3}{s + 30,000}; \quad I_2 = \frac{-2}{s + 30,000}$$


$$\therefore i_1(t) = 3e^{-30,000t}u(t) \text{ A}; \quad i_2(t) = -2e^{-30,000t}u(t) \text{ A}$$

$$w_{600} = 5400 \int_0^\infty e^{-60,000t} dt = 90 \text{ mJ}$$

$$w_{1350} = 5400 \int_0^\infty e^{-60,000t} dt = 90 \text{ mJ}$$

$$w_T = 180 \text{ mJ}$$

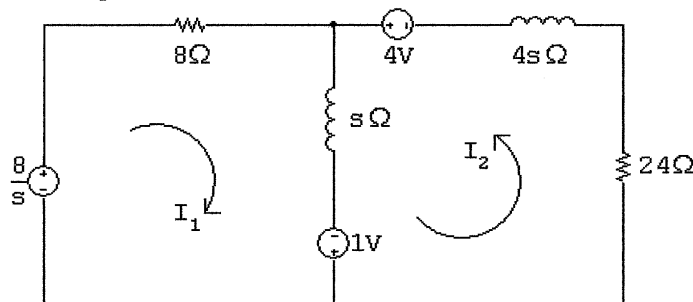P 13.39 [a]  $s$ -domain equivalent circuit is



$$[\text{b}] \quad \frac{8}{s} = 8I_1 + s(I_1 + I_2) - 1$$

$$0 = -1 + s(I_2 + I_1) + 4sI_2 - 4 + 24I_2$$

or

$$\frac{8}{s} + 1 = (s + 8)I_1 + sI_2$$

$$5 = sI_1 + (5s + 24)I_2$$

$$\Delta = \begin{vmatrix} s+8 & s \\ s & 5s+24 \end{vmatrix} = 4(s+4)(s+12)$$

$$I_2 = \frac{N_2}{\Delta}$$

$$N_2 = \begin{vmatrix} s+8 & (8/s)+1 \\ s & 5 \end{vmatrix} = 4(s+8)$$

$$\therefore I_2 = \frac{s+8}{(s+4)(s+12)}$$

$$[\text{c}] \quad sI_2 = \frac{s(s+8)}{(s+4)(s+12)}$$

$$\lim_{s \rightarrow \infty} sI_2 = i_2(0^+) = 1 \text{ A}$$


$$\lim_{s \rightarrow 0} sI_2 = i_2(\infty) = 0$$


$$[\text{d}] \quad I_2 = \frac{K_1}{s+4} + \frac{K_2}{s+12}$$

$$K_1 = K_2 = 1/2; \quad \therefore I_2 = \frac{1/2}{s+4} + \frac{1/2}{s+12}$$

$$i_2(t) = \frac{1}{2}[e^{-4t} + e^{-12t}]u(t) \text{ A}$$


P 13.40 For  $t < 0$ :

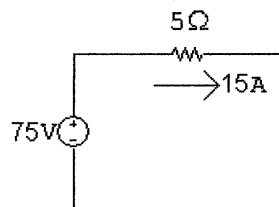

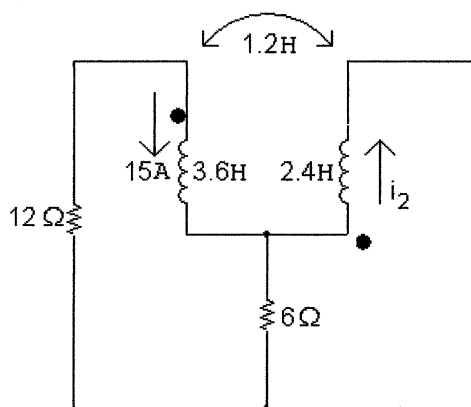For  $t > 0^+$ :

$$L_1 + M = 3.6 + 1.2 = 4.8 \text{ H}; \quad M - L_2 = 1.2 - 2.4 = -1.2 \text{ H}$$
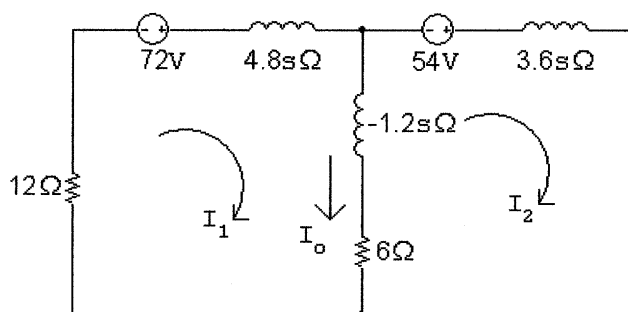
$$15 \times 4.8 = 72; \quad 15 \times 3.6 = 54$$



$$12I_o + 4.8sI_o - 72 + (I_o - I_2)(6 - 1.2s) = 0$$

$$(6 - 1.2s)(I_2 - I_o) + 3.6sI_2 - 54 = 0$$

$$\therefore \Delta = \begin{vmatrix} 3(s+5) & -(5-s) \\ -(5-s) & 2(s+2.5) \end{vmatrix} = 5(s+1)(s+10)$$

$$N_o = \begin{vmatrix} 60 & -(5-s) \\ 45 & 2(s+2.5) \end{vmatrix} = 75(s+7)$$

$$I_o = \frac{N_o}{\Delta} = \frac{75(s+7)}{5(s+1)(s+10)}$$

$$= \frac{K_1}{(s+1)} + \frac{K_2}{(s+10)}$$


$$K_1 = \frac{(15)(6)}{9} = 10$$

$$K_2 = \frac{(15)(-3)}{-9} = 5$$

$$\therefore I_o = \frac{10}{s+1} + \frac{5}{s+10}$$

$$\therefore i_o(t) = [10e^{-t} + 5e^{-10t}]u(t) \text{ A}$$

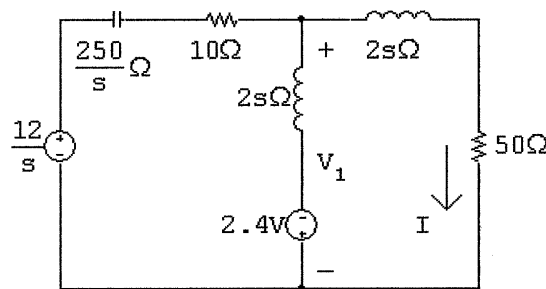P 13.41 The  $s$ -domain equivalent circuit is



$$\frac{V_1 - 12/s}{10 + (250/s)} + \frac{V_1 + 2.4}{2s} + \frac{V_1}{2s + 50} = 0$$

$$V_1 = \frac{-300(s+25)}{(s+25)(s^2+10s+125)} = \frac{-300}{s^2+10s+125}$$

$$\begin{aligned} I_o &= \frac{-300}{(2s+50)(s^2+10s+125)} \\ &= \frac{-150}{(s+25)(s+5-j10)(s+5+j10)} \\ &= \frac{K_1}{s+25} + \frac{K_2}{s+5-j10} + \frac{K_2^*}{s+5+j10} \end{aligned}$$


$$K_1 = \frac{-150}{625 - 250 + 125} = -300 \times 10^{-3}$$

$$K_2 = \frac{-150}{(-5+j10+25)(j20)} = 150\sqrt{5} \times 10^{-3} / 63.43^\circ$$

$$i_o(t) = [-300e^{-25t} + 300\sqrt{5}e^{-5t} \cos(10t + 63.43^\circ)]u(t) \text{ mA}$$





P 13.42 [a] Voltage source acting alone:

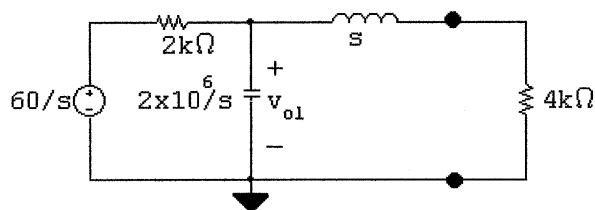

$$\frac{V_{o1} - 60/s}{2000} + \frac{V_{o1}s}{2 \times 10^6} + \frac{V_{o1}}{s + 4000} = 0$$
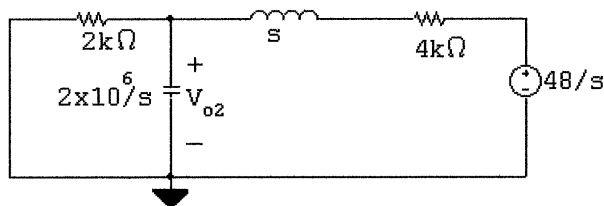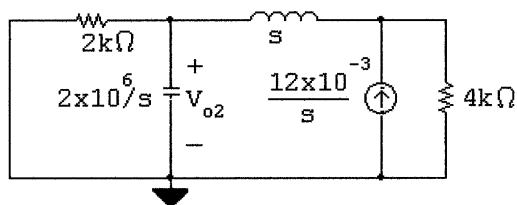
$$\therefore V_{o1} = \frac{60,000(s + 4000)}{s(s + 2000)(s + 3000)}$$



$$\frac{V_{o2}}{2000} + \frac{V_{o2}s}{2 \times 10^6} + \frac{V_{o2} - 48/s}{4000 + s} = 0$$

$$\therefore V_{o2} = \frac{96 \times 10^6}{s(s + 2000)(s + 3000)}$$

$$V_o = V_{o1} + V_{o2} = \frac{6 \times 10^4(s + 4000) + 96 \times 10^6}{s(s + 2000)(s + 3000)}$$

$$[b] V_o = \frac{K_1}{s} + \frac{K_2}{s + 2000} + \frac{K_3}{s + 3000}$$

$$= \frac{56}{s} - \frac{108}{s + 2000} + \frac{52}{s + 3000}$$

$$v_o(t) = (56 - 108e^{-2000t} + 52e^{-3000t})u(t) \text{ V}$$


$$P 13.43 \Delta = \begin{vmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{vmatrix} = Y_{11}Y_{22} - Y_{12}^2$$

$$N_2 = \begin{vmatrix} Y_{11} [(V_g/R_1) + \gamma C - (\rho/s)] \\ Y_{12} (I_g - \gamma C) \end{vmatrix}$$

$$V_2 = \frac{N_2}{\Delta}$$

Substitution and simplification lead directly to Eq. 13.90.

P 13.44

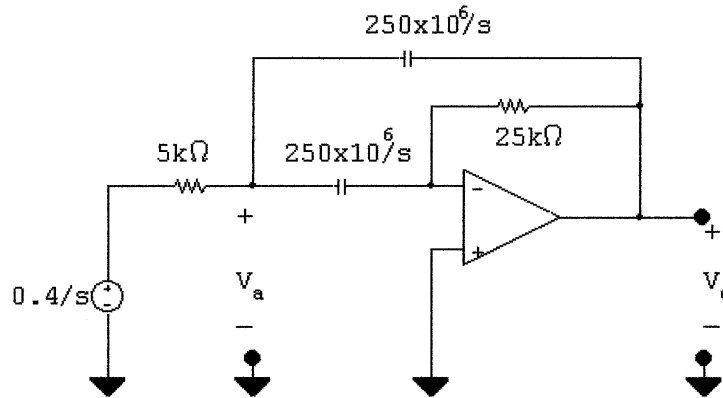

$$\frac{V_a - 0.4/s}{5000} + \frac{V_a s}{250 \times 10^6} + \frac{(V_a - V_o)s}{250 \times 10^6} = 0$$

$$\frac{(0 - V_a)s}{250 \times 10^6} + \frac{(0 - V_o)}{25,000} = 0$$

$$V_a = \frac{-10^4 V_o}{s}$$

$$\therefore V_o(s^2 + 20,000s + 500 \times 10^6) = -20,000$$

$$V_o = \frac{-20,000}{(s + 10,000 - j20,000)(s + 10,000 + j20,000)}$$

$$K_1 = \frac{-20,000}{j40,000} = j0.5 = 0.5 \angle 90^\circ$$

$$v_o(t) = e^{-10,000t} \cos(20,000t + 90^\circ) = -e^{-10,000t} \sin(20,000t) u(t) \text{ V}$$

P 13.45 [a]  $V_o = -\frac{Z_f}{Z_i} V_g$

$$Z_f = \frac{10^8}{s + \left[ \frac{10^9}{(10)(2) \times 10^4} \right]} = \frac{10^8}{s + 5000}$$

$$Z_i = \frac{8000}{s} \left( s + \frac{10^9}{(50)(8000)} \right) = \frac{8000}{s} (s + 2500)$$

$$V_g = \frac{20,000}{s^2}$$

$$\therefore V_o = \frac{-250 \times 10^6}{s(s+2500)(s+5000)}$$

$$[b] V_o = \frac{K_1}{s} + \frac{K_2}{s+2500} + \frac{K_3}{s+5000}$$

$$K_1 = \frac{-250 \times 10^6}{(5000)(2500)} = -20$$

$$K_2 = \frac{-250 \times 10^6}{(-2500)(2500)} = 40$$

$$K_3 = \frac{-250 \times 10^6}{(-5000)(-2500)} = -20$$

$$\therefore v_o(t) = (-20 + 40e^{-2500t} - 20e^{-5000t})u(t) \text{ V}$$

$$[c] -20 + 40e^{-2500t_s} - 20e^{-5000t_s} = -5$$

$$\therefore 40e^{-2500t_s} - 20e^{-5000t_s} = 15$$

Let  $x = e^{-2500t_s}$ . Then

$$40x - 20x^2 = 15; \quad \text{or } x^2 - 2x + 0.75 = 0$$

Solving,

$$x = 1 \pm 0.5 \quad \text{so} \quad x = 0.5$$

$$\therefore e^{-2500t_s} = 0.5; \quad \therefore t_s = \frac{\ln 2}{0.0025} \times 10^{-6} = 277.26 \mu\text{s}$$


$$[d] v_g = m tu(t); \quad V_g = \frac{m}{s^2}$$

$$\begin{aligned} V_o &= \frac{-10^8 s}{8000(s+2500)(s+5000)} \cdot \frac{m}{s^2} \\ &= \frac{-12,500m}{s(s+2500)(s+5000)} \end{aligned}$$

$$K_1 = \frac{-12,500m}{(2500)(5000)} = -m \times 10^{-3}$$

$$\therefore -5 = -m \times 10^{-3} \quad \therefore m = 5000 \text{ V/s}$$

P 13.46 [a]

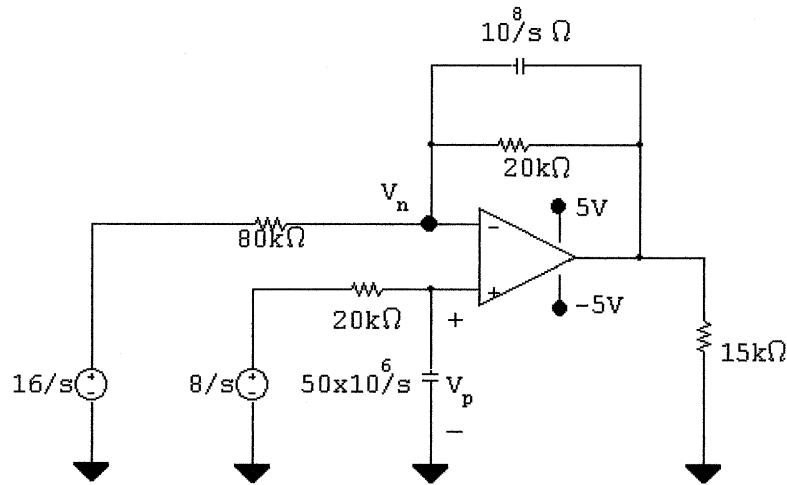

$$\frac{V_p s}{50 \times 10^6} + \frac{V_p - V_{g2}}{20,000} = 0; \quad V_p = \frac{2500}{s + 2500} V_{g2}$$

$$\frac{V_p - V_{g1}}{80,000} + \frac{V_p - V_o}{20,000} + \frac{(V_p - V_o)s}{10^8} = 0$$

$$(s + 6250)V_p - (s + 5000)V_o = 1250V_{g1}$$

$$\therefore (s + 5000)V_o = \frac{(s + 6250)(2500)}{(s + 2500)} V_{g2} - 1250V_{g1}$$

$$V_{g1} = \frac{16}{s}; \quad V_{g2} = \frac{8}{s}$$

$$\begin{aligned} \therefore V_o &= \frac{7500 \times 10^4}{s(s + 2500)(s + 5000)} \\ &= \frac{K_1}{s} + \frac{K_2}{s + 2500} + \frac{K_3}{s + 5000} \end{aligned}$$

$$K_1 = \frac{7500 \times 10^4}{(2500)(5000)} = \frac{750}{125} = 6$$

$$K_2 = \frac{7500 \times 10^4}{(-2500)(2500)} = -12$$

$$K_3 = \frac{7500 \times 10^4}{(-5000)(-2500)} = 6$$

$$v_o = [6 - 12e^{-2500t} + 6e^{-5000t}]u(t) \text{ V}$$

[b]  $6 - 12e^{-2500t_s} + 6e^{-5000t_s} = 5; \quad \text{let } x = e^{-2500t_s}$

$$6 - 12x + 6x^2 = 5$$

$$x^2 - 2x + \frac{1}{6} = 0$$

$$x = 1 - \sqrt{5/6} = 0.0871$$

$$\therefore e^{-2500t} = 0.0871; \quad t = 976.15 \mu s$$

$$\text{P 13.47 } Z_{i1} = 400,000 + \frac{(4 \times 10^5/s)(2 \times 10^5)}{2 \times 10^5 + (4 \times 10^5/s)} = \frac{4 \times 10^5(s+3)}{s+2}$$

$$Z_{f1} = 8 \times 10^5$$

$$V_{o1} = -\frac{Z_{f1}}{Z_{i1}} V_g = \frac{-8 \times 10^5(s+2)}{4 \times 10^5(s+3)} \frac{(0.18)}{s} = \frac{-0.36(s+2)}{s(s+3)}$$

The final value of  $v_{o1}$  is

$$v_{o1}(\infty) = \lim_{s \rightarrow 0} \left( \frac{-0.36(s+2)}{s+3} \right) = -0.24 \text{ V}$$

Thus, the first stage will not saturate.

$$V_o = -\frac{Z_{f2}}{Z_{i2}} V_{o1}$$

$$Z_{f2} = \frac{10^9}{250s} = \frac{4 \times 10^6}{s}; \quad Z_{i2} = 50 \times 10^3$$

$$\begin{aligned} V_o &= \frac{-0.36(s+2)}{s(s+3)} \left( \frac{-80}{s} \right) = \frac{28.8(s+2)}{s^2(s+3)} \\ &= \frac{19.2}{s^2} + \frac{3.2}{s} - \frac{3.2}{s+3} \end{aligned}$$

$$v_o(t) = (19.2t + 3.2 - 3.2e^{-3t})u(t) \text{ V}$$

The second stage saturates when  $v_o$  reaches 6.4 V. Thus

$$19.2t_s + 3.2 - 3.2e^{-3t_s} = 6.4; \quad \therefore 6t_s - 1 = e^{-3t_s}$$

$t_s$  must be greater than  $\frac{1}{6}$  or 166.68 ms. Using trial and error we find

$$t_s = 246.28 \text{ ms}$$

- P 13.48 [a] Let  $V_a$  be the voltage across the  $0.2\ \mu\text{F}$  capacitor, positive at the upper terminal and let  $V_b$  be the voltage across the  $200\ \text{k}\Omega$  resistor, positive at the upper terminal. Then

$$\frac{V_a s}{5 \times 10^6} + \frac{V_a - V_g}{400,000} + \frac{V_a}{400,000} = 0; \quad \therefore V_a = \frac{12.5}{s + 25} V_g$$

$$\frac{-V_a}{400,000} - \frac{sV_b}{10^7} = 0; \quad \therefore V_b = \frac{-25}{s} V_a = \frac{-312.5}{s(s + 25)} V_g$$

$$\frac{V_b}{200,000} + \frac{sV_b}{10^7} + \frac{(V_b - V_o)s}{10^7} = 0$$

$$\therefore V_o = \frac{2(s + 25)}{s} V_b = \left[ \frac{2(s + 25)}{s} \right] \left[ \frac{-312.5}{s(s + 25)} \right] \left( \frac{8}{s} \right) = \frac{-5000}{s^3}$$

[b]  $v_o(t) = -2500t^2 u(t)\ \text{V}$

- [c] The op amp will saturate when  $v_o = -12.5\ \text{V}$ .

$$-12.5 = -2500t^2; \quad t^2 = 0.005; \quad \therefore t = 0.071 = 71\ \text{ms}$$

P 13.49 [a]  $\frac{V_o}{V_i} = \frac{1/sC}{R + 1/sC} = \frac{1}{RCs + 1}$

$$H(s) = \frac{(1/RC)}{s + (1/RC)} = \frac{50}{s + 50}; \quad -p_1 = -50\ \text{rad/s}$$

[b]  $\frac{V_o}{V_i} = \frac{R}{R + 1/sC} = \frac{RCs}{RCs + 1} = \frac{s}{s + (1/RC)}$

$$= \frac{s}{s + 50}; \quad z_1 = 0, \quad -p_1 = -50\ \text{rad/s}$$


[c]  $\frac{V_o}{V_i} = \frac{sL}{R + sL} = \frac{s}{s + R/L} = \frac{s}{s + 3 \times 10^6}$

$$z_1 = 0; \quad -p_1 = -3 \times 10^6\ \text{rad/s}$$

[d]  $\frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{R/L}{s + (R/L)} = \frac{3 \times 10^6}{s + 3 \times 10^6}$

$$-p_1 = -3 \times 10^6\ \text{rad/s}$$

[e]

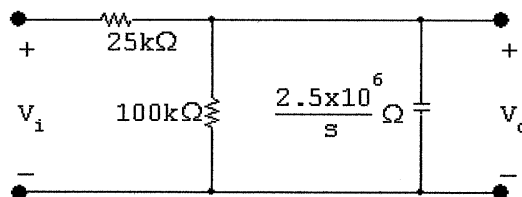

$$\frac{V_o s}{2.5 \times 10^6} + \frac{V_o}{10^5} + \frac{V_o - V_i}{25 \times 10^3} = 0$$

$$sV_o + 25V_o + 100V_o = 100V_i$$

$$H(s) = \frac{V_o}{V_i} = \frac{100}{s + 125}$$

$$-p_1 = -125 \text{ rad/s}$$

P 13.50 [a] Let  $R_1 = 40 \text{ k}\Omega$ ;  $R_2 = 10 \text{ k}\Omega$ ;  $C_2 = 500 \text{ nF}$ ; and  $C_f = 250 \text{ nF}$ . Then

$$Z_f = \frac{(R_2 + 1/sC_2)1/sC_f}{\left(R_2 + \frac{1}{sC_2} + \frac{1}{sC_f}\right)} = \frac{(s + 1/R_2C_2)}{C_f s \left(s + \frac{C_2 + C_f}{C_2 C_f R_2}\right)}$$

$$\frac{1}{C_f} = 4 \times 10^6$$

$$\frac{1}{R_2 C_2} = 200 \text{ rad/s}$$

$$\frac{C_2 + C_f}{C_2 C_f R_2} = \frac{750 \times 10^{-9}}{1.25 \times 10^{-9}} = 600 \text{ rad/s}$$

$$\therefore Z_f = \frac{4 \times 10^6 (s + 200)}{s(s + 600)} \Omega$$


$$Z_i = R_1 = 40 \times 10^3 \Omega$$

$$H(s) = \frac{V_o}{V_g} = \frac{-Z_f}{Z_i} = \frac{-100(s + 200)}{s(s + 600)}$$

[b]  $-z_1 = -200 \text{ rad/s}$

$$-p_1 = 0; \quad -p_2 = -600 \text{ rad/s}$$

P 13.51 [a]

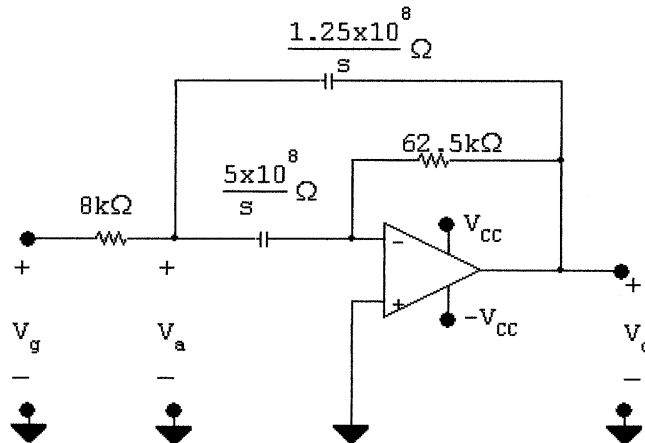

$$\frac{V_a - V_g}{8000} + \frac{V_a s}{5 \times 10^8} + \frac{(V_a - V_o)s}{1.25 \times 10^8} = 0$$

$$\frac{-V_a s}{5 \times 10^8} - \frac{V_o}{62,500} = 0; \quad V_a = \frac{-8000V_o}{s}$$

$$\therefore \frac{-8000V_o}{s}(5s + 62,500) - 4sV_o = 62,500V_g$$

$$\therefore H(s) = \frac{V_o}{V_g} = \frac{-15,625s}{s^2 + 10,000s + 125 \times 10^6}$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 125 \times 10^6} = -5000 \pm j10,000$$

$$H(s) = \frac{-15,625s}{(s + 5000 - j10,000)(s + 5000 + j10,000)}$$

[b]  $-p_1 = -5000 + j10,000$  rad/s

$$-p_2 = -5000 - j10,000$$
 rad/s

$$z = 0$$

P 13.52 [a]  $Z_i = 10,000 + \frac{10^9}{20s} = \frac{10^4(s + 5000)}{s}$


$$Z_f = \frac{25,000}{(25,000)(4 \times 10^{-9})s + 1} = \frac{250 \times 10^6}{s + 10,000}$$

$$H(s) = -\frac{Z_f}{Z_i} = \frac{-25,000s}{(s + 5000)(s + 10,000)}$$

[b] Zero at  $s = 0$

Poles at  $-p_1 = -5000$  rad/s and  $-p_2 = -10,000$  rad/s.

P 13.53 [a]

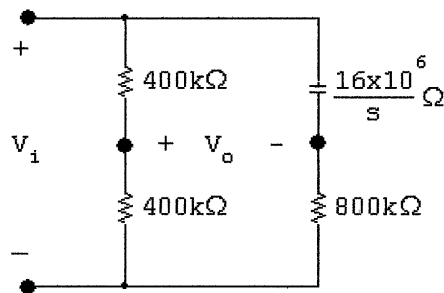

$$\frac{4}{8}V_i = V_o + \frac{800,000V_i}{800,000 + (16 \times 10^6/s)}$$

$$0.5V_i - \frac{sV_i}{s + 20} = V_o$$


$$\therefore \frac{V_o}{V_i} = H(s) = \frac{-0.5(s - 20)}{(s + 20)}$$



$$[b] -z_1 = 20 \text{ rad/s}$$

$$-p_1 = -20 \text{ rad/s}$$

P 13.54

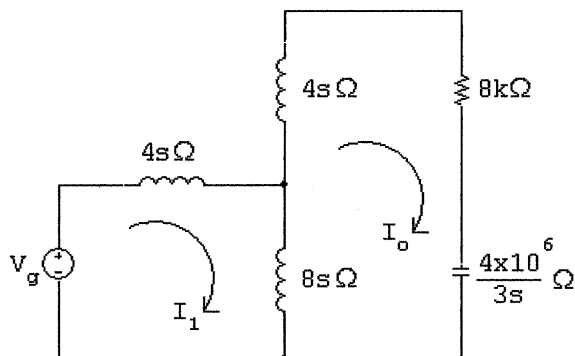

$$V_g = 12sI_1 - 8sI_o$$

$$0 = -8sI_1 + (12s + 8000 + 4 \times 10^6/3s)I_o$$

$$\Delta = \begin{vmatrix} 12s & -8s \\ -8s & 12s + 8000 + 4 \times 10^6/3s \end{vmatrix} = 80(s + 200)(s + 1000)$$


$$N_o = \begin{vmatrix} 12s & V_g \\ -8s & 0 \end{vmatrix} = 8sV_g$$

$$I_o = \frac{N_o}{\Delta} = \frac{8sV_g}{80(s + 200)(s + 1000)}$$

$$H(s) = \frac{I_o}{V_g} = \frac{0.1s}{(s + 200)(s + 1000)}$$

$$z_1 = 0; \quad -p_1 = -200 \text{ rad/s}; \quad -p_2 = -1000 \text{ rad/s}$$

P 13.55 [a]

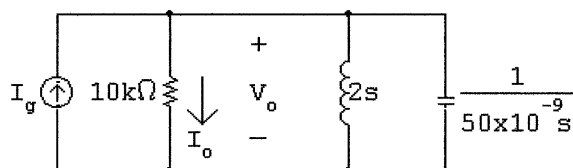

$$\frac{V_o}{10,000} + \frac{V_o}{2s} + V_o(50 \times 10^{-9})s = I_g$$

$$\therefore V_o = \frac{20 \times 10^6 s}{s^2 + 2000s + 10 \times 10^6} \cdot I_g$$

$$I_g = \frac{60 \times 10^{-3} s}{s^2 + 16 \times 10^6}; \quad I_o = \frac{V_o}{10^4}$$

$$\therefore H(s) = \frac{2000s}{s^2 + 2000s + 10^7}$$

$$[b] I_o = \frac{(2000s)(60 \times 10^{-3} s)}{(s + 1000 - j3000)(s + 1000 + j3000)(s^2 + 16 \times 10^6)}$$

$$I_o = \frac{120s^2}{(s + 1000 - j3000)(s + 1000 + j3000)(s + j4000)(s - j4000)}$$

[c] Damped sinusoid of the form

$$Me^{-1000t} \cos(3000t + \theta_1)$$

[d] Steady-state sinusoid of the form

$$N \cos(4000t + \theta_2)$$

$$[e] I_o = \frac{K_1}{s + 1000 - j3000} + \frac{K_1^*}{s + 1000 + j3000} + \frac{K_2}{s - j4000} + \frac{K_2^*}{s + j4000}$$

$$K_1 = \frac{120(-1000 + j3000)^2}{(j6000)(-1000 - j1000)(-j1000 + j7000)} = 20 \times 10^{-3} / 163.74^\circ$$

$$K_2 = \frac{120(-16 \times 10^6)}{(j8000)(1000 + j1000)(j1000 + j7000)} = 24 \times 10^{-3} / -36.87^\circ$$

$$i_o(t) = [40e^{-1000t} \cos(3000t + 163.74^\circ) + 48 \cos(4000t - 36.87^\circ)] \text{ mA}$$

Test:

$$i_o(0) = 40 \cos(163.74^\circ) + 48 \cos(-36.87^\circ) = -384 + 384 = 0$$

$$Z = \frac{1}{Y}; \quad Y = \frac{1}{10,000} + \frac{1}{j8000} + \frac{1}{-j5000} = \frac{1 + j0.75}{10,000}$$


$$\therefore Z = \frac{10,000}{1 + j0.75} = 8000 / -36.87^\circ \Omega$$

$$\mathbf{V}_o = \mathbf{I}_g Z = (60 \times 10^{-3} / 0^\circ)(8000 / -36.87^\circ) = 480 / -36.87^\circ \text{ V}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_o}{10^4} = 48 / -36.87^\circ \text{ mA}$$

$$i_{oss} = 48 \cos(4000t - 36.87^\circ) \text{ mA (checks)}$$

P 13.56 [a]

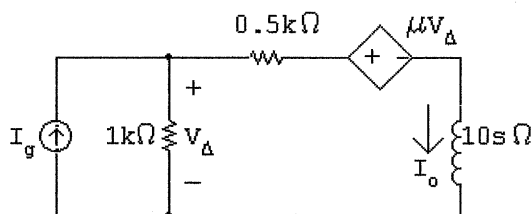

$$1000(I_o - I_g) + 500I_o + \mu(I_g - I_o)(1000) + 10sI_o = 0$$

$$\therefore I_o = \frac{100(1 - \mu)}{s + 100(1.5 - \mu)} I_g$$

$$\therefore H(s) = \frac{100(1 - \mu)}{s + 100(1.5 - \mu)}$$

[b]  $\mu < 1.5$ 

[c]

$\mu$	$H(s)$	$I_o$
-0.5	$150/(s + 200)$	$1500/s(s + 200)$
0	$100/(s + 150)$	$1000/s(s + 150)$
1.0	0	0
1.5	$-50/s$	$-500/s^2$
2.0	$-100/(s - 50)$	$-1000/s(s - 50)$

 $\mu = -0.5:$ 

$$I_o = \frac{7.5}{s} - \frac{7.5}{(s + 200)}; \quad i_o = [7.5 - 7.5e^{-200t}]u(t), \text{ A}$$

 $\mu = 0:$ 

$$I_o = \frac{20/3}{s} - \frac{20/3}{s + 150}; \quad i_o = \frac{20}{3}[1 - e^{-150t}]u(t), \text{ A}$$

 $\mu = 1: \quad i_o = 0 \text{ A}$  $\mu = 1.5:$ 


$$I_o = \frac{-500}{s^2}; \quad i_o = -500t u(t) \text{ A}$$

 $\mu = 2:$ 

$$I_o = \frac{20}{s} - \frac{20}{s - 50}; \quad i_o = 20[1 - e^{50t}]u(t), \text{ A}$$

P 13.57  $H(s) = \frac{V_o}{V_i} = \frac{1}{s+1}; \quad h(t) = e^{-t}$

For  $0 \leq t \leq 1$ :

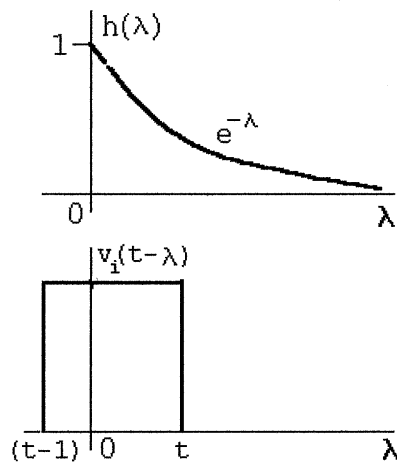

$$v_o = \int_0^t e^{-\lambda} d\lambda = (1 - e^{-t}) V$$

For  $1 \leq t \leq \infty$ :

$$v_o = \int_{t-1}^t e^{-\lambda} d\lambda = (e - 1)e^{-t} V$$

P 13.58  $H(s) = \frac{V_o}{V_i} = \frac{s}{s+1} = 1 - \frac{1}{s+1}; \quad h(t) = \delta(t) - e^{-t}$

$$h(\lambda) = \delta(\lambda) - e^{-\lambda}$$


For  $0 \leq t \leq 1$ :

$$v_o = \int_0^t [\delta(\lambda) - e^{-\lambda}] d\lambda = [1 + e^{-\lambda}] \Big|_0^t = e^{-t} V$$

For  $1 \leq t \leq \infty$ :

$$v_o = \int_{t-1}^t (-e^{-\lambda}) d\lambda = e^{-\lambda} \Big|_{t-1}^t = (1 - e)e^{-t} V$$

P 13.59 [a]

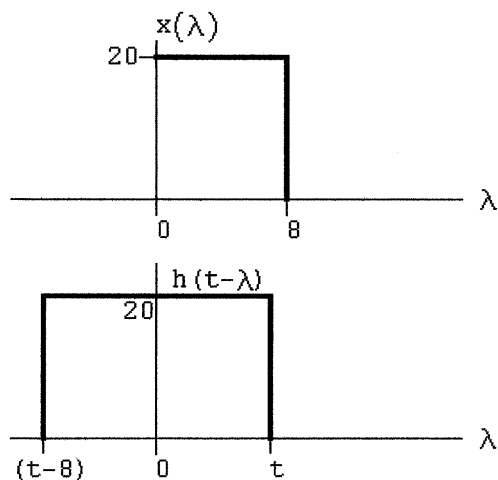


$$y(t) = 0 \quad t < 0$$


$$0 \leq t \leq 8: \quad y(t) = \int_0^t 400 \, d\lambda = 400t$$

$$8 \leq t \leq 16: \quad y(t) = \int_{t-8}^8 400 \, d\lambda = 400(8 - t + 8) = 400(16 - t)$$

$$16 \leq t < \infty: \quad y(t) = 0$$

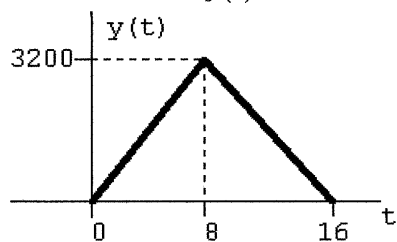

[b]

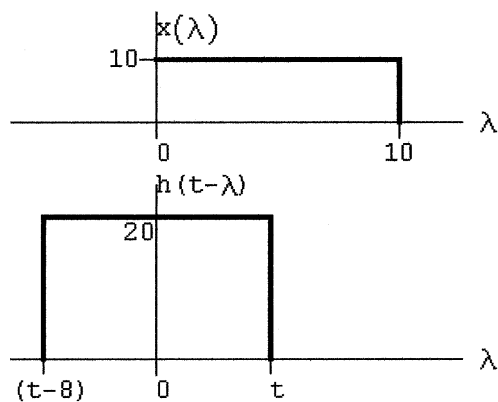


$$y(t) = 0 \quad t < 0$$

$$0 \leq t \leq 8: \quad y(t) = \int_0^t 200 \, d\lambda = 200t$$


$$8 \leq t \leq 10: \quad y(t) = \int_{t-8}^t 200 \, d\lambda = 200(t - t + 8) = 1600$$

$$10 \leq t \leq 18: \quad y(t) = \int_{t-8}^{10} 200 \, d\lambda = 200(18 - t)$$

$$18 \leq t < \infty: \quad y(t) = 0$$

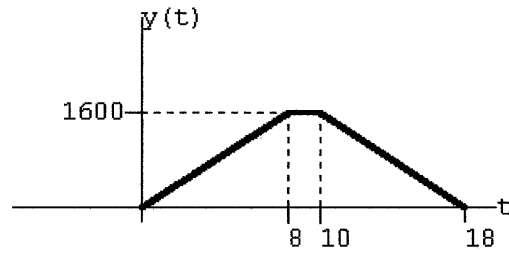

[c]

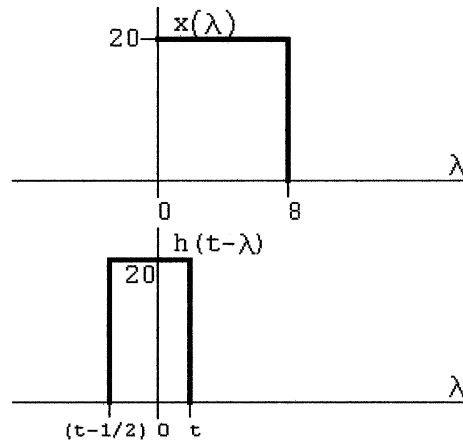


$$y(t) = 0 \quad t < 0$$


$$0 \leq t \leq 0.5: \quad y(t) = \int_0^t 400 \, d\lambda = 400t$$

$$0.5 \leq t \leq 8: \quad y(t) = \int_{t-0.5}^t 400 \, d\lambda = 400(t - t + 0.5) = 200$$


$$8 \leq t \leq 8.5: \quad y(t) = \int_{t-0.5}^8 400 \, d\lambda = 400(8.5 - t)$$

$$8.5 \leq t < \infty: \quad y(t) = 0$$

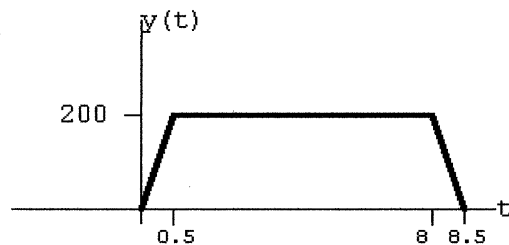

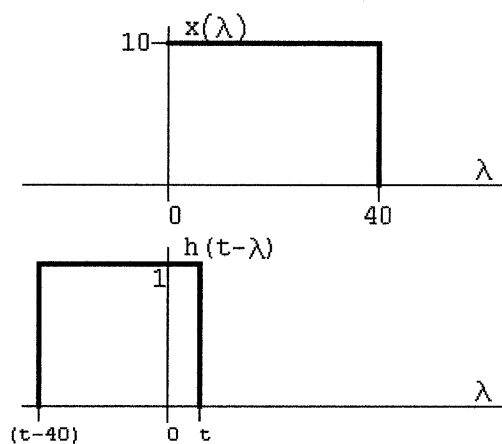P 13.60 [a]  $0 \leq t \leq 40$ :

$$y(t) = \int_0^t (10)(1)(d\lambda) = 10\lambda \Big|_0^t = 10t$$

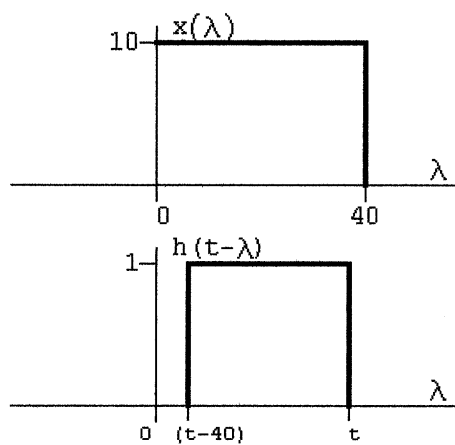 $40 \leq t \leq 80$ :


$$y(t) = \int_{t-40}^{40} (10)(1)(d\lambda) = 10\lambda \Big|_{t-40}^{40} = 10(80 - t)$$

 $t \geq 80$ :  $y(t) = 0$






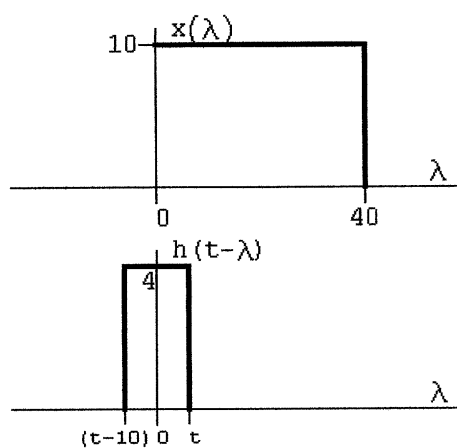


[b]  $0 \leq t \leq 10$ :

$$y(t) = \int_0^t 40 \, d\lambda = 40\lambda \Big|_0^t = 40t$$

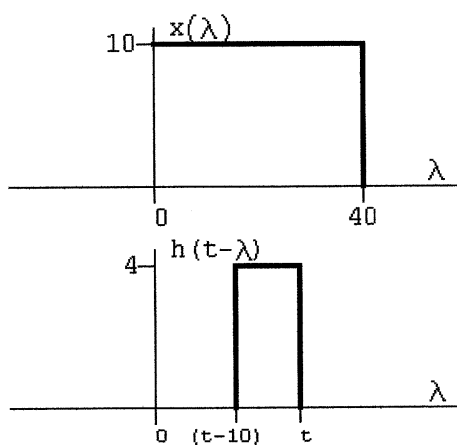 $10 \leq t \leq 40$ :

$$y(t) = \int_{t-10}^t 40 \, d\lambda = 40\lambda \Big|_{t-10}^t = 400$$

$40 \leq t \leq 50$ :

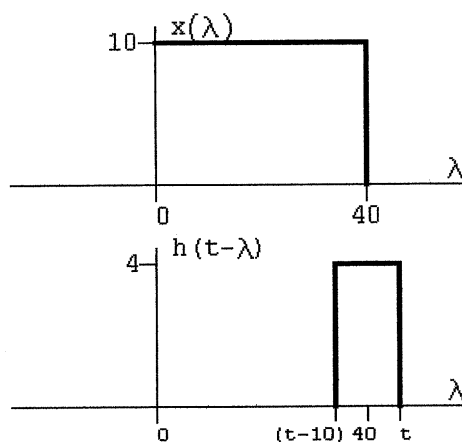

$$y(t) = \int_{t-10}^{40} 40 d\lambda = 40\lambda \Big|_{t-10}^{40} = 40(50 - t)$$

$$t \geq 50 : \quad y(t) = 0$$

[c] The expressions are


$$0 \leq t \leq 1.0 : \quad y(t) = \int_0^t 400 d\lambda = 400\lambda \Big|_0^t = 400t$$

$$1.0 \leq t \leq 40 : \quad y(t) = \int_{t-1}^t 400 d\lambda = 400\lambda \Big|_{t-1}^t = 400$$

$$40 \leq t \leq 41 : \quad y(t) = \int_{t-1}^{40} 400 d\lambda = 400\lambda \Big|_{t-1}^{40} = 400(41 - t)$$

$$41 \leq t < \infty : \quad y(t) = 0$$

[d]

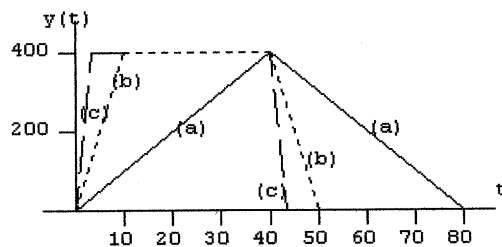

[e] Yes, note that  $h(t)$  is approaching  $40\delta(t)$ , therefore  $y(t)$  must approach  $40x(t)$ , i.e.

$$\begin{aligned} y(t) &= \int_0^t h(t-\lambda)x(\lambda) d\lambda \rightarrow \int_0^t 40\delta(t-\lambda)x(\lambda) d\lambda \\ &\rightarrow 40x(t) \end{aligned}$$

This can be seen in the plot, e.g., in part (c),  $y(t) \cong 40x(t)$ .

P 13.61 [a]  $-1 \leq t \leq 4$ :

$$v_o = 20 \int_0^{t+1} 3\lambda d\lambda = 30\lambda^2 \Big|_0^{t+1} = 30t^2 + 60t + 30$$

 $4 \leq t \leq 7$ :

$$\begin{aligned} v_o &= 20 \int_0^5 3\lambda d\lambda + 20 \int_5^{t+1} (20 - \lambda) d\lambda \\ &= 30\lambda^2 \Big|_0^5 + 400\lambda \Big|_5^{t+1} - 10\lambda^2 \Big|_5^{t+1} \\ &= -10t^2 + 380t - 610 \end{aligned}$$

 $7 \leq t \leq 12$ :

$$\begin{aligned} v_o &= 20 \int_{t-7}^5 3\lambda d\lambda + 20 \int_5^{t+1} (20 - \lambda) d\lambda \\ &= 30\lambda^2 \Big|_{t-7}^5 + 400\lambda \Big|_5^{t+1} - 10\lambda^2 \Big|_5^{t+1} \\ &= -40t^2 + 800t - 2080 \end{aligned}$$


 $12 \leq t \leq 19$ :

$$\begin{aligned} v_o &= 20 \int_{t-7}^{t+1} (20 - \lambda) d\lambda = 400\lambda \Big|_{t-7}^{t+1} - 10\lambda^2 \Big|_{t-7}^{t+1} \\ &= -160t + 3680 \end{aligned}$$

 $19 \leq t \leq 27$ :

$$\begin{aligned} v_o &= 20 \int_{t-7}^{20} (20 - \lambda) d\lambda = 400\lambda \Big|_{t-7}^{20} - 10\lambda^2 \Big|_{t-7}^{20} \\ &= 10t^2 - 540t + 7290 \end{aligned}$$

[b]

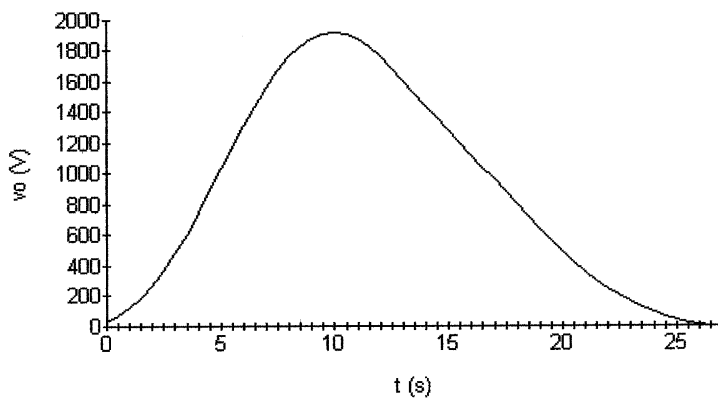

P 13.62 [a]  $h(\lambda) = \frac{5}{10}\lambda \quad 0 \leq \lambda \leq 10 \text{ s}$

$$h(\lambda) = 10 - \frac{5}{10}\lambda \quad 10 \leq \lambda \leq 20 \text{ s}$$

$$h(\lambda) = 0 \quad 20 \leq \lambda \leq \infty$$

$$0 \leq t \leq 10 \text{ s:}$$

$$v_o = \int_0^t (0.5\lambda)(4) d\lambda = 2 \frac{\lambda^2}{2} \Big|_0^t = t^2$$

$$10 \leq t \leq 20 \text{ s:}$$

$$v_o = \int_0^{10} 2\lambda d\lambda + \int_{10}^t 4(10 - 0.5\lambda) d\lambda$$


$$v_o = 100 + 40t - 400 - t^2 + 100 = 40t - 200 - t^2 \text{ V}$$

$$20 \leq t \leq \infty:$$

$$v_o = \int_0^{10} 2\lambda d\lambda + \int_{10}^{20} 4(10 - 0.5\lambda) d\lambda$$

$$v_o = 100 + 400 - (400 - 100) = 200 \text{ V}$$


[b]

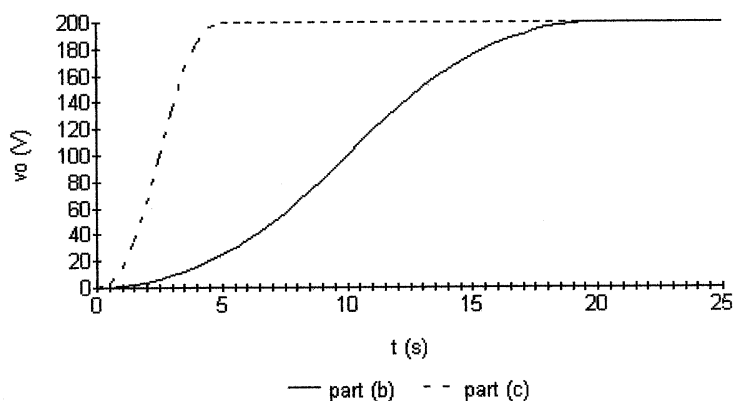

[c]  $h(\lambda) = 8\lambda \quad 0 \leq \lambda \leq 2.5 \text{ s}$

$$h(\lambda) = 40 - 8\lambda \quad 2.5 \leq \lambda \leq 5 \text{ s}$$
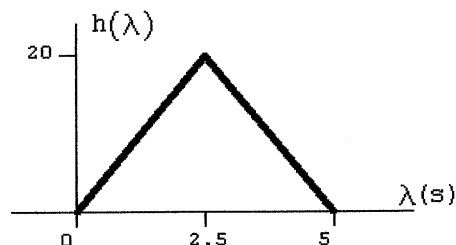
$$h(\lambda) = 0 \quad 5 \leq \lambda \leq \infty$$



$$0 \leq t \leq 2.5 \text{ s:}$$

$$v_o = \int_0^t 32\lambda d\lambda = 16t^2 \text{ V}$$

$$2.5 \leq t \leq 5 \text{ s:}$$


$$v_o = \int_0^{2.5} 32\lambda d\lambda + \int_{2.5}^t 4(40 - 8\lambda) d\lambda = 160t - 200 - 16t^2 \text{ V}$$

$$5 \leq t \leq \infty:$$

$$v_o = \int_0^{2.5} 32\lambda d\lambda + \int_{2.5}^5 4(40 - 8\lambda) d\lambda = 200 \text{ V}$$


- [d] The waveform in part (c) is closer to replicating the input waveform because in part (c)  $h(\lambda)$  is closer to being an ideal impulse response. That is, the area was preserved as the base was shortened.

P 13.63 [a]

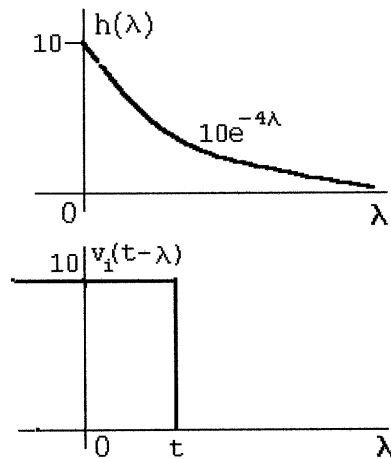

$$\begin{aligned} v_o &= \int_0^t 10(10e^{-4\lambda}) d\lambda \\ &= 100 \frac{e^{-4\lambda}}{-4} \Big|_0^t = -25[e^{-4t} - 1] \\ &= 25(1 - e^{-4t}) \text{ V}, \quad 0 \leq t \leq \infty \end{aligned}$$

[b]

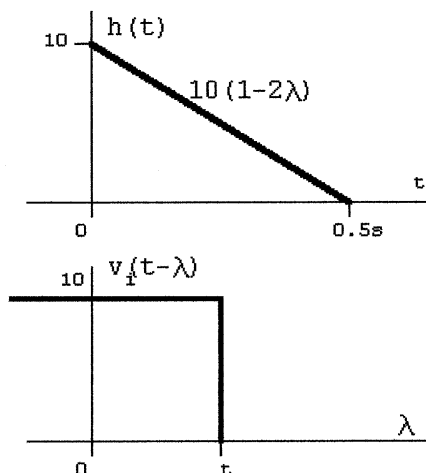


$$0 \leq t \leq 0.5:$$

$$v_o = \int_0^t 100(1 - 2\lambda) d\lambda = 100(\lambda - \lambda^2) \Big|_0^t = 100t(1 - t)$$

$$0.5 \leq t \leq \infty:$$

$$v_o = \int_0^{0.5} 100(1 - 2\lambda) d\lambda = 100(\lambda - \lambda^2) \Big|_0^{0.5} = 25$$

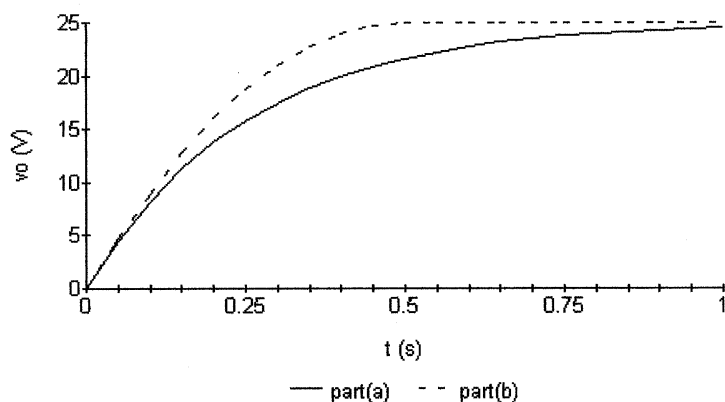

P 13.64 [a] From Problem 13.49(d)

$$H(s) = \frac{3000}{s + 3000}$$

$$h(\lambda) = 3000e^{-3000\lambda}$$


$$0 \leq t \leq 50 \mu\text{s}:$$

$$v_o = \int_0^t 20(3000)e^{-3000\lambda} d\lambda = 20(1 - e^{-3000t}) \text{ V}$$

$$50 \mu\text{s} \leq t \leq \infty:$$

$$v_o = \int_{t-50 \times 10^{-6}}^t 20(3000)e^{-3000\lambda} d\lambda = 20(e^{0.15} - 1)e^{-3000t} \text{ V}$$

[b]

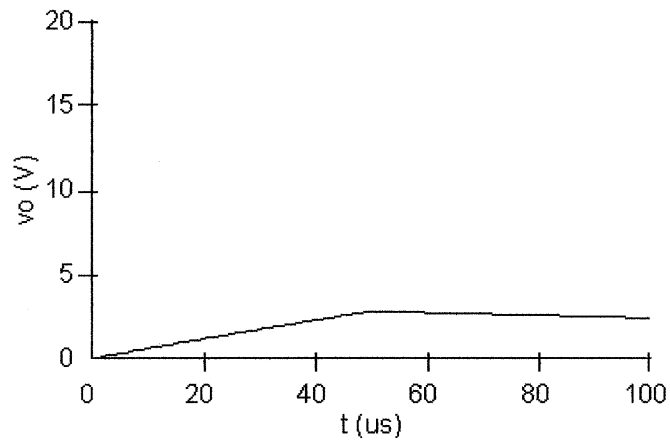


P 13.65 [a]  $H(s) = \frac{80,000}{s + 80,000} \quad \therefore h(\lambda) = 80,000e^{-80,000\lambda}$

$0 \leq t \leq 50 \mu\text{s}:$

$$v_o = \int_0^t 20(80 \times 10^3)e^{-80,000\lambda} d\lambda = 20(1 - e^{-80,000t}) \text{ V}$$

$50 \mu\text{s} \leq t \leq \infty:$
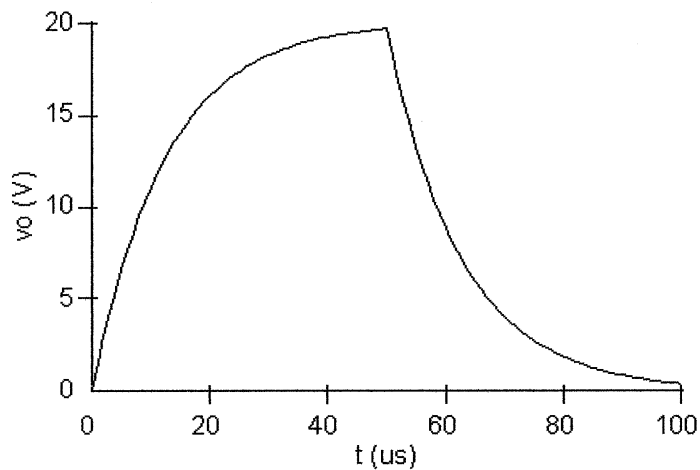
$$v_o = \int_{t-50 \times 10^{-6}}^t 20(80 \times 10^3)e^{-80,000\lambda} d\lambda = 20(e^4 - 1)e^{-80,000t} \text{ V}$$



[b] decrease


[c] The circuit with  $R = 400 \Omega$ .



$$\text{P 13.66 [a]} \quad I_o = \frac{20I_g}{25 + 0.025s} = \frac{800I_g}{s + 1000}$$

$$\frac{I_o}{I_g} = H(s) = \frac{800}{s + 1000}$$
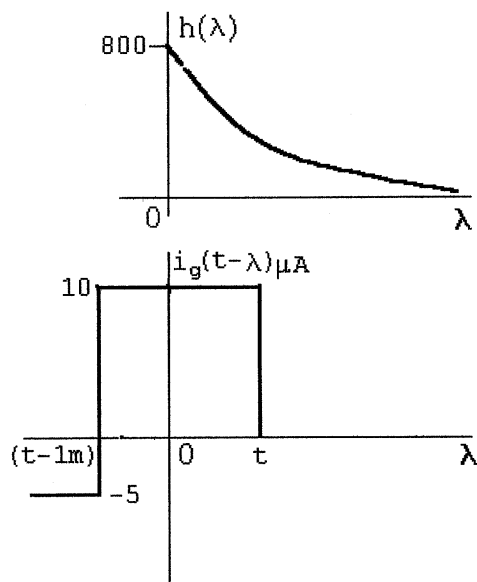
$$h(\lambda) = 800e^{-1000\lambda}u(\lambda)$$




$$0 \leq t \leq 1 \text{ ms:}$$

$$i_o = \int_0^t (10 \times 10^{-6})(800)e^{-1000\lambda} d\lambda = 0.008 \frac{e^{-1000\lambda}}{-1000} \bigg|_0^t$$


$$= 8(1 - e^{-1000t}) \mu\text{A}$$

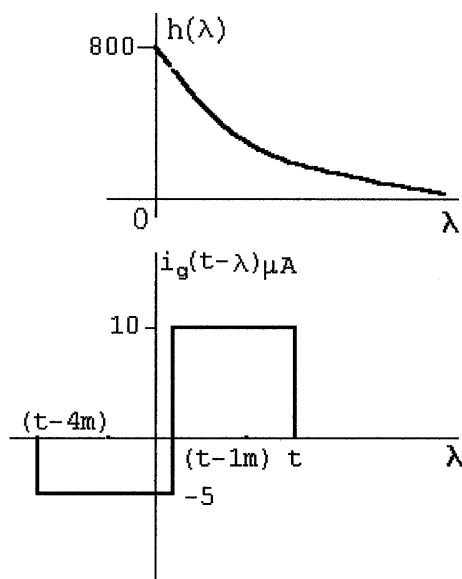$1 \text{ ms} \leq t \leq 4 \text{ ms}$ :



$$\begin{aligned}
 i_o &= \int_0^{t-1 \times 10^{-3}} (-5 \times 10^{-6})(800e^{-1000\lambda} d\lambda) \\
 &\quad + \int_{t-1 \times 10^{-3}}^t (10 \times 10^{-6})(800e^{-1000\lambda} d\lambda) \\
 &= -0.004 \frac{e^{-1000\lambda}}{-1000} \Big|_0^{t-1 \times 10^{-3}} + 0.008 \frac{e^{-1000\lambda}}{-1000} \Big|_{t-1 \times 10^{-3}}^t \\
 &= 4 \left[ e^{-1000(t-0.001)} - 1 \right] - 8 \left[ e^{-1000t} - e^{-1000(t-0.001)} \right] \\
 i_o &= [12e^{-1000(t-0.001)} - 8e^{-1000t} - 4] \mu\text{A}
 \end{aligned}$$

$4 \text{ ms} < t < \infty$ :

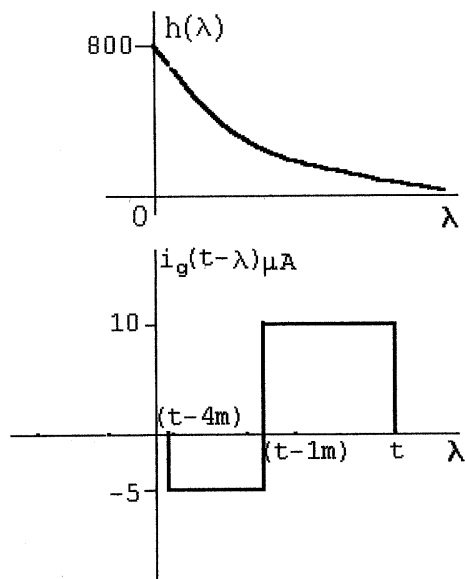

$$\begin{aligned}
 i_o &= \int_{t-0.004}^{t-0.001} -0.004e^{-1000\lambda} d\lambda + \int_{t-0.001}^t 0.008e^{-1000\lambda} d\lambda \\
 &= \left[ 4e^{-1000\lambda} \Big|_{t-0.004}^{t-0.001} - 8e^{-1000\lambda} \Big|_{t-0.001}^t \right] \times 10^{-6} \\
 i_o &= [12e^{-1000(t-0.001)} - 4e^{-1000(t-0.004)} - 8e^{-1000t}] \mu\text{A}
 \end{aligned}$$

[b]  $V_o = 0.025sI_o = \frac{20sI_g}{s+1000}$


$$\frac{V_o}{I_g} = H(s) = \frac{20s}{s+1000} = 20 - \frac{20,000}{s+1000}$$

$$h(\lambda) = 20\delta(\lambda) - 20,000e^{-1000\lambda}$$

$0 < t < 0.001 \text{ s}$ :


$$\begin{aligned}
 v_o &= \int_0^t (10 \times 10^{-6}) [20\delta(\lambda) - 20,000e^{-1000\lambda}] d\lambda \\
 &= 200 \times 10^{-6} - 0.2 \frac{e^{-1000\lambda}}{-1000} \Big|_0^t \\
 &= 200 \times 10^{-6} + 200 \times 10^{-6} [e^{-1000t} - 1] = 200e^{-1000t} \mu\text{V}
 \end{aligned}$$
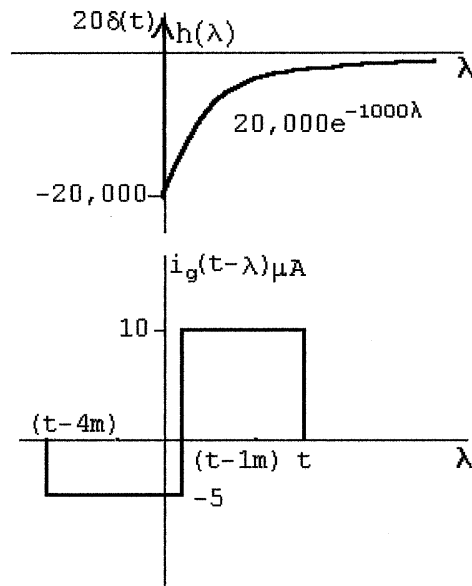
$$0.001 \text{ s} < t < 0.004 \text{ s:}$$



$$\begin{aligned}
 v_o &= \int_0^{t-0.001} (-5 \times 10^{-6}) [20\delta(\lambda) - 20,000e^{-1000\lambda}] d\lambda \\
 &\quad + \int_{t-0.001}^t (10 \times 10^{-6}) (-20,000e^{-1000\lambda}) d\lambda \\
 &= -100 \times 10^{-6} + 0.1 \frac{e^{-1000\lambda}}{-1000} \Big|_0^{t-0.001} - 0.2 \frac{e^{-1000\lambda}}{-1000} \Big|_{t-0.001}^t \\
 &= -100 \times 10^{-6} - 0.1 \times 10^{-3} e^{-1000(t-0.001)} + 0.1 \times 10^{-3} \\
 &\quad + 0.2 \times 10^{-3} e^{-1000t} - 0.2 \times 10^{-3} e^{-1000(t-0.001)} \\
 &= 200e^{-1000t} - 300e^{-1000(t-0.001)} \mu\text{V}
 \end{aligned}$$

$0.004\text{ s} < t < \infty$ :

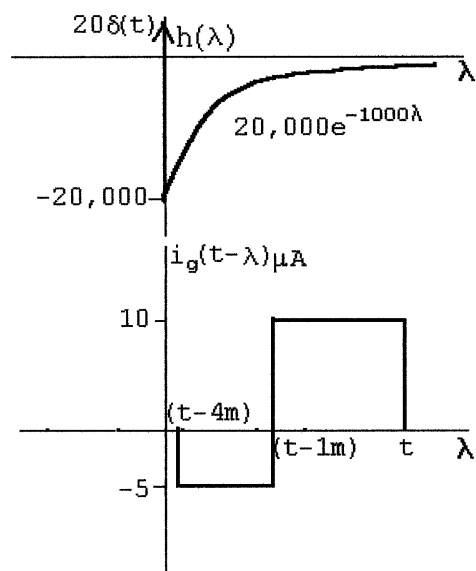

$$\begin{aligned}
 v_o &= \int_{t-0.004}^{t-0.001} (-5 \times 10^{-6})(-20,000e^{-1000\lambda}) d\lambda \\
 &\quad + \int_{t-0.001}^t (10 \times 10^{-6})(-20,000e^{-1000\lambda}) d\lambda \\
 &= 200e^{-1000t} - 300e^{-1000(t-0.001)} + 100e^{-1000(t-0.004)} \mu\text{V}
 \end{aligned}$$

[c] At  $t = 0.001^-$ :

$$i_o = 8(1 - e^{-1}) = 5.06 \mu\text{A}; \quad i_{20\Omega} = (10 - 5.06) = 4.94 \mu\text{A}$$

$$\therefore v_o = 20(4.94 \times 10^{-6}) - 5(5.06 \times 10^{-6}) = 73.58 \mu\text{V}$$

From the solution for  $v_o$  we have

$$v_o(0.001^-) = 200e^{-1} = 73.58 \mu\text{V} \quad (\text{checks})$$

At  $t = 0.001^+$ :

$$i_o(0.001^+) = i_o(0.001^-) = 5.06 \mu\text{A}$$

$$i_{20\Omega} = (-5 - 5.06) \mu\text{A} = -10.06 \mu\text{A}$$

$$\therefore v_o(0.001^+) = 20(-10.06 \times 10^{-6}) + 5(5.06 \times 10^{-6}) = -226.42 \mu\text{V}$$

From the solution for  $v_o$  we have

$$v_o(0.001^+) = 200e^{-1} - 300 = -226.42 \mu\text{V} \quad (\text{checks})$$

At  $t = 0.004^-$ :

$$i_o = 12e^{-3} - 8e^{-4} - 4 = -3.55 \mu\text{A}$$

$$i_{20\Omega} = (-5 + 3.55) = -1.45 \mu\text{A}$$

$$v_o = 20(-1.45 \times 10^{-6}) - 5(-3.55 \times 10^{-6}) = -11.27 \mu\text{V}$$

From the solution for  $v_o$ ,

$$v_o((0.004)^-) = 200e^{-4} - 300e^{-3} = -11.27 \mu\text{V} \quad (\text{checks})$$

At  $t = 0.004^+$ :

$$i_o(0.004^+) = i_o(0.004^-) = -3.55 \mu\text{A}; \quad i_{20\Omega} = 3.55 \mu\text{A}$$

$$i_o = 20(3.55 \times 10^{-6}) + 5(3.55 \times 10^{-6}) = 88.73 \mu\text{V}$$

From the solution for  $v_o$ ,


$$v_o(0.004^+) = 200e^{-4} - 300e^{-3} + 100 = 88.73 \mu\text{V} (\text{checks})$$

P 13.67  $v_i = 10 \sin \lambda [u(\lambda) - u(\lambda - \pi)]$

$$H(s) = \frac{1}{s+1}$$

$$h(\lambda) = e^{-\lambda}$$
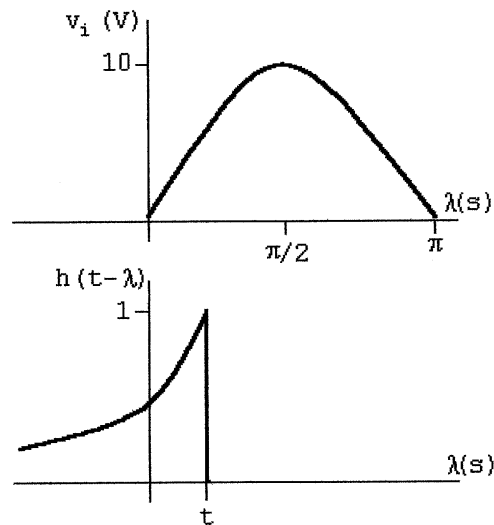
$$h(t-\lambda) = e^{-(t-\lambda)} = e^{-t}e^{\lambda}$$



$$v_o = 10e^{-t} \int_0^t e^{\lambda} \sin \lambda d\lambda$$

$$= 10e^{-t} \left[ \frac{e^{\lambda}}{2} (\sin \lambda - \cos \lambda) \right]_0^t$$

$$= 5e^{-t} [e^t (\sin t - \cos t) + 1]$$

$$= 5(\sin t - \cos t + e^{-t})$$


$$v_o(2.2) = 7.539 \text{ V}$$

P 13.68 [a]  $I_o = \frac{60}{100} I_g; \quad I_g = \frac{V_g}{30}$

$$\therefore I_o = \frac{V_g}{50}; \quad H(s) = \frac{I_o}{V_g} = \frac{1}{50}$$


$$h(\lambda) = 0.02\delta(\lambda)$$

[b]

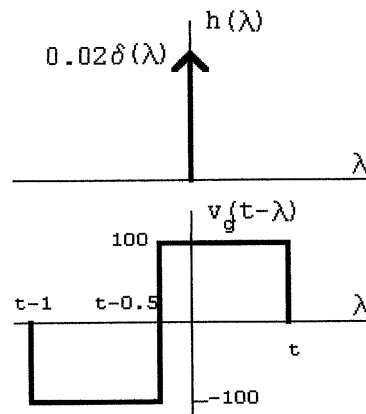

$$0 < t < 0.5 \text{ s}: \quad i_o = \int_0^t 100[0.02\delta(\lambda)] d\lambda = 2 \text{ A}$$

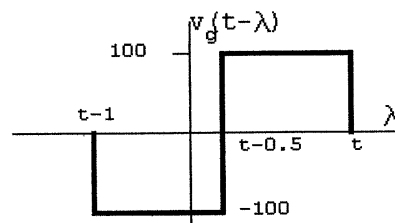
$$0.5 \text{ s} \leq t \leq 1.0 \text{ s}:$$



$$i_o = \int_0^{t-0.5} -100[0.02\delta(\lambda)] d\lambda = -2 \text{ A}$$


$$1 \text{ s} < t < \infty: \quad v_o = 0$$

[c]

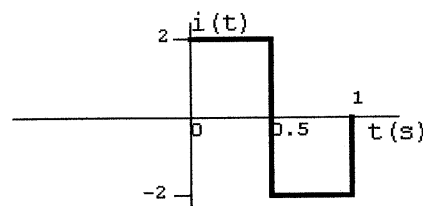

Yes, because the circuit has no memory.

P 13.69 [a]

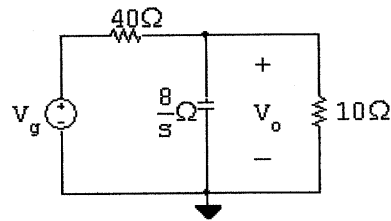


$$\frac{V_o - V_g}{40} + \frac{V_o s}{8} + \frac{V_o}{10} = 0$$

$$(5s + 5)V_o = V_g$$

$$H(s) = \frac{V_o}{V_g} = \frac{0.2}{s+1}; \quad h(\lambda) = 0.2e^{-\lambda}u(\lambda)$$

[b]

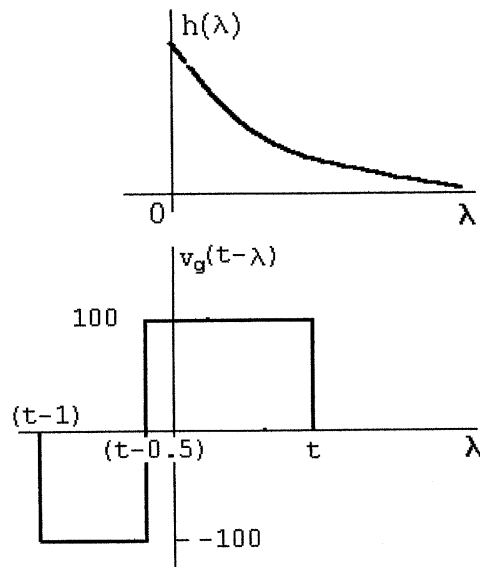


$$0 \leq t \leq 0.5 \text{ s};$$

$$v_o = \int_0^t 100(0.2e^{-\lambda}) d\lambda = 20 \frac{e^{-\lambda}}{-1} \Big|_0^t$$

$$v_o = 20 - 20e^{-t} \text{ V}, \quad 0 \leq t \leq 0.5 \text{ s}$$


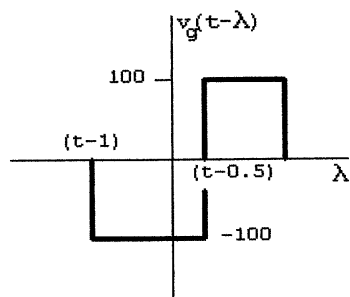
$$0.5 \text{ s} \leq t \leq 1 \text{ s}:$$



$$v_o = \int_0^{t-0.5} (-100)(0.2e^{-\lambda}) d\lambda + \int_{t-0.5}^t 100(0.2e^{-\lambda}) d\lambda$$

$$= -20 \frac{e^{-\lambda}}{-1} \Big|_0^{t-0.5} + 20 \frac{e^{-\lambda}}{-1} \Big|_{t-0.5}^t$$

$$= 40e^{-(t-0.5)} - 20e^{-t} - 20 \text{ V}, \quad 0.5 \text{ s} \leq t \leq 1 \text{ s}$$


$$1 \text{ s} \leq t \leq \infty;$$

$$v_o = \int_{t-1}^{t-0.5} (-100)(0.2e^{-\lambda}) d\lambda + \int_{t-0.5}^t 100(0.2e^{-\lambda}) d\lambda$$

$$= -20 \frac{e^{-\lambda}}{-1} \Big|_{t-1}^{t-0.5} + 20 \frac{e^{-\lambda}}{-1} \Big|_{t-0.5}^t$$


$$= 40e^{-(t-0.5)} - 20e^{-(t-1)} - 20e^{-t} \text{ V}, \quad 1 \text{ s} \leq t \leq \infty$$

[c]

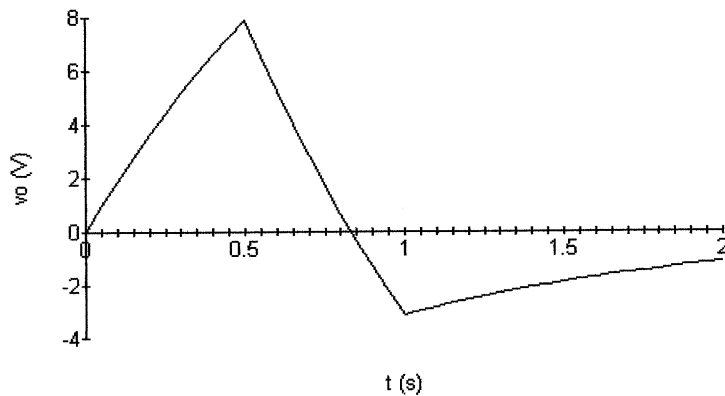

[d] No, the circuit has memory because of the capacitive storage element.

P 13.70

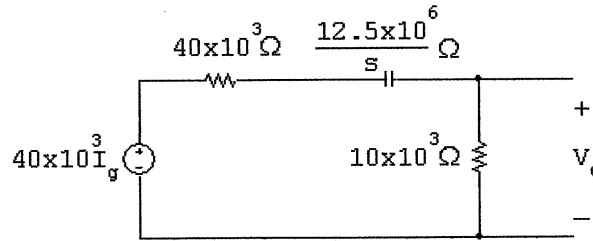

$$V_o = \frac{40 \times 10^3 I_g}{50 \times 10^3 + 12.5 \times 10^6/s} (10 \times 10^3)$$

$$\frac{V_o}{I_g} = H(s) = \frac{8000s}{s + 250}$$

$$H(s) = 8000 \left[ 1 - \frac{250}{s + 250} \right] = 8000 - \frac{2 \times 10^6}{s + 250}$$

$$h(t) = 8000\delta(t) - 2 \times 10^6 e^{-250t}$$

$$\begin{aligned} v_o &= \int_0^{5 \times 10^{-3}} (-10 \times 10^{-3}) [8000\delta(\lambda) - 2 \times 10^6 e^{-250\lambda}] d\lambda \\ &\quad + \int_{5 \times 10^{-3}}^{7 \times 10^{-3}} (5 \times 10^{-3}) [-2 \times 10^6 e^{-250\lambda}] d\lambda \\ &= -80 + 20,000 \int_0^{5 \times 10^{-3}} e^{-250\lambda} d\lambda - 10,000 \int_{5 \times 10^{-3}}^{7 \times 10^{-3}} e^{-250\lambda} d\lambda \\ &= -80 - 80(e^{-1.25} - 1) + 40(e^{-1.75} - e^{-1.25}) \\ &= -120e^{-1.25} + 40e^{-1.75} = -27.43 \text{ V} \end{aligned}$$

Alternate:


$$\begin{aligned} I_g &= \int_0^{2 \times 10^{-3}} (5 \times 10^{-3}) e^{-st} dt + \int_{2 \times 10^{-3}}^{8 \times 10^{-3}} (-10 \times 10^{-3}) e^{-st} dt \\ &= \left[ \frac{5}{s} - \frac{15}{s} e^{-2 \times 10^{-3}s} + \frac{10}{s} e^{-8 \times 10^{-3}s} \right] \times 10^{-3} \\ V_o &= I_g H(s) = \frac{8}{s + 250} [5 - 15e^{-2 \times 10^{-3}s} + 10e^{-8 \times 10^{-3}s}] \\ &= \frac{40}{s + 250} - \frac{120e^{-2 \times 10^{-3}s}}{s + 250} + \frac{80e^{-8 \times 10^{-3}s}}{s + 250} \end{aligned}$$

$$v_o(t) = 40e^{-250t} - 120e^{-250(t-2 \times 10^{-3})}u(t-2 \times 10^{-3}) \\ + 80e^{-250(t-8 \times 10^{-3})}u(t-8 \times 10^{-3})$$

$$v_o(7 \times 10^{-3}) = 40e^{-1.75} - 120e^{-1.25} + 0 = -27.43 \text{ V} \quad (\text{checks})$$

$$\text{P 13.71 [a]} \quad H(s) = \frac{V_o}{V_i} = \frac{1/LC}{s^2 + (R/L)s + (1/LC)} \\ = \frac{25}{s^2 + 10s + 25} = \frac{25}{(s+5)^2}$$
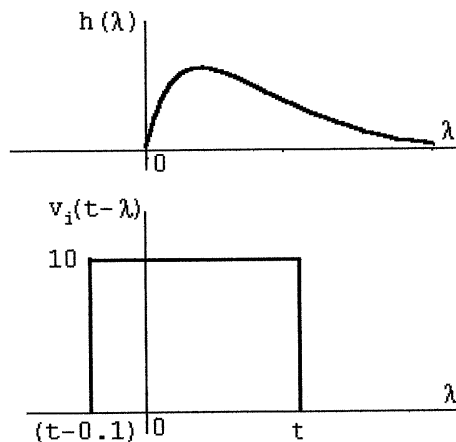
$$h(\lambda) = 25\lambda e^{-5\lambda}u(\lambda)$$




$$0 \leq t \leq 0.10\text{s}:$$

$$v_o = 250 \int_0^t \lambda e^{-5\lambda} d\lambda \\ = 250 \left\{ \frac{e^{-5\lambda}}{25} (-5\lambda - 1) \right\} \Big|_0^t \\ = 10[1 - e^{-5t}(5t + 1)]$$

$$0.1 \leq t \leq \infty:$$

$$v_o = 250 \int_{t-0.1}^t \lambda e^{-5\lambda} d\lambda \\ = 250 \left\{ \frac{e^{-5\lambda}}{25} (-5\lambda - 1) \right\} \Big|_{t-0.1}^t \\ = -10e^{-5t}[(5t + 1) - e^{0.5}(5t + 0.5)]$$

[b]

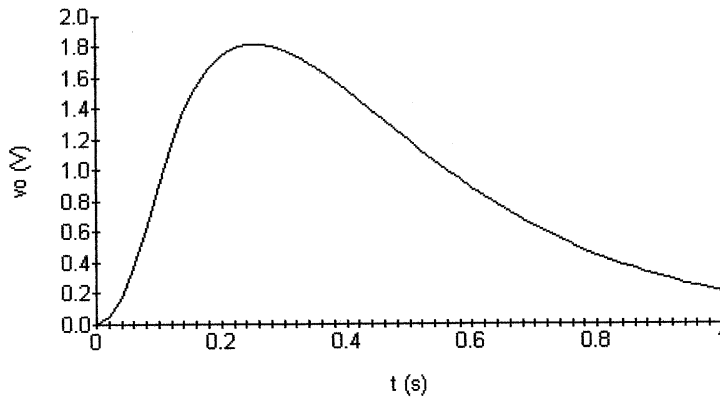

$$\begin{aligned} \text{P 13.72 } H(s) &= \frac{V_o}{V_i} = \frac{8s}{50 + 10s} = \frac{0.8s}{s + 5} \\ &= 0.8 \left[ 1 - \frac{5}{s + 5} \right] = 0.8 - \frac{4}{s + 5} \end{aligned}$$

$$h(t) = 0.8\delta(t) - 4e^{-5t}$$

$$\begin{aligned} v_o &= \int_0^t 75[0.8\delta(\lambda) - 4e^{-5\lambda}] d\lambda \\ &= \int_0^t 60\delta(\lambda) d\lambda - 300 \int_0^t e^{-5\lambda} d\lambda \\ &= 60 - 300 \left. \frac{e^{-5\lambda}}{-5} \right|_0^t \\ &= 60 + 60[e^{-5t} - 1] = 60e^{-5t} \text{ V} \quad 0 \leq t \leq \infty \end{aligned}$$

$$\text{P 13.73 [a] } Y(s) = \int_0^\infty y(t)e^{-st} dt$$

$$\begin{aligned} Y(s) &= \int_0^\infty e^{-st} \left[ \int_0^\infty h(\lambda)x(t-\lambda) d\lambda \right] dt \\ &= \int_0^\infty \int_0^\infty e^{-st} h(\lambda)x(t-\lambda) d\lambda dt \\ &= \int_0^\infty h(\lambda) \int_0^\infty e^{-st} x(t-\lambda) dt d\lambda \end{aligned}$$

But  $x(t-\lambda) = 0$  when  $t < \lambda$


$$\text{Therefore } Y(s) = \int_0^\infty h(\lambda) \int_\lambda^\infty e^{-st} x(t-\lambda) dt d\lambda$$

Let  $u = t - \lambda$ ;  $du = dt$ ;  $u = 0, \quad t = \lambda; \quad u = \infty, \quad t = \infty$


$$\begin{aligned} Y(s) &= \int_0^\infty h(\lambda) \int_0^\infty e^{-s(u+\lambda)} x(u) du d\lambda \\ &= \int_0^\infty h(\lambda) e^{-s\lambda} \int_0^\infty e^{-su} x(u) du d\lambda \\ &= \int_0^\infty h(\lambda) e^{-s\lambda} X(s) d\lambda = H(s) X(s) \end{aligned}$$

Note on  $x(t - \lambda) = 0, \quad t < \lambda$

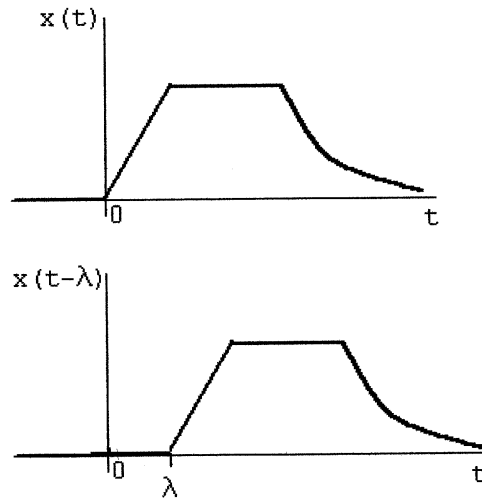We are using one-sided Laplace transforms; therefore  $h(t)$  and  $X(t)$  are assumed zero for  $t < 0$ .


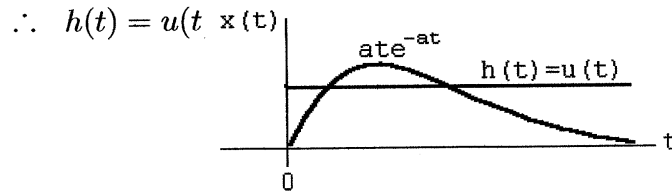
$$[b] \quad F(s) = \frac{a}{s(s+a)^2} = \frac{1}{s} \cdot \frac{a}{(s+a)^2} = H(s)X(s)$$



$$\begin{aligned} \therefore f(t) &= \int_0^t (1) a \lambda e^{-a\lambda} d\lambda = a \left[ \frac{e^{-a\lambda}}{a^2} (-a\lambda - 1) \right] \Big|_0^t \\ &= \frac{1}{a} [e^{-at}(-at - 1) - 1(-1)] = \frac{1}{a} [1 - e^{-at} - ate^{-at}] \\ &= \left[ \frac{1}{a} - \frac{1}{a} e^{-at} - te^{-at} \right] u(t) \end{aligned}$$

Check:

$$F(s) = \frac{a}{s(s+a)^2} = \frac{K_0}{s} + \frac{K_1}{(s+a)^2} + \frac{K_2}{s+a}$$

$$K_0 = \frac{1}{a}; \quad K_1 = -1; \quad K_2 = \frac{d}{ds} \left( \frac{a}{s} \right)_{s=-a} = -\frac{1}{a}$$

$$f(t) = \left[ \frac{1}{a} - te^{-at} - \frac{1}{a}e^{-at} \right] u(t)$$

$$\begin{aligned} \text{P 13.74 } H(j8000) &= \frac{10^4(6000 + j8000)}{-64 \times 10^6 + j7 \times 10^6 + 88 \times 10^6} \\ &= \frac{10^7(6 + j8)}{10^6(24 + j7)} = 4/\underline{36.87^\circ} \end{aligned}$$

$$\therefore v_o(t) = 50 \cos(8000t + 36.87^\circ) \text{ V}$$

$$\text{P 13.75 [a] } H(s) = \frac{-Z_f}{Z_i}$$

$$Z_f = \frac{(1/C_f)}{s + (1/R_f C_f)} = \frac{4 \times 10^9}{s + 16,000}$$


$$Z_i = \frac{R_i[s + (1/R_i C_i)]}{s} = \frac{25,000(s + 8000)}{s}$$

$$H(s) = \frac{-16 \times 10^4 s}{(s + 8000)(s + 16,000)}$$

$$\text{[b] } H(j8000) = \frac{-16 \times 10^4(j8000)}{(8000 + j8000)(16,000 + j8000)} = \sqrt{40}/\underline{-161.57^\circ}$$

$$\begin{aligned} v_o(t) &= (200\sqrt{10}) \times 10^{-3}(\sqrt{40}) \cos(8000t - 161.57^\circ) \\ &= 4 \cos(8000t - 161.57^\circ) \text{ V} \end{aligned}$$

P 13.76 [a]

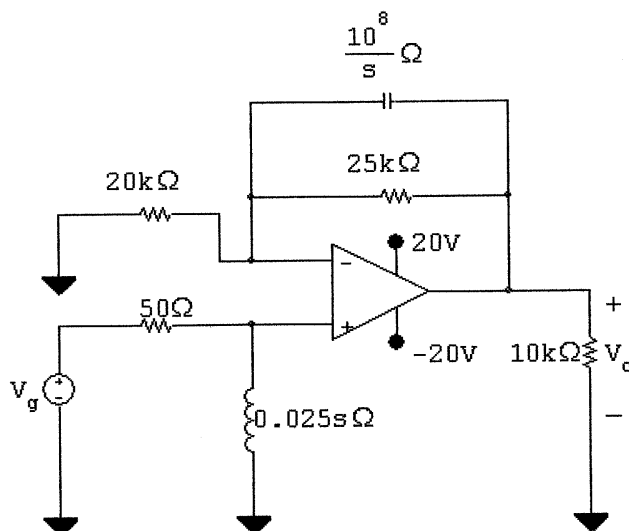

$$V_p = \frac{0.025s}{50 + 0.025s} V_g = \frac{s}{s + 2000} V_g$$

$$V_n = V_p$$

$$\frac{V_p}{20,000} + \frac{V_p - V_o}{25,000} + \frac{(V_p - V_o)s}{10^8} = 0$$

$$\therefore V_p = \frac{(s + 4000)}{(s + 9000)} V_o$$

$$\frac{sV_g}{s + 2000} = \frac{s + 4000}{s + 9000} V_o$$

$$\therefore H(s) = \frac{V_o}{V_g} = \frac{s(s + 9000)}{(s + 2000)(s + 4000)}$$

[b]  $v_g = 10u(t); \quad V_g = \frac{10}{s}$

$$V_o = \frac{10(s + 9000)}{(s + 2000)(s + 4000)} = \frac{K_1}{s + 2000} + \frac{K_2}{s + 4000}$$

$$K_1 = \frac{70,000}{2000} = 35; \quad K_2 = \frac{50,000}{-2000} = -25$$

$$\therefore v_o(t) = (35e^{-2000t} - 25e^{-4000t})u(t) \text{ V}$$

[c]  $\omega = 2000 \text{ rad/s}$

$$\begin{aligned} H(j\omega) &= \frac{j2000(9000 + j2000)}{(2000 + j2000)(4000 + j2000)} \\ &= 1.25 + j0.75 = 1.46/\underline{30.96^\circ} \end{aligned}$$

$$\begin{aligned}\therefore V_{\text{oss}} &= (8)(1.46) \cos(2000t + 30.96^\circ) \\ &= 11.68 \cos(2000t + 30.96^\circ) \text{ V}\end{aligned}$$

$$\text{P 13.77 } V_o = \frac{75}{s} - \frac{100}{s+800} + \frac{25}{s+3200} = \frac{192 \times 10^6}{s(s+800)(s+3200)}$$

$$V_o = H(s)V_g = H(s) \left( \frac{240}{s} \right)$$

$$\therefore H(s) = \frac{800,000}{(s+800)(s+3200)}$$

$$H(j1600) = \frac{8 \times 10^5}{(800 + j1600)(3200 + j1600)} = 0.125 \angle -90^\circ$$

$$\therefore v_o(t) = (40)(0.125) \cos(1600t - 90^\circ) \text{ V} = 5 \sin 1600t \text{ V}$$

$$\text{P 13.78 Original charge on } C_1; \quad q_1 = V_0 C_1$$

$$\text{The charge transferred to } C_2; \quad q_2 = V_0 C_e = \frac{V_0 C_1 C_2}{C_1 + C_2}$$

$$\text{The charge remaining on } C_1; \quad q'_1 = q_1 - q_2 = \frac{V_0 C_1^2}{C_1 + C_2}$$

$$\text{Therefore } V_2 = \frac{q_2}{C_2} = \frac{V_0 C_1}{C_1 + C_2} \quad \text{and} \quad V_1 = \frac{q'_1}{C_1} = \frac{V_0 C_1}{C_1 + C_2}$$

$$\text{P 13.79 [a] } Z_1 = \frac{1/C_1}{s + 1/R_1 C_1} = \frac{20 \times 10^{10}}{s + 20 \times 10^4} \Omega$$

$$Z_2 = \frac{1/C_2}{s + 1/R_2 C_2} = \frac{5 \times 10^{10}}{s + 12,500} \Omega$$

$$\frac{V_0}{Z_2} + \frac{V_0 - 10/s}{Z_1} = 0$$

$$\frac{V_0(s + 12,500)}{5 \times 10^{10}} + \frac{V_0(s + 20 \times 10^4)}{20 \times 10^{10}} = \frac{10}{s} \frac{(s + 20 \times 10^4)}{20 \times 10^{10}}$$

$$V_0 = \frac{2(s + 200,000)}{s(s + 50,000)} = \frac{K_1}{s} + \frac{K_2}{s + 50,000}$$

$$K_1 = \frac{2(200,000)}{50,000} = 8$$

$$K_2 = \frac{2(150,000)}{-50,000} = -6$$

$$\therefore v_o = [8 - 6e^{-50,000t}]u(t) \text{ V}$$



$$[b] \quad I_0 = \frac{V_0}{Z_2} = \frac{2(s + 200,000)(s + 12,500)}{s(s + 50,000)5 \times 10^{10}}$$

$$= 40 \times 10^{-12} \left[ 1 + \frac{162,500s + 25 \times 10^8}{s(s + 50,000)} \right]$$

$$= 40 \times 10^{-12} \left[ 1 + \frac{K_1}{s} + \frac{K_2}{s + 50,000} \right]$$

$$K_1 = 50,000; \quad K_2 = 112,500$$

$$i_o = 40\delta(t) + [2 \times 10^6 + 4.5 \times 10^6 e^{-50,000t}]u(t) \text{ pA}$$

$$[c] \quad \text{When } C_1 = 80 \text{ pF}$$

$$Z_1 = \frac{125 \times 10^8}{s + 12,500} \Omega$$

$$\frac{V_0(s + 12,500)}{500 \times 10^8} + \frac{V_0(s + 12,500)}{125 \times 10^8} = \frac{10}{s} \frac{(s + 12,500)}{125 \times 10^8}$$

$$\therefore V_0 + 4V_0 = \frac{40}{s}$$

$$V_0 = \frac{8}{s}$$

$$v_o = 8u(t) \text{ V}$$

$$I_0 = \frac{V_0}{Z_2} = \frac{8}{s} \frac{(s + 12,500)}{5 \times 10^{10}} = 160 \times 10^{-12} \left[ 1 + \frac{12,500}{s} \right]$$

$$i_o(t) = 160\delta(t) + 2 \times 10^{-6}u(t) \text{ pA}$$

P 13.80 Let  $a = \frac{1}{R_1 C_1} = \frac{1}{R_2 C_2}$

$$\text{Then } Z_1 = \frac{1}{C_1(s + a)} \quad \text{and} \quad Z_2 = \frac{1}{C_2(s + a)}$$


$$\frac{V_o}{Z_2} + \frac{V_o}{Z_1} = \frac{10/s}{Z_1}$$

$$V_o C_2(s + a) + V_o C_1(s + a) = (10/s)C_1(s + a)$$

$$V_o = \frac{10}{s} \left( \frac{C_1}{C_1 + C_2} \right)$$

$$\text{Thus, } v_o \text{ is the input scaled by the factor } \frac{C_1}{C_1 + C_2}$$

P 13.81 [a] The  $s$ -domain circuit is

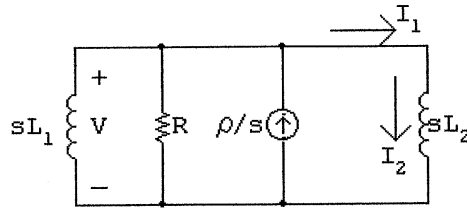

The node-voltage equation is  $\frac{V}{sL_1} + \frac{V}{R} + \frac{V}{sL_2} = \frac{\rho}{s}$

Therefore  $V = \frac{\rho R}{s + (R/L_e)}$  where  $L_e = \frac{L_1 L_2}{L_1 + L_2}$

Therefore  $v = \rho R e^{-(R/L_e)t} u(t) \text{ V}$

[b]  $I_1 = \frac{V}{R} + \frac{V}{sL_2} = \frac{\rho[s + (R/L_2)]}{s[s + (R/L_e)]} = \frac{K_0}{s} + \frac{K_1}{s + (R/L_e)}$

$K_0 = \frac{\rho L_1}{L_1 + L_2}; \quad K_1 = \frac{\rho L_2}{L_1 + L_2}$

Thus we have  $i_1 = \frac{\rho}{L_1 + L_2} [L_1 + L_2 e^{-(R/L_e)t}] u(t) \text{ A}$

[c]  $I_2 = \frac{V}{sL_2} = \frac{(\rho R/L_2)}{s[s + (R/L_e)]} = \frac{K_2}{s} + \frac{K_3}{s + (R/L_e)}$

$K_2 = \frac{\rho L_1}{L_1 + L_2}; \quad K_3 = \frac{-\rho L_1}{L_1 + L_2}$

Therefore  $i_2 = \frac{\rho L_1}{L_1 + L_2} [1 - e^{-(R/L_e)t}] u(t)$


[d]  $\lambda(t) = L_1 i_1 + L_2 i_2 = \rho L_1$

P 13.82 [a] As  $R \rightarrow \infty$ ,  $v(t) \rightarrow \rho L_e \delta(t)$  since the area under the impulse generating function is  $\rho L_e$ .

$i_1(t) \rightarrow \frac{\rho L_1}{L_1 + L_2} \text{ as } R \rightarrow \infty$

$i_2(t) \rightarrow \frac{\rho L_1}{L_1 + L_2} \text{ as } R \rightarrow \infty$

[b] The  $s$ -domain circuit is

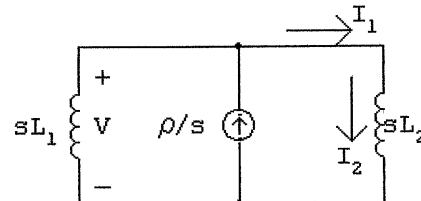

$\frac{V}{sL_1} + \frac{V}{sL_2} = \frac{\rho}{s}; \quad \text{therefore } V = \frac{\rho L_1 L_2}{L_1 + L_2} = \rho L_e$

Therefore  $v(t) = \rho L_e \delta(t)$

$$I_1 = I_2 = \frac{V}{sL_2} = \left( \frac{\rho L_1}{L_1 + L_2} \right) \left( \frac{1}{s} \right)$$

Therefore  $i_1 = i_2 = \frac{\rho L_1}{L_1 + L_2} u(t)$  A

P 13.83 [a] For  $t < 0$ ,  $0.5v_1 = 2v_2$ ; therefore  $v_1 = 4v_2$

$$v_1 + v_2 = 100; \quad \text{therefore } v_1(0^-) = 80 \text{ V}$$


$$[b] \quad v_2(0^-) = 20 \text{ V}$$

$$[c] \quad v_3(0^-) = 0 \text{ V}$$

[d] For  $t > 0$ :

$$I = \frac{100/s}{3.125/s} \times 10^{-6} = 32 \times 10^{-6}$$

$$i(t) = 32\delta(t) \mu\text{A}$$

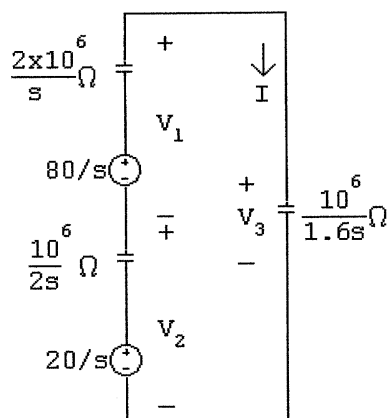

$$[e] \quad v_1(0^+) = -\frac{10^6}{0.5} \int_{0^-}^{0^+} 32 \times 10^{-6} \delta(t) dt + 80 = -64 + 80 = 16 \text{ V}$$


$$[f] \quad v_2(0^+) = -\frac{10^6}{2} \int_{0^-}^{0^+} 32 \times 10^{-6} \delta(t) dt + 20 = -16 + 20 = 4 \text{ V}$$

$$[g] \quad V_3 = \frac{0.625 \times 10^6}{s} \cdot 32 \times 10^{-6} = \frac{20}{s}$$

$$v_3(t) = 20u(t) \text{ V}; \quad v_3(0^+) = 20 \text{ V}$$

$$\text{Check: } v_1(0^+) + v_2(0^+) = v_3(0^+)$$

P 13.84 [a] For  $t < 0$ :

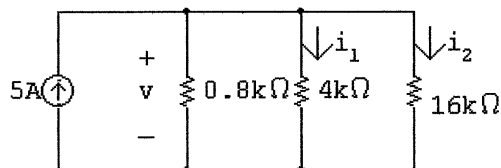

$$R_{\text{eq}} = 0.8\text{ k}\Omega \parallel 4\text{ k}\Omega \parallel 16\text{ k}\Omega = 0.64\text{ k}\Omega; \quad v = 5(640) = 3200\text{ V}$$

$$i_1(0^-) = \frac{3200}{4000} = 0.8\text{ A}; \quad i_2(0^-) = \frac{3200}{1600} = 0.2\text{ A}$$

[b] For  $t > 0$ :

$$i_1 + i_2 = 0$$

$$8(\Delta i_1) = 2(\Delta i_2)$$


$$i_1(0^-) + \Delta i_1 + i_2(0^-) + \Delta i_2 = 0; \quad \text{therefore } \Delta i_1 = -0.2\text{ A}$$

$$\Delta i_2 = -0.8\text{ A}; \quad i_1(0^+) = 0.8 - 0.2 = 0.6\text{ A}$$

[c]  $i_2(0^-) = 0.2\text{ A}$

[d]  $i_2(0^+) = 0.2 - 0.8 = -0.6\text{ A}$

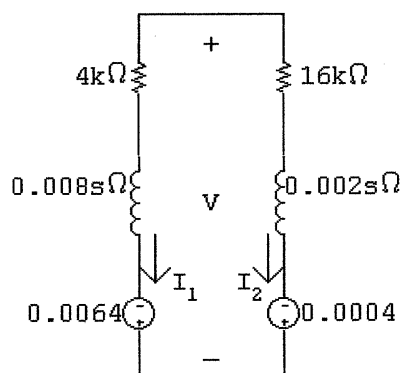[e] The  $s$ -domain equivalent circuit for  $t > 0$  is



$$I_1 = \frac{0.006}{0.01s + 20,000} = \frac{0.6}{s + 2 \times 10^6}$$

$$i_1(t) = 0.6e^{-2 \times 10^6 t} u(t)\text{ A}$$


[f]  $i_2(t) = -i_1(t) = -0.6e^{-2 \times 10^6 t} u(t)\text{ A}$

$$[\text{g}] \quad V = -0.0064 + (0.008s + 4000)I_1 = \frac{-0.0016(s + 6.5 \times 10^6)}{s + 2 \times 10^6}$$

$$= -1.6 \times 10^{-3} - \frac{7200}{s + 2 \times 10^6}$$

$$v(t) = [-1.6 \times 10^{-3}\delta(t)] - [7200e^{-2 \times 10^6 t}u(t)] \text{ V}$$

P 13.85 [a]

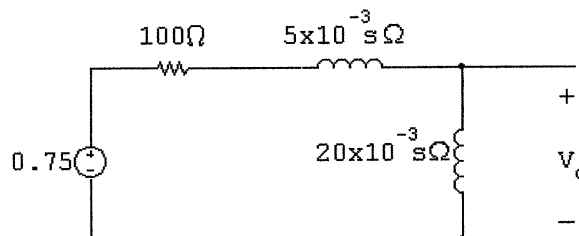

$$V_o = \frac{0.75}{100 + 25 \times 10^{-3}s} \cdot 20 \times 10^{-3}s$$

$$= \frac{0.6s}{s + 4000} = 0.6 - \frac{2400}{s + 4000}$$

$$v_o(t) = 0.6\delta(t) - 2400e^{-4000t}u(t) \text{ V}$$

[b] At  $t = 0$  the voltage impulse establishes a current in the inductors; thus


$$i_L(0) = \frac{10^3}{25} \int_{0^-}^{0^+} 750 \times 10^{-3}\delta(t) dt = 30 \text{ A}$$

It follows that since  $i_L(0^-) = 0$  that

$$\frac{di_L}{dt}(0) = 30\delta(t)$$

$$\therefore v_o(0) = (20 \times 10^{-3})(30\delta(t)) = 0.6\delta(t)$$

This agrees with our solution.

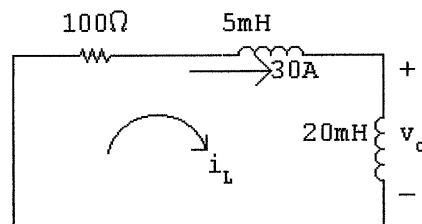At  $t = 0^+$  our circuit is

$$\therefore i_L(t) = 30e^{-t/\tau} \text{ A}, \quad t \geq 0^+$$


$$\tau = L/R = 0.25 \text{ ms}$$

$$\therefore i_L(t) = 30e^{-4000t} \text{ A}, \quad t \geq 0^+$$

$$v_o(t) = 20 \times 10^{-3} \frac{di_L}{dt} = -2400e^{-4000t} \text{ V}, \quad t \geq 0^+$$

which agrees with our solution.

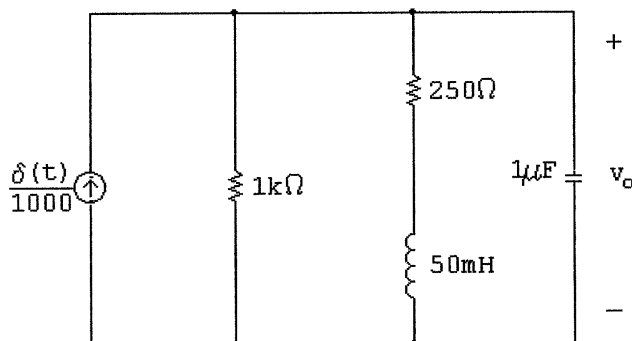- P 13.86 [a] After making a source transformation, the circuit is as shown. The impulse current will pass through the capacitive branch since it appears as a short circuit to the impulsive current,



$$\text{Therefore } v_o(0^+) = 10^6 \int_{0^-}^{0^+} \left[ \frac{\delta(t)}{1000} \right] dt = 1000 \text{ V}$$

$$\text{Therefore } w_C = (0.5)Cv^2 = 0.5 \text{ J}$$

$$\text{[b] } i_L(0^+) = 0; \quad \text{therefore } w_L = 0 \text{ J}$$

$$\text{[c] } V_o(10^{-6})s + \frac{V_o}{250 + 0.05s} + \frac{V_o}{1000} = 10^{-3}$$

Therefore


$$V_o = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

$$= \frac{K_1}{s + 3000 - j4000} + \frac{K_1^*}{s + 3000 + j4000}$$

$$K_1 = 559.02 \angle -26.57^\circ; \quad K_1^* = 559.02 \angle 26.57^\circ$$

$$v_o = [1118.03e^{-3000t} \cos(4000t - 26.57^\circ)]u(t) \text{ V}$$


[d] The  $s$ -domain circuit is

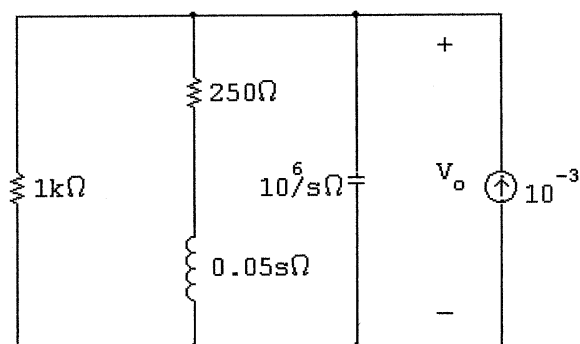

$$\frac{V_o s}{10^6} + \frac{V_o}{250 + 0.05s} + \frac{V_o}{1000} = 10^{-3}$$

Note that this equation is identical to that derived in part [c], therefore the solution for  $V_o$  will be the same.

P 13.87 [a]

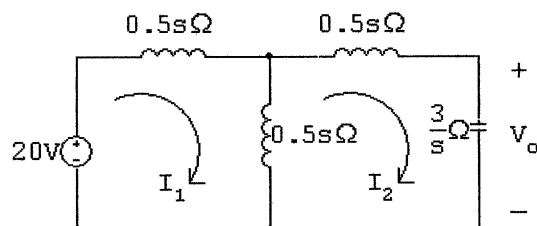

$$20 = sI_1 - 0.5sI_2$$

$$0 = -0.5sI_1 + \left(s + \frac{3}{s}\right) I_2$$

$$\Delta = \begin{vmatrix} s & -0.5s \\ -0.5s & (s + 3/s) \end{vmatrix} = s^2 + 3 - 0.25s^2 = 0.75(s^2 + 4)$$

$$N_1 = \begin{vmatrix} 20 & -0.5s \\ 0 & (s + 3/s) \end{vmatrix} = 20s + \frac{60}{s} = \frac{20s^2 + 60}{s} = \frac{20(s^2 + 3)}{s}$$

$$\begin{aligned} I_1 &= \frac{N_1}{\Delta} = \frac{20(s^2 + 3)}{s(0.75)(s^2 + 4)} = \frac{80}{3} \cdot \frac{s^2 + 3}{s(s^2 + 4)} \\ &= \frac{K_0}{s} + \frac{K_1}{s - j2} + \frac{K_1^*}{s + j2} \end{aligned}$$

$$K_0 = \frac{80}{3} \left(\frac{3}{4}\right) = 20; \quad K_1 = \frac{80}{3} \left[ \frac{-4 + 3}{(j2)(j4)} \right] = \frac{10}{3} \angle 0^\circ$$

$$\therefore i_1 = \left[ 20 + \frac{20}{3} \cos 2t \right] u(t) \text{ A}$$

$$[\text{b}] \quad N_2 = \begin{vmatrix} s & 20 \\ -0.5s & 0 \end{vmatrix} = 10s$$

$$I_2 = \frac{N_2}{\Delta} = \frac{10s}{0.75(s^2 + 4)} = \frac{40}{3} \left( \frac{s}{s^2 + 4} \right) = \frac{K_1}{s - j2} + \frac{K_1^*}{s + j2}$$

$$K_1 = \frac{40}{3} \left( \frac{j2}{j4} \right) = \frac{20}{3} \angle 0^\circ$$

$$i_2 = \frac{40}{3} \cos 2t u(t) \text{ A}$$

$$[\text{c}] \quad V_0 = \frac{3}{s} I_2 = \left( \frac{3}{s} \right) \frac{40}{3} \left( \frac{s}{s^2 + 4} \right) = \frac{40}{s^2 + 4} = \frac{K_1}{s - j2} = \frac{K_1^*}{s + j2}$$

$$K_1 = \frac{40}{j4} = -j10 = 10 \angle 90^\circ$$

$$v_o = 20 \cos(2t - 90^\circ) = 20 \sin 2t$$

$$v_o = [20 \sin 2t] u(t) \text{ V}$$

[d] Let us begin by noting  $i_1$  jumps from 0 to  $(80/3)$  A between  $0^-$  and  $0^+$  and in this same interval  $i_2$  jumps from 0 to  $(40/3)$  A. Therefore in the derivatives of  $i_1$  and  $i_2$  there will be impulses of  $(80/3)\delta(t)$  and  $(40/3)\delta(t)$ , respectively. Thus

$$\frac{di_1}{dt} = \frac{80}{3} \delta(t) - \frac{40}{3} \sin 2t \text{ A/s}$$

$$\frac{di_2}{dt} = \frac{40}{3} \delta(t) - \frac{80}{3} \sin 2t \text{ A/s}$$

From the circuit diagram we have

$$\begin{aligned} 20\delta(t) &= 1 \frac{di_1}{dt} - 0.5 \frac{di_2}{dt} \\ &= \frac{80}{3} \delta(t) - \frac{40}{3} \sin 2t - \frac{20\delta(t)}{3} + \frac{40}{3} \sin 2t \\ &= 20\delta(t) \end{aligned}$$

Thus our solutions for  $i_1$  and  $i_2$  are in agreement with known circuit behavior.

Let us also note the impulsive voltage will impart energy into the circuit. Since there is no resistance in the circuit, the energy will not dissipate.




Thus the fact that  $i_1$ ,  $i_2$ , and  $v_o$  exist for all time is consistent with known circuit behavior.

Also note that although  $i_1$  has a dc component,  $i_2$  does not. This follows from known transformer behavior.


Finally we note the flux linkage prior to the appearance of the impulsive voltage is zero. Now since  $v = d\lambda/dt$ , the impulsive voltage source must be matched to an instantaneous change in flux linkage at  $t = 0^+$  of 20. For the given polarity dots and reference directions of  $i_1$  and  $i_2$  we have

$$\lambda(0^+) = L_1 i_1(0^+) + M i_1(0^+) - L_2 i_2(0^+) - M i_2(0^+)$$
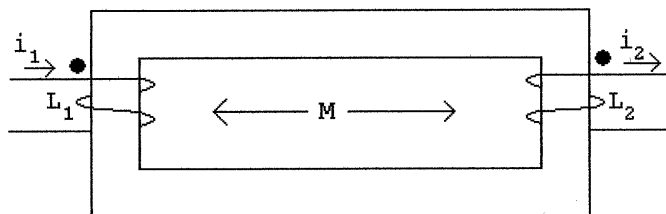
$$\begin{aligned} \lambda(0^+) &= 1 \left( \frac{80}{3} \right) + 0.5 \left( \frac{80}{3} \right) - 1 \left( \frac{40}{3} \right) - 0.5 \left( \frac{40}{3} \right) \\ &= \frac{120}{3} - \frac{60}{3} = 20 \quad (\text{checks}) \end{aligned}$$



P 13.88 [a]

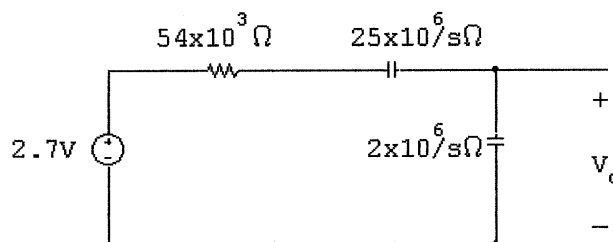

$$\begin{aligned} V_o &= \frac{2.7}{54 \times 10^3 + 25 \times 10^6/s + 2 \times 10^6/s} \cdot \frac{2 \times 10^6}{s} \\ &= \frac{5.4 \times 10^6}{54 \times 10^3 s + 27 \times 10^6} = \frac{100}{s + 500} \end{aligned}$$

$$v_o(t) = 100e^{-500t}u(t) \text{ V}$$

At  $t = 0$  the impulsive current passes through the two capacitors. The voltage on the  $0.04 \mu\text{F}$  capacitor at  $t = 0^+$  is


$$v_{0.04} = 25 \times 10^6 \int_{0^-}^{0^+} 50 \times 10^{-6} \delta(t) dt = 1250 \text{ V}$$

The voltage on the  $0.5 \mu\text{F}$  capacitor at  $t = 0^+$  is

$$v_{0.5} = 2 \times 10^6 \int_{0^-}^{0^+} 50 \times 10^{-6} \delta(t) dt = 100 \text{ V}$$

Note this agrees with our solution.

At  $t = 0^+$  the circuit is

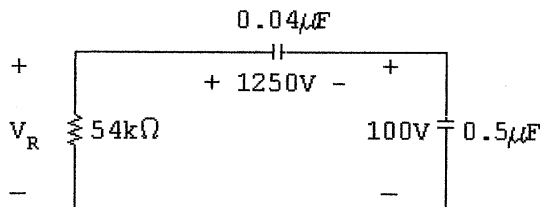

The equivalent capacitance is

$$C_e = \frac{(0.04)(0.5) \times 10^{-12}}{0.54 \times 10^{-6}} = \frac{1}{27} \mu\text{F}$$

Thus, the time constant is

$$\tau = 54 \times 10^3 C_e = 2 \text{ ms}$$

Therefore,  $1/\tau = 500$ , which agrees with our solution.

It follows that

$$v_R(t) = 1350e^{-500t} \text{ V}, \quad t \geq 0^+$$

Therefore

$$v_o(t) = \frac{0.04}{0.54} v_R = 100e^{-500t} \text{ V}, \quad t \geq 0^+$$

which also agrees with our solution.

P 13.89 [a] The circuit parameters are

$$R_a = \frac{120^2}{1200} = 12 \Omega \quad R_b = \frac{120^2}{1800} = 8 \Omega \quad X_a = \frac{120^2}{350} = \frac{1440}{35} \Omega$$

The branch currents are

$$\mathbf{I}_1 = \frac{120/\underline{0^\circ}}{12} = 10/\underline{0^\circ} \text{ A(rms)} \quad \mathbf{I}_2 = \frac{120/\underline{0^\circ}}{j1440/35} = -j\frac{35}{12} = \frac{35}{12}/\underline{-90^\circ} \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{120/\underline{0^\circ}}{8} = 15/\underline{0^\circ} \text{ A(rms)}$$

$$\therefore \mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 25 - j\frac{35}{12} = 25.17/\underline{-6.65^\circ} \text{ A(rms)}$$

Therefore,

$$i_2 = \left(\frac{35}{12}\right) \sqrt{2} \cos(\omega t - 90^\circ) \text{ A} \quad \text{and} \quad i_L = 25.17\sqrt{2} \cos(\omega t - 6.65^\circ) \text{ A}$$

Thus,

$$i_2(0^-) = i_2(0^+) = 0 \text{ A} \quad \text{and} \quad i_L(0^-) = i_L(0^+) = 25\sqrt{2} \text{ A}$$

- [b] Begin by using the s-domain circuit in Fig. 13.60 to solve for  $V_0$  symbolically. Write a single node voltage equation:

$$\frac{V_0 - (V_g + L_\ell I_o)}{sL_\ell} + \frac{V_0}{R_a} + \frac{V_0}{sL_a} = 0$$

$$\therefore V_0 = \frac{(R_a/L_\ell)V_g + I_o R_a}{s + [R_a(L_a + L_\ell)]/L_a L_\ell}$$

where  $L_\ell = 1/120\pi$  H,  $L_a = 12/35\pi$  H,  $R_a = 12\Omega$ , and  $I_o R_a = 300\sqrt{2}$  V. Thus,

$$\begin{aligned} V_0 &= \frac{1440\pi(122.92\sqrt{2}s - 3000\pi\sqrt{2})}{(s + 1475\pi)(s^2 + 14,400\pi^2)} + \frac{300\sqrt{2}}{s + 1475\pi} \\ &= \frac{K_1}{s + 1475\pi} + \frac{K_2}{s - j120\pi} + \frac{K_2^*}{s + j120\pi} + \frac{300\sqrt{2}}{s + 1475\pi} \end{aligned}$$

The coefficients are

$$K_1 = -121.18\sqrt{2} \text{ V} \quad K_2 = 61.03\sqrt{2}/\underline{6.85^\circ} \text{ V} \quad K_2^* = 61.03\sqrt{2}/\underline{-6.85^\circ}$$

Note that  $K_1 + 300\sqrt{2} = 178.82\sqrt{2}$  V. Thus, the inverse transform of  $V_0$  is

$$v_0 = 178.82\sqrt{2}e^{-1475\pi t} + 122.06\sqrt{2}\cos(120\pi t + 6.85^\circ) \text{ V}$$

Initially,

$$v_0(0^+) = 178.82\sqrt{2} + 122.06\sqrt{2}\cos 6.85^\circ = 300\sqrt{2} \text{ V}$$

Note that at  $t = 0^+$  the initial value of  $i_L$ , which is  $25\sqrt{2}$  A, exists in the  $12\Omega$  resistor  $R_a$ . Thus, the initial value of  $V_0$  is  $(25\sqrt{2})(12) = 300\sqrt{2}$  V.


- [c] The phasor domain equivalent circuit has a  $j1\Omega$  inductive impedance in series with the parallel combination of a  $12\Omega$  resistive impedance and a  $j1440/35\Omega$  inductive impedance (remember that  $\omega = 120\pi$  rad/s). Note that  $\mathbf{V}_g = 120/\underline{0^\circ} + (25.17/\underline{-6.65^\circ})(j1) = 125.43/\underline{11.50^\circ}$  V(rms). The node voltage equation in the phasor domain circuit is

$$\frac{\mathbf{V}_0 - 125.43/\underline{11.50^\circ}}{j1} + \frac{\mathbf{V}_0}{12} + \frac{35\mathbf{V}_0}{1440} = 0$$


$$\therefore \mathbf{V}_0 = 122.06/\underline{6.85^\circ} \text{ V(rms)}$$

Therefore,  $v_0 = 122.06\sqrt{2}\cos(120\pi t + 6.85^\circ)$  V, agreeing with the steady-state component of the result in part (b).

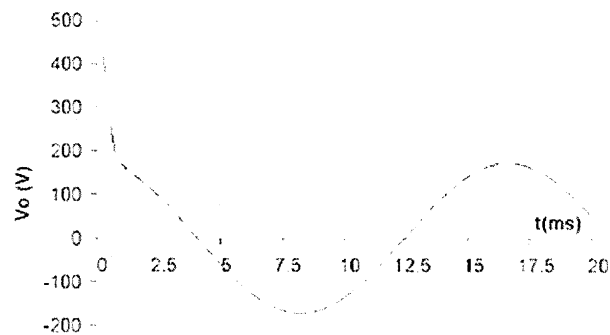[d] A plot of  $v_o$ , generated in Excel, is shown below.



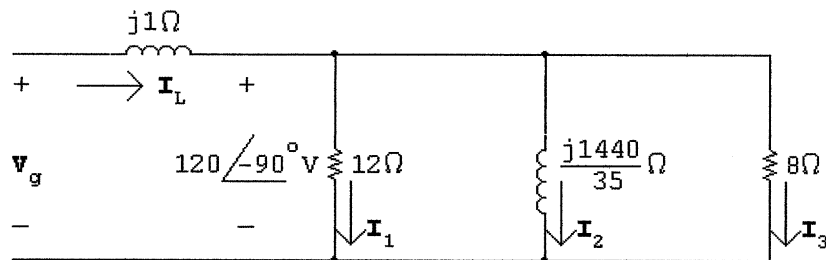P 13.90 [a] At  $t = 0^-$  the phasor domain equivalent circuit is



$$\mathbf{I}_1 = \frac{-j120}{12} = -j10 = 10\angle-90^\circ \text{ A (rms)}$$

$$\mathbf{I}_2 = \frac{-j120(35)}{j1440} = -\frac{35}{12} = \frac{35}{12}\angle 180^\circ \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{-j120}{8} = -j15 = 15\angle-90^\circ \text{ A (rms)}$$

$$\mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = -\frac{35}{12} - j25 = 25.17\angle-96.65^\circ \text{ A (rms)}$$

$$i_L = 25.17\sqrt{2}\cos(120\pi t - 96.65^\circ) \text{ A}$$

$$i_L(0^-) = i_L(0^+) = -2.92\sqrt{2} \text{ A}$$


$$i_2 = \frac{35}{12}\sqrt{2}\cos(120\pi t + 180^\circ) \text{ A}$$

$$i_2(0^-) = i_2(0^+) = -\frac{35}{12}\sqrt{2} = -2.92\sqrt{2} \text{ A}$$

$$\mathbf{V}_g = \mathbf{V}_o + j1\mathbf{I}_L$$

$$\begin{aligned}
 \mathbf{V}_g &= -j120 + 25 - j\frac{35}{12} \\
 &= 25 - j122.92 = 125.43 \angle -78.50^\circ \text{ V (rms)} \\
 v_g &= 125.43\sqrt{2} \cos(120\pi t - 78.50^\circ) \text{ V} \\
 &= 125.43\sqrt{2} [\cos 120\pi t \cos 78.50^\circ + \sin 120\pi t \sin 78.50^\circ] \\
 &= 25\sqrt{2} \cos 120\pi t + 122.92\sqrt{2} \sin 120\pi t \\
 \therefore V_g &= \frac{25\sqrt{2}s + 122.92\sqrt{2}(120\pi)}{s^2 + (120\pi)^2}
 \end{aligned}$$

$s$ -domain circuit:

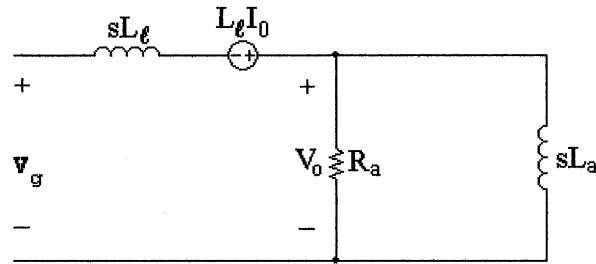

where

$$L_l = \frac{1}{120\pi} \text{ H}; \quad L_a = \frac{12}{35\pi} \text{ H}; \quad R_a = 12 \Omega$$

$$i_L(0) = -2.92\sqrt{2} \text{ A}; \quad i_2(0) = -2.92\sqrt{2} \text{ A}$$

The node voltage equation is

$$0 = \frac{V_o - (V_g + i_L(0)L_l)}{sL_l} + \frac{V_o}{R_a} + \frac{V_o + i_2(0)L_a}{sL_a}$$

Solving for  $V_o$  yields

$$V_o = \frac{V_g R_a / L_l}{[s + R_a(L_l + L_a) / L_a L_l]} + \frac{R_a [i_L(0) - i_2(0)]}{[s + R_a(L_l + L_a) / L_l L_a]}$$

$$\frac{R_a}{L_l} = 1440\pi$$

$$\frac{R_a(L_l + L_a)}{L_l L_a} = \frac{12(\frac{1}{120\pi} + \frac{12}{35\pi})}{(\frac{12}{35\pi})(\frac{1}{120\pi})} = 1475\pi$$

$$i_L(0) - i_2(0) = -2.92\sqrt{2} + 2.92\sqrt{2} = 0$$

$$\begin{aligned}
 \therefore V_o &= \frac{1440\pi [25\sqrt{2}s + 122.92\sqrt{2}(120\pi)]}{(s + 1475\pi)[s^2 + (120\pi)^2]} \\
 &= \frac{K_1}{s + 1475\pi} + \frac{K_2}{s - j120\pi} + \frac{K_2^*}{s + j120\pi}
 \end{aligned}$$


$$K_1 = -14.55\sqrt{2} \quad K_2 = 61.03\sqrt{2}/-83.15^\circ$$


$$\therefore v_o(t) = -14.55\sqrt{2}e^{-1475\pi t} + 122.06\sqrt{2}\cos(120\pi t - 83.15^\circ)\text{V}$$

Check:

$$v_o(0) = (-14.55 + 14.55)\sqrt{2} = 0$$

[b]

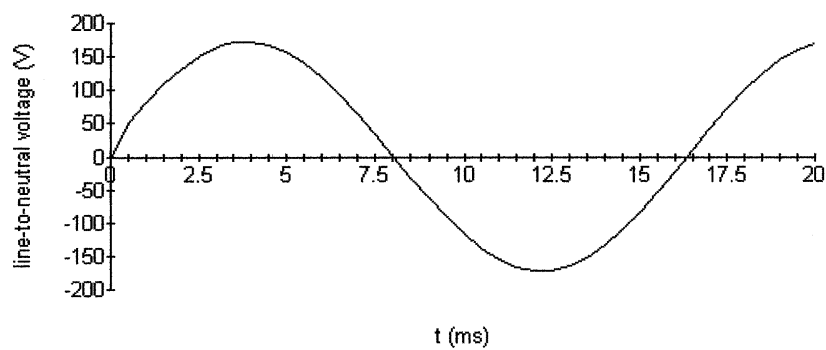

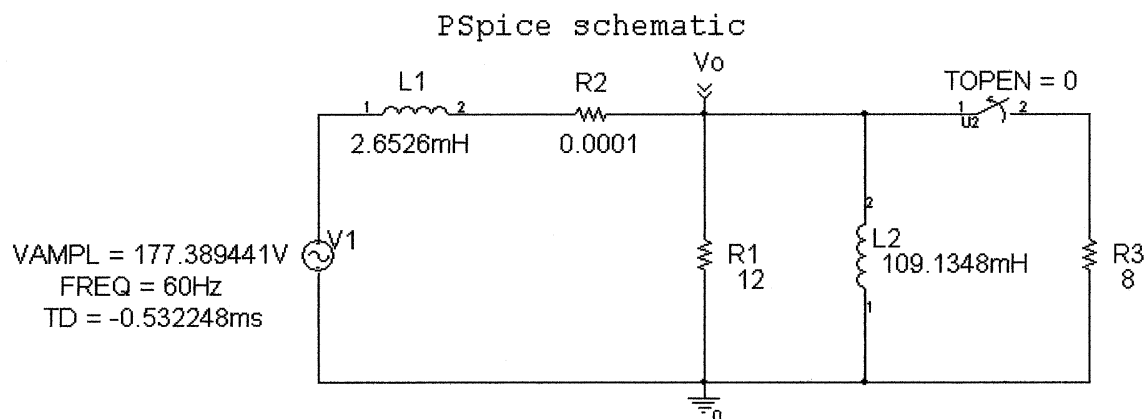

### PSpice output file

```

**** 07/15/01 07:40:45 ***** PSpice Lite (Mar 2000) *****

** Profile: "SCHEMATIC1-tran" [ C:\shortcircuits\solutions\p9_76-SCHEMATIC1-tran.sim ]

****      CIRCUIT DESCRIPTION

*****

** Creating circuit file "p9_76-SCHEMATIC1-tran.sim.cir"
** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS


*Libraries:
* Local Libraries :
* From [PSPICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:
.lib "nom.lib"

*Analysis directives:
.TRAN 0 20ms 0
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
.INC ".\p9_76-SCHEMATIC1.net"

**** INCLUDING p9_76-SCHEMATIC1.net ****
* source P9_76
V_V1      N00637 0
+SIN 0 177.389441V 60Hz -0.532248ms 0 0
L_L1      N00637 N01311 2.6526mH IC=0
L_L2      0 VO 109.1348mH IC=0
R_R1      0 VO 12
R_R2      VO N01311 0.0001
R_R3      0 N01959 8
K_U2      VO N01959 Sw_tOpen PARAMS: tOpen=0 ttran=1u Rclosed=0.01
+ Ropen=1Meg

**** RESUMING p9_76-SCHEMATIC1-tran.sim.cir ****
.END


```

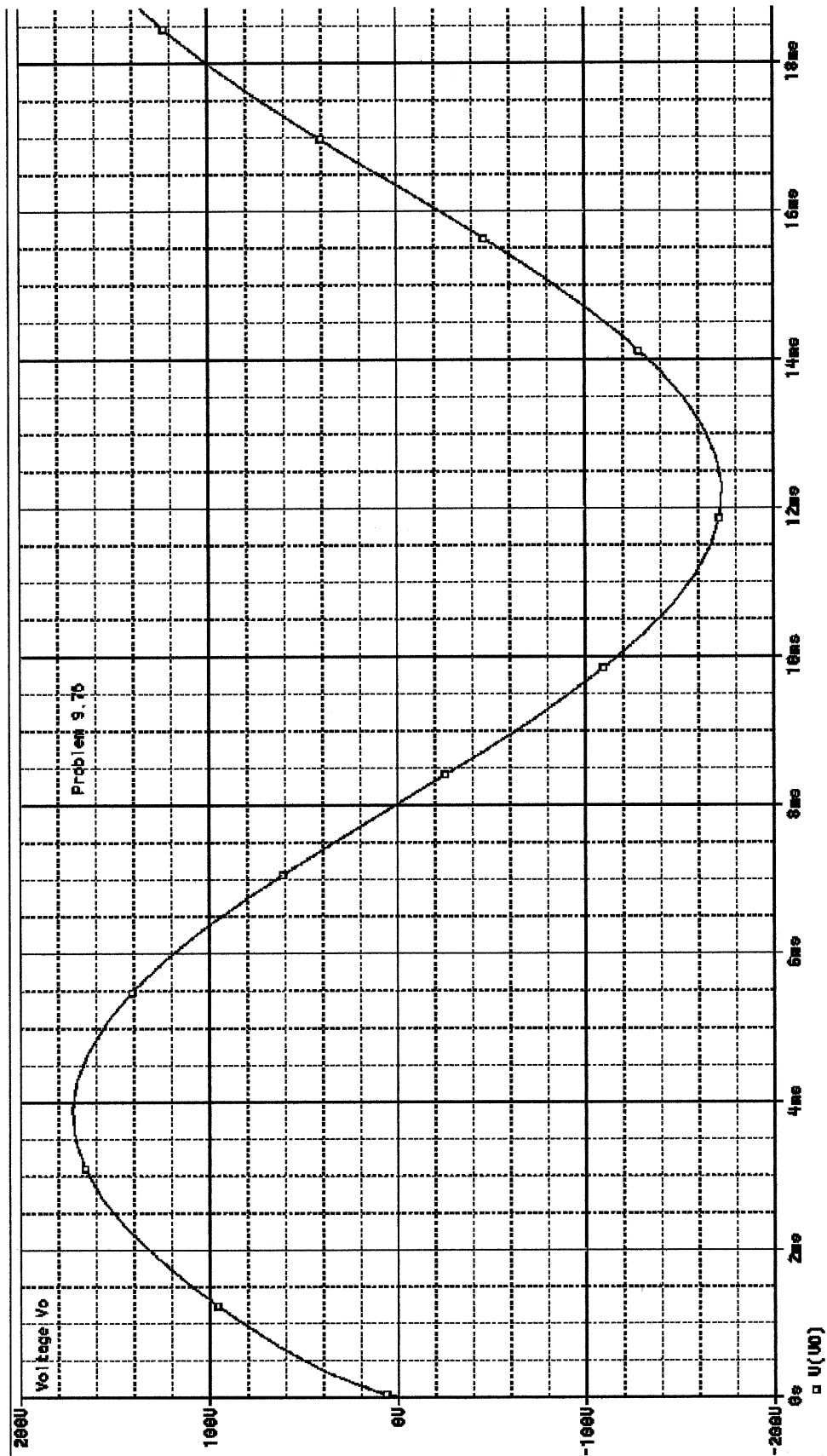



- [c] In the Practical Perspective the line-to-neutral voltage spikes at  $300\sqrt{2}$  V. In Prob. 13.89(c) the line-to-neutral voltage has no spike. Thus the amount of voltage disturbance depends on what part of the cycle the sinusoidal steady-state voltage is switched.

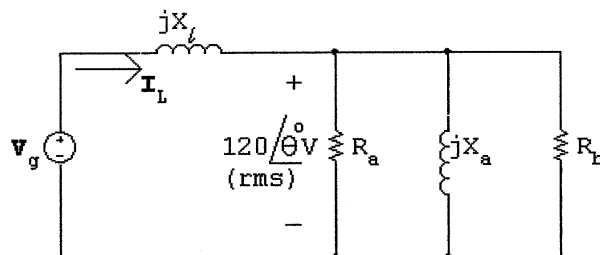P 13.91 [a] First find  $V_g$  before  $R_b$  is disconnected. The phasor domain circuit is



$$\begin{aligned} \mathbf{I}_L &= \frac{120/\theta^\circ}{R_a} + \frac{120/\theta^\circ}{R_b} + \frac{120/\theta^\circ}{jX_a} \\ &= \frac{120/\theta^\circ}{R_a R_b X_a} [(R_a + R_b)X_a = jR_a R_b] \end{aligned}$$

Since  $X_l = 1 \Omega$  we have

$$\mathbf{V}_g = 120/\theta^\circ + \frac{120/\theta^\circ}{R_a R_b X_a} [R_a R_b + j(R_a + R_b)X_a]$$

$$R_a = 12 \Omega; \quad R_b = 8 \Omega; \quad X_a = \frac{1440}{35} \Omega$$

$$\begin{aligned} \mathbf{V}_g &= \frac{120/\theta^\circ}{1400} (1475 + j300) \\ &= \frac{25}{12} \theta^\circ (59 + j12) = 125.43/(\theta + 11.50)^\circ \end{aligned}$$

$$v_g = 125.43\sqrt{2} \cos(120\pi t + \theta + 11.50^\circ) \text{ V}$$


Let  $\beta = \theta + 11.50^\circ$ . Then

$$v_g = 125.43\sqrt{2} (\cos 120\pi t \cos \beta - \sin 120\pi t \sin \beta) \text{ V}$$

Therefore

$$\mathbf{V}_g = \frac{125.43\sqrt{2}(s \cos \beta - 120\pi \sin \beta)}{s^2 + (120\pi)^2}$$

The  $s$ -domain circuit becomes

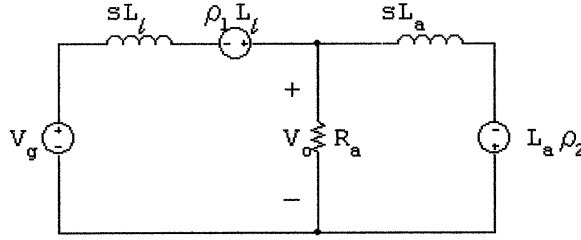

where  $\rho_1 = i_L(0^+)$  and  $\rho_2 = i_2(0^+)$ .

The  $s$ -domain node voltage equation is

$$\frac{V_o - (V_g + \rho_1 L_l)}{sL_l} + \frac{V_o}{R_a} + \frac{V_o + \rho_2 L_a}{sL_a} = 0$$

Solving for  $V_o$  yields

$$V_o = \frac{V_g R_a / L_l + (\rho_1 - \rho_2) R_a}{[s + \frac{(L_a + L_l) R_a}{L_a L_l}]}$$

Substituting the numerical values

$$L_l = \frac{1}{120\pi} \text{ H}; \quad L_a = \frac{12}{35\pi} \text{ H}; \quad R_a = 12 \Omega; \quad R_b = 8 \Omega;$$

gives

$$V_o = \frac{1440\pi V_g + 12(\rho_1 - \rho_2)}{(s + 1475\pi)}$$

Now determine the values of  $\rho_1$  and  $\rho_2$ .

$$\rho_1 = i_L(0^+) \quad \text{and} \quad \rho_2 = i_2(0^+)$$

$$\begin{aligned} \mathbf{I}_L &= \frac{120/\theta^\circ}{R_a R_b X_a} [(R_a + R_b) X_a - j R_a R_b] \\ &= \frac{120/\theta^\circ}{96(1440/35)} \left[ \frac{(20)(1440)}{35} - j96 \right] \\ &= 25.17/(\theta - 6.65^\circ) \text{ A(rms)} \end{aligned}$$

$$\therefore i_L = 25.17\sqrt{2} \cos(120\pi t + \theta - 6.65^\circ) \text{ A}$$

$$i_L(0^+) = \rho_1 = 25.17\sqrt{2} \cos(\theta - 6.65^\circ) \text{ A}$$

$$\therefore \rho_1 = 25\sqrt{2} \cos \theta + 2.92\sqrt{2} \sin \theta \text{ A}$$

$$\mathbf{I}_2 = \frac{120/\theta^\circ}{j(1440/35)} = \frac{35}{12}/(\theta - 90^\circ)$$

$$i_2 = \frac{35}{12}\sqrt{2}\cos(120\pi t + \theta - 90^\circ)\text{A}$$

$$\rho_2 = i_2(0^+) = \frac{35}{12}\sqrt{2}\sin\theta = 2.92\sqrt{2}\sin\theta\text{A}$$

$$\therefore \rho_1 = \rho_2 = 25\sqrt{2}\cos\theta$$

$$(\rho_1 - \rho_2)R_a = 300\sqrt{2}\cos\theta$$

$$\begin{aligned}\therefore V_o &= \frac{1440\pi}{s + 1475\pi} \cdot V_g + \frac{300\sqrt{2}\cos\theta}{s + 1475\pi} \\ &= \frac{1440\pi}{s + 1475\pi} \left[ \frac{125.43\sqrt{2}(s\cos\beta - 120\pi\sin\beta)}{s^2 + 14,400\pi^2} \right] + \frac{300\sqrt{2}\cos\theta}{s + 1475\pi} \\ &= \frac{K_1 + 300\sqrt{2}\cos\theta}{s + 1475\pi} + \frac{K_2}{s - j120\pi} + \frac{K_2^*}{s + j120\pi}\end{aligned}$$

Now

$$\begin{aligned}K_1 &= \frac{(1440\pi)(125.43\sqrt{2})[-1475\pi\cos\beta - 120\pi\sin\beta]}{1475^2\pi^2 + 14,400\pi^2} \\ &= \frac{-1440(125.43\sqrt{2})[1475\cos\beta + 120\sin\beta]}{1475^2 + 14,000}\end{aligned}$$

Since  $\beta = \theta + 11.50^\circ$ ,  $K_1$  reduces to

$$K_1 = -121.18\sqrt{2}\cos\theta + 14.55\sqrt{2}\sin\theta$$

From the partial fraction expansion for  $V_o$  we see  $v_o(t)$  will go directly into steady state when  $K_1 = -300\sqrt{2}\cos\theta$ . It follows that

$$14.55\sqrt{2}\sin\theta = -178.82\sqrt{2}\cos\theta$$

$$\text{or} \quad \tan\theta = -12.29$$


$$\text{Therefore,} \quad \theta = -85.35^\circ$$

[b] When  $\theta = -85.35^\circ$ ,  $\beta = -73.85^\circ$


$$\begin{aligned}\therefore K_2 &= \frac{1440\pi(125.43\sqrt{2})[-120\pi\sin(-73.85^\circ) + j120\pi\cos(-73.85^\circ)]}{(1475\pi + j120\pi)(j240\pi)} \\ &= \frac{720\sqrt{2}(120.48 + j34.88)}{-120 + j1475} \\ &= 61.03\sqrt{2}/-78.50^\circ \\ \therefore v_o &= 122.06\sqrt{2}\cos(120\pi t - 78.50^\circ)\text{V} \quad t > 0 \\ &= 172.61\cos(120\pi t - 78.50^\circ)\text{V} \quad t > 0\end{aligned}$$

$$[c] \quad v_{o1} = 169.71 \cos(120\pi t - 85.35^\circ) \text{ V} \quad t < 0$$
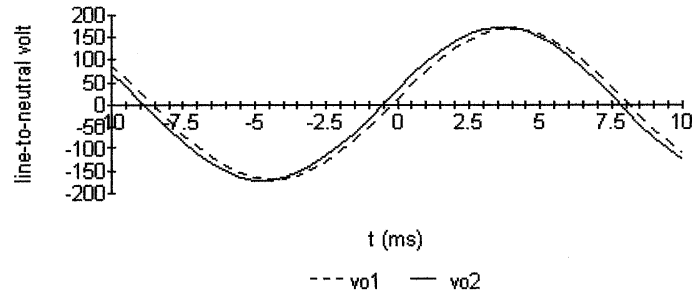
$$v_{o2} = 172.61 \cos(120\pi t - 78.50^\circ) \text{ V} \quad t > 0$$



PSpice schematic

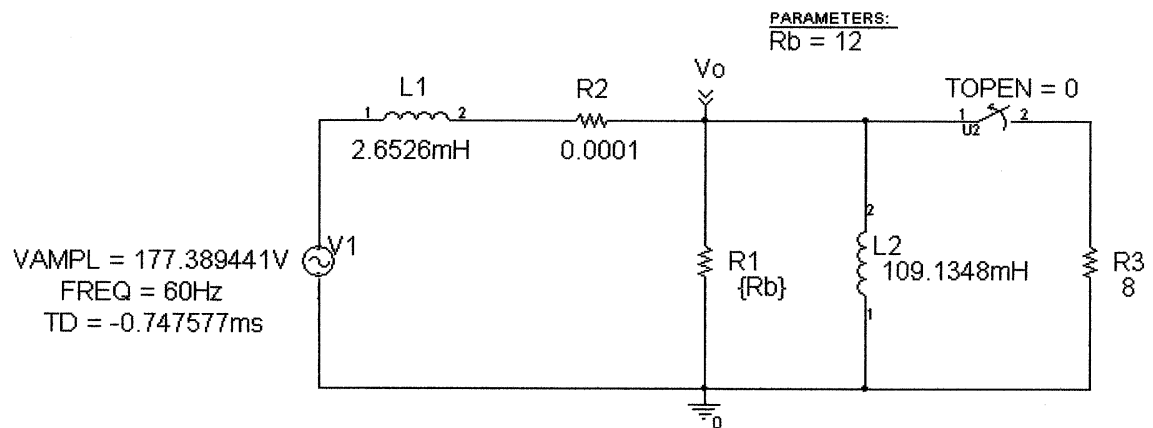

PSpice output file

```

** Creating circuit file "p9_77-SCHEMATIC1-tran.sim.cir"
** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS

*Libraries:
* Local Libraries :
* From [PSPICE NETLIST] section of C:\Program Files\OrCAD\PSpice\PSpice.ini file:
.lib "nom.lib"

*Analysis directives:
.TRAN 0 20ms 0
.STEP PARAM Rb LIST 4.8 12
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
.INC ".\p9_77-SCHEMATIC1.net"

**** INCLUDING p9_77-SCHEMATIC1.net ****
* source P9_77
V_V1      NO0637 0
+SIN 0 177.389441V 60Hz -0.747577ms 0 0
L_L1      NO0637 NO1311 2.6526mH IC=0
L_L2      0 VO 109.1348mH IC=0
R_R1      0 VO {Rb}
R_R2      VO NO1311 0.0001
R_R3      0 NO1959 8
X_U2      VO NO1959 Sw_tOpen PARAMS: tOpen=0 ttran=1u Rclosed=0.01
+ Ropen=1Meg
.PARAM Rb=12

**** RESUMING p9_77-SCHEMATIC1-tran.sim.cir ****
.END

```

