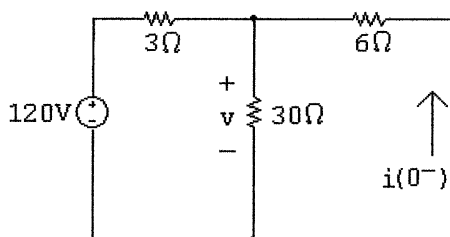


# Response of First-Order $RL$ and $RC$ Circuits

## Assessment Problems

AP 7.1 [a] The circuit for  $t < 0$  is shown below. Note that the inductor behaves like a short circuit, effectively eliminating the  $2\Omega$  resistor from the circuit.



First combine the  $30\Omega$  and  $6\Omega$  resistors in parallel:

$$30\parallel 6 = 5\Omega$$

Use voltage division to find the voltage drop across the parallel resistors:

$$v = \frac{5}{5+3}(120) = 75\text{ V}$$

Now find the current using Ohm's law:

$$i(0^-) = -\frac{v}{6} = -\frac{75}{6} = -12.5\text{ A}$$

$$[\text{b}] \quad w(0) = \frac{1}{2}Li^2(0) = \frac{1}{2}(8 \times 10^{-3})(12.5)^2 = 625\text{ mJ}$$

[c] To find the time constant, we need to find the equivalent resistance seen by the inductor for  $t > 0$ . When the switch opens, only the  $2\Omega$  resistor remains connected to the inductor. Thus,

$$\tau = \frac{L}{R} = \frac{8 \times 10^{-3}}{2} = 4\text{ ms}$$

$$[\text{d}] \quad i(t) = i(0^-)e^{t/\tau} = -12.5e^{-t/0.004} = -12.5e^{-250t}\text{ A}, \quad t \geq 0$$


$$[\text{e}] \quad i(5\text{ ms}) = -12.5e^{-250(0.005)} = -12.5e^{-1.25} = -3.58\text{ A}$$

$$\text{So } w(5 \text{ ms}) = \frac{1}{2}Li^2(5 \text{ ms}) = \frac{1}{2}(8) \times 10^{-3}(3.58)^2 = 51.3 \text{ mJ}$$

$$w(\text{dis}) = 625 - 51.3 = 573.7 \text{ mJ}$$

$$\% \text{ dissipated} = \left( \frac{573.7}{625} \right) 100 = 91.8\%$$

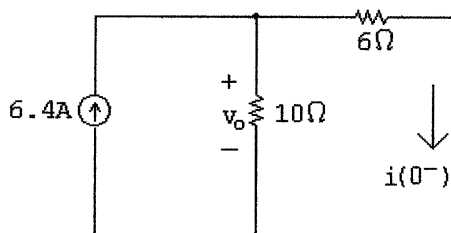
AP 7.2 [a] First, use the circuit for  $t < 0$  to find the initial current in the inductor:



Using current division,

$$i(0^-) = \frac{10}{10 + 6}(6.4) = 4 \text{ A}$$

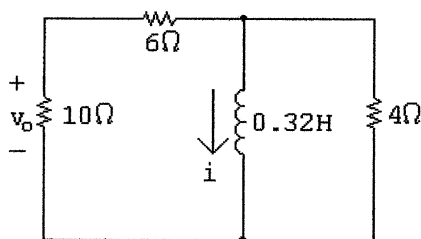Now use the circuit for  $t > 0$  to find the equivalent resistance seen by the inductor, and use this value to find the time constant:



$$R_{\text{eq}} = 4 \parallel (6 + 10) = 3.2 \Omega, \quad \therefore \quad \tau = \frac{L}{R_{\text{eq}}} = \frac{0.32}{3.2} = 0.1 \text{ s}$$

Use the initial inductor current and the time constant to find the current in the inductor:

$$i(t) = i(0^-)e^{-t/\tau} = 4e^{-t/0.1} = 4e^{-10t} \text{ A}, \quad t \geq 0$$

Use current division to find the current in the  $10 \Omega$  resistor:

$$i_o(t) = \frac{4}{4 + 10 + 6}(-i) = \frac{4}{20}(-4e^{-10t}) = -0.8e^{-10t} \text{ A}, \quad t \geq 0^+$$

Finally, use Ohm's law to find the voltage drop across the  $10 \Omega$  resistor:

$$v_o(t) = 10i_o = 10(-0.8e^{-10t}) = -8e^{-10t} \text{ V}, \quad t \geq 0^+$$

[b] The initial energy stored in the inductor is

$$w(0) = \frac{1}{2}Li^2(0^-) = \frac{1}{2}(0.32)(4)^2 = 2.56 \text{ J}$$

Find the energy dissipated in the  $4 \Omega$  resistor by integrating the power over all time:

$$v_{4\Omega}(t) = L \frac{di}{dt} = 0.32(-10)(4e^{-10t}) = -12.8e^{-10t} \text{ V}, \quad t \geq 0^+$$


$$p_{4\Omega}(t) = \frac{v_{4\Omega}^2}{4} = 40.96e^{-20t} \text{ W}, \quad t \geq 0^+$$

$$w_{4\Omega}(t) = \int_0^\infty 40.96e^{-20t} dt = 2.048 \text{ J}$$

Find the percentage of the initial energy in the inductor dissipated in the  $4\Omega$  resistor:

$$\% \text{ dissipated} = \left( \frac{2.048}{2.56} \right) 100 = 80\%$$

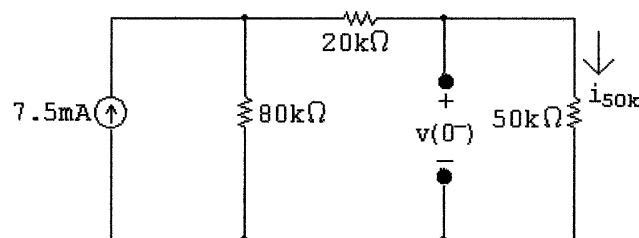AP 7.3 [a] The circuit for  $t < 0$  is shown below. Note that the capacitor behaves like an open circuit.



Find the voltage drop across the open circuit by finding the voltage drop across the  $50\text{ k}\Omega$  resistor. First use current division to find the current through the  $50\text{ k}\Omega$  resistor:

$$i_{50k} = \frac{80 \times 10^3}{80 \times 10^3 + 20 \times 10^3 + 50 \times 10^3} (7.5 \times 10^{-3}) = 4 \text{ mA}$$

Use Ohm's law to find the voltage drop:

$$v(0^-) = (50 \times 10^3) i_{50k} = (50 \times 10^3)(0.004) = 200 \text{ V}$$

[b] To find the time constant, we need to find the equivalent resistance seen by the capacitor for  $t > 0$ . When the switch opens, only the  $50\text{ k}\Omega$  resistor remains connected to the capacitor. Thus,

$$\tau = RC = (50 \times 10^3)(0.4 \times 10^{-6}) = 20 \text{ ms}$$

$$[c] \quad v(t) = v(0^-)e^{-t/\tau} = 200e^{-t/0.02} = 200e^{-50t} \text{ V}, \quad t \geq 0$$


$$[d] \quad w(0) = \frac{1}{2} C v^2 = \frac{1}{2} (0.4 \times 10^{-6}) (200)^2 = 8 \text{ mJ}$$

$$[e] \quad w(t) = \frac{1}{2} C v^2(t) = \frac{1}{2} (0.4 \times 10^{-6}) (200e^{-50t})^2 = 8e^{-100t} \text{ mJ}$$

The initial energy is 8 mJ, so when 75% is dissipated, 2 mJ remains:

$$8 \times 10^{-3} e^{-100t} = 2 \times 10^{-3}, \quad e^{100t} = 4, \quad t = (\ln 4)/100 = 13.86 \text{ ms}$$

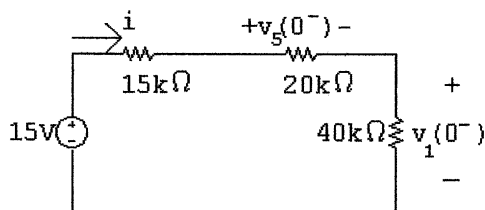AP 7.4 [a] This circuit is actually two  $RC$  circuits in series, and the requested voltage,  $v_o$ , is the sum of the voltage drops for the two  $RC$  circuits. The circuit for  $t < 0$  is shown below:



Find the current in the loop and use it to find the initial voltage drops across the two  $RC$  circuits:

$$i = \frac{15}{75,000} = 0.2 \text{ mA}, \quad v_5(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

There are two time constants in the circuit, one for each  $RC$  subcircuit.  $\tau_5$  is the time constant for the  $5 \mu\text{F} - 20 \text{ k}\Omega$  subcircuit, and  $\tau_1$  is the time constant for the  $1 \mu\text{F} - 40 \text{ k}\Omega$  subcircuit:

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}; \quad \tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}$$

Therefore,

$$v_5(t) = v_5(0^-)e^{-t/\tau_5} = 4e^{-t/0.1} = 4e^{-10t} \text{ V}, \quad t \geq 0$$

$$v_1(t) = v_1(0^-)e^{-t/\tau_1} = 8e^{-t/0.04} = 8e^{-25t} \text{ V}, \quad t \geq 0$$

Finally,

$$v_o(t) = v_1(t) + v_5(t) = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

- [b] Find the value of the voltage at 60 ms for each subcircuit and use the voltage to find the energy at 60 ms:

$$v_1(60 \text{ ms}) = 8e^{-25(0.06)} \cong 1.79 \text{ V}, \quad v_5(60 \text{ ms}) = 4e^{-10(0.06)} \cong 2.20 \text{ V}$$

$$w_1(60 \text{ ms}) = \frac{1}{2}Cv_1^2(60 \text{ ms}) = \frac{1}{2}(1 \times 10^{-6})(1.79)^2 \cong 1.59 \mu\text{J}$$

$$w_5(60 \text{ ms}) = \frac{1}{2}Cv_5^2(60 \text{ ms}) = \frac{1}{2}(5 \times 10^{-6})(2.20)^2 \cong 12.05 \mu\text{J}$$

$$w(60 \text{ ms}) = 1.59 + 12.05 = 13.64 \mu\text{J}$$

Find the initial energy from the initial voltage:


$$w(0) = w_1(0) + w_2(0) = \frac{1}{2}(1 \times 10^{-6})(8)^2 + \frac{1}{2}(5 \times 10^{-6})(4)^2 = 72 \mu\text{J}$$

Now calculate the energy dissipated at 60 ms and compare it to the initial energy:

$$w_{\text{diss}} = w(0) - w(60 \text{ ms}) = 72 - 13.64 = 58.36 \mu\text{J}$$

$$\% \text{ dissipated} = (58.36 \times 10^{-6} / 72 \times 10^{-6})(100) = 81.05 \%$$

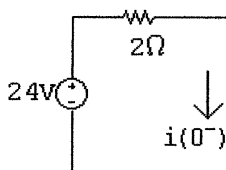
- AP 7.5 [a] Use the circuit at  $t < 0$ , shown below, to calculate the initial current in the inductor:



$$i(0^-) = 24/2 = 12 \text{ A} = i(0^+)$$

Note that  $i(0^-) = i(0^+)$  because the current in an inductor is continuous.

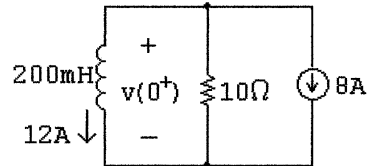- [b] Use the circuit at  $t = 0^+$ , shown below, to calculate the voltage drop across the inductor at  $0^+$ . Note that this is the same as the voltage drop across the  $10\Omega$  resistor, which has current from two sources — 8 A from the current source and 12 A from the initial current through the inductor.




$$v(0^+) = -10(8 + 12) = -200 \text{ V}$$

- [c] To calculate the time constant we need the equivalent resistance seen by the inductor for  $t > 0$ . Only the  $10\Omega$  resistor is connected to the inductor for  $t > 0$ . Thus,

$$\tau = L/R = (200 \times 10^{-3}/10) = 20 \text{ ms}$$

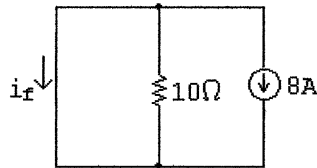- [d] To find  $i(t)$ , we need to find the final value of the current in the inductor. When the switch has been in position a for a long time, the circuit reduces to the one below:



Note that the inductor behaves as a short circuit and all of the current from the 8 A source flows through the short circuit. Thus,

$$i_f = -8 \text{ A}$$


Now,

$$\begin{aligned} i(t) &= i_f + [i(0^+) - i_f]e^{-t/\tau} = -8 + [12 - (-8)]e^{-t/0.02} \\ &= -8 + 20e^{-50t} \text{ A}, \quad t \geq 0 \end{aligned}$$

- [e] To find  $v(t)$ , use the relationship between voltage and current for an inductor:

$$v(t) = L \frac{di(t)}{dt} = (200 \times 10^{-3})(-50)(20e^{-50t}) = -200e^{-50t} \text{ V}, \quad t \geq 0^+$$

AP 7.6 [a]

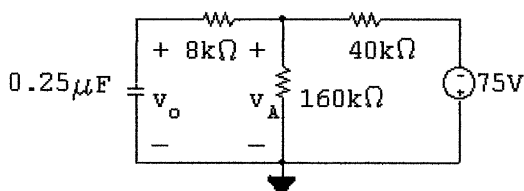

From Example 7.6,

$$v_o(t) = -60 + 90e^{-100t} \text{ V}$$

Write a KVL equation at the top node and use it to find the relationship between  $v_o$  and  $v_A$ :

$$\frac{v_A - v_o}{8000} + \frac{v_A}{160,000} + \frac{v_A + 75}{40,000} = 0$$


$$20v_A - 20v_o + v_A + 4v_A + 300 = 0$$

$$25v_A = 20v_o - 300$$

$$v_A = 0.8v_o - 12$$


Use the above equation for  $v_A$  in terms of  $v_o$  to find the expression for  $v_A$ :

$$v_A(t) = 0.8(-60 + 90e^{-100t}) - 12 = -60 + 72e^{-100t} \text{ V}, \quad t \geq 0^+$$

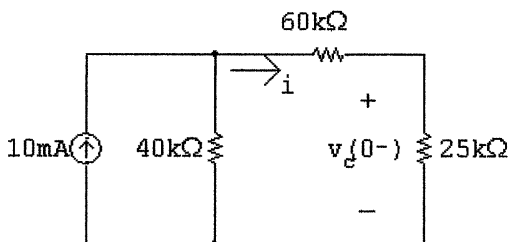[b]  $t \geq 0^+$ , since there is no requirement that the voltage be continuous in a resistor.AP 7.7 [a] Use the circuit shown below, for  $t < 0$ , to calculate the initial voltage drop across the capacitor:

$$i = \left( \frac{40 \times 10^3}{125 \times 10^3} \right) (10 \times 10^{-3}) = 3.2 \text{ mA}$$

$$v_c(0^-) = (3.2 \times 10^{-3})(25 \times 10^3) = 80 \text{ V} \quad \text{so} \quad v_c(0^+) = 80 \text{ V}$$

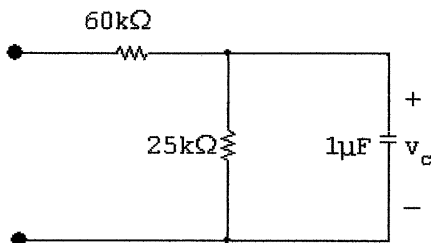Now use the next circuit, valid for  $0 \leq t \leq 10 \text{ ms}$ , to calculate  $v_c(t)$  for that interval:

For  $0 \leq t \leq 100 \text{ ms}$ :


$$\tau = RC = (25 \times 10^3)(1 \times 10^{-6}) = 25 \text{ ms}$$

$$v_c(t) = v_c(0^-)e^{t/\tau} = 80e^{-40t} \text{ V} \quad 0 \leq t \leq 10 \text{ ms}$$

- [b] Calculate the starting capacitor voltage in the interval  $t \geq 10 \text{ ms}$ , using the capacitor voltage from the previous interval:

$$v_c(0.01) = 80e^{-40(0.01)} = 53.63 \text{ V}$$

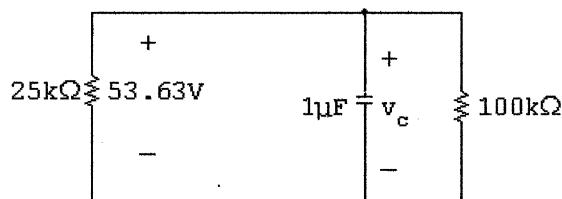Now use the next circuit, valid for  $t \geq 10 \text{ ms}$ , to calculate  $v_c(t)$  for that interval:



For  $t \geq 10 \text{ ms}$ :

$$R_{\text{eq}} = 25 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 20 \text{ k}\Omega$$

$$\tau = R_{\text{eq}}C = (20 \times 10^3)(1 \times 10^{-6}) = 0.02 \text{ s}$$

$$\text{Therefore } v_c(t) = v_c(0.01^+)e^{-(t-0.01)/\tau} = 53.63e^{-50(t-0.01)} \text{ V}, \quad t \geq 0.01 \text{ s}$$

- [c] To calculate the energy dissipated in the  $25 \text{ k}\Omega$  resistor, integrate the power absorbed by the resistor over all time. Use the expression  $p = v^2/R$  to calculate the power absorbed by the resistor.

$$w_{25 \text{ k}} = \int_0^{0.01} \frac{[80e^{-40t}]^2}{25,000} dt + \int_{0.01}^{\infty} \frac{[53.63e^{-50(t-0.01)}]^2}{25,000} dt = 2.91 \text{ mJ}$$

- [d] Repeat the process in part (c), but recognize that the voltage across this resistor is non-zero only for the second interval:

$$w_{100 \text{ k}\Omega} = \int_{0.01}^{\infty} \frac{[53.63e^{-50(t-0.01)}]^2}{100,000} dt = 0.29 \text{ mJ}$$

We can check our answers by calculating the initial energy stored in the capacitor. All of this energy must eventually be dissipated by the  $25 \text{ k}\Omega$  resistor and the  $100 \text{ k}\Omega$  resistor.


$$\text{Check: } w_{\text{stored}} = (1/2)(1 \times 10^{-6})(80)^2 = 3.2 \text{ mJ}$$

$$w_{\text{diss}} = 2.91 + 0.29 = 3.2 \text{ mJ}$$

AP 7.8 [a] Prior to switch a closing at  $t = 0$ , there are no sources connected to the inductor; thus,  $i(0^-) = 0$ .

At the instant A is closed,  $i(0^+) = 0$ .

For  $0 \leq t \leq 1$  s,

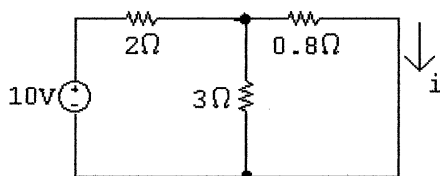

The equivalent resistance seen by the 10 V source is  $2 + (3 \parallel 0.8)$ . The current leaving the 10 V source is

$$\frac{10}{2 + (3 \parallel 0.8)} = 3.8 \text{ A}$$

The final current in the inductor, which is equal to the current in the  $0.8 \Omega$  resistor is

$$I_F = \frac{3}{3 + 0.8}(3.8) = 3 \text{ A}$$

The resistance seen by the inductor is calculated to find the time constant:

$$[(2 \parallel 3) + 0.8] \parallel 3 \parallel 6 = 1 \Omega \quad \tau = \frac{L}{R} = \frac{2}{1} = 2 \text{ s}$$


Therefore,

$$i = i_F + [i(0^+) - i_F]e^{-t/\tau} = 3 - 3e^{-0.5t} \text{ A}, \quad 0 \leq t \leq 1 \text{ s}$$

For part (b) we need the value of  $i(t)$  at  $t = 1$  s:

$$i(1) = 3 - 3e^{-0.5} = 1.18 \text{ A}$$

[b] For  $t > 1$  s

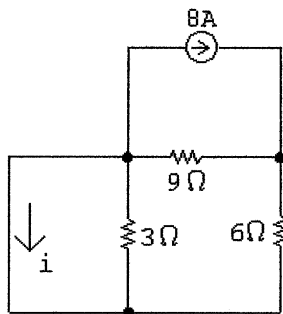

Use current division to find the final value of the current:

$$i = \frac{9}{9 + 6}(-8) = -4.8 \text{ A}$$




The equivalent resistance seen by the inductor is used to calculate the time constant:

$$3 \parallel (9 + 6) = 2.5 \Omega \quad \tau = \frac{L}{R} = \frac{2}{2.5} = 0.8 \text{ s}$$

Therefore,

$$\begin{aligned} i &= i_F + [i(1^+) - i_F]e^{-(t-1)/\tau} \\ &= -4.8 + 5.98e^{-1.25(t-1)} \text{ A}, \quad t \geq 1 \text{ s} \end{aligned}$$

AP 7.9  $0 \leq t \leq 32 \text{ ms}$ :

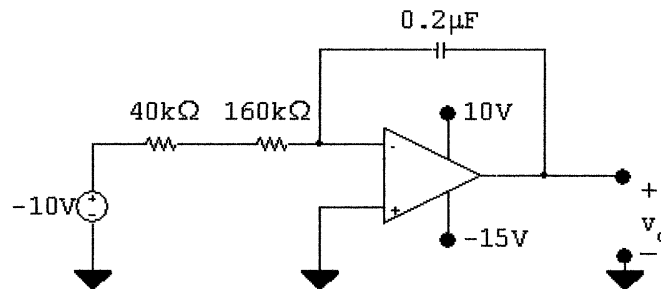


$$v_o = -\frac{1}{RC_f} \int_0^{32 \times 10^{-3}} -10 dt + 0 = -\frac{1}{RC_f} (-10t) \Big|_0^{32 \times 10^{-3}} = -\frac{1}{RC_f} (-320 \times 10^{-3})$$

$$RC_f = (200 \times 10^3)(0.2 \times 10^{-6}) = 40 \times 10^{-3} \quad \text{so} \quad \frac{1}{RC_f} = 25$$

$$v_o = -25(-320 \times 10^{-3}) = 8 \text{ V}$$

$t \geq 32 \text{ ms}$ :

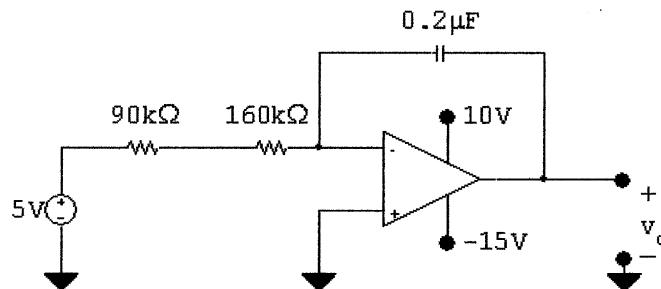

$$v_o = -\frac{1}{RC_f} \int_{32 \times 10^{-3}}^t 5 dy + 8 = -\frac{1}{RC_f} (5y) \Big|_{32 \times 10^{-3}}^t + 8 = -\frac{1}{RC_f} 5(t - 32 \times 10^{-3}) + 8$$

$$RC_f = (250 \times 10^3)(0.2 \times 10^{-6}) = 50 \times 10^{-3} \quad \text{so} \quad \frac{1}{RC_f} = 20$$

$$v_o = -20(5)(t - 32 \times 10^{-3}) + 8 = -100t + 11.2$$

The output will saturate at the negative power supply value:

$$-15 = -100t + 11.2 \quad \therefore \quad t = 262 \text{ ms}$$

AP 7.10 [a] Use RC circuit analysis to determine the expression for the voltage at the non-inverting input:

$$v_p = V_f + [V_o - V_f]e^{-t/\tau} = -2 + (0 + 2)e^{-t/\tau}$$

$$\tau = (160 \times 10^3)(10 \times 10^{-9}) = 10^{-3}; \quad 1/\tau = 625$$

$$v_p = -2 + 2e^{-625t} \text{ V}; \quad v_n = v_p$$

Write a KVL equation at the inverting input, and use it to determine  $v_o$ :

$$\frac{v_n}{10,000} + \frac{v_n - v_o}{40,000} = 0$$

$$\therefore v_o = 5v_n = 5v_p = -10 + 10e^{-625t} \text{ V}$$

The output will saturate at the negative power supply value:

$$-10 + 10e^{-625t} = -5; \quad e^{-625t} = 1/2; \quad t = \ln 2/625 = 1.11 \text{ ms}$$

[b] Use RC circuit analysis to determine the expression for the voltage at the non-inverting input:

$$v_p = V_f + [V_o - V_f]e^{-t/\tau} = -2 + (1 + 2)e^{-625t} = -2 + 3e^{-625t} \text{ V}$$

The analysis for  $v_o$  is the same as in part (a):

$$v_o = 5v_p = -10 + 15e^{-625t} \text{ V}$$

The output will saturate at the negative power supply value:

$$-10 + 15e^{-625t} = -5; \quad e^{-625t} = 1/3; \quad t = \ln 3/625 = 1.76 \text{ ms}$$

## Problems

P 7.1 [a]  $i(0) = 125/25 = 5 \text{ A}$

[b]  $\tau = \frac{L}{R} = \frac{4}{100} = 40 \text{ ms}$

[c]  $i = 5e^{-25t} \text{ A}, \quad t \geq 0$

$$v_1 = -80i = -400e^{-25t} \text{ V} \quad t \geq 0$$

$$v_2 = L \frac{di_1}{dt} = 4(-125e^{-25t}) = -500e^{-25t} \text{ V} \quad t \geq 0^+$$

[d]  $p_{\text{diss}} = i^2(20) = 25e^{-50t}(20) = 500e^{-50t} \text{ W}$


$$w_{\text{diss}} = \int_0^t 500e^{-50x} dx = 500 \left. \frac{e^{-50x}}{-50} \right|_0^t = 10 - 10e^{-50t} \text{ J}$$

$$w_{\text{diss}}(12 \text{ ms}) = 10 - 10e^{-0.6} = 4.51 \text{ J}$$

$$w(0) = \frac{1}{2}(4)(25) = 50 \text{ J}$$

$$\% \text{ dissipated} = \frac{4.51}{50}(100) = 9.02\%$$

P 7.2 [a]  $t < 0$

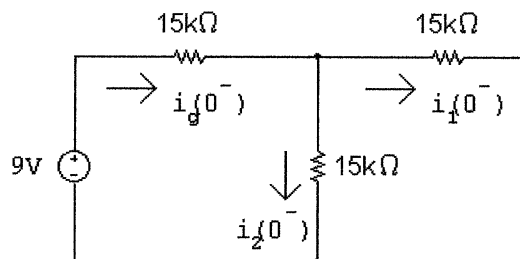

$$15 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$i_g(0^-) = \frac{9}{(15 + 7.5) \times 10^3} = 0.4 \text{ mA}$$

$$i_1(0^-) = i_2(0^-) = (0.4) \times 10^{-3} \frac{(15)}{(30)} = 0.2 \text{ mA}$$

[b]  $i_1(0^+) = i_1(0^-) = 0.2 \text{ mA}$

$$i_2(0^+) = -i_1(0^+) = -0.2 \text{ mA} \quad (\text{when switch is open})$$

[c]  $\tau = \frac{L}{R} = \frac{30 \times 10^{-3}}{30 \times 10^3} = 10^{-6}; \quad \frac{1}{\tau} = 10^6$

$$i_1(t) = i_1(0^+)e^{-t/\tau}$$

$$i_1(t) = 0.2e^{-10^6 t} \text{ mA}, \quad t \geq 0$$


[d]  $i_2(t) = -i_1(t)$  when  $t \geq 0^+$

$$\therefore i_2(t) = -0.2e^{-10^6 t} \text{ mA}, \quad t \geq 0^+$$

[e] The current in a resistor can change instantaneously. The switching operation forces  $i_2(0^-)$  to equal  $0.2 \text{ mA}$  and  $i_2(0^+) = -0.2 \text{ mA}$ .

P 7.3 [a]  $i_o(0^-) = 0$  since the switch is open for  $t < 0$ .

[b] For  $t = 0^-$  the circuit is:

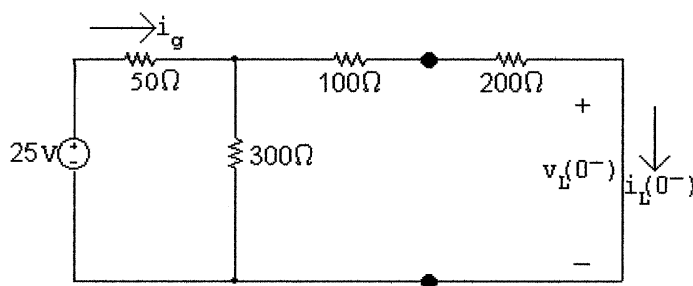


$$300\Omega \parallel 300\Omega = 150\Omega$$

$$\therefore i_g = \frac{25}{50 + 150} = 125 \text{ mA}$$

$$i_L(0^-) = \left(\frac{300}{600}\right) i_g = 62.5 \text{ mA}$$

[c] For  $t = 0^+$  the circuit is:

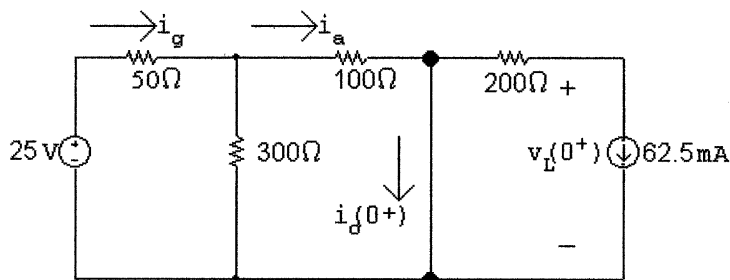

$$300\Omega \parallel 100\Omega = 75\Omega$$

$$\therefore i_g = \frac{25}{50 + 75} = 200 \text{ mA}$$

$$i_a = \left(\frac{300}{400}\right) 200 = 150 \text{ mA}$$

$$\therefore i_o(0^+) = 150 - 62.5 = 87.5 \text{ mA}$$

[d]  $i_L(0^+) = i_L(0^-) = 62.5 \text{ mA}$

[e]  $i_o(\infty) = i_a = 150 \text{ mA}$

[f]  $i_L(\infty) = 0$ , since the switch short circuits the branch containing the 200  $\Omega$  resistor and the 50 mH inductor.

[g]  $\tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{200} = 0.25 \text{ ms}; \quad \frac{1}{\tau} = 4000$

$$\therefore i_L = 0 + (62.5 - 0)e^{-4000t} = 62.5e^{-4000t} \text{ mA}, \quad t \geq 0$$

[h]  $v_L(0^-) = 0$  since for  $t < 0$  the current in the inductor is constant

[i] Refer to the circuit at  $t = 0^+$  and note:

$$200(0.0625) + v_L(0^+) = 0; \quad \therefore v_L(0^+) = -12.5 \text{ V}$$

[j]  $v_L(\infty) = 0$ , since the current in the inductor is a constant at  $t = \infty$ .

[k]  $v_L(t) = 0 + (-12.5 - 0)e^{-4000t} = -12.5e^{-4000t} \text{ V}, \quad t \geq 0^+$

[l]  $i_o = i_a - i_L = 150 - 62.5e^{-4000t} \text{ mA}, \quad t \geq 0^+$

P 7.4 [a]  $\frac{v}{i} = R = \frac{100e^{-80t}}{4e^{-80t}} = 25 \Omega$

[b]  $\tau = \frac{1}{80} = 12.5 \text{ ms}$

[c]  $\tau = \frac{L}{R} = 12.5 \times 10^{-3}$

$$L = (12.5)(25) \times 10^{-3} = 312.5 \text{ mH}$$

[d]  $w(0) = \frac{1}{2}L[i(0)]^2 = \frac{1}{2}(0.3125)(16) = 2.5 \text{ J}$

[e]  $w_{\text{diss}} = \int_0^t 400e^{-160x} dx = 2.5 - 2.5e^{-160t}$

$$0.8w(0) = (0.8)(2.5) = 2 \text{ J}$$

$$2.5 - 2.5e^{-160t} = 2 \quad \therefore e^{160t} = 5$$

Solving,  $t = 10.06 \text{ ms}$ .

P 7.5  $w(0) = \frac{1}{2}(20 \times 10^{-3})(10^2) = 1 \text{ J}$

$$0.5w(0) = 0.5 \text{ J}$$

$$i_R = 10e^{-t/\tau}$$

$$p_{\text{diss}} = i_R^2 R = 100Re^{-2t/\tau}$$

$$w_{\text{diss}} = \int_0^t R(100)e^{-2x/\tau} dx$$

$$w_{\text{diss}} = 100R \frac{e^{-2x/\tau}}{-2/\tau} \bigg|_0^{t_o} = -50\tau R(e^{-2t_o/\tau} - 1) = 50L(1 - e^{-2t_o/\tau})$$

$$50L = (50)(20) \times 10^{-3} = 1; \quad t_o = 10 \mu\text{s}$$

$$1 - e^{-2t_o/\tau} = 0.5$$

$$e^{2t_o/\tau} = 2; \quad \frac{2t_o}{\tau} = \frac{2t_o R}{L} = \ln 2$$

$$R = \frac{L \ln 2}{2t_o} = \frac{20 \times 10^{-3} \ln 2}{20 \times 10^{-6}} = 693.15 \Omega$$

P 7.6 [a]  $w(0) = \frac{1}{2} L I_g^2$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{t_o} I_g^2 R e^{-2t/\tau} dt = I_g^2 R \frac{e^{-2t/\tau}}{(-2/\tau)} \bigg|_0^{t_o} \\ &= \frac{1}{2} I_g^2 R \tau (1 - e^{-2t_o/\tau}) = \frac{1}{2} I_g^2 L (1 - e^{-2t_o/\tau}) \end{aligned}$$

$$w_{\text{diss}} = \sigma w(0)$$

$$\therefore \frac{1}{2} L I_g^2 (1 - e^{-2t_o/\tau}) = \sigma \left( \frac{1}{2} L I_g^2 \right)$$

$$1 - e^{-2t_o/\tau} = \sigma; \quad e^{2t_o/\tau} = \frac{1}{(1 - \sigma)}$$

$$\frac{2t_o}{\tau} = \ln \left[ \frac{1}{(1 - \sigma)} \right]; \quad \frac{R(2t_o)}{L} = \ln[1/(1 - \sigma)]$$

$$R = \frac{L \ln[1/(1 - \sigma)]}{2t_o}$$

[b]  $R = \frac{(20 \times 10^{-3}) \ln[1/0.5]}{20 \times 10^{-6}}$

$$R = 693.15 \Omega$$

P 7.7 [a]  $i_L(0) = \frac{80}{40} = 2 \text{ A}$

$$i_o(0^+) = \frac{80}{20} - 2 = 4 - 2 = 2 \text{ A}$$

$$i_o(\infty) = \frac{80}{20} = 4 \text{ A}$$

$$[b] \quad i_L = 2e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{20}{20} \times 10^{-3} = 1 \text{ ms}$$

$$i_L = 2e^{-1000t} \text{ A}$$


$$i_o = 4 - i_L = 4 - 2e^{-1000t} \text{ A}, \quad t \geq 0^+$$

$$[c] \quad 4 - 2e^{-1000t} = 3.8$$

$$0.2 = 2e^{-1000t}$$

$$e^{1000t} = 10 \quad \therefore t = 2.30 \text{ ms}$$


P 7.8 [a] For  $t < 0$

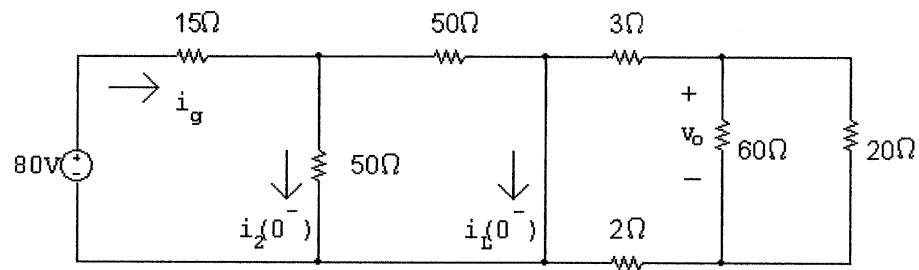

$$i_g = \frac{80}{40} = 2 \text{ A}$$

$$i_L(0^-) = \frac{2(50)}{(100)} = 1 \text{ A} = i_L(0^+)$$

For  $t > 0$

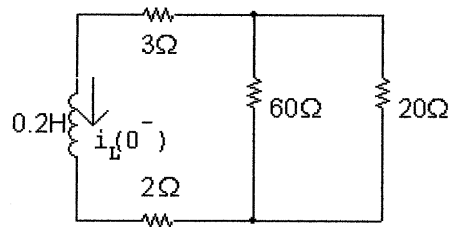

$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.20}{5 + 15} = \frac{1}{100} = 0.01 \text{ s}$$

$$i_L(0^+) = 1 \text{ A}$$

$$i_L(t) = e^{-100t} \text{ A}, \quad t \geq 0$$

$$v_o(t) = -15i_L(t)$$

$$v_o(t) = -15e^{-100t} \text{ V}, \quad t \geq 0^+$$


$$\text{P 7.9} \quad P_{20\Omega} = \frac{v_o^2}{20} = 11.25e^{-200t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{0.01} 11.25e^{-200t} dt \\ &= \left. \frac{11.25}{-200} e^{-200t} \right|_0^{0.01} \\ &= 56.25 \times 10^{-3} (1 - e^{-2}) = 48.64 \text{ mJ} \end{aligned}$$

$$w_{\text{stored}} = \frac{1}{2} (0.2)(1)^2 = 100 \text{ mJ.}$$


$$\% \text{ diss} = \frac{48.64}{100} \times 100 = 48.64\%$$

P 7.10 [a]  $t < 0$

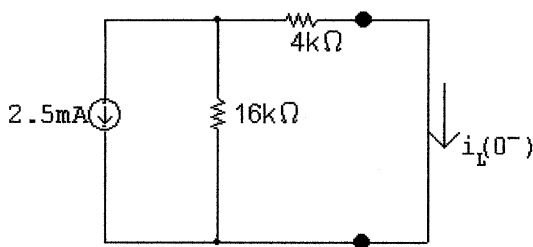

$$i_L(0^-) = \frac{-2.5(16)}{(20)} = -2 \text{ mA}$$

$t \geq 0$

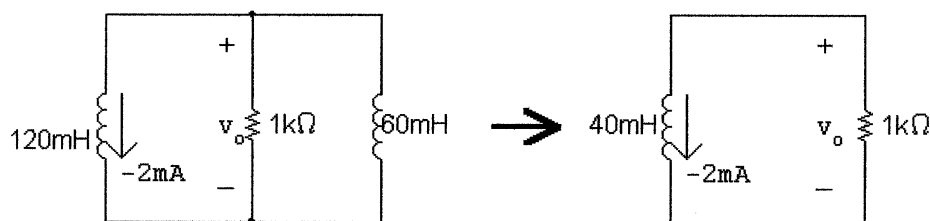

$$\tau = \frac{40 \times 10^{-3}}{10^3} = 40 \times 10^{-6}; \quad 1/\tau = 25,000$$

$$v_o = -1000(-2 \times 10^{-3})e^{-25,000t} = 2e^{-25,000t} \text{ V}, \quad t \geq 0^+$$

$$[\text{b}] \quad w_{\text{del}} = \frac{1}{2} (40 \times 10^{-3})(4 \times 10^{-6}) = 80 \text{ nJ}$$

$$[\text{c}] \quad 0.95w_{\text{del}} = 76 \text{ nJ}$$

$$\therefore 76 \times 10^{-9} = \int_0^{t_o} \frac{4e^{-50,000t}}{1000} dt$$




$$\therefore 76 \times 10^{-9} = 80 \times 10^{-9} e^{-50,000t} \Big|_0^{t_o} = 80 \times 10^{-9} (1 - e^{-50,000t_o})$$

$$\therefore e^{-50,000t_o} = 0.05$$

$$50,000t_o = \ln 20 \quad \text{so} \quad t_o = 59.9 \mu\text{s}$$


$$\therefore \frac{t_o}{\tau} = \frac{59.9}{40} = 1.498 \quad \text{so} \quad t_o \approx 1.5\tau$$

P 7.11  $t < 0$ :

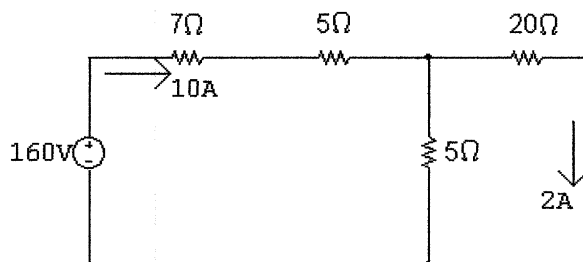

$$i_L(0^+) = 2 \text{ A}$$

$t > 0$ :

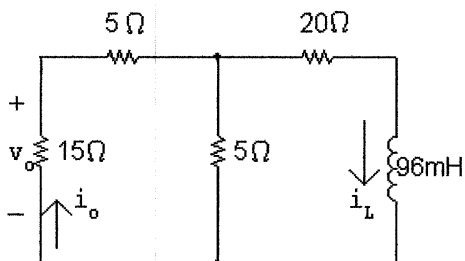

$$R_e = \frac{(20)(5)}{25} + 20 = 24 \Omega$$

$$\tau = \frac{L}{R_e} = \frac{96}{24} \times 10^{-3} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250$$

$$\therefore i_L = 2e^{-250t} \text{ A}$$

$$\therefore i_o = \frac{5}{25} i_L = 0.4e^{-250t} \text{ A}$$

$$v_o = -15i_o = -6e^{-250t} \text{ V}, \quad t \geq 0^+$$

P 7.12  $p_{20\Omega} = 20i_L^2 = 20(4)(e^{-250t})^2 = 80e^{-500t} \text{ W}$

$$w_{20\Omega} = \int_0^\infty 80e^{-500t} dt = 80 \frac{e^{-500t}}{-500} \Big|_0^\infty = 160 \text{ mJ}$$

$$w(0) = \frac{1}{2}(96)(10^{-3})(4) = 192 \text{ mJ}$$

$$\% \text{ diss} = \frac{160}{192}(100) = 83.33\%$$

P 7.13 [a]  $v_o(t) = v_o(0^+)e^{-t/\tau}$

$$\therefore v_o(0^+)e^{-5 \times 10^{-3}/\tau} = 0.25v_o(0^+)$$

$$\therefore e^{5 \times 10^{-3}/\tau} = 4$$

$$\therefore \tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{\ln 4}$$

$$\therefore L = \frac{250 \times 10^{-3}}{\ln 4} = 180.34 \text{ mH}$$

[b]  $i_L(0^-) = 60 \left( \frac{1}{6} \right) = 10 \text{ mA} = i_L(0^+)$

$$w_{\text{stored}} = \frac{1}{2} L i_L(0^+)^2 = \frac{1}{2} (R\tau) (100 \times 10^{-6}) = 2500\tau \mu\text{J}.$$

$$i_L(t) = 10e^{-t/\tau} \text{ mA}$$

$$p_{50\Omega} = i_L^2(50) = 5000 \times 10^{-6} e^{-2t/\tau}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{5 \times 10^{-3}} 5000 \times 10^{-6} e^{-2t/\tau} dt \\ &= 5000 \times 10^{-6} \left. \frac{e^{-2t/\tau}}{(-2/\tau)} \right|_0^{5 \times 10^{-3}} \\ &= 2500 \times 10^{-6} \tau \left[ 1 - e^{-\frac{10 \times 10^{-3}}{\tau}} \right] \end{aligned}$$


$$e^{-\frac{10 \times 10^{-3}}{\tau}} = e^{-2 \ln 4} = 0.0625$$

$$w_{\text{diss}} = 2500 \times 10^{-6} \tau (0.9375)$$

$$\% \text{ diss} = \frac{2500 \times 10^{-6} \tau (0.9375)}{2500 \times 10^{-6} \tau} \times 100$$


$$w_{\text{diss}} = 93.75\%$$

P 7.14  $t < 0$

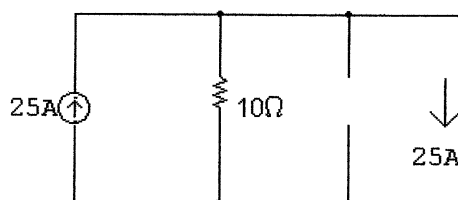


$$i_L(0^-) = i_L(0^+) = 25 \text{ A}$$

$$t > 0$$

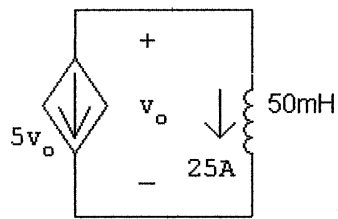


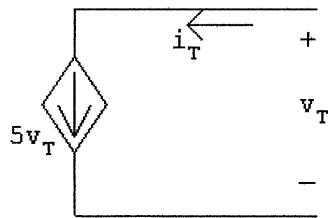Find Thévenin resistance seen by inductor



$$i_T = 5v_T; \quad \frac{v_T}{i_T} = R_{Th} = \frac{1}{5} = 0.2 \Omega$$

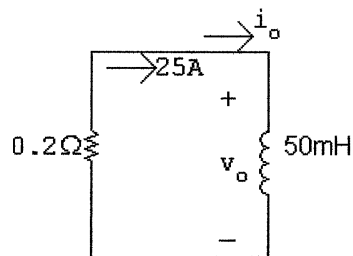
$$\tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{0.2} = 250 \text{ ms}; \quad 1/\tau = 4$$




$$i_o = 25e^{-4t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (50 \times 10^{-3})(-100e^{-4t}) = -5e^{-4t} \text{ V}, \quad t \geq 0^+$$

P 7.15 [a]  $t < 0$ :

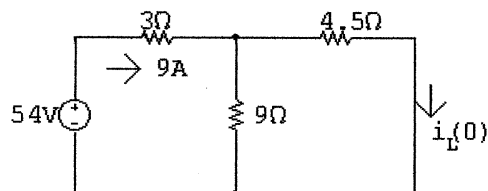


$$\frac{(9)(4.5)}{13.5} = 3 \Omega; \quad i_L(0) = 9 \frac{9}{13.5} = 6 \text{ A}$$

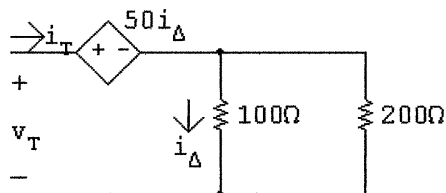$t > 0$ :

$$i_{\Delta} = \frac{i_T(200)}{300} = \frac{2}{3}i_T$$

$$v_T = 50i_{\Delta} + i_T \frac{(100)(200)}{300} = 50i_T \frac{2}{3} + \frac{200}{3}i_T$$
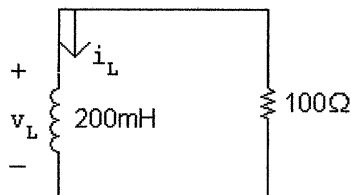
$$\frac{v_T}{i_T} = R_{Th} = \frac{100}{3} + \frac{200}{3} = 100 \Omega$$




$$\tau = \frac{L}{R} = \frac{200}{100} \times 10^{-3} \quad \frac{1}{\tau} = 500$$

$$i_L = 6e^{-500t} \text{ A}, \quad t \geq 0$$

[b]  $v_L = 200 \times 10^{-3}(-3000e^{-500t}) = -600e^{-500t} \text{ V}, \quad t \geq 0^+$

[c]

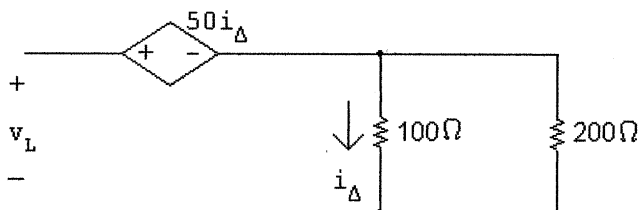

$$v_L = 50i_{\Delta} + 100i_{\Delta} = 150i_{\Delta}$$


$$i_{\Delta} = \frac{v_L}{150} = -4e^{-500t} \text{ A} \quad t \geq 0^+$$

P 7.16  $w(0) = \frac{1}{2}(200 \times 10^{-3})(36) = 3.6 \text{ J}$

$$p_{50i_{\Delta}} = -50i_{\Delta}i_L = -50(-4e^{-500t})(6e^{-500t}) = 1200e^{-1000t} \text{ W}$$

$$w_{50i_{\Delta}} = \int_0^{\infty} 1200e^{-1000t} dt = 1200 \frac{e^{-1000t}}{-1000} \Big|_0^{\infty} = 1.2 \text{ J}$$


$$\% \text{ dissipated} = \frac{1.2}{3.6}(100) = 33.33\%$$

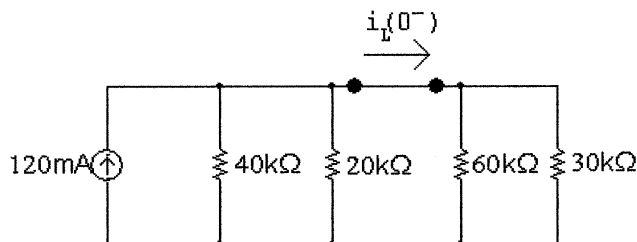P 7.17 [a]  $t < 0$ 


$$40\text{ k}\Omega \parallel 20\text{ k}\Omega = 13.33\text{ k}\Omega$$

$$60\text{ k}\Omega \parallel 30\text{ k}\Omega = 20\text{ k}\Omega$$
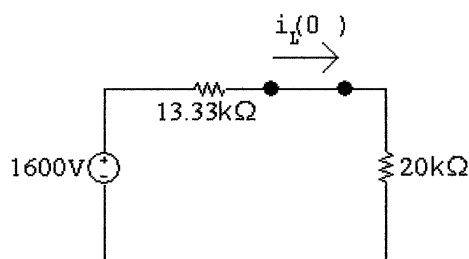
$$(120 \times 10^{-3})(13.33 \times 10^3) = 1600\text{ V}$$



$$i_L(0^-) = \frac{1600}{33,333.33} = 48\text{ mA}$$

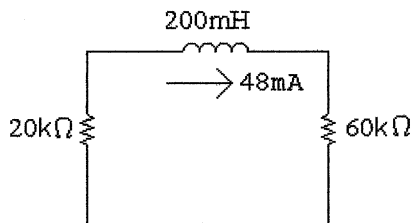 $t > 0$ 

$$\tau = \frac{L}{R} = \frac{0.2}{80,000} = 2.5\text{ }\mu\text{s}; \quad \frac{1}{\tau} = 400,000$$

$$i_L(t) = 48e^{-400,000t}\text{ mA}, \quad t \geq 0$$

$$p_{60k} = (0.048e^{-400,000t})^2(60,000) = 138.24e^{-800,000t}\text{ W}$$

$$w_{\text{diss}} = \int_0^t 138.24e^{-800,000x} dx = 172.8 \times 10^{-6}[1 - e^{-800,000t}]\text{ J}$$

$$w(0) = \frac{1}{2}(.2)(48 \times 10^{-3})^2 = 230.4\text{ }\mu\text{J}$$

$$0.25w(0) = 57.6\text{ }\mu\text{J}$$

$$172.8(1 - e^{-800,000t}) = 57.6; \quad \therefore e^{800,000t} = 1.5$$


$$t = \frac{\ln 1.5}{800,000} = 0.507\text{ }\mu\text{s}$$

[b]  $w_{\text{diss}}(\text{total}) = 230.4(1 - e^{-800,000t}) \mu\text{J}$


$w_{\text{diss}}(0.507 \mu\text{s}) = 76.82 \mu\text{J}$

$\% = (76.82/230.4)(100) = 33.3\%$

P 7.18 [a]  $t < 0$ :

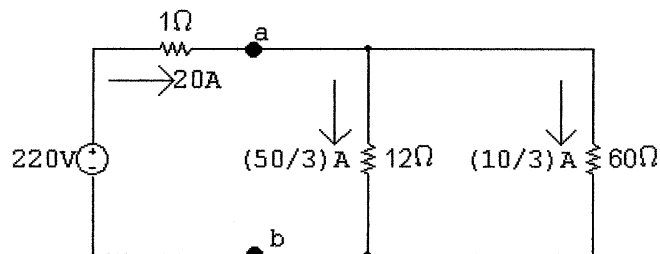


$t = 0^+$ :

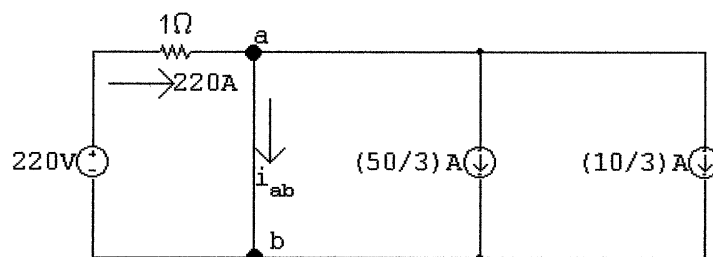


$$220 = i_{ab} + (50/3) + (10/3), \quad i_{ab} = 200 \text{ A}, \quad t = 0^+$$

[b] At  $t = \infty$ :

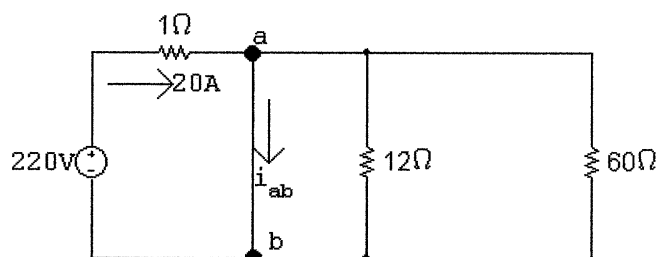
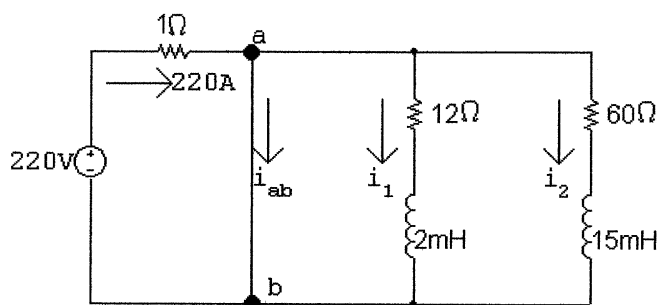
$$i_{ab} = 220/1 = 220 \text{ A}, \quad t = \infty$$



[c]  $i_1(0) = 50/3, \quad \tau_1 = \frac{2}{12} \times 10^{-3} = 0.167 \text{ ms}$

$i_2(0) = 10/3, \quad \tau_2 = \frac{15}{60} \times 10^{-3} = 0.25 \text{ ms}$

$i_1(t) = (50/3)e^{-6000t} \text{ A}, \quad t \geq 0$

$$i_2(t) = (10/3)e^{-4000t} \text{ A}, \quad t \geq 0$$

$$i_{ab} = 220 - (50/3)e^{-6000t} - (10/3)e^{-4000t} \text{ A}, \quad t \geq 0$$

$$220 - (50/3)e^{-6000t} - (10/3)e^{-4000t} = 210$$


$$30 = 50e^{-6000t} + 10e^{-4000t}$$

$$3 = 5e^{-6000t} + e^{-4000t}$$


By trial and error

$$t = 123.1 \mu\text{s}$$


P 7.19 [a]  $t < 0$ :

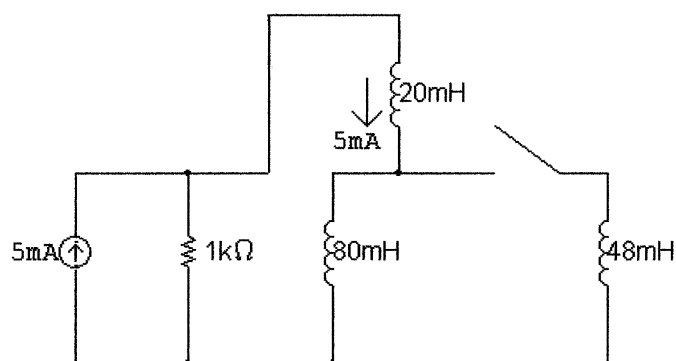

$t = 0^+$ :

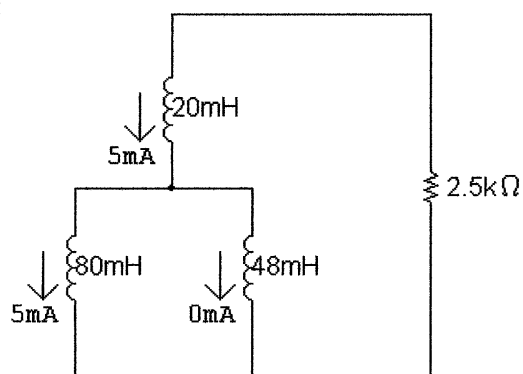


$t > 0$ :

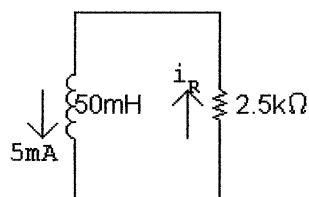

$$i_R = 5e^{t/\tau} \text{ mA}; \quad \tau = \frac{L}{R} = 20 \times 10^{-6}$$

$$i_R = 5e^{-50,000t} \text{ mA}$$

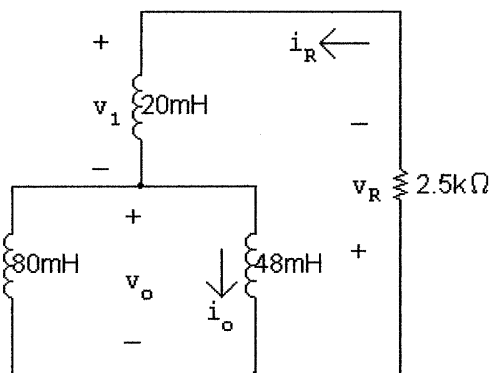

$$v_R = (2.5 \times 10^3)(5 \times 10^{-3})e^{-50,000t} = 12.5e^{-50,000t} \text{ V}$$

$$v_1 = 20 \times 10^{-3}[5 \times 10^{-3}(-50,000)e^{-50,000t}] = -5e^{-50,000t} \text{ V}$$

$$v_o = -v_1 - v_R = -7.5e^{-50,000t} \text{ V}$$

$$[b] \quad i_o = \frac{10^3}{48} \int_0^t -7.5e^{-50,000x} dx + 0 = 3.125e^{-50,000t} - 3.125 \text{ mA}$$

P 7.20 [a] From the solution to Problem 7.19,

$$i_R = 5 \times 10^{-3}e^{-50,000t} \text{ A}$$

$$p_R = (25 \times 10^{-6}e^{-100,000t})(2.5 \times 10^3) = 62.5 \times 10^{-3}e^{-100,000t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^\infty 62.5 \times 10^{-3}e^{-100,000t} dt \\ &= 62.5 \times 10^{-3} \frac{e^{-100,000t}}{-10^5} \bigg|_0^\infty = 625 \text{ nJ} \end{aligned}$$

$$[b] \quad w_{\text{trapped}} = \frac{1}{2}L_{\text{eq}}i_R^2(0) = \frac{1}{2}(50 \times 10^{-3})(5 \times 10^{-3})^2 = 625 \text{ nJ}$$


CHECK:

$$w(0) = \frac{1}{2}(20)(25 \times 10^{-6}) \times 10^{-3} + \frac{1}{2}(80)(25 \times 10^{-6}) \times 10^{-3} = 1250 \text{ nJ}$$

$$\therefore w(0) = w_{\text{diss}} + w_{\text{trapped}}$$

P 7.21 [a]  $v_1(0^-) = v_1(0^+) = 75 \text{ V}$   $v_2(0^+) = 0$

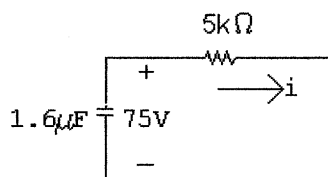
$$C_{\text{eq}} = 2 \times 8/10 = 1.6 \mu\text{F}$$



$$\tau = (5)(1.6) \times 10^{-3} = 8 \text{ ms}; \quad \frac{1}{\tau} = 125$$


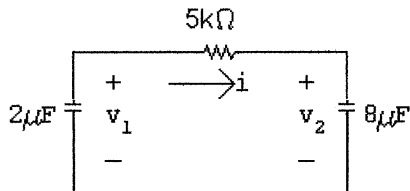
$$i = \frac{75}{5} \times 10^{-3} e^{-125t} = 15e^{-125t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-10^6}{2} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 75 = 60e^{-125t} + 15 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{10^6}{8} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 0 = -15e^{-125t} + 15 \text{ V}, \quad t \geq 0$$

$$[b] \quad w(0) = \frac{1}{2}(2 \times 10^{-6})(5625) = 5625 \mu\text{J}$$

$$[c] \quad w_{\text{trapped}} = \frac{1}{2}(2 \times 10^{-6})(225) + \frac{1}{2}(8 \times 10^{-6})225 = 1125 \mu\text{J}.$$

$$w_{\text{diss}} = \frac{1}{2}(1.6 \times 10^{-6})(5625) = 4500 \mu\text{J}.$$

$$\text{Check: } w_{\text{trapped}} + w_{\text{diss}} = 1125 + 4500 = 5625 \mu\text{J}; \quad w(0) = 5625 \mu\text{J}.$$

$$\text{P 7.22 [a]} \quad R = \frac{v}{i} = 20 \text{ k}\Omega$$

$$[b] \quad \frac{1}{\tau} = \frac{1}{RC} = 1000; \quad C = \frac{1}{(10^3)(20 \times 10^3)} = 0.05 \mu\text{F}$$

$$[c] \quad \tau = \frac{1}{1000} = 1 \text{ ms}$$

$$[d] \quad w(0) = \frac{1}{2}(0.05 \times 10^{-6})(10^4) = 250 \mu\text{J}$$


[e]

$$\begin{aligned} W_{\text{diss}} &= \int_0^{t_o} \frac{v^2}{R} dt = \int_0^{t_o} \frac{(10^4)e^{-2000t}}{(20 \times 10^3)} dt \\ &= 0.5 \frac{e^{-2000t}}{-2000} \Big|_0^{t_o} = 250(1 - e^{-2000t_o}) \mu\text{J} \end{aligned}$$


$$200 = 250(1 - e^{-2000t_o})$$

$$\therefore e^{-2000t_o} = 0.2; \quad e^{2000t_o} = 5$$

$$t_o = \frac{1}{2000} \ln 5; \quad t_o \cong 804.72 \mu\text{s}$$

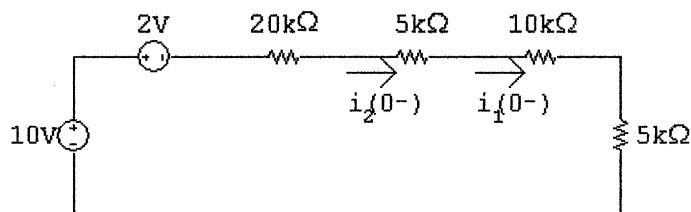P 7.23 [a]  $t < 0$ :

$$i_1(0^-) = i_2(0^-) = \left( \frac{8}{40} \times 10^{-3} \right) = 0.2 \text{ mA}$$

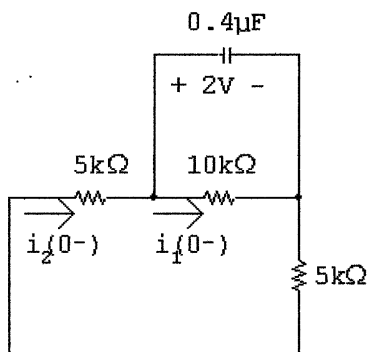[b]  $t > 0$ :

$$i_1(0^+) = \frac{2}{10} \times 10^{-3} = 0.2 \text{ mA}$$

$$i_2(0^+) = \frac{-2}{10} \times 10^{-3} = -0.2 \text{ mA}$$

[c] Capacitor voltage cannot change instantaneously, therefore,

$$i_1(0^-) = i_1(0^+) = 0.2 \text{ mA}$$

[d] Switching can cause an instantaneous change in the current in a resistive branch. In this circuit

$$i_2(0^-) = 0.2 \text{ mA} \quad \text{and} \quad i_2(0^+) = -0.2 \text{ mA}$$

[e]  $v_c = 2e^{-t/\tau} \text{ V}, \quad t \geq 0$ 

$$\tau = R_e C = 5000(0.4) \times 10^{-6} = 2 \times 10^{-3}$$

$$v_c = 2e^{-500t} \text{ V}, \quad t \geq 0$$

$$i_1 = \frac{v_c}{10,000} = 0.2e^{-500t} \text{ mA}, \quad t \geq 0$$

$$[f] \quad i_2 = \frac{-v_c}{10,000} = -0.2e^{-500t} \text{ mA}, \quad t \geq 0^+$$

P 7.24 [a]  $v(0) = \frac{(8)(27)(33)}{60} = 118.80 \text{ V}$ 

$$R_e = \frac{(3)(6)}{9} = 2 \text{ k}\Omega$$

$$\tau = R_e C = (2000)(0.25) \times 10^{-6} = 500 \mu\text{s}; \quad \frac{1}{\tau} = 2000$$

$$v = 118.80e^{-2000t} \text{ V} \quad t \geq 0$$

$$i_o = \frac{v}{3000} = 39.6e^{-2000t} \text{ mA}$$

$$[\text{b}] \quad w(0) = \frac{1}{2}(0.25)(118.80)^2 = 1764.18 \mu\text{J}$$


$$i_{4k} = \frac{118.80e^{-2000t}}{6} = 19.8e^{-2000t} \text{ mA}$$

$$p_{4k} = [(19.8)e^{-2000t}]^2(4000) \times 10^{-6} = 1568.16 \times 10^{-3}e^{-4000t}$$

$$w_{4k} = 1568.16 \times 10^{-3} \frac{e^{-4000x}}{-4000} \bigg|_0^{250 \times 10^{-6}} = 392.04(1 - e^{-1}) \mu\text{J}$$

$$\% = \frac{392.04}{1764.18}(1 - e^{-1}) \times 100 = 14.05\%$$

P 7.25 [a]  $t < 0$ :

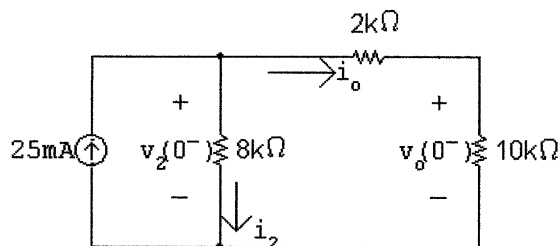


$$i_o(0^-) = \frac{(25)(8)}{(20)} = 10 \text{ mA}$$

$$v_o(0^-) = (10)(10) = 100 \text{ V}$$


$$i_2(0^-) = 25 - 10 = 15 \text{ mA}$$

$$v_2(0^-) = 15(8) = 120 \text{ V}$$

$t > 0$

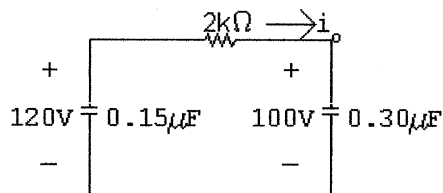

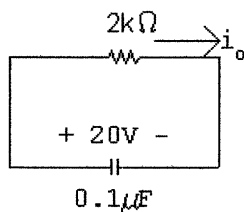
$$\tau = RC = 0.2 \text{ ms} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$



$$i_o(t) = \frac{20}{2 \times 10^3} e^{-t/\tau} = 10e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

[b]

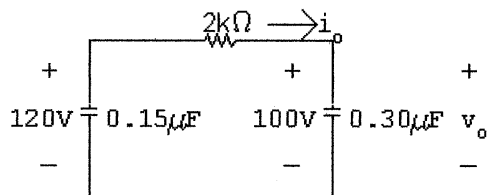

$$\begin{aligned} v_o &= \frac{10^6}{0.3} \int_0^t 10 \times 10^{-3} e^{-5000x} dx + 100 \\ &= \frac{10^5}{3} \frac{e^{-5000x}}{-5000} \bigg|_0^t + 100 \\ &= -(20/3)e^{-5000t} + (20/3) + 100 \\ v_o &= [-(20/3)e^{-5000t} + (320/3)] \text{ V}, \quad t \geq 0 \end{aligned}$$

$$[c] \quad w_{\text{trapped}} = (1/2)(0.15) \times 10^{-6}(320/3)^2 + (1/2)(0.3) \times 10^{-6}(320/3)^2$$

$$w_{\text{trapped}} = 2560 \mu\text{J}.$$


Check by combining the capacitors into a single equivalent capacitance of  $0.1 \mu\text{F}$  with a  $20 \text{ V}$  initial voltage:

$$w_{\text{diss}} = \frac{1}{2} C_{\text{eq}} (V_o)^2 = \frac{1}{2} (0.1 \times 10^{-6}) (20)^2 = 20 \mu\text{J}$$


$$w(0) = \frac{1}{2} (0.15) \times 10^{-6} (120)^2 + \frac{1}{2} (0.3 \times 10^{-6}) (100)^2 = 2580 \mu\text{J}.$$

$$w_{\text{trapped}} + w_{\text{diss}} = w(0)$$

$$2560 + 20 = 2580 \quad \text{OK.}$$

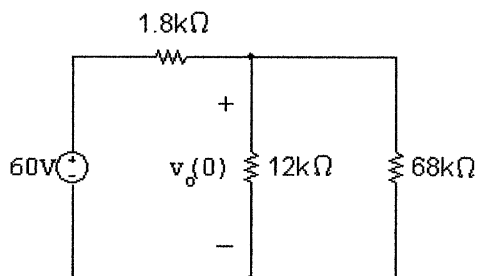P 7.26 [a]  $t < 0$ :

$$v_o(0) = \frac{(60)(10.2)}{12} = 51 \text{ V}$$

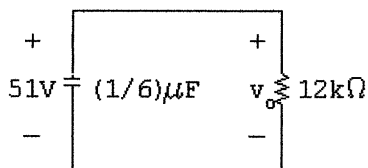 $t > 0$ :

$$\tau = \frac{1}{6}(12) \times 10^{-3} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 51e^{-500t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12} \times 10^{-3} = 216.75 \times 10^{-3} e^{-1000t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{2 \times 10^{-3}} 216.75 \times 10^{-3} e^{-1000t} dt \\ &= 216.75 \times 10^{-6} (1 - e^{-2}) = 187.42 \mu\text{J} \end{aligned}$$

$$[\text{b}] \quad w(0) = \left(\frac{1}{2}\right) \left(\frac{1}{6}\right) (51)^2 \times 10^{-6} = 216.75 \mu\text{J}$$


$$0.95w(0) = 205.9125 \mu\text{J}$$

$$\int_0^{t_o} 216.75 \times 10^{-3} e^{-1000x} dx = 205.9125 \times 10^{-6}$$


$$\int_0^{t_o} e^{-1000x} dx = 0.95 \times 10^{-3}$$

$$\therefore 1 - e^{-1000t_o} = 0.95; \quad e^{1000t_o} = 20; \quad \text{so } t_o = 3 \text{ ms}$$

P 7.27  $t < 0$

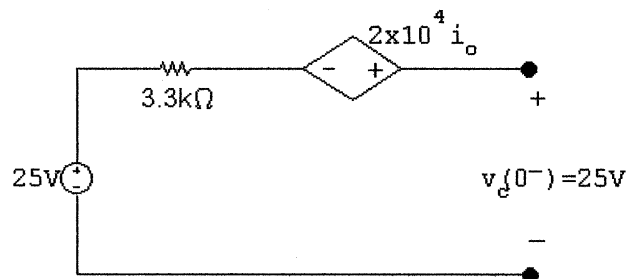


$t > 0$

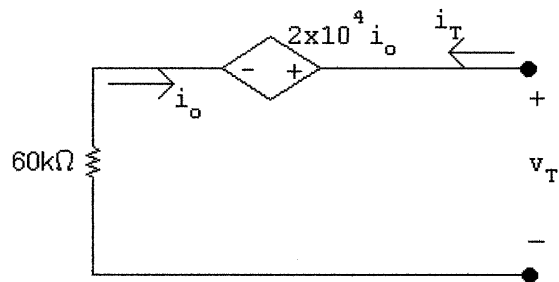

$$\begin{aligned} v_T &= 2 \times 10^4 i_o + 60,000 i_T \\ &= 20,000(-i_T) + 60,000 i_T = 40,000 i_T \end{aligned}$$
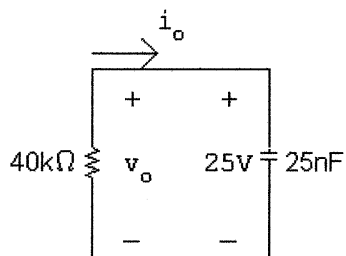
$$\therefore \frac{v_T}{i_T} = R_{Th} = 40 \text{ k}\Omega$$




$$\tau = RC = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$v_o = 25e^{-1000t} \text{ V}, \quad t \geq 0$$

$$i_o = 25 \times 10^{-9} \frac{d}{dt} [25e^{-1000t}] = -625e^{-1000t} \mu\text{A}, \quad t \geq 0^+$$

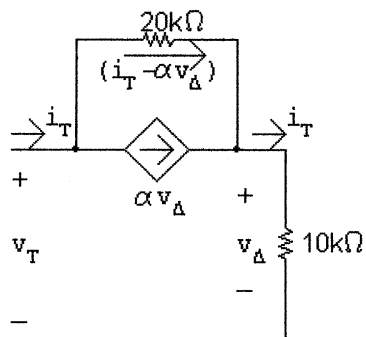P 7.28 [a]  $\tau = RC = R_{Th}(0.2) \times 10^{-6} = 10^{-3}; \quad \therefore R_{Th} = \frac{1000}{0.2} = 5 \text{ k}\Omega$



$$v_T = 20 \times 10^3(i_T - \alpha v_D) + 10 \times 10^3 i_T$$

$$v_D = 10 \times 10^3 i_T$$


$$v_T = 30 \times 10^3 i_T - 20 \times 10^3 \alpha 10 \times 10^3 i_T$$

$$\frac{v_T}{i_T} = 30 \times 10^3 - 200 \times 10^6 \alpha = 5 \times 10^3$$


$$\therefore 30 - 200,000\alpha = 5; \quad \alpha = 125 \times 10^{-6} \text{ A/V}$$

[b]  $v_o(0) = (0.018)(5000) = 90 \text{ V} \quad t < 0$

$t > 0$ :

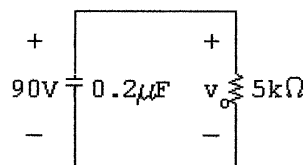
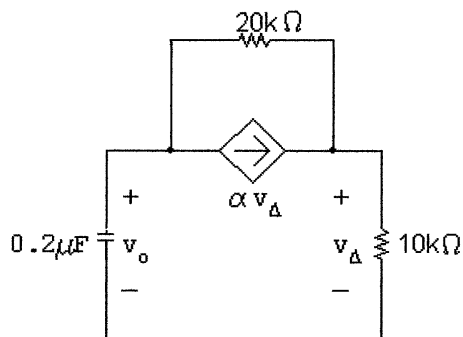
$$v_o = 90e^{-1000t} \text{ V}, \quad t \geq 0$$




$$\frac{v_D}{10 \times 10^3} + \frac{v_D - v_o}{20,000} - 125 \times 10^{-6} v_D = 0$$

$$2v_D + v_D - v_o - 2500 \times 10^{-3} v_D = 0$$

$$\therefore v_D = 2v_o = 180e^{-1000t} \text{ V}$$

P 7.29 [a]

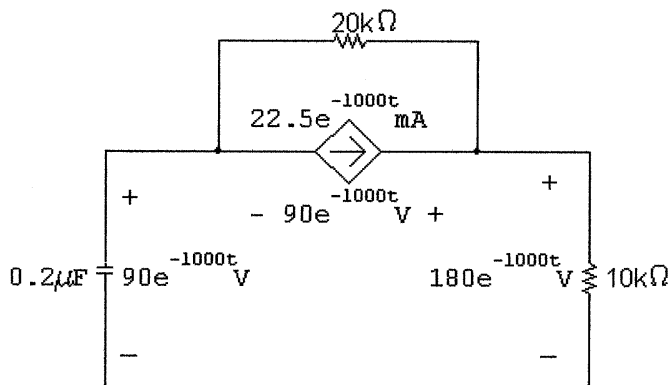

$$p_{ds} = (-90e^{-1000t})(22.5 \times 10^{-3}e^{-1000t}) = -2025 \times 10^{-3}e^{-2000t} \text{ W}$$

$$w_{ds} = \int_0^\infty p_{ds} dt = -1012.5 \mu\text{J}.$$

$\therefore$  dependent source is delivering 1012.5  $\mu\text{J}$

$$\text{[b]} \quad p_{10k} = \frac{(180)^2 e^{-2000t}}{10 \times 10^3}$$

$$w_{10k} = \int_0^\infty p_{10k} dt = 1620 \mu\text{J}$$

$$p_{20k} = \frac{(90)^2 e^{-2000t}}{20 \times 10^3}$$


$$w_{20k} = \int_0^\infty p_{20k} dt = 202.5 \mu\text{J}$$

$$w_c(0) = \frac{1}{2}(0.2) \times 10^{-6}(90)^2 = 810 \mu\text{J}$$

$$\sum w_{\text{dev}} = 810 + 1012.5 = 1822.5 \mu\text{J}$$

$$\sum w_{\text{diss}} = 202.5 + 1620 = 1822.5 \mu\text{J}.$$

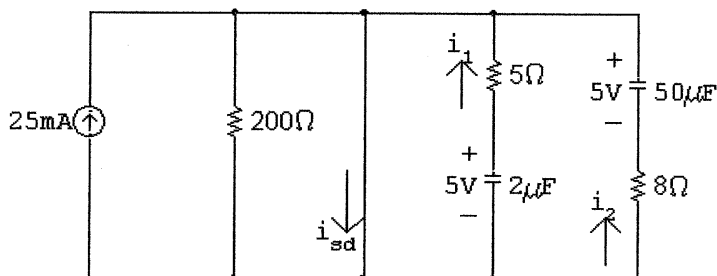P 7.30 [a] At  $t = 0^-$  the voltage on each capacitor will be  $25 \times 10^{-3} \times 200 = 5 \text{ V}$ , positive at the upper terminal. Hence at  $t \geq 0^+$  we have



$$\therefore i_{sd}(0^+) = 0.025 + \frac{5}{5} + \frac{5}{8} = 1.65 \text{ A}$$



At  $t = \infty$ , both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 25 \text{ mA}$$

$$[b] \quad i_{sd}(t) = 0.025 + i_1(t) + i_2(t)$$

$$\tau_1 = (5)(2) \times 10^{-6} = 10 \mu\text{s}$$

$$\tau_2 = (8)(50 \times 10^{-6}) = 400 \mu\text{s}$$

$$\therefore i_1(t) = e^{-10^5 t} \text{ A}, \quad t \geq 0^+$$


$$i_2(t) = 0.625e^{-2500t} \text{ A}, \quad t \geq 0$$

$$\therefore i_{sd} = 25 + 1000e^{-100,000t} + 625e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$\text{P 7.31} \quad [a] \quad \frac{1}{C_e} = 1 + \frac{1}{4} = 1.25$$

$$\therefore C_e = 0.8 \mu\text{F}; \quad v_o(0) = 60 - 10 = 50 \text{ V}$$
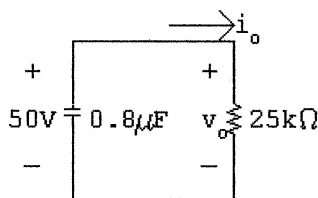
$$\tau = (0.8)(25) \times 10^{-3} = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$



$$v_o = 50e^{-50t} \text{ V}, \quad t > 0^+$$

$$[b] \quad w_o = \frac{1}{2}(1 \times 10^{-6})(3600) + \frac{1}{2}(4 \times 10^{-6})(100) = 2 \text{ mJ}$$

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(2500) = 1 \text{ mJ}$$

$$\% \text{ diss} = \frac{1}{2} \times 100 = 50\%$$

$$[c] \quad i_o = \frac{v_o}{25} \times 10^{-3} = 2e^{-50t} \text{ mA}$$

$$\begin{aligned} v_1 &= -\frac{10^6}{4} \int_0^t 2 \times 10^{-3} e^{-50x} dx - 10 = -500 \int_0^t e^{-50x} dx - 10 \\ &= -500 \left. \frac{e^{-50x}}{-50} \right|_0^t - 10 = 10e^{-50t} - 20 \text{ V} \quad t \geq 0 \end{aligned}$$


$$[d] \quad v_1 + v_2 = v_o$$

$$v_2 = v_o - v_1 = 50e^{-50t} - 10e^{-50t} + 20 = 40e^{-50t} + 20 \text{ V} \quad t \geq 0$$

$$[e] \quad w_{\text{trapped}} = \frac{1}{2}(4 \times 10^{-6})(400) + \frac{1}{2}(1 \times 10^{-6})(400) = 1 \text{ mJ}$$

$$w_{\text{diss}} + w_{\text{trapped}} = 2 \text{ mJ} \quad (\text{check})$$

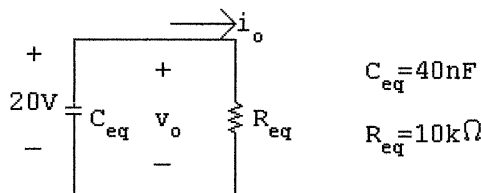P 7.32 [a] The equivalent circuit for  $t > 0$ :



$$\tau = 0.4 \text{ ms}; \quad 1/\tau = 2500$$

$$v_o = 20e^{-2500t} \text{ V}, \quad t \geq 0$$

$$i_o = 2e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$i_{25\text{k}\Omega} = 2e^{-2500t} \left( \frac{15}{40} \right) = 0.75e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{25\text{k}\Omega} = (0.5625 \times 10^{-6} e^{-5000t})(25,000) = 14,062.5 \times 10^{-6} e^{-5000t} \text{ W}$$

$$w_{25\text{k}\Omega} = \int_0^\infty 14,062.5 \times 10^{-6} e^{-5000t} dt = -2.8125 \times 10^{-6} (0 - 1) = 2.8125 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.2 \times 10^{-6})(100) + \frac{1}{2}(0.05 \times 10^{-6})(900) = 32.5 \mu\text{J}$$

$$\% \text{ diss } (25 \text{ k}\Omega) = \frac{2.8125}{32.5} \times 100 = 8.65\%$$

$$[b] \quad p_{625\Omega} = 625(2 \times 10^{-3} e^{-2500t})^2 = 2.5 \times 10^{-3} e^{-5000t}$$

$$w_{625\Omega} = \int_0^\infty p_{625} dt = 0.50 \mu\text{J}$$

$$\% \text{ diss } (625\Omega) = \frac{0.5}{32.5} \times 100 = 1.54\%$$

$$i_{15\text{k}\Omega} = 2e^{-2500t} \left( \frac{25}{40} \right) = 1.25e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{15\text{k}\Omega} = (1.25 \times 10^{-3} e^{-2500t})^2 (15,000) = 23.4375 \times 10^{-3} e^{-5000t} \text{ W}$$

$$w_{15\text{k}\Omega} = \int_0^\infty 23.4375 \times 10^{-3} e^{-5000t} dt = 4.6875 \mu\text{J}$$

$$\% \text{ diss } (15\text{k}\Omega) = 14.42\%$$


$$[c] \quad \sum w_{\text{diss}} = 2.8125 + 0.50 + 4.6875 = 8 \mu\text{J}$$

$$w_{\text{trapped}} = w(0) - \sum w_{\text{diss}} = 32.5 - 8 = 24.5 \mu\text{J}$$

$$\% \text{ trapped} = \frac{24.5}{32.5} \times 100 = 75.38\%$$

$$\text{Check: } 8.65 + 1.54 + 14.42 + 75.38 = 99.99 \approx 100\%$$

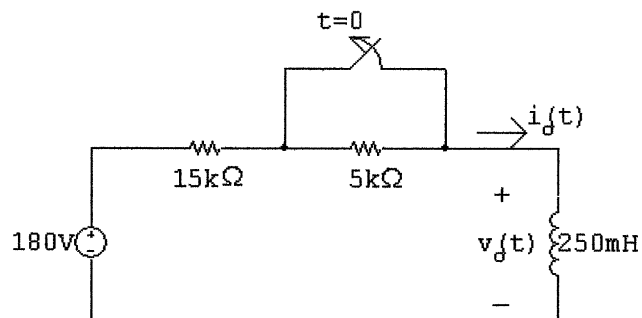P 7.33 After making a Thévenin equivalent we have



$$I_o = 180/15 = 12 \text{ mA}$$


$$\tau = (0.25/20) \times 10^{-3} = 0.125 \times 10^{-4}; \quad \frac{1}{\tau} = 80,000$$

$$I_f = \frac{V_s}{R} = \frac{180}{20} = 9 \text{ mA}$$

$$i_o = 9 + (12 - 9)e^{-80,000t} = 9 + 3e^{-80,000t} \text{ mA}$$


$$v_o = [180 - 12(20)]e^{-80,000t} = -60e^{-80,000t} \text{ V}$$

P 7.34  $t < 0$   $i_L(0^-)$

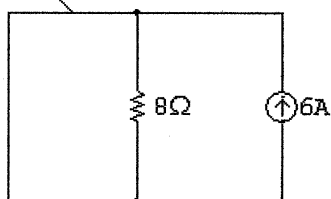

$$i_L(0^-) = 6 \text{ A}$$

$t > 0$

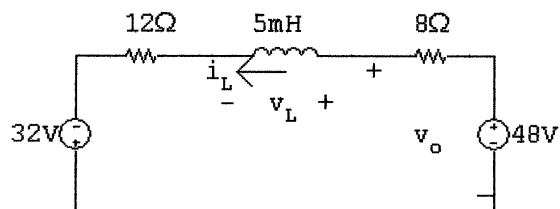

$$i_L(\infty) = \frac{32 + 48}{20} = 4 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{20} = 250 \mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$i_L = 4 + (6 - 4)e^{-4000t} = 4 + 2e^{-4000t} \text{ A}, \quad t \geq 0$$


$$v_o = -8i_L + 48 = -8(4 + 2e^{-4000t}) + 48 = 16 - 16e^{-4000t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad v_L = 5 \times 10^{-3} \frac{di_L}{dt} = 5 \times 10^{-3} [-8000e^{-4000t}] = -40e^{-4000t} \text{ V}, \quad t \geq 0^+$$

$$v_L(0^+) = -40 \text{ V}$$


$$v_o(0^+) = 0 \text{ V}$$

Check: at  $t = 0^+$  the circuit is:

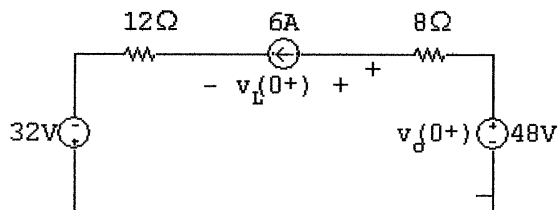

$$v_L(0^+) = 32 - 72 + 0 = -40 \text{ V}, \quad v_o(0^+) = 48 - 48 = 0 \text{ V}$$

P 7.35 [a]  $t < 0$

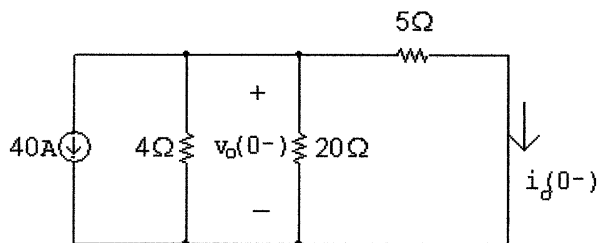


KVL equation at the top node:

$$-40 = \frac{v_o(0^-)}{4} + \frac{v_o(0^-)}{20} + \frac{v_o(0^-)}{5}$$

Multiply by 20 and solve:

$$-800 = (5 + 1 + 4)v_o; \quad v_o = -80 \text{ V}$$

$$\therefore i_o(0^-) = \frac{v_o}{5} = -80/5 = -16 \text{ A}$$

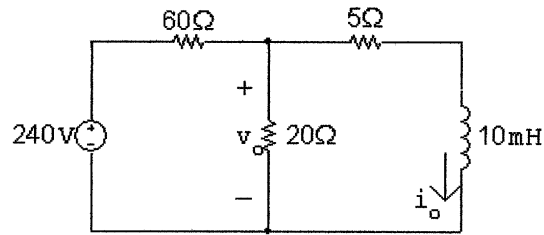$t > 0$ 


Use voltage division to find the Thévenin voltage:

$$V_{Th} = v_o = \frac{20}{20 + 60}(240) = 60 \text{ V}$$

Remove the voltage source and make series and parallel combinations of resistors to find the equivalent resistance:

$$R_{Th} = 5 + 20 \parallel 60 = 5 + 15 = 20 \Omega$$

The simplified circuit is:

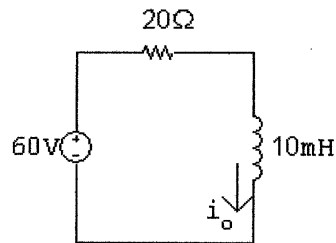


$$\tau = \frac{L}{R} = \frac{10 \times 10^{-3}}{20} = 0.5 \text{ ms}; \quad \frac{1}{\tau} = 2000$$

$$i_o(\infty) = \frac{60}{20} = 3 \text{ A}$$

$$\begin{aligned} \therefore i_o &= i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} \\ &= 3 + (-16 - 3)e^{-2000t} = 3 - 19e^{-2000t} \text{ A}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad v_o &= 5i_o + (0.01)\frac{di_o}{dt} \\ &= 15 - 95e^{-2000t} + 0.01(38,000)(e^{-2000t}) \\ &= 15 - 95e^{-2000t} + 380e^{-2000t} \\ v_o &= 15 + 285e^{-2000t} \text{ V}, \quad t \geq 0^+ \end{aligned}$$

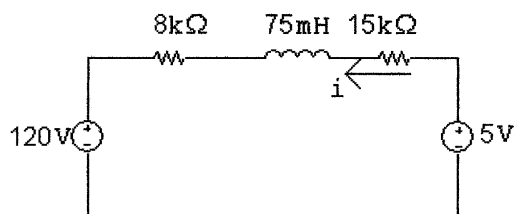
P 7.36 [a] For  $t < 0$ , calculate the Thévenin equivalent for the circuit to the left and right of the 75 mH inductor. We get



$$i(0^-) = \frac{5 - 120}{15\text{k} + 8\text{k}} = -5\text{ mA}$$

$$i(0^-) = i(0^+) = -5\text{ mA}$$

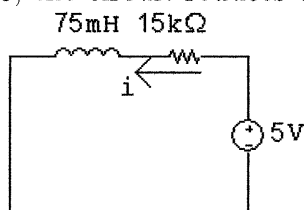[b] For  $t > 0$ , the circuit reduces to



$$\text{Therefore } i(\infty) = 5/15,000 = 0.333\text{ mA}$$

$$[c] \tau = \frac{L}{R} = \frac{75 \times 10^{-3}}{15,000} = 5\text{ }\mu\text{s}$$

$$[d] i(t) = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau}$$

$$= 0.333 + [-5 - 0.333]e^{-200,500t} = 0.333 - 5.333e^{-200,500t}\text{ mA}, \quad t \geq 0$$

P 7.37 [a] From Eqs. (7.35) and (7.42)

$$i = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R}\right)e^{-(R/L)t}$$

$$v = (V_s - I_o R)e^{-(R/L)t}$$

$$\therefore \frac{V_s}{R} = 10; \quad I_o - \frac{V_s}{R} = -10$$

$$V_s - I_o R = 200; \quad \frac{R}{L} = 500$$

$$\therefore I_o = -10 + \frac{V_s}{R} = 0\text{ A}$$

$$\text{Therefore, } V_s = 200\text{ V.}$$

$$i(\infty) = 10 = \frac{200}{R} \quad \text{so} \quad R = 20\text{ }\Omega$$

$$L = \frac{R}{500} = 40\text{ mH}$$

$$[b] \quad i = 10 - 10e^{-500t}; \quad i^2 = 100 - 200e^{-500t} + 100e^{-1000t}$$

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(0.04)[100 - 200e^{-500t} + 100e^{-1000t}] = 2 - 4e^{-500t} + 2e^{-1000t}$$

$$w(\infty) = 2 \text{ J}$$

$$w(t_o) = 2 - 4e^{-500t_o} + 2e^{-1000t_o} = 0.25(2)$$

$$\therefore 1 - 2x + x^2 = 0.25 \quad \text{and thus} \quad x^2 - 2x + 0.75 = 0$$

Solving,  $x = 1.5$  and  $x = 0.5$  but only the second solution is possible

$$\therefore 0.5 = e^{-500t_o} \quad \text{so} \quad t_o = \frac{\ln 2}{500} = 1.386 \text{ ms}$$

$$P 7.38 \quad [a] \quad v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-(R_1 + R_2)/L t} \text{ V}, \quad t \geq 0^+$$

[b]  $v_o(0^+) \rightarrow \infty$ , and the duration of  $v_o(t) \rightarrow \text{zero}$

$$[c] \quad v_{sw} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$$

$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$

$$\text{Therefore} \quad i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[ I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-[(R_1 + R_2)/L]t}$$


$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-[(R_1 + R_2)/L]t}$$

$$\text{Therefore} \quad v_{sw} = \frac{R_1 I_g}{(1 + R_1/R_2)} + \frac{R_2 I_g}{(1 + R_1/R_2)} e^{-[(R_1 + R_2)/L]t}, \quad t \geq 0^+$$

[d]  $|v_{sw}(0^+)| \rightarrow \infty$ ; duration  $\rightarrow 0$

P 7.39 Opening the inductive circuit causes a very large voltage to be induced across the inductor  $L$ . This voltage also appears across the switch (part [e] of Problem 7.38) causing the switch to arc over. At the same time, the large voltage across  $L$  damages the meter movement.

P 7.40 [a]

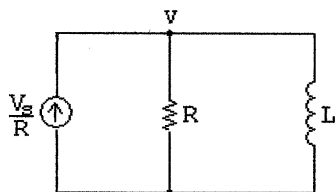

$$-\frac{V_s}{R} + \frac{v}{R} + \frac{1}{L} \int_0^t v dt + I_o = 0$$

Differentiating both sides,

$$\frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$\therefore \frac{dv}{dt} + \frac{R}{L} v = 0$$

$$[b] \frac{dv}{dt} = -\frac{R}{L} v$$


$$\frac{dv}{dt} dt = -\frac{R}{L} v dt \quad \text{so} \quad dv = -\frac{R}{L} v dt$$

$$\frac{dv}{v} = -\frac{R}{L} dt$$

$$\int_{V_o}^{v(t)} \frac{dx}{x} = -\frac{R}{L} \int_0^t dy$$

$$\ln \frac{v(t)}{V_o} = -\frac{R}{L} t$$

$$\therefore v(t) = V_o e^{-(R/L)t} = (V_s - RI_o) e^{-(R/L)t}$$

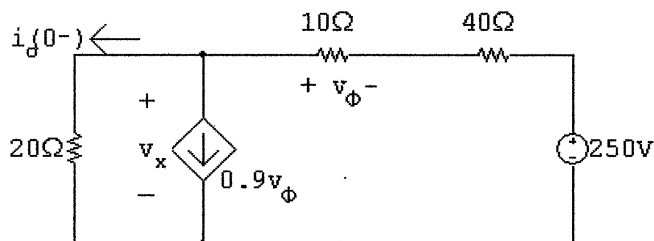P 7.41 For  $t < 0$ 

$$\frac{v_x}{20} + 9 \left[ \frac{v_x - 250}{50} \right] + \left[ \frac{v_x - 250}{50} \right] = 0$$



$$\frac{v_x}{20} + 10 \frac{(v_x - 250)}{50} = 0$$

$$5v_x - 5000 + 20v_x = 0; \quad v_x = 200 \text{ V}$$




$$i_o(0^-) = 200/20 = 10 \text{ A}$$


$$t > 0$$

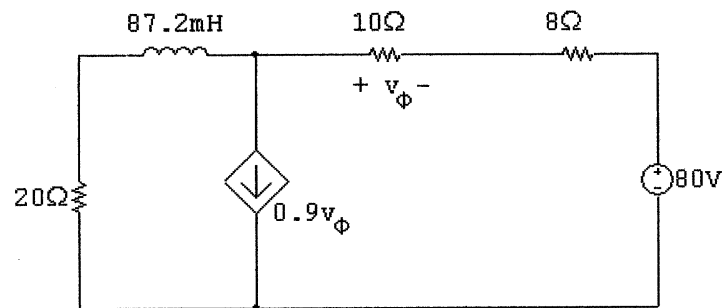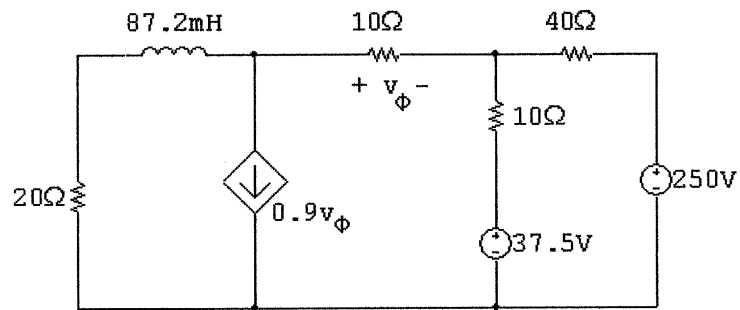

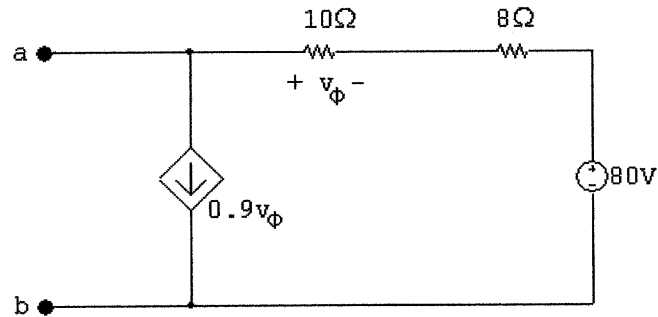Find Thévenin equivalent with respect to a, b



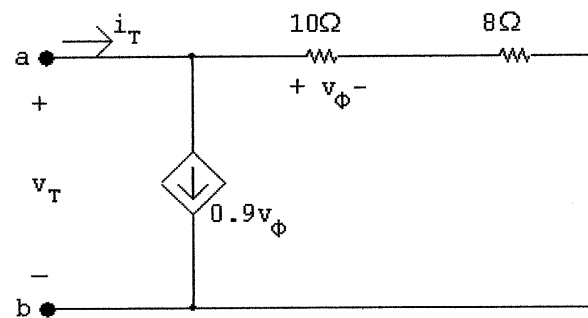
$$\frac{V_{Th} - 80}{18} + 9 \frac{(V_{Th} - 80)}{18} = 0 \quad V_{Th} = 80 \text{ V}$$



$$v_T = (i_T - 0.9v_\phi)18 = \left[ i_T - 0.9 \left( \frac{10v_T}{18} \right) \right] 18$$

$$v_T = 18i_T - 9v_T \quad \therefore 10v_T = 18i_T$$
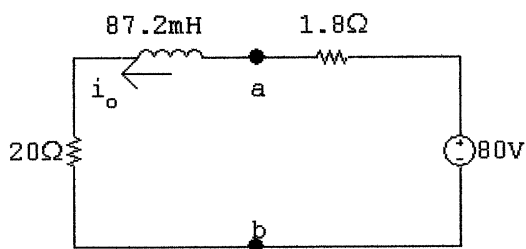
$$\frac{v_T}{i_T} = R_{Th} = 1.8 \Omega$$




$$i_o(\infty) = 80/21.8 = 3.67 \text{ A}$$

$$\tau = \frac{87.2}{21.8} \times 10^{-3} = 4 \text{ ms}; \quad 1/\tau = 250$$

$$i_o = 3.67 + (10 - 3.67)e^{-250t} = 3.67 + 6.33e^{-250t} \text{ A}, \quad t \geq 0$$


P 7.42  $t < 0$ ;

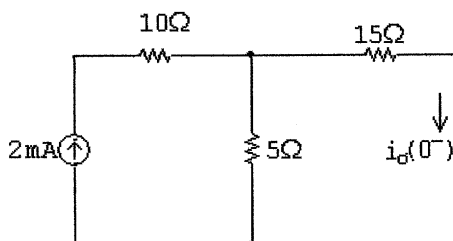

$$i_o(0^-) = \frac{5}{5 + 15}(0.002) = 0.5 \text{ mA}$$

$$i_o(0^+) = i_o(0^-) = 0.5 \text{ mA}$$

$t > 0$ ;

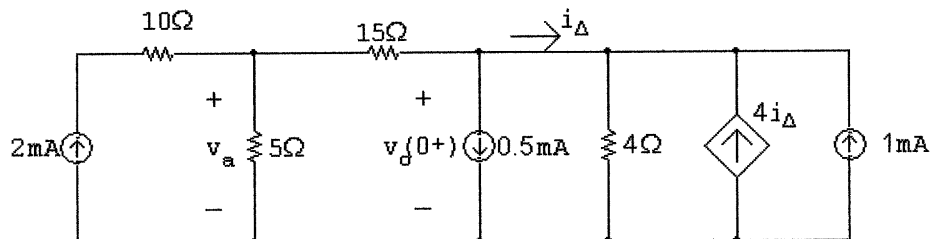

$$-0.002 + \frac{v_a}{5} + \frac{v_a - v_o}{15} = 0$$

$$\frac{v_o - v_a}{15} + 5 \times 10^{-4} + \frac{v_o}{4} - 4i_\Delta - 0.001 = 0$$

$$i_{\Delta} = \frac{v_o}{4} - 4i_{\Delta} - 0.001$$


Solving,

$$v_o(0^+) = 2 \text{ mV}$$

We also know that

$$v_o(\infty) = 0$$

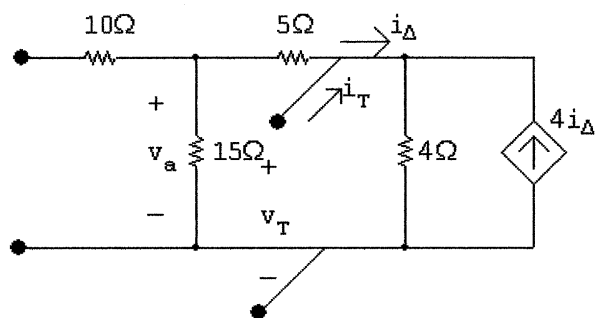Find the Thévenin resistance seen by the 2 mH inductor:



$$i_T = \frac{v_T}{20} + \frac{v_T}{4} - 4i_{\Delta}$$

$$i_{\Delta} = \frac{v_T}{4} - 4i_{\Delta} \quad \therefore 5i_{\Delta} = \frac{v_T}{4}; \quad i_{\Delta} = \frac{v_T}{20}$$

$$i_T = \frac{v_T}{20} + \frac{v_T}{4} - \frac{4v_T}{20}$$

$$\frac{i_T}{v_T} = \frac{1}{20} + \frac{1}{4} - \frac{1}{5} = \frac{2}{20} = 0.1 \text{ S}$$

$$\therefore R_{Th} = 10\Omega$$

$$\tau = \frac{2 \times 10^{-3}}{10} = 0.2 \text{ ms}; \quad 1/\tau = 5000$$

$$\therefore v_o = 0 + (2 - 0)e^{-5000t} = 2e^{-5000t} \text{ mV}, \quad t \geq 0^+$$

P 7.43 [a] Let  $v$  be the voltage drop across the parallel branches, positive at the top node, then

$$-I_g + \frac{v}{R_g} + \frac{1}{L_1} \int_0^t v \, dx + \frac{1}{L_2} \int_0^t v \, dx = 0$$

$$\frac{v}{R_g} + \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \int_0^t v \, dx = I_g$$

$$\frac{v}{R_g} + \frac{1}{L_e} \int_0^t v \, dx = I_g$$

$$\frac{1}{R_g} \frac{dv}{dt} + \frac{v}{L_e} = 0$$

$$\frac{dv}{dt} + \frac{R_g}{L_e} v = 0$$

Therefore  $v = I_g R_g e^{-t/\tau}$ ;  $\tau = L_e/R_g$


Thus

$$i_1 = \frac{1}{L_1} \int_0^t I_g R_g e^{-x/\tau} \, dx = \frac{I_g R_g}{L_1} \frac{e^{-x/\tau}}{(-1/\tau)} \Big|_0^t = \frac{I_g L_e}{L_1} (1 - e^{-t/\tau})$$

$$i_1 = \frac{I_g L_2}{L_1 + L_2} (1 - e^{-t/\tau}) \quad \text{and} \quad i_2 = \frac{I_g L_1}{L_1 + L_2} (1 - e^{-t/\tau})$$

[b]  $i_1(\infty) = \frac{L_2}{L_1 + L_2} I_g$ ;  $i_2(\infty) = \frac{L_1}{L_1 + L_2} I_g$

P 7.44  $t > 0$

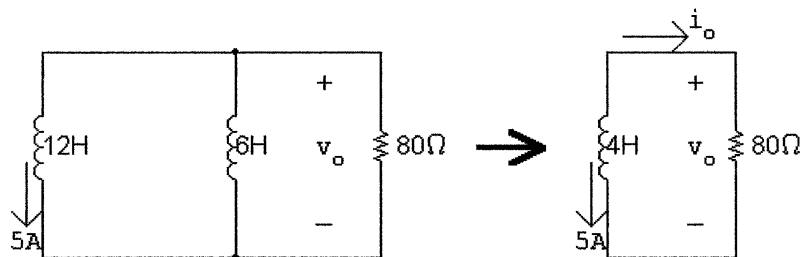

$$\tau = \frac{4}{80} = \frac{1}{20}$$

$$i_o = -5e^{-20t} \text{ A}, \quad t \geq 0$$

$$v_o = 80i_o = -400e^{-20t} \text{ V}, \quad t > 0^+$$

$$-400e^{-20t} = -80; \quad e^{20t} = 5$$

$$\therefore t = \frac{1}{20} \ln 5 = 80.47 \text{ ms}$$

P 7.45 [a]  $w_{\text{diss}} = \frac{1}{2} L_e i^2(0) = \frac{1}{2} (4)(25) = 50 \text{ J}$


[b]

$$\begin{aligned} i_{12H} &= \frac{1}{12} \int_0^t (-400) e^{-20x} dx + 5 \\ &= \frac{-100}{3} \frac{e^{-20x}}{-20} \Big|_0^t + 5 = \frac{5}{3} e^{-20t} + \frac{10}{3} \text{ A} \\ i_{6H} &= \frac{1}{6} \int_0^t (-400) e^{-20x} dx + 0 \\ &= \frac{-200}{3} \frac{e^{-20x}}{-20} \Big|_0^t + 0 = \frac{10}{3} e^{-20t} - \frac{10}{3} \text{ A} \end{aligned}$$


$$w_{\text{trapped}} = \frac{1}{2} (18)(100/9) = 100 \text{ J}$$

[c]  $w(0) = \frac{1}{2} (12)(25) = 150 \text{ J}$

P 7.46 [a]  $t < 0$

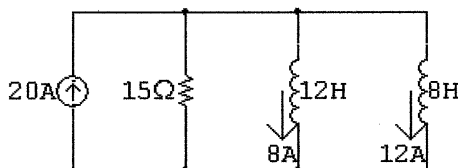

$t > 0$

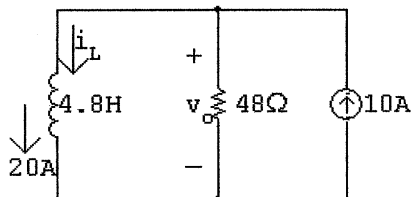

$$i_L(0^-) = i_L(0^+) = 20 \text{ A}; \quad \tau = \frac{4.8}{48} = 0.1 \text{ s}; \quad \frac{1}{\tau} = 10$$

$$i_L(\infty) = 10 \text{ A}$$


$$i_L = 10 + [20 - 10]e^{-10t} = 10 + 10e^{-10t} \text{ A}, \quad t \geq 0$$

$$v_o = 4.8[-100e^{-10t}] = -480e^{-10t} \text{ V}, \quad t \geq 0^+$$

[b]  $i_1 = \frac{1}{12} \int_0^t -480e^{-10x} dx + 8 = 4e^{-10t} + 4 \text{ A}, \quad t \geq 0$

[c]  $i_2 = \frac{1}{8} \int_0^t -480e^{-10x} dx + 12 = 6e^{-10t} + 6 \text{ A}, \quad t \geq 0$

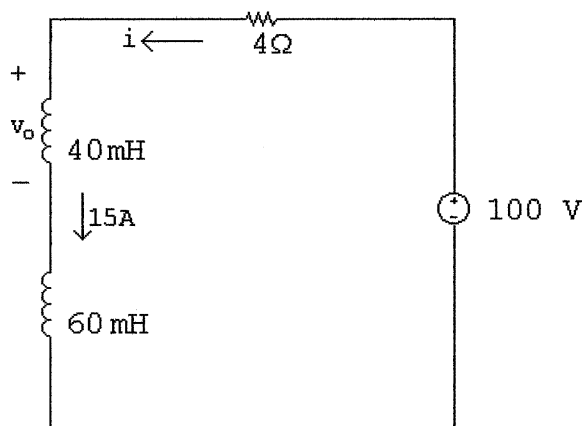- P 7.47 For  $t < 0$ ,  $i_{40\text{mH}}(0) = 75/5 = 15 \text{ A}$   
 For  $t > 0$ , after making a Thévenin equivalent we have



$$i = \frac{V_s}{R} + \left( I_o - \frac{V_s}{R} \right) e^{-t/\tau}$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{4}{100} \times 10^3 = 40$$

$$I_o = 15 \text{ A}; \quad \frac{V_s}{R} = \frac{100}{4} = 25 \text{ A}$$


$$i = 25 + (15 - 25)e^{-40t} = 25 - 10e^{-40t} \text{ A}, \quad t \geq 0$$

$$v_o = 0.04 \frac{di}{dt} = 0.04(400e^{-40t}) = 16e^{-40t} \text{ V}, \quad t > 0^+$$

- P 7.48 [a]  $v_c(0^-) = \frac{16}{20}(30) = 24 \text{ V}$

$$C_{\text{eq}} = \left( \frac{1}{30} + \frac{1}{15} \right)^{-1} = 10 \text{ nF}$$

For  $t > 0$ :

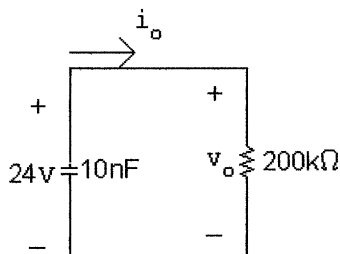

$$\tau = RC = 200 \times 10^3 \times 10 \times 10^{-9} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 24e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad i_o = \frac{v_o}{200,000} = \frac{24e^{-500t}}{200,000} = 120e^{-500t} \mu\text{A}$$

$$v_1 = \frac{1}{15 \times 10^{-9}} \times 120 \times 10^{-6} \int_0^t e^{-500x} dx + 0 = 16 - 16e^{-500t} \text{ V}, \quad t \geq 0$$

P 7.49 [a] The energy delivered to the  $200 \text{ k}\Omega$  resistor is equal to the energy stored in the equivalent capacitor. From the solution to Problem 7.48 we have

$$w = \frac{1}{2} C_{\text{eq}} v_o^2 = \frac{1}{2} (10 \times 10^{-9}) (24)^2 = 2.88 \mu\text{J}$$


[b] From the solution to Problem 7.48 we know the voltage on the  $15 \text{ nF}$  capacitor at  $t = \infty$  is  $16 \text{ V}$ . Therefore, the voltage across the  $30 \text{ nF}$  capacitor at  $t = \infty$  is  $-16 \text{ V}$ . It follows that the total energy trapped is

$$w_{\text{trapped}} = \frac{1}{2} (30 \times 10^{-9}) (-16)^2 + \frac{1}{2} (15 \times 10^{-9}) (16)^2 = 5.76 \mu\text{J}$$

$$[c] \quad w(0) = \frac{1}{2} (30 \times 10^{-9}) (24^2) = 8.64 \mu\text{J}$$

$$\text{Check:} \quad w_{\text{trapped}} + w_{\text{diss}} = 5.76 + 2.88 = 8.64 = w(0)$$

P 7.50 [a]  $t > 0$

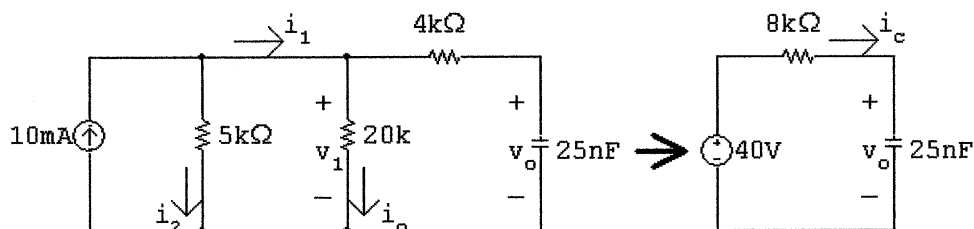

$$v_o(0^-) = v_o(0^+) = 0 \text{ V}$$

$$v_o(\infty) = 40 \text{ V}$$

$$\tau = (8 \times 10^3)(25) \times 10^{-9} = 0.2 \text{ ms} \quad 1/\tau = 5000$$

$$v_o = (40 - 40e^{-5000t}) \text{ V}, \quad t \geq 0$$

$$[b] \quad i_c = 25 \times 10^{-9} \frac{dv_o}{dt}$$

$$i_c = 25 \times 10^{-9} (200,000e^{-5000t}) = 5e^{-5000t} \text{ mA}$$

$$v_1 = 4(5e^{-5000t}) + 40 - 40e^{-5000t} = 40 - 20e^{-5000t}$$

$$i_o = \frac{v_1}{20 \times 10^3} = 2 - e^{-5000t} \text{ mA}$$

$$[c] \quad i_1(t) = i_o + i_c = 2 + 4e^{-5000t} \text{ mA}$$

$$[d] \ i_2(t) = \frac{v_1}{5 \times 10^3} = 8 - 4e^{-5000t} \text{ mA}$$

$$[e] \ i_1(0^+) = 2 + 4 = 6 \text{ mA}$$



$$\text{Checks: } i_1 + i_2 = 10 \text{ mA}$$

$$i_c(0^+) = \frac{10 \left( \frac{1}{4} \right)}{\left( \frac{1}{5} + \frac{1}{20} + \frac{1}{4} \right)} = 5 \text{ mA}$$

$$i_o(0^+) = \frac{10 \left( \frac{1}{20} \right)}{\left( \frac{1}{5} + \frac{1}{20} + \frac{1}{4} \right)} = 1 \text{ mA}$$



$$i_1(0^+) = 5 + 1 = 6 \text{ mA}$$

P 7.51 For  $t < 0$

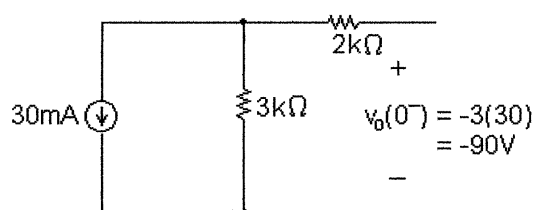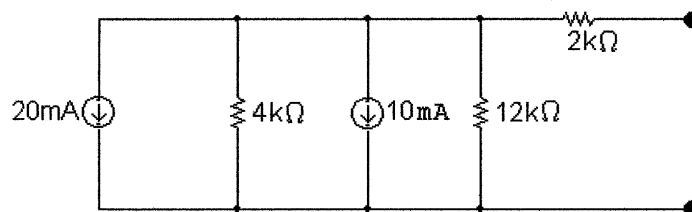


$$\therefore v_o(0^-) = v_o(0^+) = -90 \text{ V}$$

$t > 0$

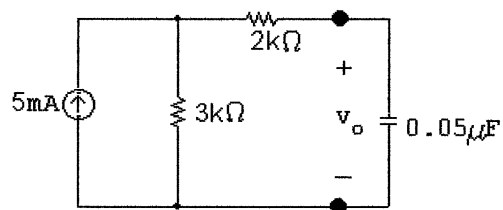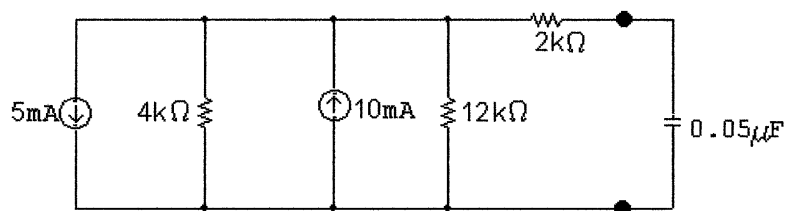



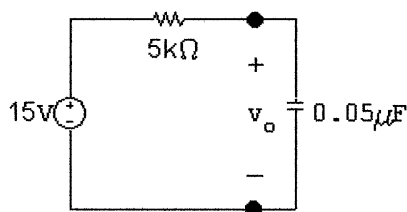

$$v_o(\infty) = 15 \text{ V}; \quad \tau = RC = (5 \text{ k})(0.05 \mu) = 0.25 \text{ ms}; \quad \frac{1}{\tau} = 4000$$

$$\begin{aligned} v_o &= v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = 15 + [-90 - 15]e^{-4000t} \\ &= 15 - 105e^{-4000t} \text{ V} \quad t \geq 0 \end{aligned}$$

P 7.52 [a]  $I_s = i(0^+) = 50 \text{ mA}; \quad V_o = 0 \text{ V}$

$$I_s R = v(\infty) = 80$$

$$\therefore R = \frac{80}{0.05} = 1.6 \text{ k}\Omega$$

$$RC = \frac{1}{2500}; \quad C = \frac{1}{2500(1600)} = 250 \text{ nF}$$

[b]  $w(t) = \frac{1}{2}(250 \times 10^{-9})[80 - 80e^{-2500t}]^2$

$$= 125 \times 10^{-9}(6400)[1 - e^{-2500t}]^2$$

$$= 800[1 - 2e^{-2500t} + e^{-5000t}] \mu\text{J}$$

Let  $x = e^{-2500t}$ ; then  $800[1 - 2x + x^2] = 0.64(800)$

$$\therefore x^2 - 2x + 0.36 = 0$$

The two solutions are  $x = 1.8, \quad x = 0.2$

Only the second solution is valid  $\therefore e^{+2500t} = 5$

$$2500t = \ln 5 \quad \text{so} \quad t = 400 \ln 5 \mu\text{s} = 643.787 \mu\text{s}$$

P 7.53 [a]  $v_c(0^+) = 120 \text{ V}$

[b] Use voltage division to find the final value of voltage:


$$v_c(\infty) = \frac{150}{150 + 50}(-200) = -150 \text{ V}$$

- [c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{Th} = -150 \text{ V}, \quad R_{Th} = 12.5 \text{ k} + 150 \text{ k} \parallel 50 \text{ k} = 50 \text{ k}\Omega,$$

$$\text{Therefore } \tau = R_{eq}C = (50,000)(40 \times 10^{-9}) = 2 \text{ ms}$$

The simplified circuit for  $t > 0$  is:

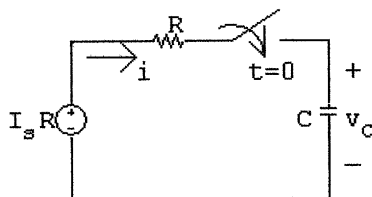

$$[d] \quad i(0^+) = \frac{-150 - 120}{50,000} = -5.4 \text{ mA}$$

$$[e] \quad v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau}$$

$$= -150 + [120 - (-150)]e^{-t/\tau} = -150 + 270e^{-500t} \text{ V}, \quad t \geq 0$$

$$[f] \quad i = C \frac{dv_c}{dt} = (40 \times 10^{-9})(-500)(270e^{-500t}) = 5.4e^{-500t} \text{ mA}, \quad t \geq 0^+$$

- P 7.54 [a] Use voltage division to find the initial value of the voltage:

$$v_c(0^+) = v_{10k} = \frac{10 \text{ k}}{10 \text{ k} + 15 \text{ k}}(-75) = -30 \text{ V}$$

- [b] Use Ohm's law to find the final value of voltage:

$$v_c(\infty) = v_{5k} = (5 \times 10^{-3})(5000) = 25 \text{ V}$$

- [c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{Th} = 25 \text{ V}, \quad R_{Th} = 5 \text{ k} + 20 \text{ k} = 25 \text{ k}\Omega$$

$$\tau = R_{Th}C = 2.5 \text{ ms}$$


$$[d] \quad v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau}$$

$$= 25 + (-30 - 25)e^{-400t} = 25 - 55e^{-400t} \text{ V}, \quad t \geq 0$$

$$\text{We want } v_c = 25 - 55e^{-400t} = 0:$$

$$\text{Therefore } t = \frac{\ln(55/25)}{400} = 1.97 \text{ ms}$$

P 7.55 [a]

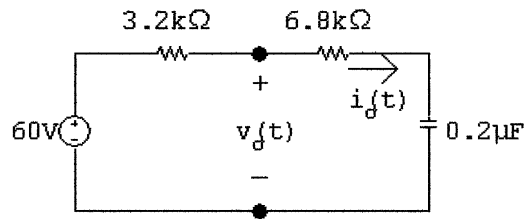


$$i_o(0^+) = \frac{60}{10} \times 10^{-3} = 6 \text{ mA}$$

$$[b] \quad i_o(\infty) = 0$$

$$[c] \quad \tau = RC = (10 \times 10^3)(0.2 \times 10^{-6}) = 2 \text{ ms}$$

$$[d] \quad i_o = 0 + (6 - 0)e^{-500t} = 6e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$[e] \quad v_o = 60 - 3.2 \times 10^3 i_o = 60 - 19.2e^{-500t} \text{ V}, \quad t \geq 0^+$$

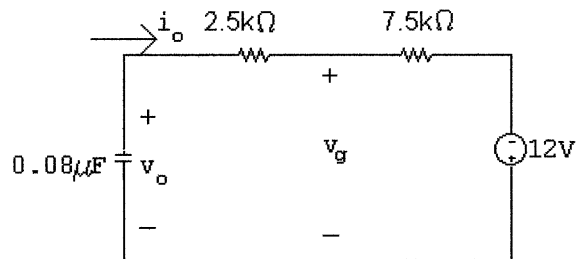P 7.56 [a]  $v_o(0^-) = v_o(0^+) = 48 \text{ V}$ 

$$v_o(\infty) = -12 \text{ V}; \quad \tau = 0.8 \text{ ms}; \quad \frac{1}{\tau} = 1250$$

$$v_o = -12 + (48 - (-12))e^{-1250t}$$

$$v_o = -12 + 60e^{-1250t} \text{ V}, \quad t \geq 0$$

$$[b] \quad i_o = -0.08 \times 10^{-6}[-75,000e^{-1250t}]$$

$$i_o = 6e^{-1250t} \text{ mA}, \quad t \geq 0^+$$

$$[c] \quad v_g = v_o - 2.5 \times 10^3 i_o$$

$$v_g = -12 + 45e^{-1250t} \text{ V}$$

$$[d] \quad v_g(0^+) = -12 + 45 = 33 \text{ V}$$

Checks:

$$v_g(0^+) = i_o(0^+)7.5 \times 10^3 - 12 = 45 - 12 = 33 \text{ V}$$

$$i_{10k} = \frac{v_g}{10k} = -1.2 + 4.5e^{-1250t} \text{ mA}$$


$$i_{30k} = \frac{v_g}{30k} = -0.4 + 1.5e^{-1250t} \text{ mA}$$

$$-i_o + i_{10} + i_{30} + 1.6 = 0 \quad (\text{ok})$$

P 7.57  $t < 0$ ;

$$i_o(0^-) = (15)\frac{20}{50} = 6 \text{ mA}; \quad v_o(0^-) = (6)(10) = 60 \text{ V}$$

$t = \infty$ :

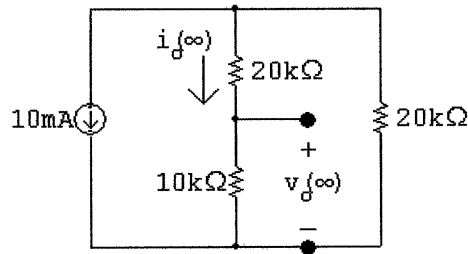


$$i_o(\infty) = -10 \left( \frac{20}{50} \right) = -4 \text{ mA}; \quad v_o(\infty) = i_o(\infty)(10) = -40 \text{ V}$$

$$R_{Th} = 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega = 8 \text{ k}\Omega; \quad C = 125 \text{ nF}$$

$$\tau = (8)(0.125) = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$
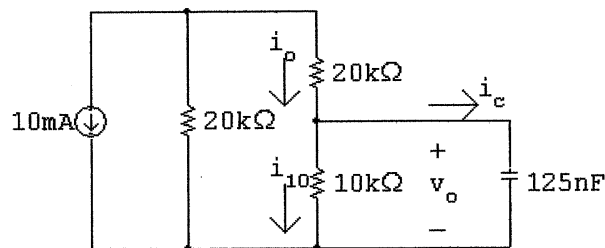
$$\therefore v_o(t) = -40 + 100e^{-1000t} \text{ V}, \quad t \geq 0^+$$



$$i_c = C \frac{dv_o}{dt} = -12.5e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$i_{10} = \frac{v_o}{10} = -4 + 10e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$i_o = i_c + i_{10} = -(4 + 2.5e^{-1000t}) \text{ mA}, \quad t \geq 0^+$$


P 7.58 For  $t > 0$ 

$$V_{Th} = (-15)(30)i_b = -450 \times 10^3 i_b$$

$$i_b = \frac{400(12)}{48} = 100 \mu\text{A}$$

$$V_{Th} = -450 \times 10^3 (100 \times 10^{-6}) = -45 \text{ V}$$

$$R_{Th} = 15 \text{ k}\Omega$$

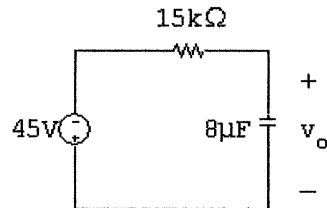

$$v_o(\infty) = -45 \text{ V}; \quad v_o(0^+) = 0$$

$$\tau = (15,000)(8)10^{-6} = 120 \text{ ms}; \quad 1/\tau = 8.33$$

$$v_o = -45 + 45e^{-8.33t} \text{ V}, \quad t \geq 0$$

$$w(t) = \frac{1}{2}(8 \times 10^{-6})v_o^2 = 8100(1 - 2e^{-8.33t} + e^{-16.67t}) \mu\text{J}$$

$$w(\infty) = 8100 \mu\text{J}$$

$$\therefore 8100(1 - 2e^{-8.33t_o} + e^{-16.67t_o}) = 0.90(8100)$$


$$\therefore 1 - 2x + x^2 = 0.90; \quad x = e^{-8.33t_o}$$

$$\therefore x^2 - 2x + 0.10 = 0$$


$$x_{1,2} = 1.9487, \quad 0.0513$$

$$e^{-(25/3)t_o} = 0.0513; \quad (25/3)t_o = \ln 19.4868; \quad t_o = 356.4 \text{ ms}$$

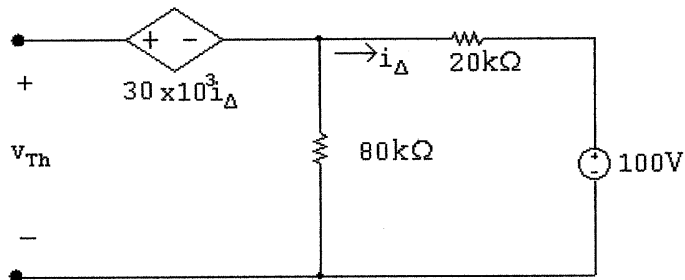P 7.59 For  $t < 0$ ,  $v_o(0) = 80 \text{ V}$   
 $t > 0$ :



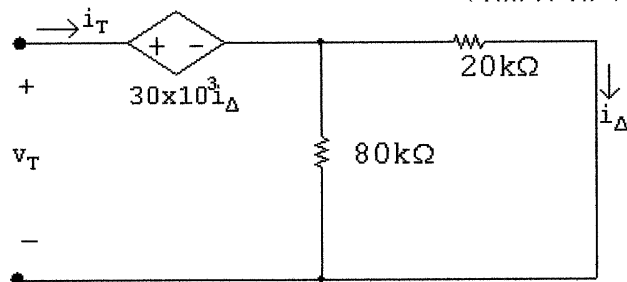
$$v_{Th} = 30 \times 10^3 i_D + 0.8(100) = 30 \times 10^3 \left( \frac{-100}{100 \times 10^3} \right) + 80 = 50 \text{ V}$$



$$v_T = 30 \times 10^3 i_D + 16 \times 10^3 i_T = 30 \times 10^3 (0.8) i_T + 16 \times 10^3 i_T = 40 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = 40 \text{ k}\Omega$$

$t > 0$

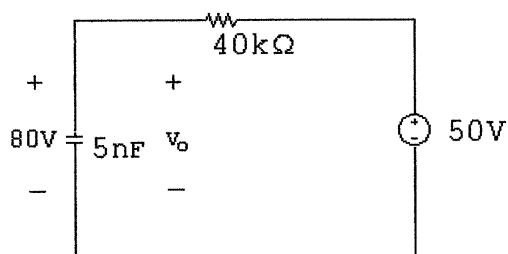

$$v_o = 50 + (80 - 50)e^{-t/\tau}$$

$$\tau = RC = (40 \times 10^3)(5 \times 10^{-9}) = 200 \times 10^{-6}; \quad \frac{1}{\tau} = 5000$$

$$v_o = 50 + 30e^{-5000t} \text{ V}$$


P 7.60  $v_o(0) = 50 \text{ V}$ ;  $v_o(\infty) = 80 \text{ V}$

$$R_{Th} = 16 \text{ k}\Omega$$

$$\tau = (16)(5 \times 10^{-6}) = 80 \times 10^{-6}; \quad \frac{1}{\tau} = 12,500$$

$$v = 80 + (50 - 80)e^{-12,500t} = 80 - 30e^{-12,500t} \text{ V}$$

P 7.61 [a]

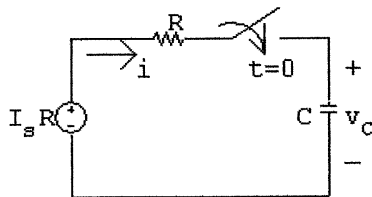

$$I_s R = Ri + \frac{1}{C} \int_{0^+}^t i \, dx + V_o$$

$$0 = R \frac{di}{dt} + \frac{i}{C} + 0$$

$$\therefore \frac{di}{dt} + \frac{i}{RC} = 0$$

$$[b] \quad \frac{di}{dt} = -\frac{i}{RC}; \quad \frac{di}{i} = -\frac{dt}{RC}$$

$$\int_{i(0^+)}^{i(t)} \frac{dy}{y} = -\frac{1}{RC} \int_{0^+}^t dx$$

$$\ln \frac{i(t)}{i(0^+)} = \frac{-t}{RC}$$

$$i(t) = i(0^+) e^{-t/RC}; \quad i(0^+) = \frac{I_s R - V_o}{R} = \left( I_s - \frac{V_o}{R} \right)$$

$$\therefore i(t) = \left( I_s - \frac{V_o}{R} \right) e^{-t/RC}$$

P 7.62 [a] Let  $i$  be the current in the clockwise direction around the circuit. Then

$$\begin{aligned} V_g &= iR_g + \frac{1}{C_1} \int_0^t i \, dx + \frac{1}{C_2} \int_0^t i \, dx \\ &= iR_g + \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int_0^t i \, dx = iR_g + \frac{1}{C_e} \int_0^t i \, dx \end{aligned}$$

Now differentiate the equation

$$0 = R_g \frac{di}{dt} + \frac{i}{C_e} \quad \text{or} \quad \frac{di}{dt} + \frac{1}{R_g C_e} i = 0$$

$$\text{Therefore } i = \frac{V_g}{R_g} e^{-t/R_g C_e} = \frac{V_g}{R_g} e^{-t/\tau}; \quad \tau = R_g C_e$$


$$v_1(t) = \frac{1}{C_1} \int_0^t \frac{V_g}{R_g} e^{-x/\tau} dx = \frac{V_g}{R_g C_1} \frac{e^{-x/\tau}}{-1/\tau} \Big|_0^t = -\frac{V_g C_e}{C_1} (e^{-t/\tau} - 1)$$

$$v_1(t) = \frac{V_g C_2}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$


$$v_2(t) = \frac{V_g C_1}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$

$$[b] \quad v_1(\infty) = \frac{C_2}{C_1 + C_2} V_g; \quad v_2(\infty) = \frac{C_1}{C_1 + C_2} V_g$$

P 7.63 [a]  $t < 0$

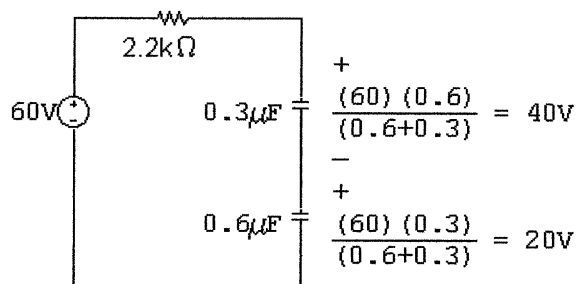

$t > 0$

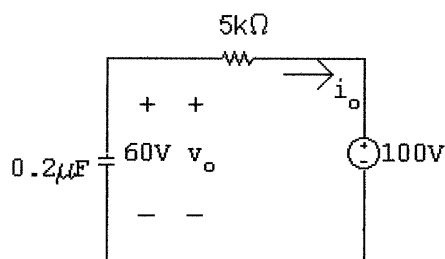

$$v_o(0^-) = v_o(0^+) = 60\text{ V}$$

$$v_o(\infty) = 100\text{ V}$$

$$\tau = (0.2)(5) \times 10^{-3} = 1\text{ ms}; \quad 1/\tau = 1000$$

$$v_o = 100 - 40e^{-1000t}\text{ V}, \quad t \geq 0$$

$$[b] \quad i_o = -C \frac{dv_o}{dt} = -0.2 \times 10^{-6} [40,000e^{-1000t}]$$

$$= -8e^{-1000t}\text{ mA}; \quad t \geq 0^+$$

$$[c] \quad v_1 = \frac{-10^6}{0.3} \int_0^t -8 \times 10^{-3} e^{-1000x} dx + 40$$

$$= 66.67 - 26.67e^{-1000t}\text{ V}, \quad t \geq 0$$

$$[d] \quad v_2 = \frac{-10^6}{0.6} \int_0^t -8 \times 10^{-3} e^{-1000x} dx + 20$$

$$= 33.33 - 13.33e^{-1000t}\text{ V}, \quad t \geq 0$$



$$\begin{aligned} \text{[e]} \quad w_{\text{trapped}} &= \frac{1}{2}(0.3)10^{-6}(66.67)^2 + \frac{1}{2}(0.6)10^{-6}(33.33)^2 \\ &= 666.67 + 333.33 = 1000 \mu\text{J}. \end{aligned}$$

$$\text{P 7.64} \quad v_o(0) = \frac{120}{120}(80) = 80 \text{ V}$$

$$v_o(\infty) = -6(25) = -150 \text{ V}$$

$$\tau = (25 \times 10^3)(40 \times 10^{-9}) = 10^{-3} \text{ s}; \quad \frac{1}{\tau} = 1000$$

$$v_o = -150 + (80 + 150)e^{-1000t} = -150 + 230e^{-1000t} \text{ V}, \quad t \geq 0$$

P 7.65 [a] From Example 7.10,

$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{(8 \text{ m})(20 \text{ m}) - (10 \text{ m})^2}{8 \text{ m} + 20 \text{ m} - 2(10 \text{ m})} = 7.5 \text{ mH}$$

$$\tau = \frac{L_{\text{eq}}}{R} = \frac{(7.5 \text{ m})}{75} = \frac{1}{10,000}$$

$$i_o = \frac{15}{75} - \frac{15}{75}e^{-10,000t} = 0.2 - 0.2e^{-10,000t} \text{ A} \quad t \geq 0$$

$$\text{[b]} \quad v_o = 15 - 75i_o = 15 - 75(0.2 - 0.2e^{-10,000t}) = 15e^{-10,000t} \text{ V} \quad t \geq 0^+$$

$$\text{[c]} \quad v_o = 0.008 \frac{di_1}{dt} + 0.01 \frac{di_2}{dt}$$

$$i_o = i_1 + i_2$$

$$\frac{di_o}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$\frac{di_2}{dt} = \frac{di_o}{dt} - \frac{di_1}{dt} = 2000e^{-10,000t} - \frac{di_1}{dt}$$

$$\therefore 15e^{-10,000t} = 0.008 \frac{di_1}{dt} + 0.01 \left( 2000e^{-10,000t} - \frac{di_1}{dt} \right)$$

$$\therefore \frac{di_1}{dt} = 2500e^{-10,000t}$$

$$di_1 = 2500e^{-10,000t} dt$$

$$\int_0^{i_1} dx = 2500 \int_0^t e^{-10,000y} dy$$

$$\therefore i_1 = 2500 \frac{e^{-10,000y}}{-10,000} \Big|_0^t = 0.25 - 0.25e^{-10,000t} \text{ A}, \quad t \geq 0$$

$$\begin{aligned}
 \text{[d]} \quad i_2 &= i_o - i_1 \\
 &= 0.2 - 0.2e^{-10,000t} - 0.25 + 0.25e^{-10,000t} \\
 &= -50 + 50e^{-10,000t} \text{ mA}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[e]} \quad v_o &= L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \\
 &= 0.02(-500e^{-10,000t}) + 0.01(2500e^{-10,000t}) \\
 &= 15e^{-10,000t} \text{ V}, \quad t \geq 0^+ \quad (\text{checks})
 \end{aligned}$$

$i_1(0) = 0.25 - 0.25 = 0$ ; agrees with initial conditions;

$i_2(0) = -0.05 + 0.05 = 0$ ; agrees with initial conditions;

The final values of  $i_o$ ,  $i_1$ , and  $i_2$  can be checked via the conservation of Wb-turns:

$$i_o(\infty)L_{\text{eq}} = 0.2 \times (7.5 \text{ m}) = 1.5 \text{ mWb-turns}$$

$$i_1(\infty)L_1 + i_2(\infty)M = 0.25(8 \text{ m}) - 0.05(10 \text{ m}) = 15 \text{ mWb-turns}$$

$$i_2(\infty)L_2 + i_1(\infty)M = -0.05(0.02) + 0.25(0.01) = 15 \text{ mWb-turns}$$

Thus our solutions make sense in terms of known circuit behavior.

$$\text{P 7.66 [a]} \quad L_{\text{eq}} = \frac{(3)(15)}{3 + 15} = 2.5 \text{ H}$$

$$\tau = \frac{L_{\text{eq}}}{R} = \frac{2.5}{7.5} = \frac{1}{3} \text{ s}$$

$$i_o(0) = 0; \quad i_o(\infty) = \frac{120}{7.5} = 16 \text{ A}$$

$$\therefore i_o = 16 - 16e^{-3t} \text{ A}, \quad t \geq 0$$

$$v_o = 120 - 7.5i_o = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

$$i_1 = \frac{1}{3} \int_0^t 120e^{-3x} dx = \frac{40}{3} - \frac{40}{3}e^{-3t} \text{ A}, \quad t \geq 0$$

$$i_2 = i_o - i_1 = \frac{8}{3} - \frac{8}{3}e^{-3t} \text{ A}, \quad t \geq 0$$

$$\begin{aligned}
 \text{[b]} \quad i_o(0) &= i_1(0) = i_2(0) = 0, \text{ consistent with initial conditions.} \\
 v_o(0^+) &= 120 \text{ V, consistent with } i_o(0) = 0.
 \end{aligned}$$

$$v_o = 3 \frac{di_1}{dt} = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

or

$$v_o = 15 \frac{di_2}{dt} = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

The voltage solution is consistent with the current solutions.

$$\lambda_1 = 3i_1 = 40 - 40e^{-3t} \text{ Wb-turns}$$

$$\lambda_2 = 15i_2 = 40 - 40e^{-3t} \text{ Wb-turns}$$

$\therefore \lambda_1 = \lambda_2$  as it must, since

$$v_o = \frac{d\lambda_1}{dt} = \frac{d\lambda_2}{dt}$$

$$\lambda_1(\infty) = \lambda_2(\infty) = 40 \text{ Wb-turns}$$

$$\lambda_1(\infty) = 3i_1(\infty) = 3(40/3) = 40 \text{ Wb-turns}$$

$$\lambda_2(\infty) = 15i_2(\infty) = 15(8/3) = 40 \text{ Wb-turns}$$

$\therefore i_1(\infty)$  and  $i_2(\infty)$  are consistent with  $\lambda_1(\infty)$  and  $\lambda_2(\infty)$ .

P 7.67 [a] From Example 7.10,

$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{0.125 - 0.0625}{0.75 + 0.5} = 50 \text{ mH}$$

$$\tau = \frac{L}{R} = \frac{1}{5000}; \quad \frac{1}{\tau} = 5000$$

$$\therefore i_o(t) = 40 - 40e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$[b] \quad v_o = 10 - 250i_o = 10 - 250(0.04 + 0.04e^{-5000t}) = 10e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$[c] \quad v_o = 0.5 \frac{di_1}{dt} - 0.25 \frac{di_2}{dt} = 10e^{-5000t} \text{ V}$$

$$i_o = i_1 + i_2$$

$$\frac{di_o}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = 200e^{-5000t} \text{ A/s}$$

$$\therefore \frac{di_2}{dt} = 200e^{-5000t} - \frac{di_1}{dt}$$

$$\therefore 10e^{-5000t} = 0.5 \frac{di_1}{dt} - 50e^{-5000t} + 0.25 \frac{di_1}{dt}$$

$$\therefore 0.75 \frac{di_1}{dt} = 60e^{-5000t}; \quad di_1 = 80e^{-5000t} dt$$

$$\int_0^{t_1} dx = \int_0^t 80e^{-5000y} dy$$

$$i_1 = \frac{80}{-5000} e^{-5000y} \Big|_0^t = 16 - 16e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$\begin{aligned}
 \text{[d]} \quad i_2 &= i_o - i_1 = 40 - 40e^{-5000t} - 16 + 16e^{-5000t} \\
 &= 24 - 24e^{-5000t} \text{ mA}, \quad t \geq 0
 \end{aligned}$$

[e]  $i_o(0) = i_1(0) = i_2(0) = 0$ , consistent with zero initial stored energy.

$$v_o = L_{\text{eq}} \frac{di_o}{dt} = (0.05)(200)e^{-5000t} = 10e^{-5000t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

Also,

$$v_o = 0.5 \frac{di_1}{dt} - 0.25 \frac{di_2}{dt} = 10e^{-5000t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o = 0.25 \frac{di_2}{dt} - 0.25 \frac{di_1}{dt} = 10e^{-5000t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$v_o(0^+) = 10 \text{ V}$ , which agrees with  $i_o(0^+) = 0 \text{ A}$

$$i_o(\infty) = 40 \text{ mA}; \quad i_o(\infty)L_{\text{eq}} = (0.04)(0.05) = 2 \text{ mWb-turns}$$

$$i_1(\infty)L_1 + i_2(\infty)M = (16 \text{ m})(500) + (24 \text{ m})(-250) = 2 \text{ mWb-turns (ok)}$$

$$i_2(\infty)L_2 + i_1(\infty)M = (24 \text{ m})(250) + (16 \text{ m})(-250) = 2 \text{ mWb-turns (ok)}$$

Therefore, the final values of  $i_o$ ,  $i_1$ , and  $i_2$  are consistent with conservation of flux linkage. Hence, the answers make sense in terms of known circuit behavior.

P 7.68 [a]  $L_{\text{eq}} = 4 + 8 - 2(5) = 2 \text{ H}$

$$\tau = \frac{L}{R} = \frac{2}{50} = \frac{1}{25}; \quad \frac{1}{\tau} = 25$$

$$i = 4 - 4e^{-25t} \text{ A}, \quad t \geq 0$$

$$\text{[b]} \quad v_1(t) = 4 \frac{di}{dt} - 5 \frac{di}{dt} = -\frac{di}{dt} = -(100e^{-25t}) = -100e^{-25t} \text{ V}, \quad t \geq 0^+$$

$$\text{[c]} \quad v_2(t) = 8 \frac{di}{dt} - 5 \frac{di}{dt} = 3 \frac{di}{dt} = 3(100e^{-25t}) = 300e^{-25t} \text{ V}, \quad t \geq 0^+$$

[d]  $i(0) = 4 - 4 = 0$ , which agrees with initial conditions.

$$200 = 50i_1 + v_1 + v_2 = 50(4 - 4e^{-25t}) - 100e^{-25t} + 300e^{-25t} = 200 \text{ V}$$

Therefore, Kirchhoff's voltage law is satisfied for all values of  $t \geq 0$ . Thus, the answers make sense in terms of known circuit behavior.

P 7.69 [a]  $L_{\text{eq}} = 4 + 8 + 2(5) = 22 \text{ H}$

$$\tau = \frac{L}{R} = \frac{22}{50}; \quad \frac{1}{\tau} = 2.273$$

$$i = 4 - 4e^{-2.273t} \text{ A}, \quad t \geq 0$$

$$[b] \quad v_1(t) = 4 \frac{di}{dt} + 5 \frac{di}{dt} = 9 \frac{di}{dt} = 9(9.09e^{-2.273t}) = 81.81e^{-2.273t} \text{ V}, \quad t \geq 0^+$$

$$[c] \quad v_2(t) = 8 \frac{di}{dt} + 5 \frac{di}{dt} = 13 \frac{di}{dt} = 13(9.09e^{-2.273t}) = 118.18e^{-2.273t} \text{ V}, \quad t \geq 0^+$$


[d]  $i(0) = 0$ , which agrees with initial conditions.

$$200 = 50i_1 + v_1 + v_2 = 50(4 - 4e^{-2.273t}) + 81.81e^{-2.273t} + 118.18e^{-2.273t} = 200 \text{ V}$$

Therefore, Kirchhoff's voltage law is satisfied for all values of  $t \geq 0$ .


Thus, the answers make sense in terms of known circuit behavior.

P 7.70  $t < 0$ :

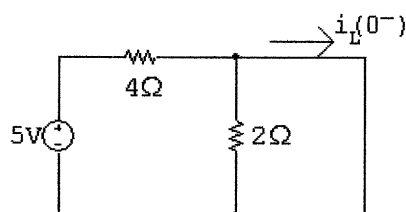

$$i_L(0^-) = 5/4 = 1.25 \text{ A} = i_L(0^+)$$

$0 \leq t \leq 1$ :

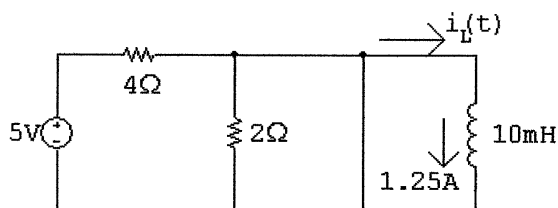


$$\tau = 5/0 = \infty$$

$$i_L(t) = 1.25e^{-t/\infty} = 1.25e^{-0} = 1.25$$

$$i_L(t) = 1.25 \text{ A}$$


$1 \leq t < \infty$ :

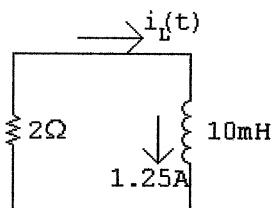

$$\tau = \frac{10 \times 10^{-3}}{2} = 5 \text{ ms}; \quad 1/\tau = 200$$

$$i_L(t) = 1.25e^{-200(t-1)} \text{ A}$$

P 7.71  $0 \leq t \leq 3 \mu\text{s}$ :

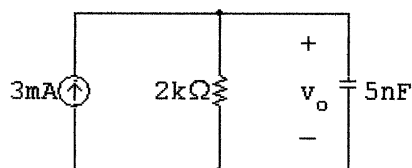


$$\tau = RC = (2 \times 10^3)(5 \times 10^{-9}) = 10 \mu\text{s}; \quad 1/\tau = 100,000$$


$$v_o(0) = 0 \text{ V}; \quad v_o(\infty) = 6 \text{ V}$$

$$v_o = 6 - 6e^{-100,000t} \text{ V} \quad 0 \leq t \leq 3 \mu\text{s}$$

$3 \mu\text{s} \leq t < \infty$ :

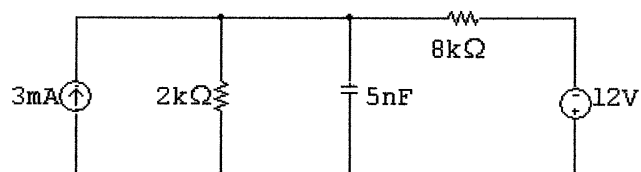

$t = \infty$ :

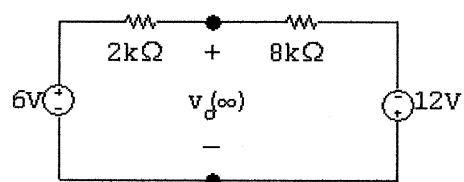

$$i = \frac{6 - (-12)}{10} = 1.8 \text{ mA}$$

$$v_o(\infty) = 6 - 2i = 2.4 \text{ V}$$


$$v_o(3 \mu\text{s}) = 6 - 6e^{-0.3} = 1.555 \text{ V}$$

$$v_o = 2.4 + (1.555 - 2.4)e^{-(t-3 \mu\text{s})/\tau}$$


$$R_{\text{Th}} = 2 \text{ k}\Omega \parallel 8 \text{ k}\Omega = 1.6 \text{ k}\Omega$$

$$\tau = (1.6)(5) = 8 \mu\text{s}; \quad 1/\tau = 125,000$$

$$v_o = 2.4 - 0.845e^{-125,000(t-3 \mu\text{s})} \quad 3 \mu\text{s} \leq t < \infty$$

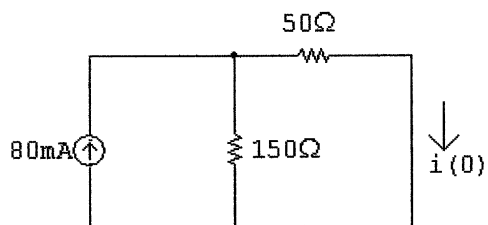
P 7.72 For  $t < 0$ :

$$i(0) = \frac{80(150)}{200} = 60 \text{ mA}$$

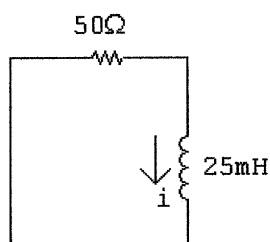 $0 \leq t \leq 250 \mu\text{s}$ :

$$i = 60e^{-2000t} \text{ mA}$$

$$i(250 \mu\text{s}) = 60e^{-0.5} = 36.39 \text{ mA}$$

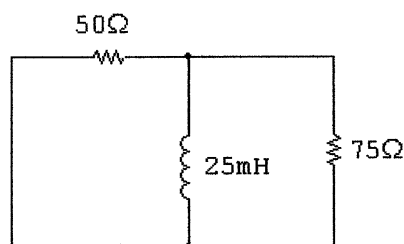 $250 \mu\text{s} \leq t \leq 650 \mu\text{s}$ :

$$R_{\text{eq}} = \frac{(50)(75)}{125} = 30 \Omega$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{30}{25} \times 10^3 = 1200$$

$$i = 36.39e^{-1200(t-250 \times 10^{-6})} \text{ mA}$$

 $650 \mu\text{s} \leq t < \infty$ :

$$i(650 \mu\text{s}) = 36.39e^{-0.48} = 22.52 \text{ mA}$$

$$i = 22.52e^{-2000(t-650 \times 10^{-6})} \text{ mA}$$

$$v = L \frac{di}{dt}; \quad L = 25 \text{ mH}$$

$$\frac{di}{dt} = 22.52(-2000) \times 10^{-3} e^{-2000(t-650 \times 10^{-6})} = -45.04e^{-2000(t-650 \times 10^{-6})}$$

$$v = (25 \times 10^{-3})(-45.04)e^{-2000(t-650 \times 10^{-6})}$$

$$= -1.13e^{-2000(t-650 \times 10^{-6})} \text{ V}, \quad t > 650^+ \mu\text{s}$$

$$v(1\text{ms}) = -1.13e^{-2000(350) \times 10^{-6}} = -559.12 \text{ mV}$$

P 7.73 From the solution to Problem 7.72, the initial energy is

$$w(0) = \frac{1}{2}(25 \text{ mH})(60 \text{ mA})^2 = 45 \mu\text{J}$$


For  $650 \mu\text{s} \leq t < \infty$ :

$$w(t) = \frac{1}{2}(25 \text{ mH})(22.52e^{-2000(t-650 \times 10^{-6})} \text{ mA})^2 = (0.04)(45 \mu\text{J})$$

Solving,

$$t = 964.72 \mu\text{s}$$

P 7.74  $0 \leq t \leq 50 \mu\text{s}$ ;

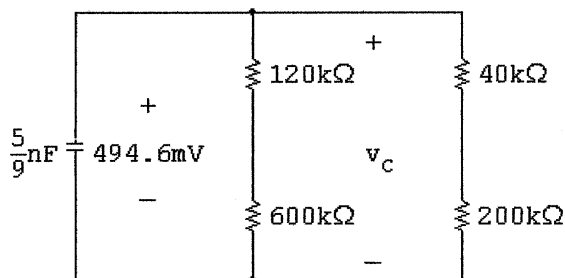


$$R_e = 720 \parallel 240 = 180 \text{ k}\Omega; \quad \tau = \left(\frac{5}{9}\right)(180) = 100 \mu\text{s}$$

$$v_c = 494.6e^{-10,000t} \text{ mV}$$

$$v_c(50 \mu\text{s}) = 494.6e^{-0.5} = 300 \text{ mV}$$



$$50 \mu s \leq t < \infty:$$

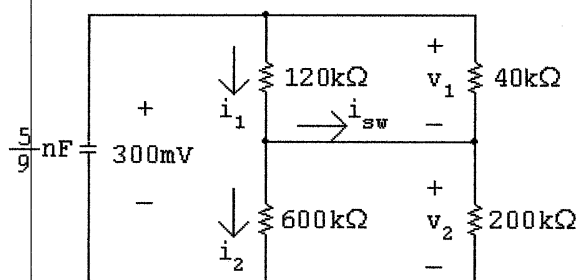

$$R_e = 120 \parallel 40 + 600 \parallel 200 = 30 + 150 = 180 \text{ k}\Omega$$

$$\tau = \left(\frac{5}{9}\right)(180) = 100 \mu s; \quad \frac{1}{\tau} = 10,000$$

$$v_c = 300e^{-10,000(t-50 \mu s)} \text{ mV}$$

$$v_1 = \frac{30}{180}v_c = 50e^{-10,000(t-50 \mu s)} \text{ mV}$$

$$v_2 = \frac{150}{180}v_c = 250e^{-10,000(t-50 \mu s)} \text{ mV}$$


$$i_1 = \frac{v_1}{120 \times 10^3} = 416.7e^{-10,000(t-50 \mu s)} \text{ nA}$$

$$i_2 = \frac{v_2}{600 \times 10^3} = 416.7e^{-10,000(t-50 \mu s)} \text{ nA}$$

$$i_{sw} = i_1 - i_2 = 0 \text{ A}$$

$$i_{sw}(100 \mu s) = 0 \text{ A}$$

P 7.75 [a]  $t < 0$ :

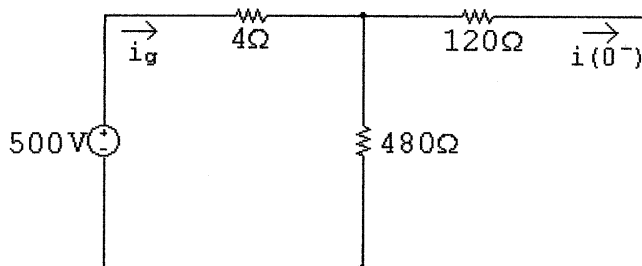

$$i_g = \frac{500}{4 + 96} = 5 \text{ A}$$

$$i(0^-) = \frac{5(480)}{600} = 4 \text{ A} = i(0^+)$$


[b]  $0 \leq t \leq 100 \mu\text{s}$ :

$$i = 4e^{-t/\tau}$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{120 + 96 \parallel 480}{20 \times 10^{-3}} = 10,000$$

$$i = 4e^{-10,000t}$$

$$i(25 \mu\text{s}) = 4e^{-10^4(25) \times 10^{-6}} = 4e^{-0.25} = 3.12 \text{ A}$$

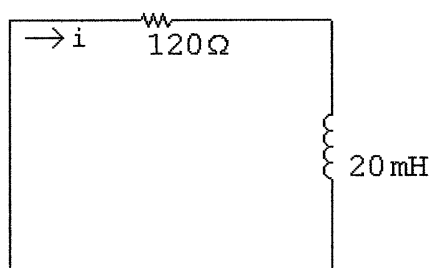[c]  $i(100 \mu\text{s}) = 4e^{-1} = 1.47 \text{ A}$  $100 \mu\text{s} \leq t < \infty$ :

$$\frac{1}{\tau} = \frac{R}{L} = \frac{120}{20} \times 10^3 = 6000$$

$$i = 1.47e^{-6000(t-100 \times 10^{-6})} \text{ A}$$

$$i(200 \mu\text{s}) = 1.47e^{-6000(100) \times 10^{-6}} = 1.47e^{-0.6} = 807.59 \text{ mA}$$

[d]  $0 \leq t \leq 100 \mu\text{s}$ :

$$i = 4e^{-10,000t}$$

$$v = L \frac{di}{dt} = (20 \times 10^{-3})(4)(-10^4)e^{-10^4 t} = -800e^{-10^4 t} \text{ V}$$

$$v(100^- \mu\text{s}) = -800e^{-10^4(100 \times 10^{-6})} = -800e^{-1} = -294.30 \text{ V}$$


[e]  $100 \mu\text{s} \leq t < \infty$ :

$$i = 1.47e^{-6000(t-100 \times 10^{-6})}$$


$$v = (20 \times 10^{-3})(1.47)(-6000)e^{-6000(t-100 \times 10^{-6})}$$

$$= -176.58e^{-6000(t-100 \times 10^{-6})} \text{ V}$$


$$v(100^+ \mu\text{s}) = -176.58 \text{ V}$$

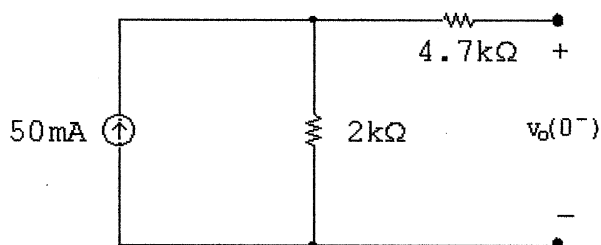P 7.76  $t < 0$ :

$$v_o(0^-) = (50)(2000) \times 10^{-3} = 100\text{ V} = v_o(0^+)$$

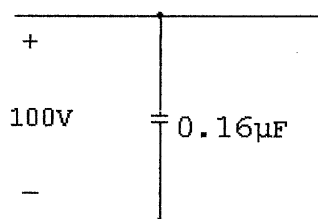 $0 \leq t \leq 250\text{ ms}$ :

$$\tau = \infty; \quad 1/\tau = 0; \quad v_o = 100e^{-0} = 100\text{ V}$$

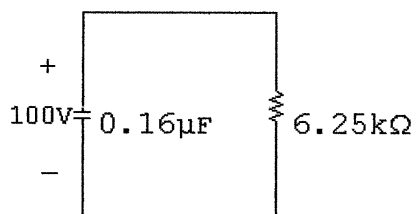 $250\text{ ms} \leq t < \infty$ :

$$\tau = (6.25)(0.16)10^{-3} = 1\text{ ms}; \quad 1/\tau = 1000; \quad v_o = 100e^{-1000(t-0.25)}\text{ V}$$


Summary:

$$v_o = 100\text{ V}, \quad 0 \leq t \leq 250\text{ ms}$$

$$v_o = 100e^{-1000(t-0.25)}\text{ V}, \quad 250\text{ ms} \leq t < \infty$$


P 7.77 Note that for  $t > 0$ ,  $v_o = (35/40)v_c$ , where  $v_c$  is the voltage across the 50 nF capacitor. Thus we will find  $v_c$  first.

$t < 0$

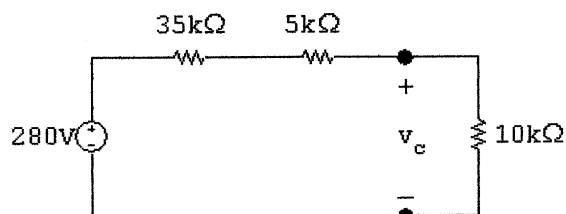

$$v_c(0) = \frac{280}{50}(10) = 56 \text{ V}$$

$0 \leq t \leq 400 \mu\text{s}$ :

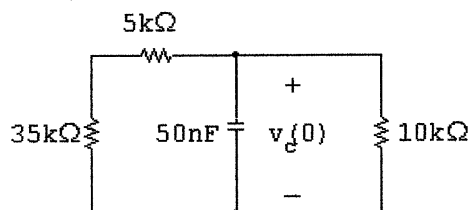


$$\tau = R_e C, \quad R_e = \frac{(10)(40)}{50} = 8 \text{ k}\Omega$$

$$\tau = (8 \times 10^3)(50 \times 10^{-9}) = 400 \mu\text{s}, \quad \frac{1}{\tau} = 2500$$

$$v_c = 56e^{-2500t} \text{ V}, \quad t \geq 0$$

$$v_c(400 \mu\text{s}) = 56e^{-1} = 20.60 \text{ V}$$

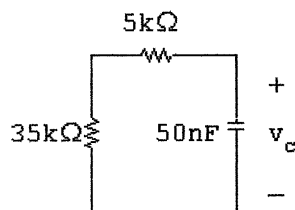
$400 \mu\text{s} \leq t \leq 1.4 \text{ ms}$ :



$$\tau = (40 \times 10^3)(50 \times 10^{-9}) = 2 \text{ ms}, \quad \frac{1}{\tau} = 500$$

$$v_c = 20.60e^{-500(t-400 \times 10^{-6})} \text{ V}$$

$$1.4 \text{ ms} \leq t < \infty:$$

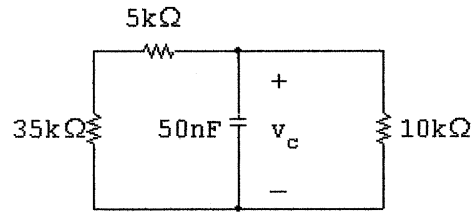

$$\tau = 400 \mu\text{s}, \quad \frac{1}{\tau} = 2500$$

$$v_c(1.4\text{ms}) = 20.60e^{-500(1400-400)10^{-6}} = 20.60e^{-0.5} = 12.50 \text{ V}$$

$$v_c = 12.50e^{-2500(t-1.4 \times 10^{-3})} \text{ V}$$

$$v_c(1.6\text{ms}) = 12.50e^{-2500(1.6-1.4)10^{-3}} = 12.50e^{-0.5} = 7.58 \text{ V}$$

$$v_o = (35/40)(7.58) = 6.63 \text{ V}$$

P 7.78  $w(0) = \frac{1}{2}(50 \times 10^{-9})(56)^2 = 78.4 \mu\text{J}$

$$0 \leq t \leq 400 \mu\text{s}:$$

$$v_c = 56e^{-2500t}; \quad v_c^2 = 3136e^{-5000t}$$

$$p_{10k} = 3136 \times 10^{-4}e^{-5000t}$$

$$\begin{aligned} w_{10k} &= \int_0^{400 \times 10^{-6}} 3136 \times 10^{-4} e^{-5000t} dt \\ &= 3136 \times 10^{-4} \left. \frac{e^{-5000t}}{-5000} \right|_0^{400 \times 10^{-6}} \\ &= -6272 \times 10^{-8} (e^{-2} - 1) = 54.23 \mu\text{J} \end{aligned}$$

$$1.4 \text{ ms} \leq t < \infty:$$

$$v_c = 12.50e^{-2500(t-1.4 \times 10^{-3})} \text{ V}; \quad v_c^2 = 156.13e^{-5000(t-1.4 \times 10^{-3})}$$

$$p_{10k} = 156.13 \times 10^{-4}e^{-5000(t-1.4 \times 10^{-3})}$$

$$\begin{aligned} w_{10k} &= \int_{1.4 \times 10^{-3}}^{\infty} 156.13 \times 10^{-4} e^{-5000(t-1.4 \times 10^{-3})} dt \\ &= 156.13 \times 10^{-4} \left. \frac{e^{-5000(t-1.4 \times 10^{-3})}}{-5000} \right|_{1.4 \times 10^{-3}}^{\infty} \\ &= -311.83 \times 10^{-8} (0 - 1) = 3.12 \mu\text{J} \end{aligned}$$

$$w_{10k} = 54.23 + 3.12 = 57.35 \mu\text{J}$$

$$\% = \frac{57.35}{78.4}(100) = 73.15\%$$

To check, find the energy dissipated in the  $40\text{ k}\Omega$  resistance:  
 $0 \leq t \leq 400 \mu\text{s}$ :

$$v_c = 56e^{-2500t}, \quad v_c^2 = 3136e^{-5000t}$$

$$p_{40k} = \frac{3136}{40} \times 10^{-3} e^{-5000t}$$

$$\begin{aligned} w_{40k} &= 784 \times 10^{-4} \frac{e^{-5000t}}{-5000} \bigg|_0^{400 \times 10^{-6}} \\ &= -156.8(10^{-7})(e^{-2} - 1) = 13.56 \text{ mJ} \end{aligned}$$

$400 \mu\text{s} \leq t \leq 1 \text{ ms}$ :

$$v_c = 20.60e^{-500(t-400 \times 10^{-6})}, \quad v_c^2 = 424.41e^{-1000(t-400 \times 10^{-6})}$$

$$\begin{aligned} w_{40k} &= 106.10 \times 10^{-4} \int_{400 \times 10^{-6}}^{10^{-3}} e^{-1000(t-400 \times 10^{-6})} dt \\ &= 106.10 \times 10^{-4} \frac{e^{-1000(t-400 \times 10^{-6})}}{-1000} \bigg|_{400 \times 10^{-6}}^{10^{-3}} \\ &= -106.10(10^{-7})(e^{-0.6} - 1) = 4.79 \text{ mJ} \end{aligned}$$

$1.4 \text{ ms} \leq t < \infty$ :


$$v_c = 12.49e^{-2500(t-1.4 \times 10^{-3})}, \quad v_c^2 = 156.13e^{-5000(t-1.4 \times 10^{-3})}$$

Note in this interval the energy dissipated in the  $40\text{ k}\Omega$  resistor will be  $1/4$ th that dissipated in the  $10\text{ k}\Omega$  resistor.

$$w_{40k} = \frac{1}{4}(3.12) = 0.78 \mu\text{J}$$

$$w_{40k} = 13.56 + 6.71 + 0.78 = 21.05 \mu\text{J}$$

$$w_{40k} + w_{10k} = 57.35 + 21.05 = 78.40 \mu\text{J}$$

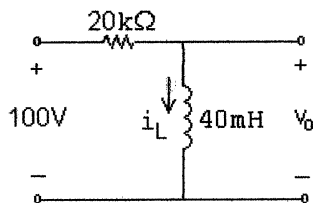P 7.79 [a]  $0 \leq t \leq 2 \mu\text{s}$ 


$$i_L(0) = 0; \quad i_L(\infty) = 5 \text{ mA}$$

$$\tau = \frac{L}{R} = \frac{0.04}{20,000} = 2 \mu\text{s}$$

$$i_L = 5 - 5e^{-500,000t} \text{ mA}, \quad 0 \leq t \leq 2 \mu\text{s}$$

$$v_o = (0.04)[(500,000)(0.005)e^{-500,000t}] = 100e^{-500,000t} \text{ V}, \quad 0^+ \leq t < 2 \mu\text{s}$$

$$2 \mu\text{s} \leq t < \infty$$

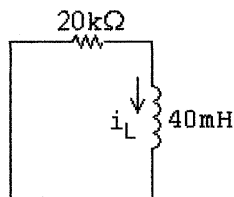

$$i_L(2 \mu\text{s}) = 5 - 5e^{-1} \approx 3.16 \text{ mA}$$

$$i_L(\infty) = 0; \quad \tau = 2 \mu\text{s}; \quad 1/\tau = 500,000$$

$$i_L = 0 + (3.16 - 0)e^{-500,000(t-2 \mu\text{s})} \text{ mA}$$


$$= 3.16e^{-500,000(t-2 \mu\text{s})} \text{ mA}, \quad 2 \mu\text{s} \leq t < \infty$$

$$v_o = L \frac{di_L}{dt} = (0.04)(3.16 \times 10^{-3})[-500,000e^{-500,000(t-2 \mu\text{s})}]$$

$$= (-5)(4)(3.16)e^{-500,000(t-2 \mu\text{s})}$$

$$= -63.21e^{-500,000(t-2 \mu\text{s})} \text{ V}, \quad 2 \mu\text{s} \leq t < \infty$$

[b]

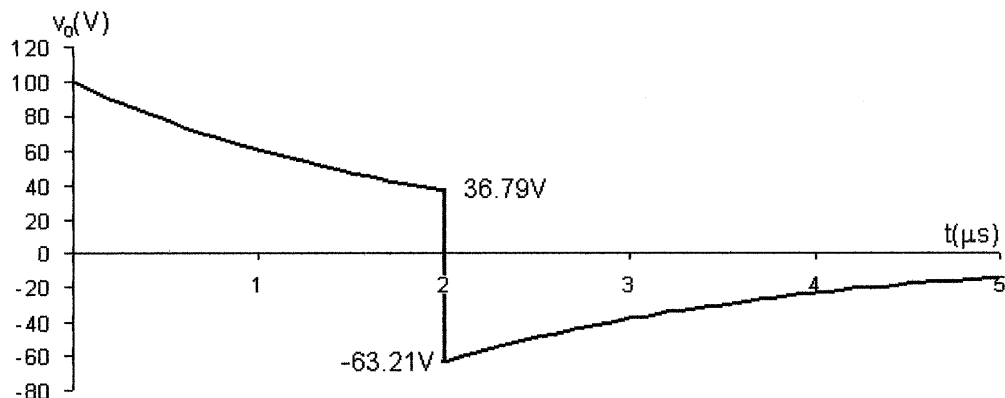

$$[c] \quad v_o(4 \mu s) = -23.25 \text{ V}$$

$$i_o = \frac{+23.25}{20,000} = 1.16 \text{ mA}$$

$$P \ 7.80 \quad [a] \quad i_o(0) = 0; \quad i_o(\infty) = 25 \text{ mA}$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{8000}{250} \times 10^3 = 32,000$$

$$i_o = (25 - 25e^{-32,000t}) \text{ mA}, \quad 0 \leq t \leq 50 \mu s$$

$$v_o = 0.25 \frac{di_o}{dt} = 200e^{-32,000t} \text{ V}, \quad 0 \leq t \leq 50 \mu s$$

$$50 \mu s \leq t < \infty:$$

$$i_o(50 \mu s) = 25 - 25e^{-1.6} = 19.95 \text{ mA}; \quad i_o(\infty) = 0$$

$$i_o = 19.95e^{-32,000(t-50 \times 10^{-6})} \text{ mA}$$

$$v_o = (0.25) \frac{di_o}{dt} = -159.62e^{-32,000(t-50 \mu s)}$$

$$\therefore t < 0: \quad v_o = 0$$

$$0 \leq t \leq 50 \mu s: \quad v_o = 200e^{-32,000t} \text{ V}$$

$$50 \mu s \leq t < \infty: \quad v_o = -159.62e^{-32,000(t-50 \mu s)}$$

$$[b] \quad v_o(50^- \mu s) = 200e^{-1.6} = 40.38 \text{ V}$$

$$v_o(50^+ \mu s) = -159.62 \text{ V}$$

$$[c] \quad i_o(50^- \mu s) = i_o(50^+ \mu s) = 19.95 \text{ mA}$$

$$P \ 7.81 \quad [a] \quad 0 \leq t \leq 6 \text{ ms:}$$

$$v_c(0^+) = 0; \quad v_c(\infty) = 40 \text{ V};$$

$$RC = 500 \times 10^3(0.02 \times 10^{-6}) = 10 \text{ ms}; \quad 1/RC = 100$$

$$v_c = 40 - 40e^{-100t}$$

$$v_o = 40 - 40 + 40e^{-100t} = 40e^{-100t} \text{ V}, \quad 0 \leq t \leq 6 \text{ ms}$$

$$6 \text{ ms} \leq t < \infty:$$

$$v_c(6 \text{ ms}) = 40 - 40e^{-0.6} = 18.05 \text{ V}$$

$$v_c(\infty) = 0 \text{ V}$$


$$\tau = 10 \text{ ms}; \quad 1/\tau = 100$$

$$v_c = 18.05e^{-100(t-0.006)} \text{ V}$$

$$v_o = -v_c = -18.05e^{-100(t-0.006)} \text{ V}, \quad t \geq 6 \text{ ms}$$



[b]

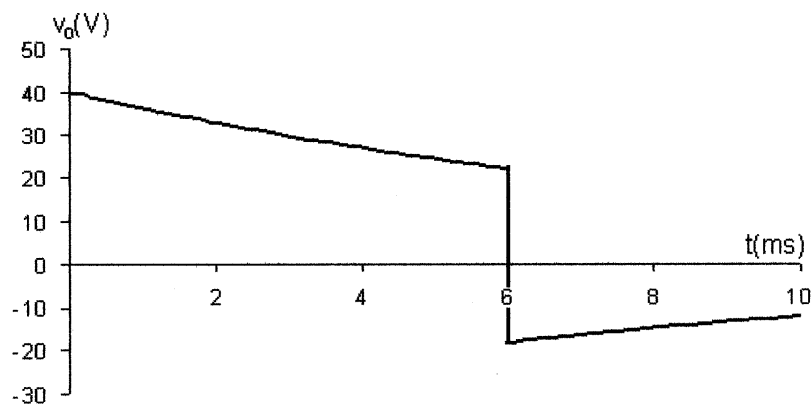P 7.82 [a]  $t < 0$ ;  $v_o = 0$  $0 \leq t \leq 10 \text{ ms}$ :

$$\tau = (50)(0.4) \times 10^{-3} = 20 \text{ ms}; \quad 1/\tau = 50$$

$$v_o = 40 - 40e^{-50t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$v_o(10 \text{ ms}) = 40(1 - e^{-0.5}) = 15.74 \text{ V}$$

 $10 \text{ ms} \leq t \leq 20 \text{ ms}$ :


$$v_o = -40 + 55.74e^{-50(t-0.01)} \text{ V}$$

$$v_o(20 \text{ ms}) = -40 + 55.74e^{-0.5} = -6.19 \text{ V}$$

 $20 \text{ ms} \leq t \leq \infty$ :

$$v_o = -6.19e^{-50(t-0.02)} \text{ V}$$

[b]

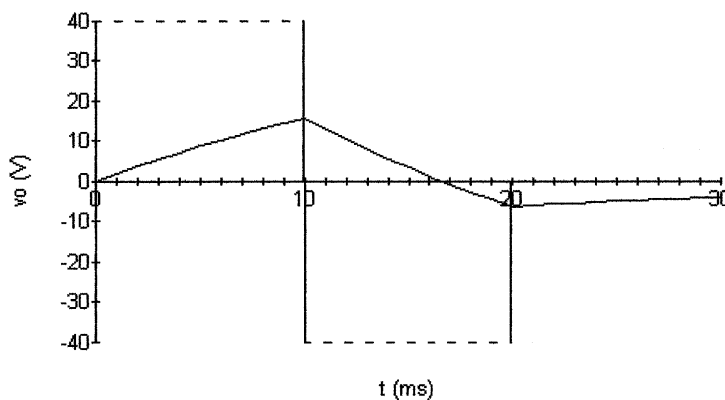[c]  $t \leq 0$ ;  $v_o = 0$  $0 \leq t \leq 10 \text{ ms}$ :

$$\tau = 10(0.4 \times 10^{-3}) = 4 \text{ ms}$$

$$v_o = 40 - 40e^{-250t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$v_o(10 \text{ ms}) = 40 - 40e^{-2.5} = 36.72 \text{ V}$$


$$10 \text{ ms} \leq t \leq 20 \text{ ms:}$$

$$v_o = -40 + 76.72e^{-250(t-0.01)} \text{ V}, \quad 10 \text{ ms} \leq t \leq 20 \text{ ms}$$

$$v_o(20 \text{ ms}) = -40 + 76.72e^{-2.5} = -33.7 \text{ V}$$

$$20 \text{ ms} \leq t \leq \infty:$$
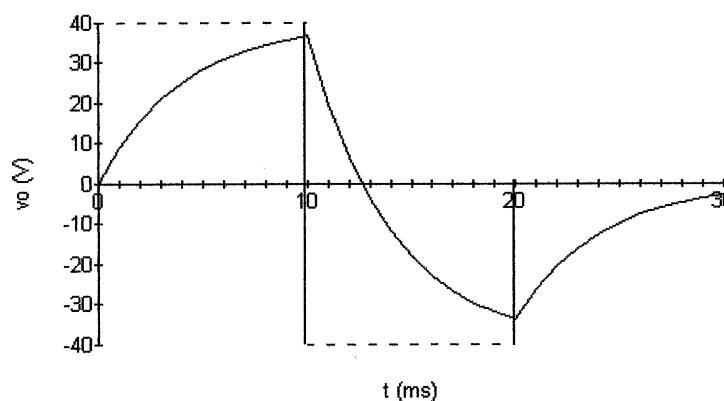
$$v_o = -33.7e^{-250(t-0.02)} \text{ V}, \quad 20 \text{ ms} \leq t \leq \infty$$



P 7.83 [a]  $\tau = RC = (8000)(100) \times 10^{-9} = 800 \mu\text{s}; \quad 1/\tau = 1250$

$$i_o = v_o = 0 \quad t < 0$$

$$i_o(0^+) = 20 \left( \frac{6}{8} \right) = 15 \text{ mA}, \quad i_o(\infty) = 0$$

$$\therefore i_o = 15e^{-1250t} \text{ mA} \quad 0^+ \leq t \leq 0.5^- \text{ ms}$$

$$i_{6k\Omega} = 20 - 15e^{-1250t} \text{ mA}$$

$$\therefore v_o = 120 - 90e^{-1250t} \text{ V} \quad 0^+ \leq t \leq 0.5^- \text{ ms}$$

$$v_c = v_o - 2 \times 10^3 i_o = 120 - 120e^{-1250t} \text{ V} \quad 0 \leq t \leq 0.5 \text{ ms}$$

$$v_c(0.5 \text{ ms}) = 120 - 120e^{-0.625} = 55.77 \text{ V}$$

$$\therefore i_o(0.5^+ \text{ ms}) = \frac{-55.77}{8} = -6.97 \text{ mA}$$

$$i_o(\infty) = 0$$

$$i_o = -6.97e^{-1250(t-500\mu\text{s})} \text{ mA}, \quad 0.5^+ \text{ ms} \leq t < \infty$$

$$v_o = -6000i_o = 41.83e^{-1250(t-500\mu\text{s})} \text{ V} \quad 0.5^+ \text{ ms} \leq t < \infty$$

Summary part (a)

$$i_o = 0 \quad t < 0$$

$$i_o = 15e^{-1250t} \text{ mA} \quad (0^+ \leq t \leq 0.5^- \text{ ms})$$

$$i_o = -6.97e^{-1250(t-500\mu\text{s})} \text{ mA} \quad 0.5^+ \text{ ms} \leq t < \infty$$

$$v_o = 0 \quad t < 0$$

$$v_o = 120 - 90e^{-1250t} \text{ V}, \quad 0 \leq t \leq 0.5^- \text{ ms}$$

$$v_o = 41.83e^{-1250(t-500\mu\text{s})} \text{ V}, \quad 0.5^+ \text{ ms} \leq t < \infty$$

[b]  $i_o(0^-) = 0$

$$i_o(0^+) = 15 \text{ mA}$$

$$i_o(0.5^- \text{ ms}) = 15e^{-0.625} = 8.03 \text{ mA}$$

$$i_o(0.5^+ \text{ ms}) = -6.97 \text{ mA}$$


[c]  $v_o(0^-) = 0$

$$v_o(0^+) = 30 \text{ V}$$


$$v_o(0.5^- \text{ ms}) = 120 - 90e^{-0.625} = 71.83 \text{ V}$$

$$v_o(0.5^+ \text{ ms}) = 41.83$$


[d]

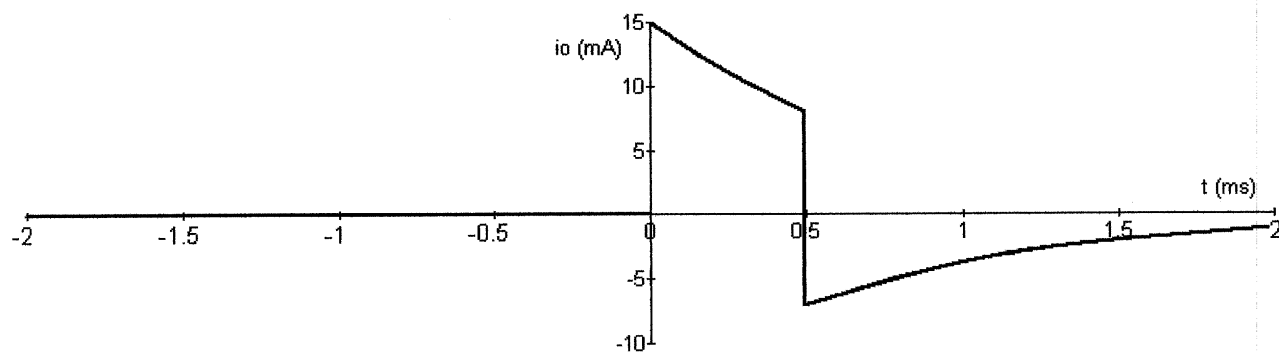

[e]

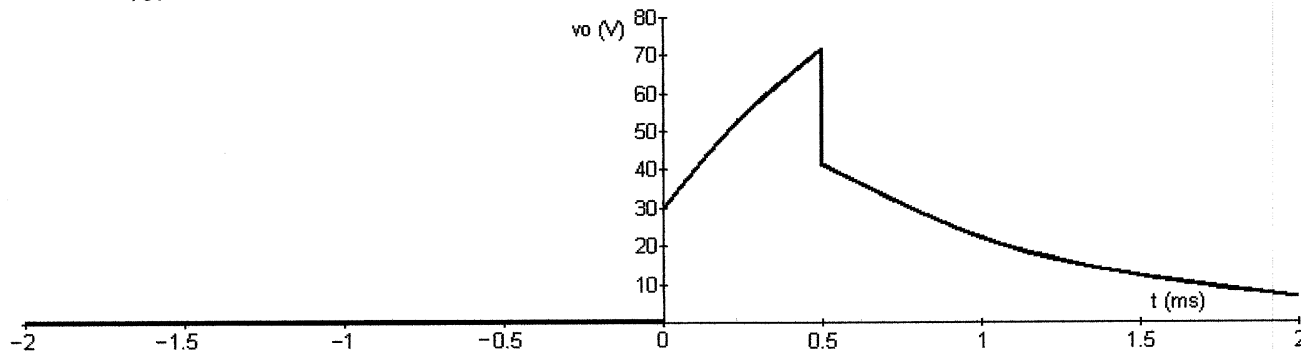


P 7.84

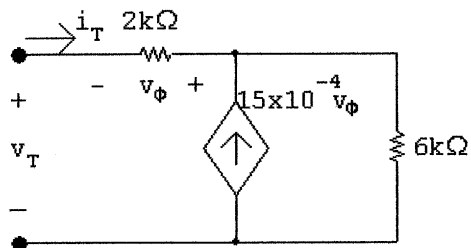

$$v_T = 2000i_T + 6000(i_T + 15 \times 10^{-4}v_\phi) = 8000i_T + 9v_\phi$$

$$= 8000i_T + 9(-2000i_T)$$


$$\frac{v_T}{i_T} = -10,000$$

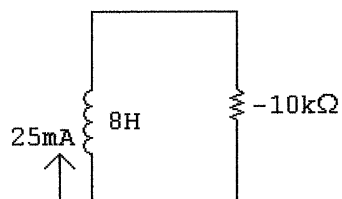

$$\tau = \frac{8}{-10} \times 10^{-3} = -0.8 \text{ ms}; \quad 1/\tau = -1250$$

$$i = 25e^{1250t} \text{ mA}$$

$$\therefore 25e^{1250t} \times 10^{-3} = 12; \quad t = \frac{\ln 480}{1250} = 4.94 \text{ ms}$$

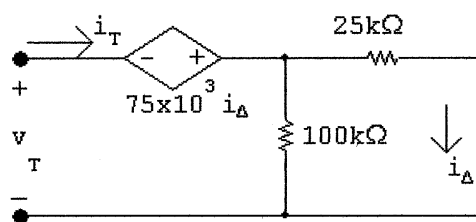P 7.85  $t > 0$ :

$$v_T = -75 \times 10^3 i_\Delta + 20 \times 10^3 i_T$$

$$i_\Delta = \frac{100}{125} i_T = 0.8 i_T$$

$$\therefore v_T = -60 \times 10^3 i_T + 20 \times 10^3 i_T$$


$$R_{Th} = \frac{v_T}{i_T} = -40 \text{ k}\Omega$$

$$\tau = RC = -40 \times 10^3 (0.025) \times 10^{-6} = -10^{-3}$$

$$v_c = 25e^{1000t} \text{ V}; \quad 25e^{1000t} = 50,000$$

$$1000t = \ln 2000 \quad \therefore \quad t = 7.6 \text{ ms}$$

P 7.86 [a]

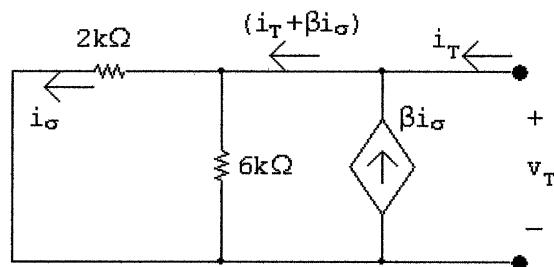

$$v_T = 2000i_\sigma$$

$$i_\sigma = \frac{6}{8}(i_T + \beta i_\sigma) = 0.75i_T + 0.75\beta i_\sigma$$


$$i_\sigma(1 - 0.75\beta) = 0.75i_T$$

$$i_\sigma = \frac{0.75i_T}{1 - 0.75\beta}; \quad 2000i_\sigma = \frac{1500i_T}{(1 - 0.75\beta)}$$

$$R_{Th} = \frac{v_T}{i_T} = \frac{1500}{1 - 0.75\beta} = -3000$$


$$1 - 0.75\beta = -0.5 \quad \therefore \quad \beta = 2$$

[b] Find  $V_{Th}$ ;

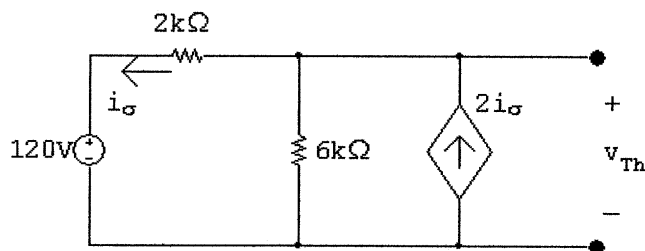

$$\frac{V_{Th} - 120}{2000} + \frac{V_{Th}}{6000} - 2 \frac{(V_{Th} - 120)}{2000} = 0$$

$$V_{Th} = 180 \text{ V}$$

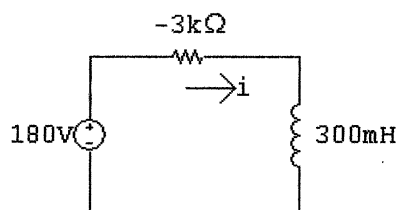

$$180 = -3000i + 0.3 \frac{di}{dt}$$

$$\frac{di}{dt} = 600 + 10,000i = 10,000(i + 0.06)$$

$$\frac{di}{i + 0.06} = 10,000 dt$$

$$\int_0^i \frac{dx}{x + 0.06} = \int_0^t 10,000 dx$$


$$\therefore i = -60 + 60e^{10,000t} \text{ mA}$$

$$\frac{di}{dt} = (60 \times 10^{-3})(10,000)e^{10,000t} = 600e^{10,000t}$$

$$v = 0.3 \frac{di}{dt} = 180e^{10,000t} = 36,000; \quad e^{10,000t} = 200$$

$$\therefore t = \frac{\ln 200}{10,000} = 529.83 \mu\text{s}$$

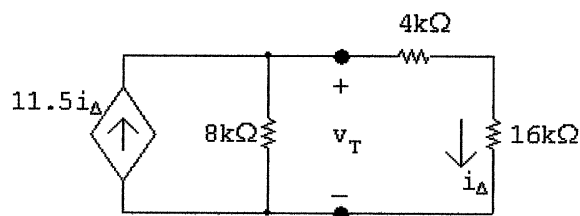P 7.87 Find the Thévenin equivalent with respect to the terminals of the capacitor.  
 $R_{Th}$  calculation:




$$i_T = \frac{v_T}{8000} + \frac{v_T}{20,000} - 11.5 \frac{v_T}{20,000}$$

$$\frac{i_T}{v_T} = \frac{2.5 + 1 - 11.5}{20,000} = \frac{-8}{20,000}$$

$$\therefore \frac{v_T}{i_T} = \frac{-20,000}{8} = -2500 \Omega$$

Open circuit voltage calculation:

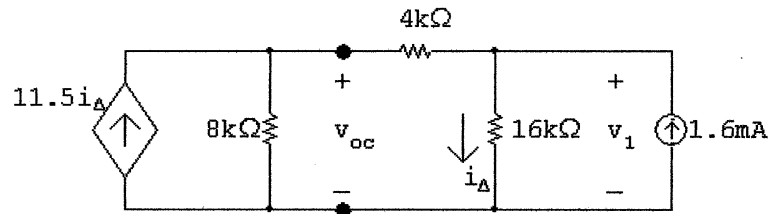


$$\frac{v_{oc}}{8000} + \frac{v_{oc} - v_1}{4000} - 11.5i_{\Delta} = 0$$

$$\frac{v_1 - v_{oc}}{4000} + \frac{v_1}{16,000} - 1.6 \times 10^{-3} = 0$$

$$i_{\Delta} = \frac{v_1}{16,000}$$

Solving,  $v_{oc} = -12.4 \text{ V}$

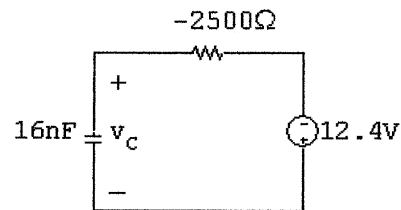


$$v_c(0) = 0; \quad v_c(\infty) = -12.4 \text{ V}$$

$$\tau = RC = (-2500)(16 \times 10^{-9}) = -40 \times 10^{-6}; \quad \frac{1}{\tau} = -25,000$$

$$v_c = -12.4 + 12.4e^{25,000t} = 930$$

$$e^{25,000t} = 76; \quad 25,000t = \ln 76; \quad t = 173.23 \mu\text{s}$$

P 7.88 [a]

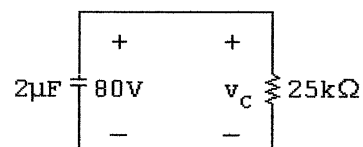

$$\tau = (25)(2) \times 10^{-3} = 50 \text{ ms}; \quad 1/\tau = 20$$

$$v_c(0^+) = 80 \text{ V}; \quad v_c(\infty) = 0$$


$$v_c = 80e^{-20t} \text{ V}$$

$$\therefore 80e^{-20t} = 5; \quad e^{20t} = 16; \quad t = \frac{\ln 16}{20} = 138.63 \text{ ms}$$

[b]  $0^+ < t < 138.63 \text{ ms}$ :

$$i = (2 \times 10^{-6})(-1600e^{-20t}) = -3.2e^{-20t} \text{ mA}$$

$t \geq 138.63^+ \text{ ms}$ :

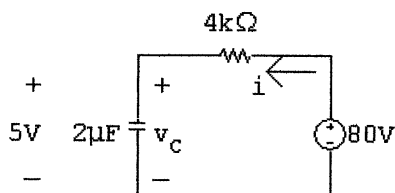

$$\tau = (2)(4) \times 10^{-3} = 8 \text{ ms}; \quad 1/\tau = 125$$

$$v_c(138.63^+ \text{ ms}) = 5 \text{ V}; \quad v_c(\infty) = 80 \text{ V}$$

$$v_c = 80 - 75e^{-125(t-0.13863)} \text{ V}, \quad t \geq 138.63 \text{ ms}$$

$$i = 2 \times 10^{-6}(9375)e^{-125(t-0.13863)} \\ = 18.75e^{-125(t-0.13863)} \text{ mA}, \quad t \geq 138.63^+ \text{ ms}$$

[c]  $80 - 75e^{-125\Delta t} = 0.85(80) = 68$

$$80 - 68 = 75e^{-125\Delta t} = 12$$

$$e^{125\Delta t} = 6.25; \quad \Delta t = \frac{\ln 6.25}{125} \cong 14.66 \text{ ms}$$

P 7.89  $\frac{0 - 15}{R} - 60 \times 10^{-9} \frac{dv_o}{dt} = 0$

$$\therefore v_o = \frac{-250 \times 10^6 t}{R}$$

$$\therefore R = \frac{(-250 \times 10^6)(3 \times 10^{-3})}{-15} = 50 \times 10^3 = 50 \text{ k}\Omega$$

P 7.90  $\frac{0 - 15}{R} - C \frac{dv_o}{dt} = 0; \quad dv_o = \frac{-15}{RC} dt$

$$v_o - v_o(0) = \frac{-15}{RC} t$$



$$v_o = \frac{-15}{RC}t + v_o(0) = \frac{-250 \times 10^6 t}{R} + 5 = -15$$

$$\therefore R = \frac{250 \times 10^6 (8 \times 10^{-3})}{20} = 100 \text{ k}\Omega$$

P 7.91 [a]  $\frac{C dv_p}{dt} + \frac{v_p - v_b}{R} = 0$ ; therefore  $\frac{dv_p}{dt} + \frac{1}{RC}v_p = \frac{v_b}{RC}$

$$\frac{v_n - v_a}{R} + C \frac{d(v_n - v_o)}{dt} = 0;$$

$$\text{therefore } \frac{dv_o}{dt} = \frac{dv_n}{dt} + \frac{v_n}{RC} - \frac{v_a}{RC}$$

But  $v_n = v_p$

$$\text{Therefore } \frac{dv_n}{dt} + \frac{v_n}{RC} = \frac{dv_p}{dt} + \frac{v_p}{RC} = \frac{v_b}{RC}$$

$$\text{Therefore } \frac{dv_o}{dt} = \frac{1}{RC}(v_b - v_a); \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy$$

[b] The output is the integral of the difference between  $v_b$  and  $v_a$  and then scaled by a factor of  $1/RC$ .

[c]  $v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dx$

$$RC = (40) \times 10^3 (25) \times 10^{-9} = 1 \text{ ms}$$

$$v_b - v_a = 50 \text{ mV}$$

$$v_o = 50 \int_0^t dx = 50t; \quad 50t_{\text{sat}} = 12; \quad t_{\text{sat}} = 240 \text{ ms}$$

P 7.92  $v_2 = \frac{15(20)}{(50)} = 6 \text{ V}$

$$\frac{6+4}{50,000} + C \frac{d}{dt}(6 - v_o) = 0$$

$$\therefore \frac{dv_o}{dt} = \frac{10 \times 10^6}{50,000(0.5)} = 400$$

$$dv_o = 400 dt; \quad v_o = 400t + v_o(0)$$

$$v_o(0) = 6 - 16 = -10 \text{ V}$$

$$\therefore v_o = 400t - 10 \text{ V}$$

$$0 = 400t_o - 10$$

$$t_o = \frac{10}{400} = 25 \text{ ms}$$

$$\text{P 7.93} \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy + v_o(0)$$

$$RC = (40 \times 10^3)(12.5 \times 10^{-9}) = 500 \times 10^{-6} = 0.5 \text{ ms}$$

$$\frac{1}{RC} = 2000; \quad v_b - v_a = 10 - (-5) = 15 \text{ mV}$$

$$v_o(0) = 15 - 45 = -30 \text{ mV}$$

$$v_o = (2000)(15) \times 10^{-3}t - 30 \times 10^{-3} = (30,000t - 30) \text{ mV}$$

$$v_2 = 10 + (15 - 10)e^{-2000t} \text{ mV} = [10 + 5e^{-2000t}] \text{ mV}$$

$$v_f = v_o - v_p = (30,000t - 40 - 5e^{-2000t}) \text{ mV}$$

$$\text{P 7.94} \quad [\text{a}] \quad RC = 40(50) \times 10^{-6} = 2 \text{ ms}; \quad \frac{1}{RC} = 500; \quad v_o = 0, \quad t < 0$$

$$[\text{b}] \quad 0 \leq t \leq 50 \text{ ms} :$$

$$v_o = -500 \int_0^t -0.50 dx = 250t \text{ V}$$

$$[\text{c}] \quad 50 \text{ ms} \leq t \leq 100 \text{ ms};$$


$$v_o(0.05) = 250(0.05) = 12.5 \text{ V}$$

$$v_o(t) = -500 \int_{0.05}^t 0.50 dx + 12.5 = -250(t - 0.05) + 12.5 = -250t + 25 \text{ V}$$

$$[\text{d}] \quad 100 \text{ ms} \leq t \leq \infty :$$

$$v_o(0.1) = -25 + 25 = 0 \text{ V}$$

$$v_o(t) = 0 \text{ V}$$

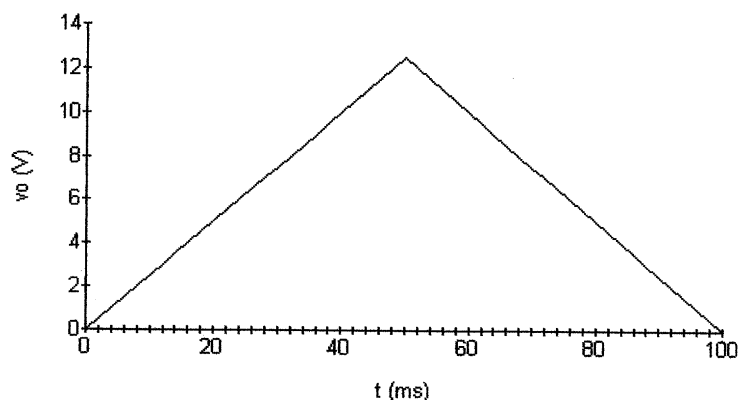

P 7.95 Write a KCL equation at the inverting input to the op amp, where the voltage is 0:

$$\frac{0 - v_g}{R_i} + \frac{0 - v_o}{R_f} + C_f \frac{d}{dt}(0 - v_o) = 0$$

$$\therefore \frac{dv_o}{dt} + \frac{1}{R_f C_f} v_o = -\frac{v_g}{R_i}$$

Note that this first-order differential equation is in the same form as Eq. 7.50 if  $I_s = -v_g/R_i$ . Therefore, its solution is the same as Eq. 7.51:

$$v_o = \frac{-v_g R_f}{R_i} + \left( V_o - \frac{-v_g R_f}{R_i} \right) e^{-t/R_f C_f}$$

$$[a] \quad v_o = 0, \quad t < 0$$

$$[b] \quad R_f C_f = (4 \times 10^6)(50 \times 10^{-9}) = 0.2; \quad \frac{1}{R_f C_f} = 5$$

$$\frac{-v_g R_f}{R_i} = \frac{-(-0.5)(4 \times 10^6)}{40,000} = 50$$

$$V_o = v_o(0) = 0$$

$$\therefore v_o = 50 + (0 - 50)e^{-5t} = 50(1 - e^{-5t}) \text{ V}, \quad 0 \leq t \leq 50 \text{ ms}$$

$$[c] \quad \frac{1}{R_f C_f} = 5$$

$$\frac{-v_g R_f}{R_i} = \frac{-(0.5)(4 \times 10^6)}{40,000} = -50$$

$$V_o = v_o(0.05) = 50(1 - e^{-0.25}) \cong 11.06 \text{ V}$$


$$\begin{aligned} \therefore v_o &= -50 + [11.06 - (-50)]e^{-5(t-0.05)} \\ &= 61.06e^{-5(t-0.05)} - 50 \text{ V}, \quad 50 \text{ ms} \leq t \leq 100 \text{ ms} \end{aligned}$$

$$[d] \quad \frac{1}{R_f C_f} = 5$$

$$\frac{-v_g R_f}{R_i} = 0$$

$$V_o = v_o(0.10) = 61.06e^{-0.25} - 50 \cong -2.45 \text{ V}$$
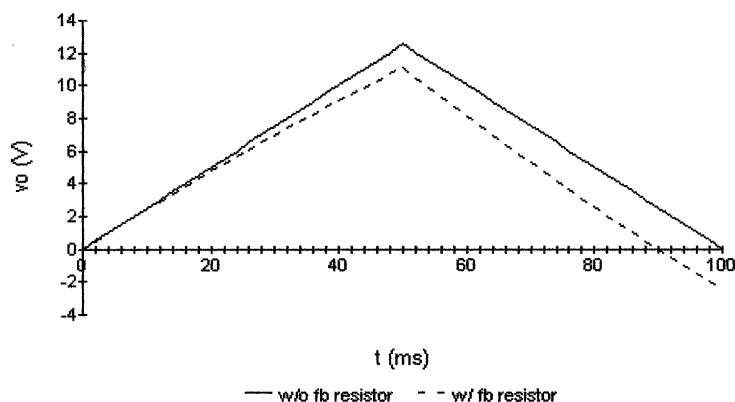
$$v_o = 0 + (-2.45 - 0)e^{-5(t-0.1)} = -2.45e^{-5(t-0.1)} \text{ V}, \quad 100 \text{ ms} \leq t \leq \infty$$



P 7.96 [a]  $RC = (200 \times 10^3)(25 \times 10^{-9}) = 5 \times 10^{-3}$ ;  $\frac{1}{RC} = 200$

$0 \leq t \leq 5 \mu\text{s}$ :

$$v_g = 0.6 \times 10^6 t$$

$$v_o = -200 \int_0^t 0.6 \times 10^6 x \, dx + 0$$

$$= -12 \times 10^7 \frac{x^2}{2} \Big|_0^t = -6 \times 10^7 t^2$$

$$v_o(5 \mu\text{s}) = -6 \times 10^7 (5 \times 10^{-6})^2 = -1.5 \times 10^{-3} \text{ V}$$

$5 \mu\text{s} \leq t \leq 15 \mu\text{s}$ :

$$v_g = 6 - 0.6 \times 10^6 t$$

$$v_o = -200 \int_{5 \times 10^{-6}}^t (6 - 0.6 \times 10^6 x) \, dx - 1.5 \times 10^{-3}$$

$$= - \left[ 1200x \Big|_{5 \times 10^{-6}}^t + 12 \times 10^7 \frac{x^2}{2} \Big|_{5 \times 10^{-6}}^t \right] - 1.5 \times 10^{-3}$$

$$= -1200t + 6 \times 10^{-3} + 6 \times 10^7 t^2 - 1.5 \times 10^{-3} - 1.5 \times 10^{-3}$$

$$= 6 \times 10^7 t^2 - 1200t + 3 \times 10^{-3}$$

$$v_o(15 \mu\text{s}) = 6 \times 10^7 (15 \times 10^{-6})^2 - 1200(15 \times 10^{-6}) + 3 \times 10^{-3} \\ = -1.5 \times 10^{-3}$$

$15 \mu\text{s} \leq t \leq 20 \mu\text{s}$ :

$$v_g = -12 + 0.6 \times 10^6 t$$

$$v_o = -200 \int_{15 \times 10^{-6}}^t (-12 + 0.6 \times 10^6 x) \, dx - 1.5 \times 10^{-3}$$


$$= - \left[ 2400x \Big|_{15 \times 10^{-6}}^t - 12 \times 10^7 \frac{x^2}{2} \Big|_{15 \times 10^{-6}}^t \right] - 1.5 \times 10^{-3}$$

$$= 2400t - 36 \times 10^{-3} - 6 \times 10^7 t^2 + 13.5 \times 10^{-3} - 1.5 \times 10^{-3}$$

$$= -6 \times 10^7 t^2 + 2400t - 24 \times 10^{-3}$$


$$v_o(20\mu s) = -6 \times 10^7(20 \times 10^{-6})^2 + 2400(20 \times 10^{-6}) - 24 \times 10^{-3} = 0$$

[b]

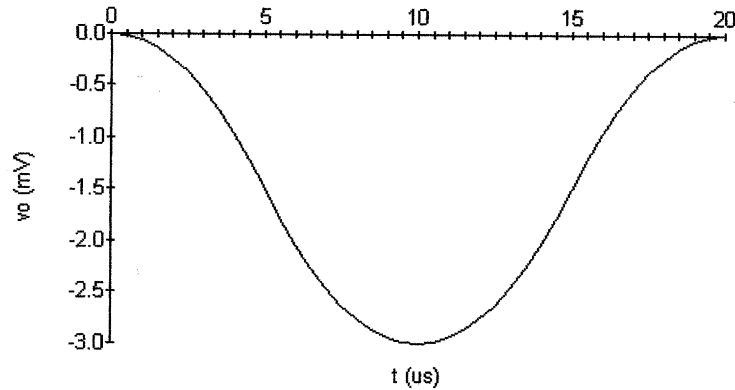


- [c] The output voltage will also repeat. This follows from the observation that at  $t = 20\mu s$  the output voltage is zero, hence there is no energy stored in the capacitor. This means the circuit is in the same state at  $t = 20\mu s$  as it was at  $t = 0$ , thus as  $v_g$  repeats itself, so will  $v_o$ .

P 7.97 [a] While  $T_2$  has been ON,  $C_2$  is charged to  $V_{CC}$ , positive on the left terminal. At the instant  $T_1$  turns ON the capacitor  $C_2$  is connected across  $b_2 - e_2$ , thus  $v_{be2} = -V_{CC}$ . This negative voltage snaps  $T_2$  OFF. Now the polarity of the voltage on  $C_2$  starts to reverse, that is, the right-hand terminal of  $C_2$  starts to charge toward  $+V_{CC}$ . At the same time,  $C_1$  is charging toward  $V_{CC}$ , positive on the right. At the instant the charge on  $C_2$  reaches zero,  $v_{be2}$  is zero,  $T_2$  turns ON. This makes  $v_{be1} = -V_{CC}$  and  $T_1$  snaps OFF. Now the capacitors  $C_1$  and  $C_2$  start to charge with the polarities to turn  $T_1$  ON and  $T_2$  OFF. This switching action repeats itself over and over as long as the circuit is energized. At the instant  $T_1$  turns ON, the voltage controlling the state of  $T_2$  is governed by the following circuit:

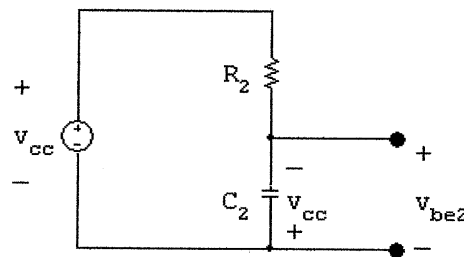

It follows that  $v_{be2} = V_{CC} - 2V_{CC}e^{-t/R_2C_2}$ .

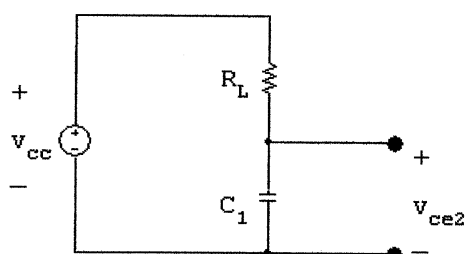- [b] While  $T_2$  is OFF and  $T_1$  is ON, the output voltage  $v_{ce2}$  is the same as the voltage across  $C_1$ , thus




It follows that  $v_{ce2} = V_{CC} - V_{CC}e^{-t/R_L C_1}$ .

- [c]  $T_2$  will be OFF until  $v_{be2}$  reaches zero. As soon as  $v_{be2}$  is zero,  $i_{b2}$  will become positive and turn  $T_2$  ON.  $v_{be2} = 0$  when  $V_{CC} - 2V_{CC}e^{-t/R_2 C_2} = 0$ , or when  $t = R_2 C_2 \ln 2$ .

- [d] When  $t = R_2 C_2 \ln 2$ , we have

$$v_{ce2} = V_{CC} - V_{CC}e^{-[(R_2 C_2 \ln 2)/(R_L C_1)]} = V_{CC} - V_{CC}e^{-10 \ln 2} \cong V_{CC}$$

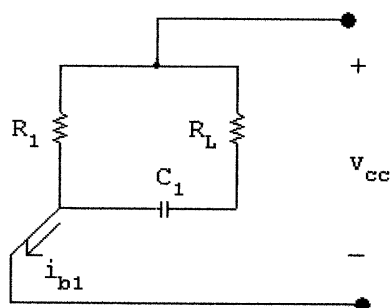- [e] Before  $T_1$  turns ON,  $i_{b1}$  is zero. At the instant  $T_1$  turns ON, we have




$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L}e^{-t/R_L C_1}$$

- [f] At the instant  $T_2$  turns back ON,  $t = R_2 C_2 \ln 2$ ; therefore


$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L}e^{-10 \ln 2} \cong \frac{V_{CC}}{R_1}$$

When  $T_2$  turns OFF,  $i_{b1}$  drops to zero instantaneously.

- [g]

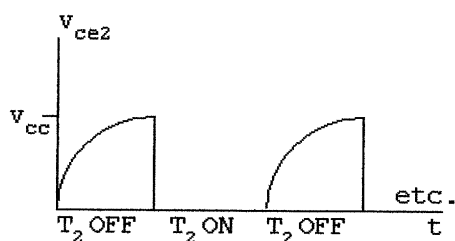

[h]

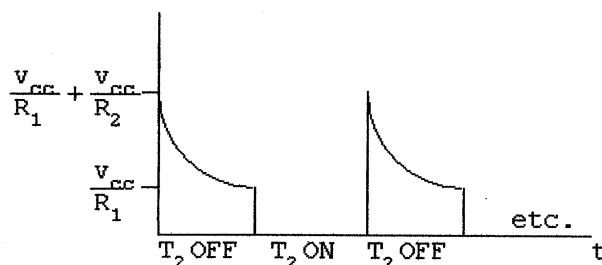

P 7.98 [a]  $t_{\text{OFF}2} = R_2 C_2 \ln 2 = 18 \times 10^3 (2 \times 10^{-9}) \ln 2 \cong 25 \mu\text{s}$

[b]  $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 25 \mu\text{s}$

[c]  $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 25 \mu\text{s}$

[d]  $t_{\text{ON}1} = R_2 C_2 \ln 2 \cong 25 \mu\text{s}$

[e]  $i_{b1} = \frac{9}{3} + \frac{9}{18} = 3.5 \text{ mA}$

[f]  $i_{b1} = \frac{9}{18} + \frac{9}{3} e^{-25/6} \cong 0.5465 \text{ mA}$

[g]  $v_{ce2} = 9 - 9e^{-25/6} \cong 8.86 \text{ V}$

P 7.99 [a]  $t_{\text{OFF}2} = R_2 C_2 \ln 2 = (18 \times 10^3)(2.8 \times 10^{-9}) \ln 2 \cong 35 \mu\text{s}$

[b]  $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 37.4 \mu\text{s}$

[c]  $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 37.4 \mu\text{s}$

[d]  $t_{\text{ON}1} = R_2 C_2 \ln 2 = 35 \mu\text{s}$

[e]  $i_{b1} = 3.5 \text{ mA}$

[f]  $i_{b1} = \frac{9}{18} + 3e^{-35/9} \cong 0.561 \text{ mA}$

[g]  $v_{ce2} = 9 - 9e^{-35/9} \cong 8.81 \text{ V}$

Note in this circuit  $T_2$  is OFF  $35 \mu\text{s}$  and ON  $37.4 \mu\text{s}$  of every cycle, whereas  $T_1$  is ON  $35 \mu\text{s}$  and OFF  $37.4 \mu\text{s}$  every cycle.

P 7.100 If  $R_1 = R_2 = 50R_L = 100 \text{ k}\Omega$ , then

$$C_1 = \frac{48 \times 10^{-6}}{100 \times 10^3 \ln 2} = 692.49 \text{ pF}; \quad C_2 = \frac{36 \times 10^{-6}}{100 \times 10^3 \ln 2} = 519.37 \text{ pF}$$

If  $R_1 = R_2 = 6R_L = 12 \text{ k}\Omega$ , then

$$C_1 = \frac{48 \times 10^{-6}}{12 \times 10^3 \ln 2} = 5.77 \text{ nF}; \quad C_2 = \frac{36 \times 10^{-6}}{12 \times 10^3 \ln 2} = 4.33 \text{ nF}$$


Therefore  $692.49 \text{ pF} \leq C_1 \leq 5.77 \text{ nF}$  and  $519.37 \text{ pF} \leq C_2 \leq 4.33 \text{ nF}$

- P 7.101 [a]  $T_2$  is normally ON since its base current  $i_{b2}$  is greater than zero, i.e.,  
 $i_{b2} = V_{CC}/R$  when  $T_2$  is ON. When  $T_2$  is ON,  $v_{ce2} = 0$ , therefore  $i_{b1} = 0$ .  
 When  $i_{b1} = 0$ ,  $T_1$  is OFF. When  $T_1$  is OFF and  $T_2$  is ON, the capacitor  $C$  is charged to  $V_{CC}$ , positive at the left terminal. This is a stable state; there is nothing to disturb this condition if the circuit is left to itself.
- [b] When  $S$  is closed momentarily,  $v_{be2}$  is changed to  $-V_{CC}$  and  $T_2$  snaps OFF. The instant  $T_2$  turns OFF,  $v_{ce2}$  jumps to  $V_{CC}R_1/(R_1 + R_L)$  and  $i_{b1}$  jumps to  $V_{CC}/(R_1 + R_L)$ , which turns  $T_1$  ON.
- [c] As soon as  $T_1$  turns ON, the charge on  $C$  starts to reverse polarity. Since  $v_{be2}$  is the same as the voltage across  $C$ , it starts to increase from  $-V_{CC}$  toward  $+V_{CC}$ . However,  $T_2$  turns ON as soon as  $v_{be2} = 0$ . The equation for  $v_{be2}$  is  $v_{be2} = V_{CC} - 2V_{CC}e^{-t/RC}$ .  $v_{be2} = 0$  when  $t = RC \ln 2$ , therefore  $T_2$  stays OFF for  $RC \ln 2$  seconds.

- P 7.102 [a] For  $t < 0$ ,  $v_{ce2} = 0$ . When the switch is momentarily closed,  $v_{ce2}$  jumps to

$$v_{ce2} = \left( \frac{V_{CC}}{R_1 + R_L} \right) R_1 = \frac{6(5)}{25} = 1.2 \text{ V}$$

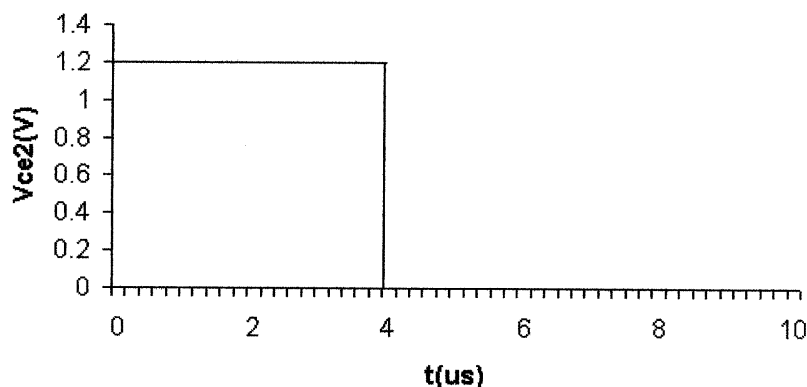$T_2$  remains open for  $(23,083)(250) \times 10^{-12} \ln 2 \cong 4 \mu\text{s}$ .




[b]  $i_{b2} = \frac{V_{CC}}{R} = 259.93 \mu\text{A}, \quad -5 \leq t \leq 0 \mu\text{s}$

$$i_{b2} = 0, \quad 0 < t < RC \ln 2$$


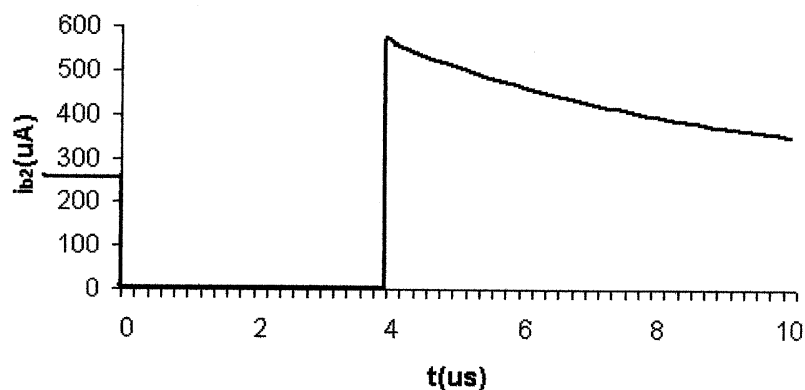
$$\begin{aligned}
 i_{b2} &= \frac{V_{CC}}{R} + \frac{V_{CC}}{R_L} e^{-(t-RC \ln 2)/R_L C} \\
 &= 259.93 + 300e^{-0.2 \times 10^6 (t-4 \times 10^{-6})} \mu\text{A}, \quad RC \ln 2 < t
 \end{aligned}$$



P 7.103 [a] We want the lamp to be in its nonconducting state for no more than 10 s, the value of  $t_o$ :

$$10 = R(10 \times 10^{-6}) \ln \frac{1-6}{4-6} \quad \text{and} \quad R = 1.091 \text{ M}\Omega$$

[b] When the lamp is conducting

$$V_{Th} = \frac{20 \times 10^3}{20 \times 10^3 + 1.091 \times 10^6} (6) = 0.108 \text{ V}$$


$$R_{Th} = 20 \text{ k}\Omega \parallel 1.091 \text{ M}\Omega = 19,640 \Omega$$

So,

$$(t_c - t_o) = (19,640)(10 \times 10^{-6}) \ln \frac{4 - 0.108}{1 - 0.108} = 0.289 \text{ s}$$

The flash lasts for 0.289 s.

P 7.104 [a] At  $t = 0$  we have

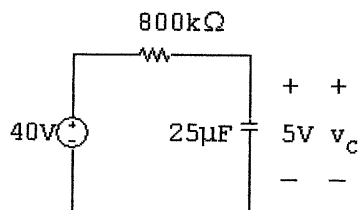

$$\tau = (800)(25) \times 10^{-3} = 20 \text{ sec}; \quad 1/\tau = 0.05$$


$$v_c(\infty) = 40 \text{ V}; \quad v_c(0) = 5 \text{ V}$$

$$v_c = 40 - 35e^{-0.05t} \text{ V}, \quad 0 \leq t \leq t_o$$


$$40 - 35e^{-0.05t_o} = 15; \quad \therefore e^{0.05t_o} = 1.4$$

$$t_o = 20 \ln 1.4 \text{ s} = 6.73 \text{ s}$$

At  $t = t_o$  we have

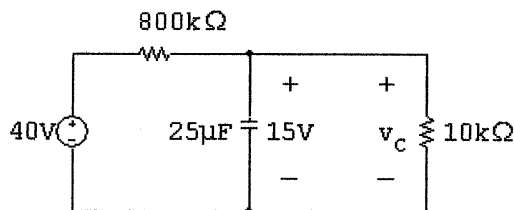

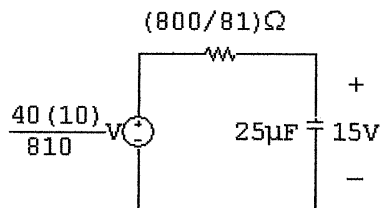The Thévenin equivalent with respect to the capacitor is



$$\tau = \left(\frac{800}{81}\right)(25) \times 10^{-3} = \frac{20}{81} \text{ s}; \quad \frac{1}{\tau} = \frac{81}{20} = 4.05$$

$$v_c(t_o) = 15 \text{ V}; \quad v_c(\infty) = \frac{40}{81} \text{ V}$$

$$v_c(t) = \frac{40}{81} + \left(15 - \frac{40}{81}\right)e^{-4.05(t-t_o)} \text{ V} = \frac{40}{81} + \frac{1175}{81}e^{-4.05(t-t_o)}$$

$$\therefore \frac{40}{81} + \frac{1175}{81}e^{-4.05(t-t_o)} = 5$$

$$\frac{1175}{81}e^{-4.05(t-t_o)} = \frac{365}{81}$$


$$e^{4.05(t-t_o)} = \frac{1175}{365} = 3.22$$

$$t - t_o = \frac{1}{4.05} \ln 3.22 \cong 0.29 \text{ s}$$

One cycle = 7.02 seconds.

$$N = 60/7.02 = 8.55 \text{ flashes per minute}$$

[b] At  $t = 0$  we have

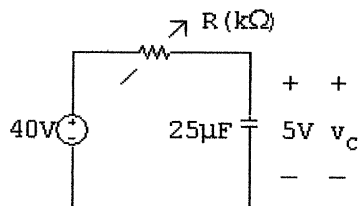


$$\tau = 25R \times 10^{-3}; \quad 1/\tau = 40/R$$

$$v_c = 40 - 35e^{-(40/R)t}$$

$$40 - 35e^{-(40/R)t_o} = 15$$

$$\therefore t_o = \frac{R}{40} \ln 1.4, \quad R \text{ in } k\Omega$$

At  $t = t_o$ :

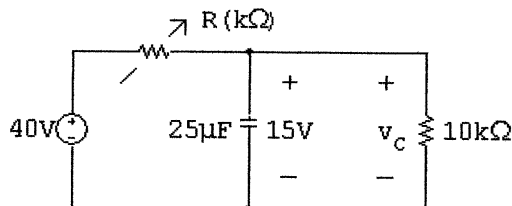

$$v_{Th} = \frac{10}{R+10}(40) = \frac{400}{R+10}; \quad R_{Th} = \frac{10R}{R+10} k\Omega$$

$$\tau = \frac{(25)(10R) \times 10^{-3}}{R+10} = \frac{0.25R}{R+10}; \quad \frac{1}{\tau} = \frac{4(R+10)}{R}$$

$$v_c = \frac{400}{R+10} + \left(15 - \frac{400}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)}$$

$$\therefore \frac{400}{R+10} + \left[\frac{15R-250}{R+10}\right] e^{-\frac{4(R+10)}{R}(t-t_o)} = 5$$

$$\text{or } \left(\frac{15R-250}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)} = \frac{5R-350}{(R+10)}$$

$$\therefore e^{\frac{4(R+10)}{R}(t-t_o)} = \frac{3R-50}{R-70}$$

$$\therefore t - t_o = \frac{R}{4(R+10)} \ln \left(\frac{3R-50}{R-70}\right)$$

At 12 flashes per minute  $t_o + (t - t_o) = 5 \text{ s}$

$$\therefore \underbrace{\frac{R}{40} \ln 1.4}_{\text{dominant term}} + \frac{R}{4(R+10)} \ln \left(\frac{3R-50}{R-70}\right) = 5$$

dominant  
term

Start the trial-and-error procedure by setting  $(R/40) \ln 1.4 = 5$ , then  $R = 200/(\ln 1.4)$  or  $594.40 k\Omega$ . If  $R = 594.40 k\Omega$  then  $t - t_o \cong 0.29 \text{ s}$ . Second trial set  $(R/40) \ln 1.4 = 4.7 \text{ s}$  or  $R = 558.74 k\Omega$ .

With  $R = 558.74 k\Omega$ ,  $t - t_o \cong 0.30 \text{ s}$

This procedure converges to  $R = 559.3 k\Omega$ .

$$\text{P 7.105 [a]} \quad t_o = RC \ln \left( \frac{V_{\min} - V_s}{V_{\max} - V_s} \right) = (3700)(250 \times 10^{-6}) \ln \left( \frac{-700}{-100} \right)$$

$$= 1.80 \text{ s}$$

$$t_c - t_o = \frac{RCR_L}{R + R_L} \ln \left( \frac{V_{\max} - V_{\text{Th}}}{V_{\min} - V_{\text{Th}}} \right)$$

$$\frac{R_L}{R + R_L} = \frac{1.3}{1.3 + 3.7} = 0.26; \quad RC = (3700)(250 \times 10^{-6}) = 0.925 \text{ s}$$

$$V_{\text{Th}} = \frac{1000(1.3)}{1.3 + 3.7} = 260 \text{ V}; \quad R_{\text{Th}} = 3.7 \text{ k} \parallel 1.3 \text{ k} = 962 \Omega$$

$$\therefore t_c - t_o = (0.925)(0.26) \ln(640/40) = 0.67 \text{ s}$$

$$\therefore t_c = 1.8 + 0.67 = 2.47 \text{ s}$$

$$\text{flashes/min} = \frac{60}{2.47} = 24.32$$

[b]  $0 \leq t \leq t_o$ :

$$v_L = 1000 - 700e^{-t/\tau_1}$$

$$\tau_1 = RC = 0.925 \text{ s}$$

$t_o \leq t \leq t_c$ :


$$v_L = 260 + 640e^{-(t-t_o)/\tau_2}$$

$$\tau_2 = R_{\text{Th}}C = 962(250) \times 10^{-6} = 0.2405 \text{ s}$$

$$0 \leq t \leq t_o: \quad i = \frac{1000 - v_L}{3700} = \frac{7}{37}e^{-t/0.925} \text{ A}$$

$$t_o \leq t \leq t_c: \quad i = \frac{1000 - v_L}{3700} = \frac{74}{370} - \frac{64}{370}e^{-(t-t_o)/0.2405}$$

Graphically,  $i$  versus  $t$  is

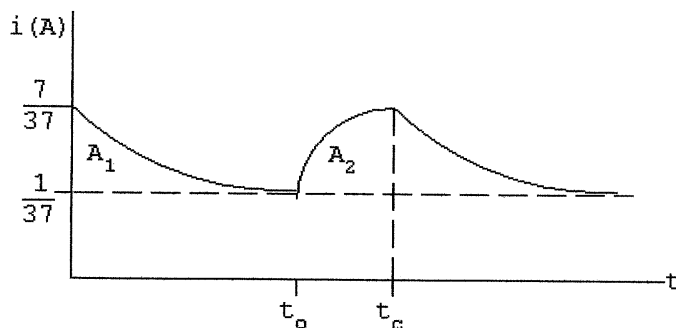

The average value of  $i$  will equal the areas ( $A_1 + A_2$ ) divided by  $t_c$ .

$$\therefore i_{\text{avg}} = \frac{A_1 + A_2}{t_c}$$

$$\begin{aligned} A_1 &= \frac{7}{37} \int_0^{t_o} e^{-t/0.925} dt \\ &= \frac{6.475}{37} (1 - e^{-\ln 7}) = 0.15 \text{ A-s} \end{aligned}$$

$$\begin{aligned} A_2 &= \int_{t_o}^{t_c} \frac{74 - 64e^{-(t-t_o)/0.2405}}{370} dt \\ &= \frac{74}{370} (t_c - t_o) + \frac{15.392}{370} (e^{-\ln 16} - 1) \\ &= \frac{17.797}{370} \ln 16 - \frac{15.392}{370} (1 - e^{-\ln 16}) \\ &= 0.09436 \text{ A-s} \end{aligned}$$


$$i_{\text{avg}} = \frac{(0.15 + 0.09436)}{0.925 \ln 7 + 0.2405 \ln 16} (1000) = 99.06 \text{ mA}$$

$$[c] P_{\text{avg}} = (1000)(99.06 \times 10^{-3}) = 99.06 \text{ W}$$

$$\text{No. of kw hrs/yr} = \frac{(99.06)(24)(365)}{1000} = 867.77$$

$$\text{Cost/year} = (867.77)(0.05) = 43.39 \text{ dollars/year}$$

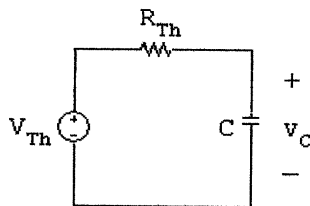P 7.106 [a] Replace the circuit attached to the capacitor with its Thévenin equivalent, where the equivalent resistance is the parallel combination of the two resistors, and the open-circuit voltage is obtained by voltage division across the lamp resistance. The resulting circuit is



$$R_{\text{Th}} = R \parallel R_L = \frac{RR_L}{R + R_L}; \quad V_{\text{Th}} = \frac{R_L}{R + R_L} V_s$$

From this circuit,

$$v_C(\infty) = V_{\text{Th}}; \quad v_C(0) = V_{\text{max}}; \quad \tau = R_{\text{Th}}C$$

Thus,

$$v_C(t) = V_{\text{Th}} + (V_{\text{max}} - V_{\text{Th}})e^{-(t-t_o)/\tau}$$

where

$$\tau = \frac{RR_L C}{R + R_L}$$

[b] Now, set  $v_C(t_c) = V_{\min}$  and solve for  $(t_c - t_o)$ :

$$V_{Th} + (V_{\max} - V_{Th})e^{-(t_c - t_o)/\tau} = V_{\min}$$

$$e^{-(t_c - t_o)/\tau} = \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$\frac{-(t_c - t_o)}{\tau} = \ln \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$(t_c - t_o) = -\frac{RR_L C}{R + R_L} \ln \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}} = \frac{RR_L C}{R + R_L} \ln \frac{V_{\max} - V_{Th}}{V_{\min} - V_{Th}}$$

P 7.107 [a]  $0 \leq t \leq 0.5$ :

$$i = \frac{21}{60} + \left( \frac{30}{60} - \frac{21}{60} \right) e^{-t/\tau} \quad \text{where } \tau = L/R.$$

$$i = 0.35 + 0.15e^{-60t/L}$$

$$i(0.5) = 0.35 + 0.15e^{-30/L} = 0.40$$

$$\therefore e^{30/L} = 3; \quad L = \frac{30}{\ln 3} = 27.31 \text{ H}$$

[b]  $0 \leq t \leq t_r$ , where  $t_r$  is the time the relay releases:

$$i = 0 + \left( \frac{30}{60} - 0 \right) e^{-60t/L} = 0.5e^{-60t/L}$$

$$\therefore 0.4 = 0.5e^{-60t_r/L}; \quad e^{60t_r/L} = 1.25$$

$$t_r = \frac{27.31 \ln 1.25}{60} \cong 0.10 \text{ s}$$