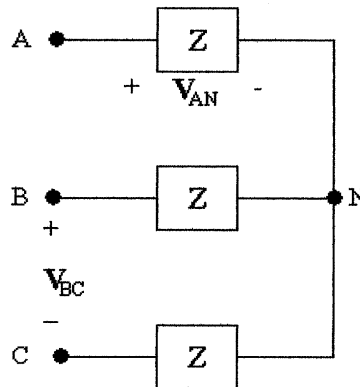


Balanced Three-Phase Circuits

Assessment Problems

AP 11.1 Make a sketch:



We know V_{AN} and wish to find V_{BC} . To do this, write a KVL equation to find V_{AB} , and use the known phase angle relationship between V_{AB} and V_{BC} to find V_{BC} .

$$V_{AB} = V_{AN} + V_{NB} = V_{AN} - V_{BN}$$

Since V_{AN} , V_{BN} , and V_{CN} form a balanced set, and $V_{AN} = 240/\underline{-30^\circ}\text{V}$, and the phase sequence is positive,

$$V_{BN} = |V_{AN}|/\underline{V_{AN} - 120^\circ} = 240/\underline{-30^\circ - 120^\circ} = 240/\underline{-150^\circ}\text{V}$$

Then,

$$V_{AB} = V_{AN} - V_{BN} = (240/\underline{-30^\circ}) - (240/\underline{-150^\circ}) = 415.46/\underline{0^\circ}\text{V}$$


Since V_{AB} , V_{BC} , and V_{CA} form a balanced set with a positive phase sequence, we can find V_{BC} from V_{AB} :

$$V_{BC} = |V_{AB}|/\underline{V_{AB} - 120^\circ} = 415.69/\underline{0^\circ - 120^\circ} = 415.69/\underline{-120^\circ}\text{V}$$

Thus,

$$V_{BC} = 415.69/\underline{-120^\circ}\text{V}$$

AP 11.2 Make a sketch:

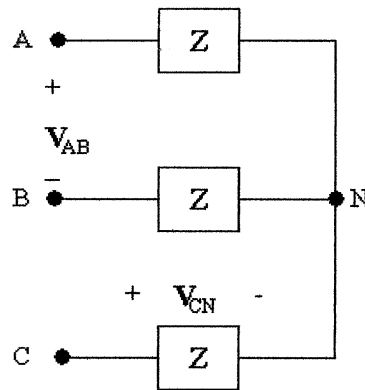

We know V_{CN} and wish to find V_{AB} . To do this, write a KVL equation to find V_{BC} , and use the known phase angle relationship between V_{AB} and V_{BC} to find V_{AB} .

$$V_{BC} = V_{BN} + V_{NC} = V_{BN} - V_{CN}$$

Since V_{AN} , V_{BN} , and V_{CN} form a balanced set, and $V_{CN} = 450 \angle -25^\circ$ V, and the phase sequence is negative,

$$V_{BN} = |V_{CN}| \angle \angle V_{CN} - 120^\circ = 450 \angle -25^\circ - 120^\circ = 450 \angle -145^\circ \text{ V}$$

Then,

$$V_{BC} = V_{BN} - V_{CN} = (450 \angle -145^\circ) - (450 \angle -25^\circ) = 779.42 \angle -175^\circ \text{ V}$$


Since V_{AB} , V_{BC} , and V_{CA} form a balanced set with a negative phase sequence, we can find V_{AB} from V_{BC} :

$$V_{AB} = |V_{BC}| \angle \angle V_{BC} - 120^\circ = 779.42 \angle -295^\circ \text{ V}$$

But we normally want phase angle values between $+180^\circ$ and -180° . We add 360° to the phase angle computed above. Thus,

$$V_{AB} = 779.42 \angle 65^\circ \text{ V}$$

AP 11.3 Sketch the a-phase circuit:

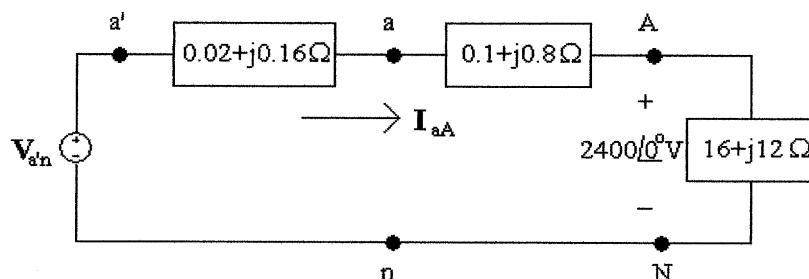

- [a] We can find the line current using Ohm's law, since the a-phase line current is the current in the a-phase load. Then we can use the fact that \mathbf{I}_{aA} , \mathbf{I}_{bB} , and \mathbf{I}_{cC} form a balanced set to find the remaining line currents. Note that since we were not given any phase angles in the problem statement, we can assume that the phase voltage given, \mathbf{V}_{AN} , has a phase angle of 0° .

$$2400/0^\circ = \mathbf{I}_{aA}(16 + j12)$$

so

$$\mathbf{I}_{aA} = \frac{2400/0^\circ}{16 + j12} = 96 - j72 = 120/\underline{-36.87^\circ} \text{ A}$$

With an acb phase sequence,

$$\underline{\mathbf{I}_{bB}} = \underline{\mathbf{I}_{aA}} + 120^\circ \quad \text{and} \quad \underline{\mathbf{I}_{cC}} = \underline{\mathbf{I}_{aA}} - 120^\circ$$

so

$$\mathbf{I}_{aA} = 120/\underline{-36.87^\circ} \text{ A}$$

$$\mathbf{I}_{bB} = 120/\underline{83.13^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = 120/\underline{-156.87^\circ} \text{ A}$$

- [b] The line voltages at the source are \mathbf{V}_{ab} , \mathbf{V}_{bc} , and \mathbf{V}_{ca} . They form a balanced set. To find \mathbf{V}_{ab} , use the a-phase circuit to find \mathbf{V}_{AN} , and use the relationship between phase voltages and line voltages for a y-connection (see Fig. 11.9[b]). From the a-phase circuit, use KVL:

$$\begin{aligned} \mathbf{V}_{an} &= \mathbf{V}_{aA} + \mathbf{V}_{AN} = (0.1 + j0.8)\mathbf{I}_{aA} + 2400/0^\circ \\ &= (0.1 + j0.8)(96 - j72) + 2400/0^\circ = 2467.2 + j69.6 \\ &= 2468.18/\underline{1.62^\circ} \text{ V} \end{aligned}$$

From Fig. 11.9(b),

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3}/\underline{-30^\circ}) = 4275.02/\underline{-28.38^\circ} \text{ V}$$

With an acb phase sequence,

$$\underline{\mathbf{V}_{bc}} = \underline{\mathbf{V}_{ab}} + 120^\circ \quad \text{and} \quad \underline{\mathbf{V}_{ca}} = \underline{\mathbf{V}_{ab}} - 120^\circ$$

so

$$\mathbf{V}_{ab} = 4275.02/\underline{-28.38^\circ} \text{ V}$$

$$\mathbf{V}_{bc} = 4275.02/\underline{91.62^\circ} \text{ V}$$

$$\mathbf{V}_{ca} = 4275.02/\underline{-148.38^\circ} \text{ V}$$

[c] Using KVL on the a-phase circuit

$$\begin{aligned}\mathbf{V}_{a'n} &= \mathbf{V}_{a'a} + \mathbf{V}_{an} = (0.2 + j0.16)\mathbf{I}_{aA} + \mathbf{V}_{an} \\ &= (0.02 + j0.16)(96 - j72) + (2467.2 + j69.9) \\ &= 2480.64 + j83.52 = 2482.05/\underline{1.93^\circ} \text{ V}\end{aligned}$$

With an acb phase sequence,

$$\underline{\mathbf{V}_{b'n}} = \underline{\mathbf{V}_{a'n}} + 120^\circ \quad \text{and} \quad \underline{\mathbf{V}_{c'n}} = \underline{\mathbf{V}_{a'n}} - 120^\circ$$

so

$$\mathbf{V}_{a'n} = 2482.05/\underline{1.93^\circ} \text{ V}$$

$$\mathbf{V}_{b'n} = 2482.05/\underline{121.93^\circ} \text{ V}$$

$$\mathbf{V}_{c'n} = 2482.05/\underline{-118.07^\circ} \text{ V}$$

AP 11.4

$$\mathbf{I}_{cC} = (\sqrt{3}/\underline{-30^\circ})\mathbf{I}_{CA} = (\sqrt{3}/\underline{-30^\circ}) \cdot 8/\underline{-15^\circ} = 13.86/\underline{-45^\circ} \text{ A}$$

AP 11.5

$$\begin{aligned}\mathbf{I}_{aA} &= 12/(\underline{65^\circ} - \underline{120^\circ}) = 12/\underline{-55^\circ} \\ \mathbf{I}_{AB} &= \left[\left(\frac{1}{\sqrt{3}} \right) \underline{-30^\circ} \right] \mathbf{I}_{aA} = \left(\frac{\underline{-30^\circ}}{\sqrt{3}} \right) \cdot 12/\underline{-55^\circ} \\ &= 6.93/\underline{-85^\circ} \text{ A}\end{aligned}$$

AP 11.6 [a] $\mathbf{I}_{AB} = \left[\left(\frac{1}{\sqrt{3}} \right) \underline{30^\circ} \right] [69.28/\underline{-10^\circ}] = 40/\underline{20^\circ} \text{ A}$

$$\text{Therefore } Z_\phi = \frac{4160/\underline{0^\circ}}{40/\underline{20^\circ}} = 104/\underline{-20^\circ} \Omega$$

[b] $\mathbf{I}_{AB} = \left[\left(\frac{1}{\sqrt{3}} \right) \underline{-30^\circ} \right] [69.28/\underline{-10^\circ}] = 40/\underline{-40^\circ} \text{ A}$

$$\text{Therefore } Z_\phi = 104/\underline{40^\circ} \Omega$$

AP 11.7

$$\mathbf{I}_\phi = \frac{110}{3.667} + \frac{110}{j2.75} = 30 - j40 = 50/\underline{-53.13^\circ} \text{ A}$$

$$\text{Therefore } |\mathbf{I}_{aA}| = \sqrt{3}\mathbf{I}_\phi = \sqrt{3}(50) = 86.60 \text{ A}$$

AP 11.8 [a] $|S| = \sqrt{3}(208)(73.8) = 26,587.67 \text{ VA}$

$$Q = \sqrt{(26,587.67)^2 - (22,659)^2} = 13,909.50 \text{ VAR}$$

$$[\text{b}] \text{ pf} = \frac{22,659}{26,587.67} = 0.8522 \text{ lagging}$$

$$\text{AP 11.9 } [\text{a}] \mathbf{V}_{\text{AN}} = \left(\frac{4160}{\sqrt{3}} \right) \angle 0^\circ \text{ V}; \quad \mathbf{V}_{\text{AN}} \mathbf{I}_{\text{aA}}^* = S_\phi = 384 + j288 \text{ kVA}$$

Therefore

$$\mathbf{I}_{\text{aA}}^* = \frac{(384 + j288)1000}{4160/\sqrt{3}} = (159.88 + j119.91) \text{ A}$$

$$\mathbf{I}_{\text{aA}} = 159.88 - j119.91 = 199.85 \angle -36.87^\circ \text{ A}$$

$$|\mathbf{I}_{\text{aA}}| = 199.85 \text{ A}$$

$$[\text{b}] P = \frac{(4160)^2}{R}; \quad \text{therefore } R = \frac{(4160)^2}{384,000} = 45.07 \Omega$$

$$Q = \frac{(4160)^2}{X}; \quad \text{therefore } X = \frac{(4160)^2}{288,000} = 60.09 \Omega$$

$$[\text{c}] Z_\phi = \frac{\mathbf{V}_{\text{AN}}}{\mathbf{I}_{\text{aA}}} = \frac{4160/\sqrt{3}}{199.85 \angle -36.87^\circ} = 12.02 \angle 36.87^\circ = (9.61 + j7.21) \Omega$$

$$\therefore R = 9.61 \Omega, \quad X = 7.21 \Omega$$

Problems

P 11.1 [a] First, convert the cosine waveforms to phasors:

$$\underline{V}_a = 120/\underline{54^\circ}; \quad \underline{V}_b = 120/\underline{-66^\circ}; \quad \underline{V}_c = 120/\underline{174^\circ}$$

Subtract the phase angle of the a-phase from all phase angles:

$$\underline{V}'_a = 54^\circ - 54^\circ = 0^\circ$$

$$\underline{V}'_b = -66^\circ - 54^\circ = -120^\circ$$

$$\underline{V}'_c = 174^\circ - 54^\circ = 120^\circ$$

Compare the result to Eqs. 11.1 and 11.2:

Therefore abc

[b] First, convert the cosine waveforms to phasors:

$$\underline{V}_a = 3240/\underline{-26^\circ}; \quad \underline{V}_b = 3240/\underline{94^\circ}; \quad \underline{V}_c = 3240/\underline{-146^\circ}$$

Subtract the phase angle of the a-phase from all phase angles:

$$\underline{V}'_a = -26^\circ + 26^\circ = 0^\circ$$

$$\underline{V}'_b = 94^\circ + 26^\circ = 120^\circ$$

$$\underline{V}'_c = -146^\circ + 26^\circ = -120^\circ$$

Compare the result to Eqs. 11.1 and 11.2:

Therefore acb

P 11.2 [a] $\underline{V}_a = 339/\underline{0^\circ} \text{ V}$

$$\underline{V}_b = 339/\underline{-120^\circ} \text{ V}$$

$$\underline{V}_c = 339/\underline{120^\circ} \text{ V}$$

Balanced, positive phase sequence

[b] $\underline{V}_a = 622/\underline{0^\circ} \text{ V}$

$$\underline{V}_b = 622/\underline{-240^\circ} \text{ V} = 622/\underline{120^\circ} \text{ V}$$

$$\underline{V}_c = 622/\underline{240^\circ} \text{ V} = 622/\underline{-120^\circ} \text{ V}$$

Balanced, negative phase sequence

[c] $\underline{V}_a = 933/\underline{-90^\circ} \text{ V}$

$$\underline{V}_b = 933/\underline{150^\circ} \text{ V}$$

$$\underline{V}_c = 933/\underline{30^\circ} \text{ V}$$

Balanced, positive phase sequence

$$[d] \quad \mathbf{V}_a = 170/\underline{-30^\circ} \text{ V}$$

$$\mathbf{V}_b = 170/\underline{90^\circ} \text{ V}$$

$$\mathbf{V}_c = 170/\underline{-150^\circ} \text{ V}$$

Balanced, negative phase sequence

[e] Unbalanced, due to unequal amplitudes

[f] Unbalanced, due to unequal phase angle separation

$$P \ 11.3 \quad \mathbf{V}_a = V_m/\underline{0^\circ} = V_m + j0$$

$$\mathbf{V}_b = V_m/\underline{-120^\circ} = -V_m(0.5 + j0.866)$$

$$\mathbf{V}_c = V_m/\underline{120^\circ} = V_m(-0.5 + j0.866)$$

$$\begin{aligned} \mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c &= (V_m)(1 + j0 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= V_m(0) = 0 \end{aligned}$$

$$P \ 11.4 \quad \mathbf{I} = \frac{\mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c}{3(R_W + jX_W)} = 0$$

P 11.5 [a] The circuit is unbalanced, because the impedance in each phase of the load is not the same.

$$[b] \quad \mathbf{I}_{aA} = \frac{240/\underline{0^\circ}}{10 + j30} = 2.4 - j7.2 \text{ A}$$

$$\mathbf{I}_{bB} = \frac{240/\underline{120^\circ}}{20 + j20} = 2.2 + j8.2 \text{ A}$$

$$\mathbf{I}_{cC} = \frac{240/\underline{-120^\circ}}{20 - j40} = 2.96 - j4.48 \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 7.55 - j3.48 = 8.32/\underline{-24.75^\circ} \text{ A}$$

$$P \ 11.6 \quad [a] \quad \mathbf{I}_{aA} = \frac{240/\underline{0^\circ}}{80 + j60} = 2.4/\underline{-36.87^\circ} \text{ A}$$

$$\mathbf{I}_{bB} = \frac{240/\underline{120^\circ}}{80 + j60} = 2.4/\underline{83.13^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = \frac{240/\underline{-120^\circ}}{80 + j60} = 2.4/\underline{-156.87^\circ} \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 0$$

$$[b] \quad \mathbf{V}_{AN} = (79 + j55)\mathbf{I}_{aA} = (79 + j55)(2.4/\underline{-36.87^\circ}) = 231.0/\underline{-2.02^\circ} \text{ V}$$

$$[c] \mathbf{V}_{BN} = (79 + j52)\mathbf{I}_{bB} = 226.99/\underline{116.48^\circ} \text{ V}$$

$$\therefore \mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} = 393.6/\underline{-32.5^\circ} \text{ V}$$

[d] Unbalanced

$$P \ 11.7 \quad Z_{ga} + Z_{la} + Z_{La} = 80 + j60 \Omega$$

$$Z_{gb} + Z_{lb} + Z_{Lb} = 40 + j30 \Omega$$

$$Z_{gc} + Z_{lc} + Z_{Lc} = 160 + j120 \Omega$$

$$\frac{\mathbf{V}_N - 480}{80 + j60} + \frac{\mathbf{V}_N - 480/\underline{-120^\circ}}{40 + j30} + \frac{\mathbf{V}_N - 480/\underline{120^\circ}}{160 + j120} + \frac{\mathbf{V}_N}{20} = 0$$

Solving for \mathbf{V}_N yields

$$\mathbf{V}_N = 78.61/\underline{-122.69^\circ} \text{ V}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_N}{20} = 3.93/\underline{-122.69^\circ} \text{ A}$$

$$P \ 11.8 \quad \mathbf{V}_{AN} = 7967/\underline{0^\circ} \text{ V}$$

$$\mathbf{V}_{BN} = 7967/\underline{+120^\circ} \text{ V}$$

$$\mathbf{V}_{CN} = 7967/\underline{-120^\circ} \text{ V}$$

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} = 13,799.25/\underline{-30^\circ} \text{ V}$$

$$\mathbf{V}_{BC} = \mathbf{V}_{BN} - \mathbf{V}_{CN} = 13,799.25/\underline{90^\circ} \text{ V}$$


$$\mathbf{V}_{CA} = \mathbf{V}_{CN} - \mathbf{V}_{AN} = 13,799.25/\underline{-150^\circ} \text{ V}$$

$$v_{AB} = 13,799.25 \cos(\omega t - 30^\circ) \text{ V}$$

$$v_{BC} = 13,799.25 \cos(\omega t + 90^\circ) \text{ V}$$

$$v_{CA} = 13,799.25 \cos(\omega t - 150^\circ) \text{ V}$$

P 11.9 [a]

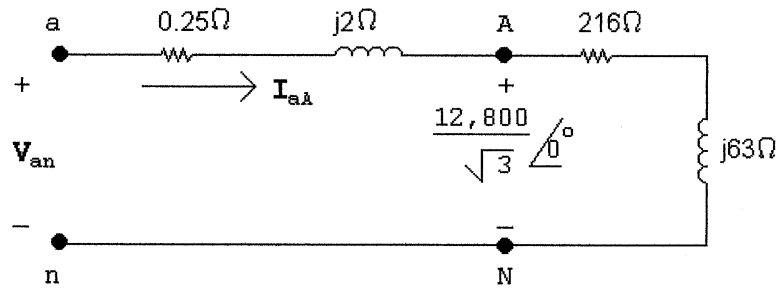

$$\mathbf{I}_{aA} = \frac{12,800}{\sqrt{3}(216 + j63)} = 32.84 \angle -16.26^\circ \text{ A(rms)}$$

$$|\mathbf{I}_{aA}| = |\mathbf{I}_L| = 32.84 \text{ A(rms)}$$

$$[\text{b}] \quad \mathbf{V}_{an} = \frac{12,800}{\sqrt{3}} + (32.84 \angle -16.26^\circ)(0.25 + j2) = 7416.61 \angle 0.47^\circ$$

$$|\mathbf{V}_{AB}| = \sqrt{3}(7416.61) = 12,845.94 \text{ V(rms)}$$

$$\text{P 11.10 [a]} \quad \mathbf{I}_{aA} = \frac{4800 \angle 0^\circ}{192 + j56} = 24 \angle -16.26^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 24 \angle 120 - 16.26^\circ = 24 \angle 103.74^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 24 \angle -136.26^\circ \text{ A}$$

$$[\text{b}] \quad \mathbf{V}_{an} = 4800 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_{bn} = 4800 \angle 120^\circ \text{ V}$$

$$\mathbf{V}_{cn} = 4800 \angle -120^\circ \text{ V}$$

$$\mathbf{V}_{ab} = \sqrt{3} \angle -30^\circ \mathbf{V}_{an} = 8313.84 \angle -30^\circ \text{ V}$$

$$\mathbf{V}_{bc} = 8313.84 \angle 90^\circ \text{ V}$$

$$\mathbf{V}_{ca} = 8313.84 \angle -150^\circ \text{ V}$$

$$[\text{c}] \quad \mathbf{V}_{AN} = (24 \angle -16.26^\circ)(190 + j40) = 4659.96 \angle -4.37^\circ \text{ V}$$

$$\mathbf{V}_{BN} = 4659.96 \angle 115.63^\circ \text{ V}$$

$$\mathbf{V}_{CN} = 4659.96 \angle -124.37^\circ \text{ V}$$


$$[\text{d}] \quad \mathbf{V}_{AB} = \sqrt{3} \angle -30^\circ \mathbf{V}_{AN} = 8071.28 \angle -34.37^\circ \text{ V}$$

$$\mathbf{V}_{BC} = 8071.28 \angle 85.63^\circ \text{ V}$$

$$\mathbf{V}_{CA} = 8071.28 \angle -154.37^\circ \text{ V}$$

P 11.11 [a] $\mathbf{V}_{an} = 1/\sqrt{3}/-30^\circ \mathbf{V}_{ab} = 120/-30^\circ \text{ V(rms)}$

The a-phase circuit is

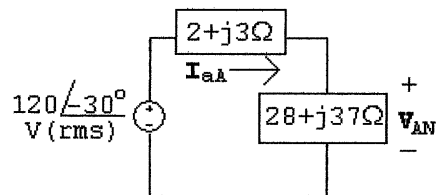

[b] $\mathbf{I}_{aA} = \frac{120/-30^\circ}{30 + j40} = 2.4/-83.13^\circ \text{ A(rms)}$

[c] $\mathbf{V}_{AN} = (28 + j37)\mathbf{I}_{aA} = 111.36/-30.25^\circ \text{ V(rms)}$

$\mathbf{V}_{AB} = \sqrt{3}/30^\circ \mathbf{V}_{AN} = 192.88/-0.25^\circ \text{ A(rms)}$

P 11.12 [a] $\mathbf{I}_{AB} = \frac{33,000}{360 + j105} = 88/-16.26^\circ \text{ A}$

$\mathbf{I}_{BC} = 88/-136.26^\circ \text{ A}$


$\mathbf{I}_{CA} = 88/103.74^\circ \text{ A}$

[b] $\mathbf{I}_{aA} = \sqrt{3}/-30^\circ \mathbf{I}_{AB} = 152.42/-46.26^\circ \text{ A}$

$\mathbf{I}_{bB} = 152.42/-166.26^\circ \text{ A}$

$\mathbf{I}_{cC} = 152.42/73.74^\circ \text{ A}$

[c]

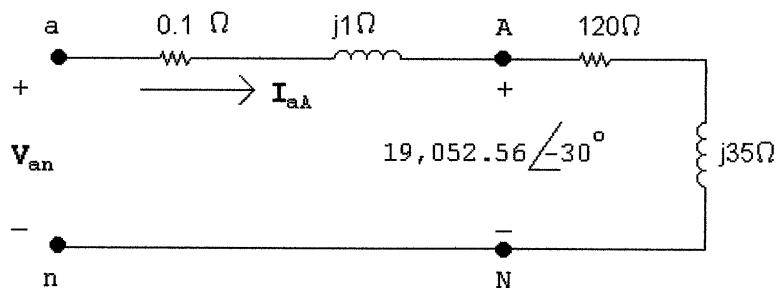


$$\begin{aligned} \mathbf{V}_{an} &= 19,052.56/-30^\circ + (0.1 + j1.0)(152.42/-46.26^\circ) \\ &= 19,110.40/-29.57^\circ \text{ V} \end{aligned}$$

$\mathbf{V}_{ab} = \sqrt{3}/30^\circ \mathbf{V}_{an} = 33,100.18/0.43^\circ \text{ V}$

$\mathbf{V}_{bc} = 33,100.18/-119.57^\circ \text{ V}$

$\mathbf{V}_{ca} = 33,100.18/120.43^\circ \text{ V}$

P 11.13 [a]

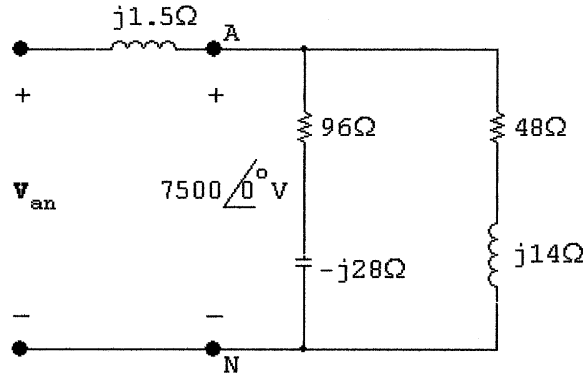

$$\mathbf{I}_{aA} = \frac{7500}{96 - j28} + \frac{7500}{48 + j14} = 217.02 \angle -5.55^\circ \text{ A}$$

$$|\mathbf{I}_{aA}| = 217.02 \text{ A}$$

$$[\text{b}] \quad \mathbf{I}_{AB} = \frac{7500\sqrt{3}/30^\circ}{144 + j42} = 86.60 \angle 13.74^\circ \text{ A}$$

$$|\mathbf{I}_{AB}| = 86.60 \text{ A}$$

$$[\text{c}] \quad \mathbf{I}_{AN} = \frac{7500/0^\circ}{96 - j28} = 75 \angle 16.26^\circ \text{ A}$$

$$|\mathbf{I}_{AN}| = 75 \text{ A}$$


$$[\text{d}] \quad \mathbf{V}_{an} = (216 - j21)(j1.5) + 7500/0^\circ = 7538.47 \angle 2.46^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(7538.47) = 13,057.01 \text{ V}$$

P 11.14 [a] $\mathbf{V}_{an} = \mathbf{V}_{bn} - \angle 120^\circ = 20 \angle -210^\circ = 20 \angle 150^\circ \text{ V(rms)}$

$$\mathbf{Z}_y = \mathbf{Z}_\Delta/3 = 39 - j33 \Omega$$

The a-phase circuit is

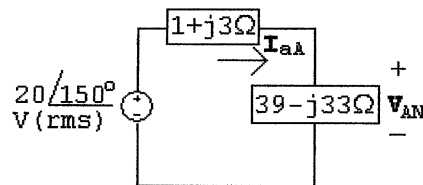

$$\mathbf{I}_{aA} = \frac{20 \angle 150^\circ}{40 - j30} = 0.4 \angle -173.13^\circ \text{ A(rms)}$$

$$\mathbf{V}_{AN} = (39 + j33)\mathbf{I}_{aA} = 20.44 \angle 146.63^\circ \text{ V(rms)}$$

$$\mathbf{V}_{AB} = \sqrt{3} \angle -30^\circ \mathbf{V}_{AN} = 35.39 \angle 116.63^\circ \text{ V(rms)}$$


$$[b] \mathbf{I}_{AB} = \frac{1}{\sqrt{3}} \angle -30^\circ \mathbf{I}_{aA} = 0.23 \angle 156.87^\circ \text{ A(rms)}$$

$$[c] \mathbf{V}_{AB} = (117 - j99) \mathbf{I}_{AB} = 35.3 \angle 116.63^\circ \text{ V(rms)}$$

$$P \ 11.15 \ \mathbf{V}_{an} = 1/\sqrt{3} \angle -30^\circ \mathbf{V}_{ab} = \frac{208}{\sqrt{3}} \angle 20^\circ \text{ V(rms)}$$

$$Z_y = Z_\Delta/3 = 1 - j3 \Omega$$

The a-phase circuit is

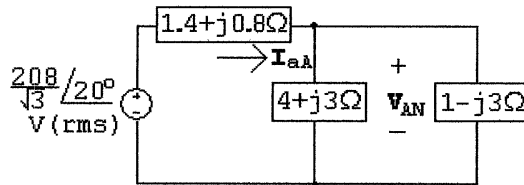


$$Z_{eq} = (4 + j3) \parallel (1 - j3) = 2.6 - j1.8 \Omega$$

$$\mathbf{V}_{AN} = \frac{2.6 - j1.8}{(1.4 + j0.8) + (2.6 - j1.8)} \left(\frac{208}{\sqrt{3}} \right) \angle 20^\circ = 92.1 \angle -0.66^\circ \text{ V(rms)}$$

$$\mathbf{V}_{AB} = \sqrt{3} \angle 30^\circ \mathbf{V}_{AN} = 159.5 \angle 29.34^\circ \text{ V(rms)}$$

$$P \ 11.16 \ Z_y = Z_\Delta/3 = 4 + j3 \Omega$$

The a-phase circuit is

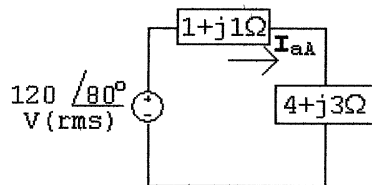

$$\mathbf{I}_{aA} = \frac{120 \angle 80^\circ}{(1 + j1) + (4 + j3)} = 18.74 \angle 41.34^\circ \text{ A(rms)}$$

$$\mathbf{I}_{AB} = \frac{1}{\sqrt{3}} \angle 30^\circ \mathbf{I}_{aA} = 10.82 \angle 71.34^\circ \text{ A(rms)}$$


P 11.17 [a] Since the phase sequence is acb (negative) we have:

$$V_{an} = 7200 \angle 30^\circ \text{ V}$$

$$V_{bn} = 7200 \angle 150^\circ \text{ V}$$

$$V_{cn} = 7200 \angle -90^\circ \text{ V}$$

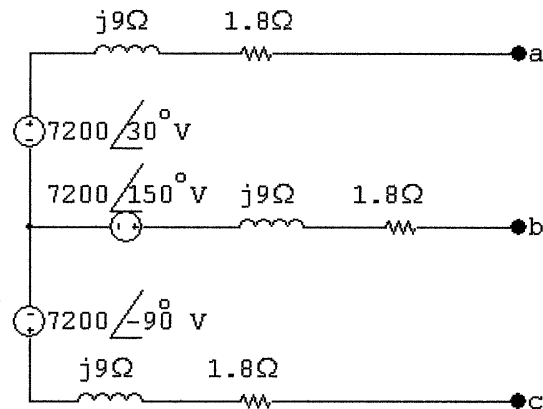
$$Z_Y = \frac{1}{3} Z_\Delta = 1.8 + j9.0 \Omega / \phi$$



[b] $V_{ab} = 7200 \angle 30^\circ - 7200 \angle 150^\circ = 7200\sqrt{3} \angle 0^\circ \text{ V}$

Since the phase sequence is negative, it follows that
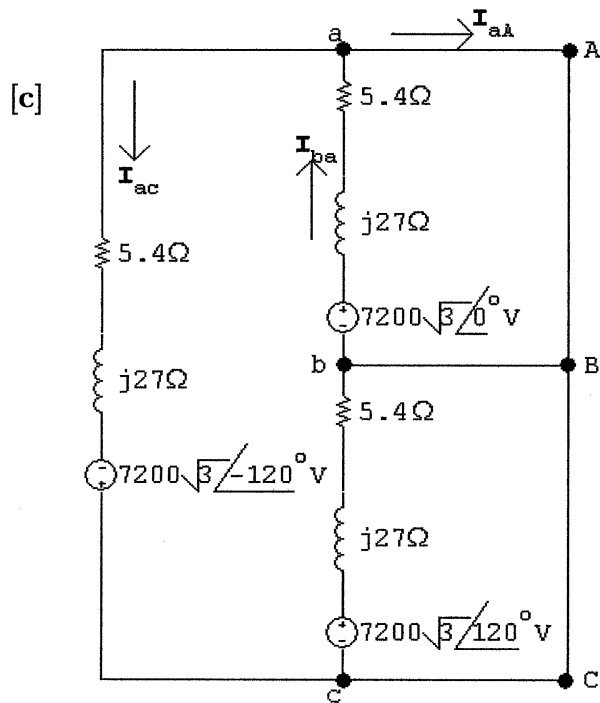
$$V_{bc} = 7200\sqrt{3} \angle 120^\circ \text{ V}$$



$$I_{ba} = \frac{7200\sqrt{3}}{5.4 + j27} = 452.91 \angle -78.69^\circ \text{ A}$$

$$\mathbf{I}_{ac} = \frac{7200\sqrt{3}/-120^\circ}{5.4 + j27} = 452.91/-198.69^\circ \text{ A}$$


$$\mathbf{I}_{aA} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = 784.46/-48.69^\circ \text{ A}$$

Since we have a balanced three-phase circuit and a negative phase sequence we have:

$$\mathbf{I}_{bB} = 784.46/71.31^\circ \text{ A}$$


$$\mathbf{I}_{cC} = 784.46/-168.69^\circ \text{ A}$$

[d]

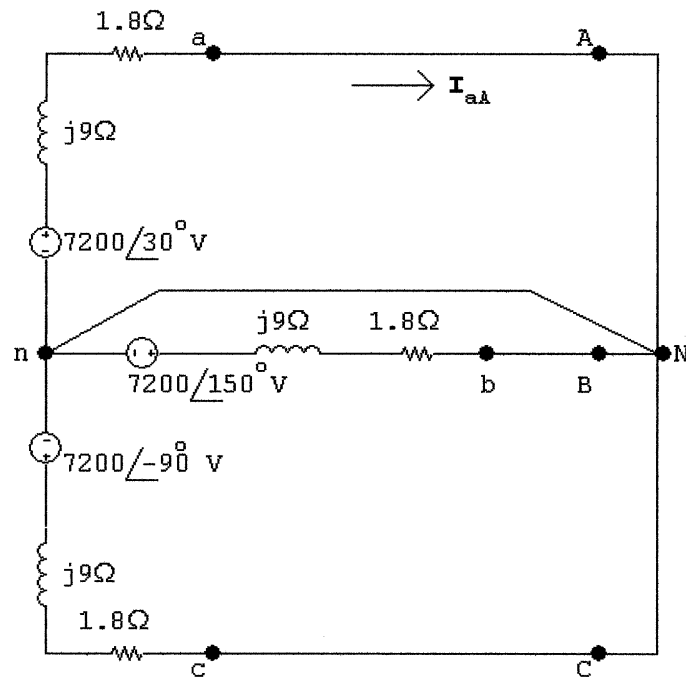

$$\mathbf{I}_{aA} = \frac{7200/30^\circ}{1.8 + j9} = 784.46/-48.69^\circ \text{ A}$$

P 11.18 [a]

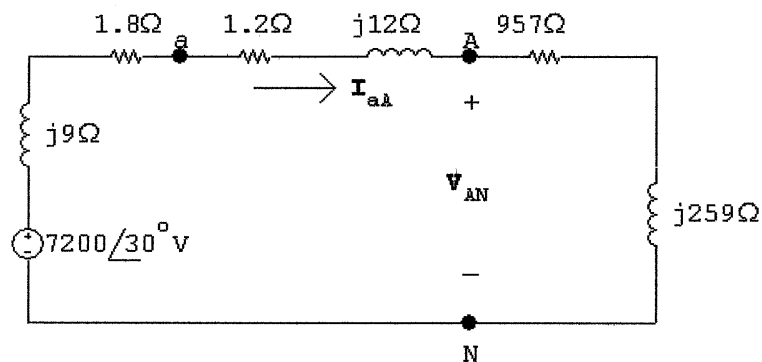

$$[b] \mathbf{I}_{aA} = \frac{7200/30^\circ}{960 + j280} = 7.2/13.74^\circ \text{ A}$$

$$\mathbf{V}_{AN} = (957 + j259)(7.2/13.74^\circ) = 7138.28/28.88^\circ \text{ V}$$


$$|\mathbf{V}_{AB}| = \sqrt{3}(7138.28) = 12,363.87 \text{ V}$$

$$[c] |\mathbf{I}_{ba}| = \frac{7.2}{\sqrt{3}} = 4.16 \text{ A}$$

$$[d] \mathbf{V}_{an} = (958.2 + j271)(7.20/13.74^\circ) = 7169.65/29.54^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(7169.65) = 12,418.20 \text{ V}$$

P 11.19 [a]

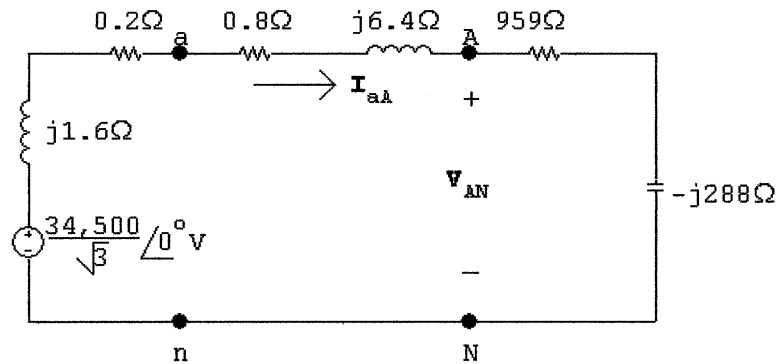

$$[b] \mathbf{I}_{aA} = \frac{34,500}{\sqrt{3}(960 - j280)} = 19.92/16.26^\circ \text{ A}$$

$$|\mathbf{I}_{aA}| = 19.92 \text{ A}$$

$$[c] \mathbf{V}_{AN} = (959 - j288)(19.92/16.26^\circ) = 19,944.71/-0.46^\circ \text{ V}$$

$$|\mathbf{V}_{AB}| = \sqrt{3}|\mathbf{V}_{AN}| = 34,545.25 \text{ V}$$

$$[d] \mathbf{V}_{an} = (959.8 - j281.6)(19.92/16.26^\circ) = 19,923.71/-0.09^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}|\mathbf{V}_{an}| = 34,508.88 \text{ V}$$

$$[e] |\mathbf{I}_{AB}| = \frac{|\mathbf{I}_{aA}|}{\sqrt{3}} = 11.50 \text{ A}$$

$$[f] |\mathbf{I}_{ba}| = |\mathbf{I}_{AB}| = 11.50 \text{ A}$$

$$P 11.20 [a] \mathbf{I}_{AB} = \frac{69,000/0^\circ}{600 + j450} = 92/-36.87^\circ \text{ A}$$

$$\mathbf{I}_{BC} = 92/-156.87^\circ \text{ A}$$

$$\mathbf{I}_{CA} = 92/83.13^\circ \text{ A}$$

$$[b] \mathbf{I}_{aA} = \sqrt{3}/-30^\circ \mathbf{I}_{AB} = 159.35/-66.87^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 159.35/-186.87^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 159.35/53.13^\circ \text{ A}$$

$$[c] \mathbf{I}_{ba} = \mathbf{I}_{AB} = 92/\underline{-36.87^\circ} \text{ A}$$

$$\mathbf{I}_{cb} = \mathbf{I}_{BC} = 92/\underline{-156.87^\circ} \text{ A}$$

$$\mathbf{I}_{ac} = \mathbf{I}_{CA} = 92/\underline{83.13^\circ} \text{ A}$$

$$P \ 11.21 \ [a] \ \mathbf{I}_{AB} = \frac{720/\underline{0^\circ}}{4.8 + j1.4} = 144/\underline{-16.26^\circ} \text{ A}$$

$$\mathbf{I}_{BC} = \frac{720/\underline{-120^\circ}}{16 - j12} = 36/\underline{-83.13^\circ} \text{ A}$$

$$\mathbf{I}_{CA} = \frac{720/\underline{120^\circ}}{25 + j25} = 20.36/\underline{75^\circ} \text{ A}$$

$$\begin{aligned} [b] \ \mathbf{I}_{aA} &= \mathbf{I}_{AB} - \mathbf{I}_{CA} \\ &= 138.24 - j40.32 - 5.27 - j19.67 \\ &= 132.97 - j59.99 = 145.88/\underline{-24.28^\circ} \text{ A} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_{bB} &= \mathbf{I}_{BC} - \mathbf{I}_{AB} \\ &= 4.31 - j35.74 - 138.24 + j40.32 \\ &= -133.93 + j4.58 = 134.01/\underline{178.04^\circ} \text{ A} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_{cC} &= \mathbf{I}_{CA} - \mathbf{I}_{BC} \\ &= 5.27 + j19.67 - 4.31 + j35.74 \\ &= 0.96 + j55.41 = 55.42/\underline{89.01^\circ} \text{ A} \end{aligned}$$

P 11.22 The complex power of the source per phase is
 $S_s = 30,000/(\cos^{-1} 0.8) = 30,000/\underline{36.87^\circ} = 24,000 + j18,000 \text{ kVA}$. This
 complex power per phase must equal the sum of the per-phase impedances of
 the two loads:

$$S_s = S_1 + S_2 \quad \text{so} \quad 24,000 + j18,000 = 20,000 + S_2$$

$$\therefore S_2 = 4000 + j18,000 \text{ VA}$$

$$\text{Also, } S_2 = \frac{|V_{\text{rms}}|^2}{Z_2^*}$$

$$|V_{\text{rms}}| = \frac{|V_{\text{load}}|}{\sqrt{3}} = \frac{415.69}{\sqrt{3}} = 240 \text{ V(rms)}$$

$$\text{Thus, } Z_2^* = \frac{|V_{\text{rms}}|^2}{S_2} = \frac{(240)^2}{4000 + j18,000} = 0.68 - j3.05 \Omega$$

$$\therefore Z_2 = 0.68 + j3.05 \Omega$$


$$\text{P 11.23 } |I_{\text{line}}| = \frac{1200}{208/\sqrt{3}} = 10 \text{ A(rms)}$$

$$|Z_y| = \frac{|V|}{|I|} = \frac{208/\sqrt{3}}{10} = 12$$

$$Z_y = 12/\underline{25^\circ} \Omega$$

$$Z_\Delta = 3Z_y = 36/\underline{25^\circ} = 32.63 + j15.21 \Omega/\phi$$

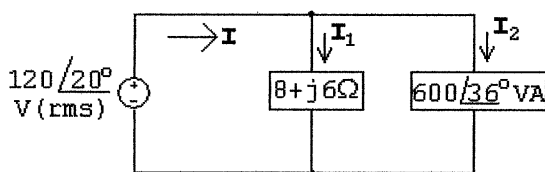P 11.24 The a-phase of the circuit is shown below:



$$I_1 = \frac{120/\underline{20^\circ}}{8 + j6} = 12/\underline{-16.87^\circ} \text{ A(rms)}$$

$$I_2^* = \frac{600/\underline{36^\circ}}{120/\underline{20^\circ}} = 5/\underline{16^\circ} \text{ A(rms)}$$

$$I = I_1 + I_2 = 12/\underline{-16.87^\circ} + 5/\underline{-16^\circ} = 17/\underline{-16.61^\circ} \text{ A(rms)}$$

$$S_a = \mathbf{VI}^* = (120/\underline{20^\circ})(17/\underline{16.61^\circ}) = 2040/\underline{36.61^\circ} \text{ VA}$$

$$S_T = 3S_a = 6120/\underline{36.61^\circ} \text{ VA}$$

$$\text{P 11.25 [a] } S_{T\Delta} = 14,000/\underline{41.41^\circ} - 9000/\underline{53.13^\circ} = 5.5/\underline{22^\circ} \text{ kVA}$$

$$S_\Delta = S_{T\Delta}/3 = 1833.46/\underline{22^\circ} \text{ VA}$$

$$\text{[b] } |V_{\text{an}}| = \left| \frac{3000/\underline{53.13^\circ}}{10/\underline{-30^\circ}} \right| = 300 \text{ V(rms)}$$


$$|V_{\text{line}}| = |V_{\text{ab}}| = \sqrt{3}|V_{\text{an}}| = 300\sqrt{3} = 519.62 \text{ V(rms)}$$

P 11.26 From the solution to Problem 11.21 we have:

$$S_{AB} = (720/\underline{0^\circ})(144/\underline{16.26^\circ}) = 99,532.9 + j29,030.04 \text{ VA}$$

$$S_{BC} = (720/\underline{-120^\circ})(36/\underline{83.13^\circ}) = 20,735.97 - j15,552.04 \text{ VA}$$
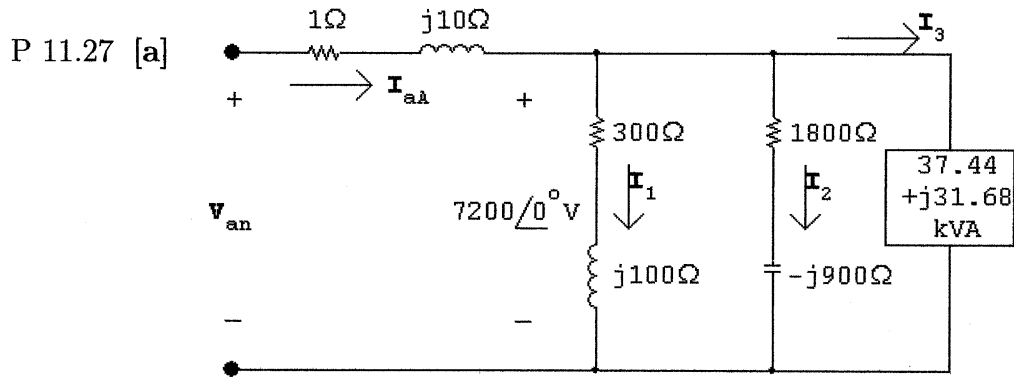
$$S_{CA} = (720/\underline{120^\circ})(20.36/\underline{-75^\circ}) = 10,365.62 + j10,365.62 \text{ VA}$$



$$I_1 = \frac{7200\angle 0^\circ}{300 + j100} = 21.6 - j7.2 \text{ A}$$

$$I_2 = \frac{7200\angle 0^\circ}{1800 - j900} = 3.2 + j1.6 \text{ A}$$

$$I_3^* = \frac{37,440 + j31,680}{7200} = 5.2 + j4.4$$

$$I_3 = 5.2 - j4.4 \text{ A}$$

$$I_{aA} = I_1 + I_2 + I_3 = 30 - j10 \text{ A} = \sqrt{1000}\angle -18.43^\circ \text{ A}$$

$$V_{an} = 7200 + j0 + (30 - j10)(1 + j10) = 7330 + j290 \text{ V}$$

$$S_\phi = V_{an} I_{aA}^* = (7330 + j290)(30 + j10) = 217,000 + j82,000 \text{ VA}$$

$$S_T = 3S_\phi = 651 + j246 \text{ kVA}$$

[b] $S_{1/\phi} = 7200(21.6 + j7.2) = 155.52 + j51.84 \text{ kVA}$


$$S_{2/\phi} = 7200(3.2 - j1.6) = 23.04 - j11.52 \text{ kVA}$$

$$S_{3/\phi} = 37.44 + j31.68 \text{ kVA}$$

$$S_\phi(\text{load}) = 216 + j72 \text{ kVA}$$

$$\% \text{ delivered} = \left(\frac{216}{217} \right) (100) = 99.54\%$$

P 11.28 [a]

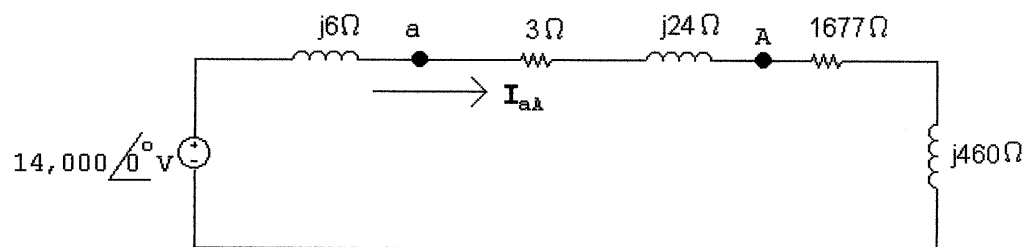

$$I_{aA} = \frac{14,000\angle 0^\circ}{1680 + j490} = 8\angle -16.26^\circ \text{ A}$$

$$I_{CA} = \frac{I_{aA}}{\sqrt{3}}\angle 150^\circ = 4.62\angle 133.74^\circ \text{ A}$$

$$[b] S_{g/\phi} = -14,000\mathbf{I}_{aA}^* = -107,520 - j31,360 \text{ VA}$$

$$\therefore P_{\text{developed/phase}} = 107.52 \text{ kW}$$

$$P_{\text{absorbed/phase}} = |\mathbf{I}_{aA}|^2 1677 = 107.328 \text{ kW}$$

$$\% \text{ delivered} = \frac{107.328}{107.52}(100) = 99.82\%$$

P 11.29 Let p_a , p_b , and p_c represent the instantaneous power of phases a, b, and c, respectively. Then assuming a positive phase sequence, we have

$$p_a = v_{an}i_{aA} = [V_m \cos \omega t][I_m \cos(\omega t - \theta_\phi)]$$

$$p_b = v_{bn}i_{bB} = [V_m \cos(\omega t - 120^\circ)][I_m \cos(\omega t - \theta_\phi - 120^\circ)]$$

$$p_c = v_{cn}i_{cC} = [V_m \cos(\omega t + 120^\circ)][I_m \cos(\omega t - \theta_\phi + 120^\circ)]$$

The total instantaneous power is $p_T = p_a + p_b + p_c$, so

$$\begin{aligned} p_T = V_m I_m [\cos \omega t \cos(\omega t - \theta_\phi) + \cos(\omega t + 120^\circ) \cos(\omega t - \theta_\phi - 120^\circ) \\ + \cos(\omega t - 120^\circ) \cos(\omega t - \theta_\phi + 120^\circ)] \end{aligned}$$

Now simplify using trigonometric identities. In simplifying, collect the coefficients of $\cos(\omega t - \theta_\phi)$ and $\sin(\omega t - \theta_\phi)$. We get

$$\begin{aligned} p_T &= V_m I_m [\cos \omega t (1 + 2 \cos^2 120^\circ) \cos(\omega t - \theta_\phi) \\ &\quad + 2 \sin \omega t \sin^2 120^\circ \sin(\omega t - \theta_\phi)] \\ &= 1.5 V_m I_m [\cos \omega t \cos(\omega t - \theta_\phi) + \sin \omega t \sin(\omega t - \theta_\phi)] \\ &= 1.5 V_m I_m \cos \theta_\phi \end{aligned}$$

P 11.30 [a] $S_1 = 72 - j21 \text{ kVA}$


$$S_2 = 120 + j90 \text{ kVA}$$

$$S_3 = 168 + j36 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 360 + j105 \text{ kVA}$$

$$S_T/\phi = 120 + j35 \text{ kVA}$$

Single phase equivalent circuit

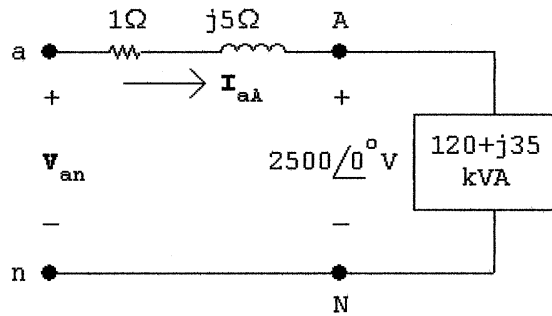

$$\therefore I_{aA}^* = \frac{120,000 + j35,000}{2500} = 48 + j14$$

$$\therefore I_{aA} = 48 - j14 \text{ A} = 50 \angle -16.26^\circ \text{ A}$$

$$\begin{aligned} V_{an} &= 2500 + (1 + j5)(48 - j14) = 2618 + j226 \\ &= 2627.74 \angle 4.93^\circ \text{ V} \end{aligned}$$

$$\therefore |V_{ab}| = \sqrt{3}(2627.74) = 4551.4 \text{ V}$$

[b] $P_L/\phi = 120 \text{ kW}$

$$P_S/\phi = 120,000 + |I_{aA}|^2(1) = 122,500 \text{ W} = 122.5 \text{ kW}$$

$$\eta = \left(\frac{120}{122.5} \right) 100 = 97.96\%$$

P 11.31 [a] $S_1 = (5.742 + j4.008) \text{ kVA}$

$$S_2 = 18.566(0.93) + j18.566(0.37) = (17.266 + j6.824) \text{ kVA}$$

$$\sqrt{3}V_L I_L \sin \theta_3 = 11,623; \quad \sin \theta_3 = \frac{11,623}{\sqrt{3}(208)(81.6)} = 0.395$$

Therefore $\cos \theta_3 = 0.919$

Therefore

$$P_3 = \frac{11,623}{0.395} \times 0.919 = 27,041.67 \text{ W}$$

$$S_3 = 27.042 + j11.623 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 50.05 + j22.455 \text{ kVA}$$


$$S_{T/\phi} = \frac{1}{3} S_T = 16.68 + j7.49 \text{ kVA}$$

$$\frac{208}{\sqrt{3}} I_{aA}^* = (16.68 + j7.49) 10^3; \quad I_{aA}^* = 138.92 + j62.33 \text{ A}$$

$$I_{aA} = 138.92 - j62.33 = 152.26 \angle -24.16^\circ \text{ A (rms)}$$

[b] $\text{pf} = \cos(-24.16^\circ) = 0.912$ leading

P 11.32

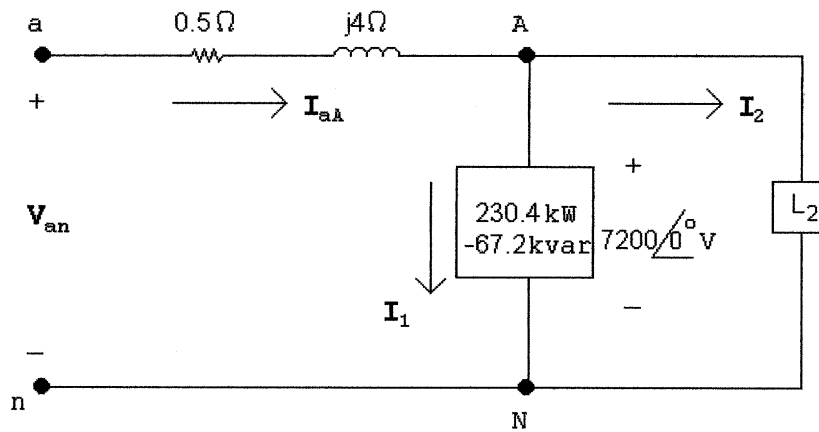

$$7200\mathbf{I}_1^* = (230.4 - j67.2)10^3$$

$$\mathbf{I}_1^* = 32 - j9.33 \text{ A}$$

$$\mathbf{I}_1 = 32 + j9.33 \text{ A}$$

$$\mathbf{Z}_y = \frac{1}{3}\mathbf{Z}_\Delta = 207.36 + j60.48 \Omega$$

$$\mathbf{I}_2 = \frac{7200/0^\circ}{207.36 + j60.48} = 32 - j9.33 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = \mathbf{I}_1 + \mathbf{I}_2 = 64 + j0 \text{ A}$$

$$\mathbf{V}_{an} = 7200 + j0 + 64(0.5 + j4) = 7236.53/2.03^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}|\mathbf{V}_{an}| = 12,534.04 \text{ V}$$

P 11.33 [a] $P_{\text{OUT}} = 746 \times 200 = 149,200 \text{ W}$

$$P_{\text{IN}} = 149,200/(0.96) = 155,416.67 \text{ W}$$

$$\sqrt{3}V_L I_L \cos \theta = 155,416.67$$


$$I_L = \frac{155,416.67}{\sqrt{3}(208)(0.92)} = 468.91 \text{ A}$$

[b] $Q = \sqrt{3}V_L I_L \sin \phi = \sqrt{3}(208)(468.91)(0.39) = 66,207.79 \text{ VAR}$

$$\text{P 11.34 } \mathbf{I}_{aA}^* = \frac{(48 + j36)10^3}{480} = 100 + j75$$

$$\mathbf{I}_{aA} = 100 - j75 \text{ A}$$
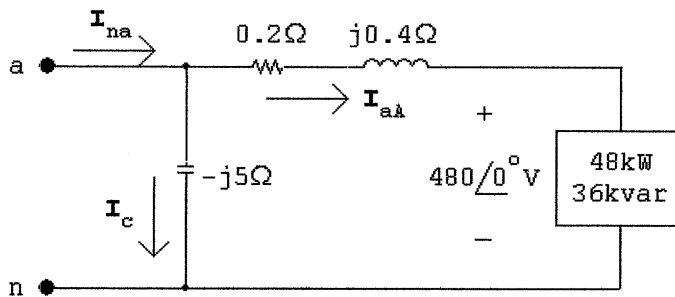
$$\mathbf{V}_{an} = 480 + j0 + (100 - j75)(0.2 + j0.4) = 530 + j25 \text{ V}$$



$$\mathbf{I}_C = \frac{530 + j25}{-j5} = -5 + j106 \text{ A}$$

$$\mathbf{I}_{na} = \mathbf{I}_{aA} + \mathbf{I}_C = 95 + j31 = 99.93/18.07^\circ \text{ A}$$

$$[b] S_{g/\phi} = (530 + j25)(95 - j31) = 51,125 - j14,055 \text{ VA}$$

$$S_{gT} = 3S_{g/\phi} = 153,375 - j42,165 \text{ VA}$$

Therefore, the source is delivering 153,375 W and absorbing 42,165 vars.


$$[c] P_{\text{del}} = 153,375 \text{ W}$$

$$\begin{aligned} P_{\text{abs}} &= 3(48,000) + 3|\mathbf{I}_{aA}|^2(0.2) = 144,000 + 9375 \\ &= 153,375 \text{ W} = P_{\text{del}} \end{aligned}$$

$$[d] Q_{\text{del}} = 3|\mathbf{I}_C|^2(5) = 168,915 \text{ VAR}$$

$$\begin{aligned} Q_{\text{abs}} &= 3(36,000) + 42,165 + 3|\mathbf{I}_{aA}|^2(0.4) \\ &= 168,915 \text{ VAR} = Q_{\text{del}} \end{aligned}$$

P 11.35 [a]

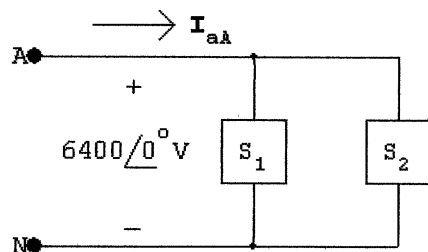

$$S_1 = \frac{1}{3}(1800)(0.96 - j0.28) = 576 - j168 \text{ kVA}$$


$$S_2 = \frac{1}{3}(192 + j1464) = 64 + j488 \text{ kVA}$$

$$S_1 + S_2 = 640 + j320 \text{ kVA}$$

$$\therefore \mathbf{I}_{aA}^* = \frac{(640 + j320)10^3}{6400} = 100 + j50$$


$$\mathbf{I}_{aA} = 100 - j50 \text{ A}$$
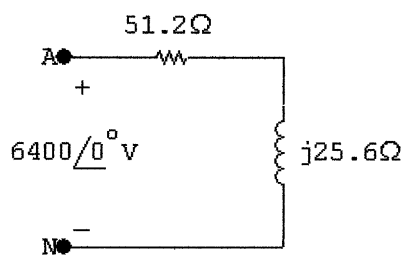
$$Z = \frac{6400}{100 - j50} = 51.2 + j25.6 \Omega$$



$$[\text{b}] \quad R = \frac{(6400)^2}{640 \times 10^3} = 64 \Omega$$
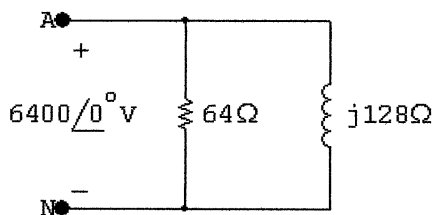
$$X_L = \frac{(6400)^2}{320 \times 10^3} = 128 \Omega$$




P 11.36 Assume a Δ -connect load (series):

$$S_\phi = \frac{1}{3}(190.44 \times 10^3)(0.8 - j0.6) = 50,784 - j38,088 \text{ VA}$$


$$Z_{\Delta\phi}^* = \frac{|13,800|^2}{50,784 - j38,088} = 3000/36.87^\circ \Omega$$
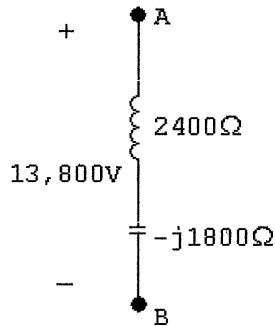
$$Z_{\Delta\phi} = 3000/-36.87^\circ = 2400 - j1800 \Omega$$



Now assume a Y-connected load (series):
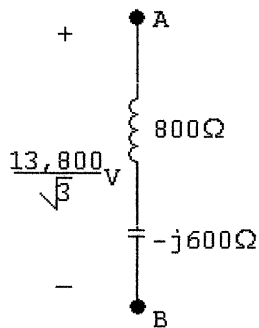
$$Z_{Y\phi} = \frac{1}{3}Z_{\Delta\phi} = 800 - j600 \Omega$$




Now assume a Δ -connected load (parallel):

$$P_\phi = \frac{|13,800|^2}{R_\Delta}$$

$$R_{\Delta\phi} = \frac{|13,800|^2}{50,784} = 3750 \Omega$$

$$Q_\phi = \frac{|13,800|^2}{X_\Delta}$$


$$X_{\Delta\phi} = \frac{|13,800|^2}{-38,088} = -5000 \Omega$$

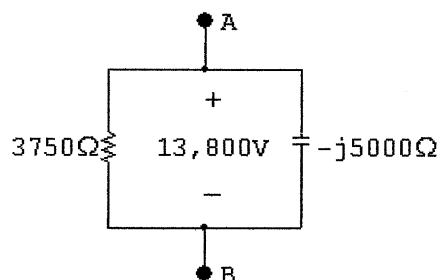

Now assume a Y-connected load (parallel):

$$R_{Y\phi} = \frac{1}{3}R_{\Delta\phi} = 1250 \Omega$$

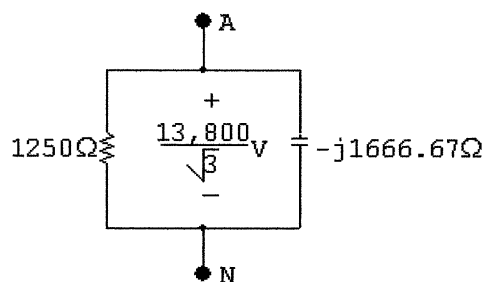
$$X_{Y\phi} = \frac{1}{3}X_{\Delta\phi} = -1666.67 \Omega$$



P 11.37 $S_{g/\phi} = \frac{1}{3}(78)(0.8 - j0.6) \times 10^3 = 20,800 - j15,600 \text{ VA}$

$$\mathbf{I}_{aA}^* = \frac{20,800 - j15,600}{208} = 100 - j75 \text{ A}$$
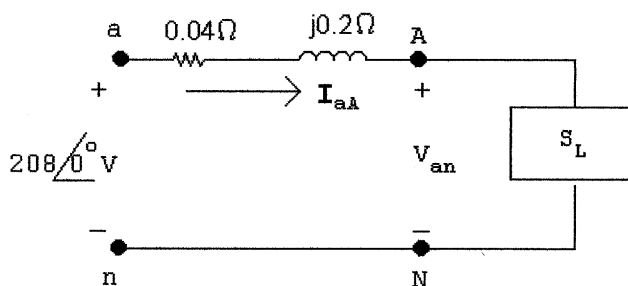
$$\mathbf{I}_{aA} = 100 + j75 \text{ A}$$



$$\mathbf{V}_{AN} = 208 - (100 + j75)(0.04 + j0.20)$$

$$= 219 - j23 = 220.20 \angle -6^\circ \text{ V}$$

$$|V_{AB}| = \sqrt{3}(220.20) = 381.41 \text{ V}$$

$$[b] S_{L/\phi} = (219 - j23)(100 - j75) = 20,175 - j18,725 \text{ VA}$$

$$S_L = 3S_{L/\phi} = 60,525 - j56,175 \text{ VA}$$

Check:

$$S_g = 3(20,800 - j15,600) = 62,400 - j46,800 \text{ VA}$$


$$P_\ell = 3|I_{aA}|^2(0.04) = 1875 \text{ W}$$

$$P_g = P_L + P_\ell = 60,525 + 1875 = 62,400 \text{ W} \quad (\text{checks})$$

$$Q_\ell = 3|I_{aA}|^2(0.20) = 9375 \text{ VAR}$$

$$Q_g = Q_L + Q_\ell = -56,175 + 9375 = -46,800 \text{ VAR} \quad (\text{checks})$$

P 11.38 [a]

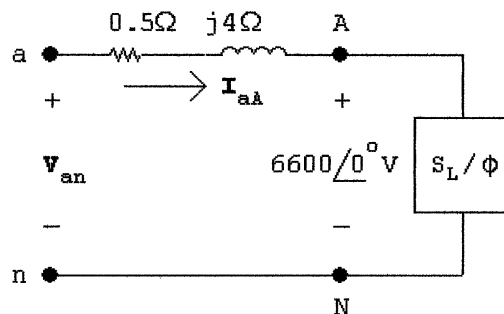

$$S_{L/\phi} = \frac{1}{3} \left[1188 + j \frac{1188}{0.6} (0.8) \right] 10^3 = 396,000 + j528,000 \text{ VA}$$


$$I_{aA}^* = \frac{396,000 + j528,000}{6600} = 60 + j80 \text{ A}$$

$$I_{aA} = 60 - j80 \text{ A}$$

$$\begin{aligned} V_{an} &= 6600 + (60 - j80)(0.5 + j4) \\ &= 6950 + j200 = 6952.88 / 1.65^\circ \text{ V} \end{aligned}$$

$$|V_{ab}| = \sqrt{3}(6952.88) = 12,042.74 \text{ V}$$

[b]

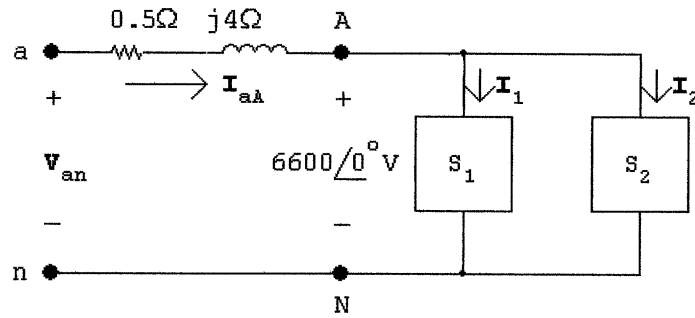

$$\mathbf{I}_1 = 60 - j80 \text{ A} \quad (\text{from part [a]})$$

$$S_2 = 0 - j\frac{1}{3}(1920) \times 10^3 = -j640,000 \text{ VAR}$$

$$\mathbf{I}_2^* = \frac{-j640,000}{6600} = -j96.97 \text{ A}$$

$$\therefore \mathbf{I}_2 = j96.97 \text{ A}$$

$$\mathbf{I}_{aA} = 60 - j80 + j96.97 = 60 + j16.97 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= 6600 + (60 + j16.97)(0.5 + j4) \\ &= 6562.12 + j248.485 = 6566.82 \angle 2.17^\circ \text{ V} \end{aligned}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(6566.82) = 11,374.07 \text{ V}$$

$$[c] \quad |\mathbf{I}_{aA}| = 100 \text{ A}$$

$$P_{\text{loss}/\phi} = (100)^2(0.5) = 5000 \text{ W}$$

$$P_{g/\phi} = 396,000 + 5000 = 401 \text{ kW}$$

$$\% \eta = \frac{396}{401}(100) = 98.75\%$$

$$[d] \quad |\mathbf{I}_{aA}| = 62.354 \text{ A}$$

$$P_{\ell/\phi} = (3887.98)(0.5) = 1943.99 \text{ W}$$

$$\% \eta = \frac{396,000}{397,944}(100) = 99.51\%$$

$$[e] \quad Z_{\text{cap}/Y} = -j\frac{6600}{96.97} = -j68.062 \Omega$$

$$Z_{\text{cap}/\Delta} = 3Z_{\text{cap}/Y} = -j204.187 \Omega$$

$$\therefore \frac{1}{\omega C} = 204.187; \quad C = \frac{1}{(204.187)(120\pi)} = 12.99 \mu\text{F}$$

P 11.39 [a] From Assessment Problem 11.9, $\mathbf{I}_{aA} = (159.88 - j119.91) \text{ A}$

Therefore $\mathbf{I}_{\text{cap}} = j119.91 \text{ A}$

$$\text{Therefore } Z_{CY} = \frac{4160/\sqrt{3}}{j119.91} = -j20.03 \Omega$$

$$\text{Therefore } C_Y = \frac{1}{(20.03)(2\pi)(60)} = 132.43 \mu\text{F}$$

$$Z_{C\Delta} = (-j20.03)(3) = -j60.09 \Omega$$

$$\text{Therefore } C_{\Delta} = \frac{132.43}{3} = 44.14 \mu\text{F}$$

$$[\text{b}] C_Y = 132.43 \mu\text{F}$$

$$[\text{c}] |\mathbf{I}_{aA}| = 159.88 \text{ A}$$

$$\text{P 11.40 } Z_{\phi} = |Z|/\underline{\theta} = \frac{\mathbf{V}_{AN}}{\mathbf{I}_{aA}}$$

$$\theta = \angle \mathbf{V}_{AN} - \angle \mathbf{I}_{aA}$$

$$\theta_1 = \angle \mathbf{V}_{AB} - \angle \mathbf{I}_{aA}$$

For a positive phase sequence,

$$\angle \mathbf{V}_{AB} = \angle \mathbf{V}_{AN} + 30^\circ$$

Thus,

$$\theta_1 = \angle \mathbf{V}_{AN} + 30^\circ - \angle \mathbf{I}_{aA} = \theta + 30^\circ$$

Similarly,

$$Z_{\phi} = |Z|/\underline{\theta} = \frac{\mathbf{V}_{CN}}{\mathbf{I}_{cC}}$$

$$\theta = \angle \mathbf{V}_{CN} - \angle \mathbf{I}_{cC}$$

$$\theta_2 = \angle \mathbf{V}_{CB} - \angle \mathbf{I}_{cC}$$

For a positive phase sequence,

$$\angle \mathbf{V}_{CB} = \angle \mathbf{V}_{BA} - 120^\circ = \angle \mathbf{V}_{AB} + 60^\circ$$

$$\angle \mathbf{I}_{cC} = \angle \mathbf{I}_{aA} + 120^\circ$$

Thus,

$$\begin{aligned} \theta_2 &= \angle \mathbf{V}_{AB} + 60^\circ - \angle \mathbf{I}_{aA} + 120^\circ = \theta_1 - 60^\circ \\ &= \theta + 30^\circ - 60^\circ = \theta - 30^\circ \end{aligned}$$

$$\text{P 11.41 } W_{m1} = |\mathbf{V}_{AB}| |\mathbf{I}_{aA}| \cos(\angle \mathbf{V}_{AB} - \angle \mathbf{I}_{aA}) = (199.58)(2.4) \cos(65.68^\circ) = 197.26 \text{ W}$$

$$W_{m2} = |\mathbf{V}_{CB}| |\mathbf{I}_{cC}| \cos(\angle \mathbf{V}_{CB} - \angle \mathbf{I}_{cC}) = (199.58)(2.4) \cos(5.68^\circ) = 476.64 \text{ W}$$

$$\text{CHECK: } W_1 + W_2 = 673.9 = (2.4)^2(39)(3) = 673.9 \text{ W}$$

$$\text{P 11.42 [a] } W_2 - W_1 = V_L I_L [\cos(\theta - 30^\circ) - \cos(\theta + 30^\circ)]$$

$$= V_L I_L [\cos \theta \cos 30^\circ + \sin \theta \sin 30^\circ \\ - \cos \theta \cos 30^\circ + \sin \theta \sin 30^\circ]$$

$$= 2V_L I_L \sin \theta \sin 30^\circ = V_L I_L \sin \theta,$$

$$\text{therefore } \sqrt{3}(W_2 - W_1) = \sqrt{3}V_L I_L \sin \theta = Q_T$$

$$\text{[b] } Z_\phi = (8 + j6) \Omega$$

$$Q_T = \sqrt{3}[2476.25 - 979.75] = 2592 \text{ VAR},$$

$$Q_T = 3(12)^2(6) = 2592 \text{ VAR};$$

$$Z_\phi = (8 - j6) \Omega$$

$$Q_T = \sqrt{3}[979.75 - 2476.25] = -2592 \text{ VAR},$$

$$Q_T = 3(12)^2(-6) = -2592 \text{ VAR};$$

$$Z_\phi = 5(1 + j\sqrt{3}) \Omega$$

$$Q_T = \sqrt{3}[2160 - 0] = 3741.23 \text{ VAR},$$

$$Q_T = 3(12)^2(5\sqrt{3}) = 3741.23 \text{ VAR};$$

$$Z_\phi = 10/\underline{75^\circ} \Omega$$

$$Q_T = \sqrt{3}[-645.53 - 1763.63] = -4172.79 \text{ VAR},$$

$$Q_T = 3(12)^2[-10 \sin 75^\circ] = -4172.79 \text{ VAR}$$

$$\text{P 11.43 } \mathbf{I}_{aA} = \frac{\mathbf{V}_{AN}}{Z_\phi} = |\mathbf{I}_L| \angle -\theta_\phi \text{ A},$$

$$Z_\phi = |Z| \angle \theta_\phi, \quad \mathbf{V}_{BC} = |\mathbf{V}_L| \angle -90^\circ \text{ V},$$

$$W_m = |\mathbf{V}_L| |\mathbf{I}_L| \cos[-90^\circ - (-\theta_\phi)]$$

$$= |\mathbf{V}_L| |\mathbf{I}_L| \cos(\theta_\phi - 90^\circ)$$

$$= |\mathbf{V}_L| |\mathbf{I}_L| \sin \theta_\phi,$$

$$\text{therefore } \sqrt{3}W_m = \sqrt{3}|\mathbf{V}_L| |\mathbf{I}_L| \sin \theta_\phi = Q_{\text{total}}$$

P 11.44 [a] $Z = 96 + j72 = 120/\underline{36.87^\circ} \Omega$

$$\mathbf{V}_{AN} = 720/\underline{0^\circ} \text{ V}; \quad \therefore \mathbf{I}_{aA} = 6/\underline{-36.87^\circ} \text{ A}$$

$$\mathbf{V}_{BC} = \mathbf{V}_{BN} - \mathbf{V}_{CN} = 720\sqrt{3}/\underline{-90^\circ} \text{ V}$$

$$W_m = (720\sqrt{3})(6) \cos(-90 + 36.87^\circ) = 4489.48 \text{ W}$$

$$\sqrt{3}W_m = 7776 \text{ VAR}$$

[b] $Q_\phi = (36)(72) = 2592 \text{ VAR}$

$$Q_T = 3Q_\phi = 7776 \text{ VAR} = \sqrt{3}W_m$$

P 11.45 [a] $Z_\phi = 600 + j450 = 750/\underline{36.87^\circ} \Omega$

$$S_\phi = \frac{(69 \times 10^3)^2}{750/\underline{-36.87^\circ}} = 5,078,400 + j3,808,800 \text{ VA}$$

$$S_T = 3S_\phi = 15,235,200 + j11,426,400 \text{ VA}$$

[b] $W_{m1} = (69,000)\sqrt{3}(92) \cos(0 + 66.87^\circ) = 4,318,082.44 \text{ W}$

$$W_{m2} = (69,000)\sqrt{3}(92) \cos(60 - 53.13^\circ) = 10,916,117.56 \text{ W}$$

Check: $P_T = 15,235,200 \text{ W} = W_{m1} + W_{m2}.$

P 11.46 [a] $\mathbf{I}_{aA}^* = \frac{(192 + j56)10^3}{4800} = 41.67/\underline{16.26^\circ} \text{ A}$

$$\mathbf{I}_{aA} = 41.67/\underline{-16.26^\circ} \text{ A}$$

$$\mathbf{I}_{bB} = 41.67/\underline{-136.26^\circ} \text{ A}$$

$$\mathbf{V}_{AB} = 4800\sqrt{3}/\underline{30^\circ} \text{ V}$$

$$\mathbf{V}_{BC} = 4800\sqrt{3}/\underline{-90^\circ} \text{ V}$$

$$W_1 = (4800\sqrt{3})(41.67) \cos 46.26^\circ = 239,502.58 \text{ W}$$

[b] Current coil in line aA, measure \mathbf{I}_{aA} .
Voltage coil across AC, measure \mathbf{V}_{AC} .

[c] $\mathbf{I}_{aA} = 41.67/\underline{-16.76^\circ} \text{ A}$

$$\mathbf{V}_{CA} = 4800\sqrt{3}/\underline{150^\circ} \text{ V}$$

$$\therefore \mathbf{V}_{AC} = 4800\sqrt{3}/\underline{-30^\circ} \text{ V}$$

$$W_2 = (4800\sqrt{3})(41.67) \cos 13.74^\circ = 336,497.42 \text{ W}$$

$$[d] W_1 + W_2 = 576,000 = 576 \text{ kW}$$

$$P_T = 600(0.96) = 576 \text{ kW} = W_1 + W_2$$

$$P 11.47 [a] W_1 = |\mathbf{V}_{BA}| |\mathbf{I}_{bB}| \cos \theta$$

Positive phase sequence, using the equivalent Y-connected load impedances:

$$\mathbf{V}_{BA} = 480\sqrt{3}/-150^\circ \text{ V}$$

$$\mathbf{I}_{aA} = \frac{480/0^\circ}{20/30^\circ} = 24/-30^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 24/-150^\circ \text{ A}$$

$$W_1 = (24)(480)\sqrt{3} \cos 0^\circ = 19,953.23 \text{ W}$$

$$W_2 = |\mathbf{V}_{CA}| |\mathbf{I}_{cC}| \cos \theta$$

$$\mathbf{V}_{CA} = 480\sqrt{3}/150^\circ \text{ V}$$

$$\mathbf{I}_{cC} = 24/90^\circ \text{ A}$$

$$W_2 = (24)(480)\sqrt{3} \cos 60^\circ = 9976.61 \text{ W}$$

$$[b] P_\phi = (24)^2(20) \cos 30^\circ = 5760\sqrt{3} \text{ W}$$

$$P_T = 3P_\phi = 17,280\sqrt{3} \text{ W}$$

$$W_1 + W_2 = 11,520\sqrt{3} + 5760\sqrt{3} = 17,280\sqrt{3} \text{ W}$$

$$\therefore W_1 + W_2 = P_T \quad (\text{checks})$$

$$P 11.48 [a] \text{ Negative phase sequence:}$$

$$\mathbf{V}_{AB} = 480\sqrt{3}/-30^\circ \text{ V}$$

$$\mathbf{V}_{BC} = 480\sqrt{3}/90^\circ \text{ V}$$

$$\mathbf{V}_{CA} = 480\sqrt{3}/-150^\circ \text{ V}$$

$$\mathbf{I}_{AB} = \frac{480\sqrt{3}/-30^\circ}{60/-30^\circ} = 8\sqrt{3}/0^\circ \text{ A}$$

$$\mathbf{I}_{BC} = \frac{480\sqrt{3}/90^\circ}{24/30^\circ} = 20\sqrt{3}/60^\circ \text{ A}$$

$$\mathbf{I}_{CA} = \frac{480\sqrt{3}/-150^\circ}{80/0^\circ} = 6\sqrt{3}/-150^\circ \text{ A}$$

$$\begin{aligned}\mathbf{I}_{aA} &= \mathbf{I}_{AB} + \mathbf{I}_{AC} \\ &= 8\sqrt{3}/0^\circ + 6\sqrt{3}/30^\circ = 23.44/12.81^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_{cC} &= \mathbf{I}_{CB} + \mathbf{I}_{CA} \\ &= 20\sqrt{3}/-120^\circ + 6\sqrt{3}/-150^\circ = 43.95/-126.79^\circ \text{ A}\end{aligned}$$

$$W_{m1} = 480\sqrt{3}(23.44) \cos(-30 - 12.81^\circ) = 14,296.61 \text{ W}$$

$$W_{m2} = 480\sqrt{3}(43.95) \cos(-90 + 126.79^\circ) = 29,261.53 \text{ W}$$

$$[\mathbf{b}] \quad W_{m1} + W_{m2} = 43,558.14 \text{ W}$$

$$P_A = (8\sqrt{3})^2(60 \cos 30^\circ) = 9976.61 \text{ W}$$

$$P_B = (20\sqrt{3})^2(24 \cos 30^\circ) = 24,941.53 \text{ W}$$

$$P_C = (6\sqrt{3})^2(80) = 8640 \text{ W}$$

$$P_A + P_B + P_C = 43,558.14 = W_{m1} + W_{m2}$$

$$\text{P 11.49} \quad \tan \phi = \frac{\sqrt{3}(W_2 - W_1)}{W_1 + W_2} = \frac{873,290.66}{732,777.88} = 1.1918$$

$$\therefore \phi = 50^\circ$$

$$\therefore 7600\sqrt{3}|\mathbf{I}_L| \cos 80^\circ = 114,291.64$$

$$|\mathbf{I}_L| = 50 \text{ A}$$

$$|Z| = \frac{7600}{50} = 152 \Omega \quad \therefore Z = 152/50^\circ \Omega$$

$$\text{P 11.50} \quad [\mathbf{a}] \quad Z = 276 - j207 = 345/-36.87^\circ \Omega$$

$$\mathbf{I}_{aA} = \frac{6900/0^\circ}{345/-36.87^\circ} = 20/36.87^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 20/-83.13^\circ \text{ A}$$

$$\mathbf{V}_{AC} = 6900\sqrt{3}/-30^\circ \text{ V}$$

$$\mathbf{V}_{BC} = 6900\sqrt{3}/-90^\circ \text{ V}$$

$$W_1 = (6900\sqrt{3})(20) \cos(-30 - 36.87^\circ) = 93,893.10 \text{ W}$$

$$W_2 = (6900\sqrt{3})(20) \cos(-90 + 83.13^\circ) = 237,306.90 \text{ W}$$

$$[b] \quad W_1 + W_2 = 331,200 \text{ W}$$

$$P_T = 3(20)^2(276) = 331,200 \text{ W}$$

$$[c] \quad \sqrt{3}(W_1 - W_2) = -248,400 \text{ VAR}$$

$$Q_T = 3(20)^2(-207) = -248,400 \text{ VAR}$$

P 11.51 From the solution to Prob. 11.21 we have

$$\mathbf{I}_{aA} = 145.88 / -24.28^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_{bB} = 134.01 / 178.04^\circ \text{ A}$$

$$[a] \quad W_1 = |\mathbf{V}_{ac}| |\mathbf{I}_{aA}| \cos(\theta_{ac} - \theta_{aA}) \\ = 720(145.88) \cos(-60^\circ + 24.28^\circ) = 85,274.70 \text{ W}$$

$$[b] \quad W_2 = |\mathbf{V}_{bc}| |\mathbf{I}_{bB}| \cos(\theta_{bc} - \theta_{bB}) \\ = 720(134.01) \cos(-120^\circ - 178.04^\circ) = 45,357.50 \text{ W}$$

$$[c] \quad W_1 + W_2 = 130,632 \text{ W}$$

$$P_{AB} = (144)^2(4.8) = 99,532.8 \text{ W}$$


$$P_{BC} = (36)^2(16) = 20,736 \text{ W}$$

$$P_{CA} = (20.36)^2(25) = 10,363.2 \text{ W}$$


$$P_{AB} + P_{BC} + P_{CA} = 130,632$$

$$\text{therefore } W_1 + W_2 = P_{\text{total}}$$


P 11.52 [a]

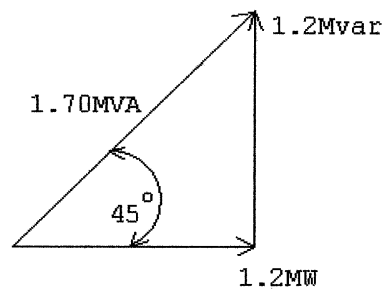


[b]

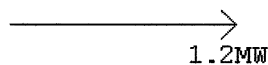

[c]

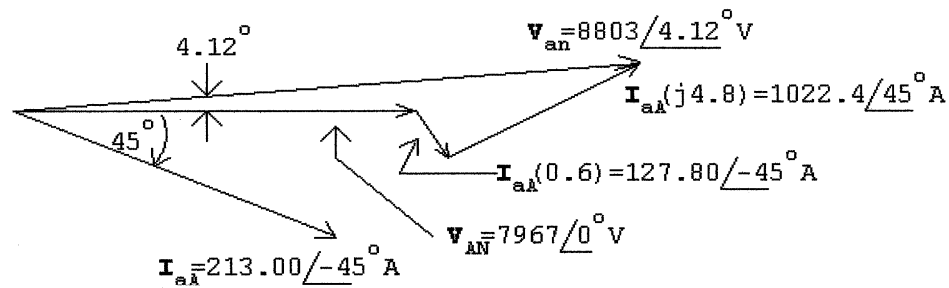

[d]

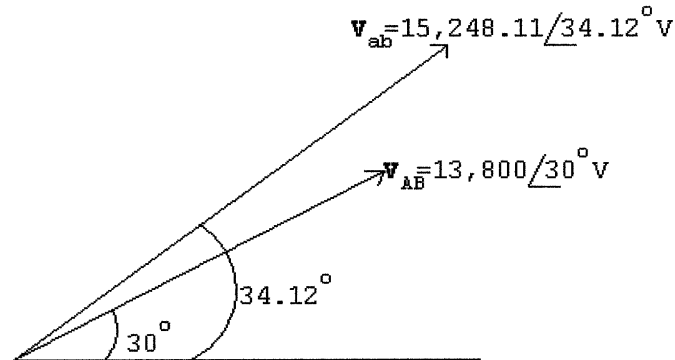

P 11.53 [a] $Q = \frac{|V|^2}{X_C}$

$$\therefore |X_C| = \frac{(13,800)^2}{1.2 \times 10^6} = 158.70 \Omega$$

$$\therefore \frac{1}{\omega C} = 158.70; \quad C = \frac{1}{2\pi(60)(158.70)} = 16.71 \mu\text{F}$$

[b] $|X_C| = \frac{(13,800/\sqrt{3})^2}{1.2 \times 10^6} = \frac{1}{3}(158.70)$

$$\therefore C = 3(16.71) = 50.14 \mu\text{F}$$

P 11.54 If the capacitors remain connected when the substation drops its load, the expression for the line current becomes

$$\frac{13,800}{\sqrt{3}} \mathbf{I}_{aA}^* = -j1.2 \times 10^6$$

or $\mathbf{I}_{aA}^* = -j150.61 \text{ A}$

Hence $\mathbf{I}_{aA} = j150.61 \text{ A}$

Now,

$$\mathbf{V}_{an} = \frac{13,800}{\sqrt{3}} \angle 0^\circ + (0.6 + j4.8)(j150.61) = 7244.49 + j90.37 = 7245.05 \angle 0.71^\circ \text{ V}$$

The magnitude of the line-to-line voltage at the generating plant is

$$|V_{ab}| = \sqrt{3}(7245.05) = 12,548.80 \text{ V.}$$

This is a problem because the voltage is below the acceptable minimum of 13 kV. Thus when the load at the substation drops off, the capacitors must be switched off.

P 11.55 Before the capacitors are added the total line loss is

$$P_L = 3|150.61 + j150.61|^2(0.6) = 81.66 \text{ kW}$$

After the capacitors are added the total line loss is

$$P_L = 3|150.61|^2(0.6) = 40.83 \text{ kW}$$

Note that adding the capacitors to control the voltage level also reduces the amount of power loss in the lines, which in this example is cut in half.

P 11.56 [a] $\frac{13,800}{\sqrt{3}} \mathbf{I}_{aA}^* = 80 \times 10^3 + j200 \times 10^3 - j1200 \times 10^3$

$$\mathbf{I}_{aA}^* = \frac{80\sqrt{3} - j1000\sqrt{3}}{13.8} = 10.04 - j125.51 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = 10.04 + j125.51 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= \frac{13,800}{\sqrt{3}} \angle 0^\circ + (0.6 + j4.8)(10.04 + j125.51) \\ &= 7371.01 + j123.50 = 7372.04 \angle 0.96^\circ \text{ V} \end{aligned}$$

$$\therefore |V_{ab}| = \sqrt{3}(7372.04) = 12,768.75 \text{ V}$$

[b] Yes, the magnitude of the line-to-line voltage at the power plant is less than the allowable minimum of 13 kV.

P 11.57 [a] $\frac{13,800}{\sqrt{3}} \mathbf{I}_{aA}^* = (80 + j200) \times 10^3$

$$\mathbf{I}_{aA}^* = \frac{80\sqrt{3} + j200\sqrt{3}}{13.8} = 10.04 + j25.1 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = 10.04 - j25.1 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= \frac{13,800}{\sqrt{3}} \angle 0^\circ + (0.6 + j4.8)(10.04 - j25.1) \\ &= 8093.95 + j33.13 = 8094.02 \angle 0.23^\circ \text{ V} \end{aligned}$$

$$\therefore |V_{ab}| = \sqrt{3}(8094.02) = 14,019.25 \text{ V}$$

[b] Yes: $13 \text{ kV} < 14,019.25 < 14.6 \text{ kV}$

[c] $P_{\text{loss}} = 3|10.04 + j125.51|^2(0.6) = 28.54 \text{ kW}$

[d] $P_{\text{loss}} = 3|10.04 + j25.1|^2(0.6) = 1.32 \text{ kW}$

[e] Yes, the voltage at the generating plant is at an acceptable level and the line loss is greatly reduced.