

# Sinusoidal Steady State Power Calculations

## Assessment Problems

AP 10.1 [a]  $\mathbf{V} = 100/\underline{-45^\circ} \text{ V}, \quad \mathbf{I} = 20/\underline{15^\circ} \text{ A}$

Therefore

$$P = \frac{1}{2}(100)(20) \cos[-45 - (15)] = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin -60^\circ = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

[b]  $\mathbf{V} = 100/\underline{-45^\circ}, \quad \mathbf{I} = 20/\underline{165^\circ}$

$$P = 1000 \cos(-210^\circ) = -866.03 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-210^\circ) = 500 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

[c]  $\mathbf{V} = 100/\underline{-45^\circ}, \quad \mathbf{I} = 20/\underline{-105^\circ}$

$$P = 1000 \cos(60^\circ) = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin(60^\circ) = 866.03 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

[d]  $\mathbf{V} = 100/\underline{0^\circ}, \quad \mathbf{I} = 20/\underline{120^\circ}$

$$P = 1000 \cos(-120^\circ) = -500 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-120^\circ) = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

AP 10.2

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos[15 - (75)] = \cos(-60^\circ) = 0.5 \text{ leading}$$

$$\text{rf} = \sin(\theta_v - \theta_i) = \sin(-60^\circ) = -0.866$$

AP 10.3

From Ex. 9.4  $I_{\text{eff}} = \frac{I_{\rho}}{\sqrt{3}} = \frac{0.18}{\sqrt{3}} \text{ A}$

$$P = I_{\text{eff}}^2 R = \left( \frac{0.0324}{3} \right) (5000) = 54 \text{ W}$$

AP 10.4 [a]  $Z = (39 + j26) \parallel (-j52) = 48 - j20 = 52 / -22.62^\circ \Omega$ 

Therefore  $\mathbf{I}_{\ell} = \frac{250 / 0^\circ}{48 - j20 + 1 + j4} = 4.85 / 18.08^\circ \text{ A(rms)}$

$$\mathbf{V}_L = \mathbf{Z} \mathbf{I}_{\ell} = (52 / -22.62^\circ) (4.85 / 18.08^\circ) = 252.20 / -4.54^\circ \text{ V(rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{39 + j26} = 5.38 / -38.23^\circ \text{ A(rms)}$$

[b]  $S_L = \mathbf{V}_L \mathbf{I}_L^* = (252.20 / -4.54^\circ) (5.38 / +38.23^\circ) = 1357 / 33.69^\circ$   
 $= (1129.09 + j752.73) \text{ VA}$

$$P_L = 1129.09 \text{ W}; \quad Q_L = 752.73 \text{ VAR}$$

[c]  $P_{\ell} = |\mathbf{I}_{\ell}|^2 1 = (4.85)^2 \cdot 1 = 23.52 \text{ W}; \quad Q_{\ell} = |\mathbf{I}_{\ell}|^2 4 = 94.09 \text{ VAR}$

[d]  $S_g(\text{delivering}) = 250 \mathbf{I}_{\ell}^* = (1152.62 - j376.36) \text{ VA}$

Therefore the source is delivering 1152.62 W and absorbing 376.36 magnetizing VAR.

[e]  $Q_{\text{cap}} = \frac{|\mathbf{V}_L|^2}{-52} = \frac{(252.20)^2}{-52} = -1223.18 \text{ VAR}$

Therefore the capacitor is delivering 1223.18 magnetizing VAR.

Check:  $94.09 + 752.73 + 376.36 = 1223.18 \text{ VAR}$  and  
 $1129.09 + 23.52 = 1152.62 \text{ W}$

AP 10.5 Series circuit derivation:

$$S = 250 \mathbf{I}^* = (40,000 - j30,000)$$

Therefore  $\mathbf{I}^* = 160 - j120 = 200 / -36.87^\circ \text{ A(rms)}$

$$\mathbf{I} = 200 / 36.87^\circ \text{ A(rms)}$$

$$Z = \frac{\mathbf{V}}{\mathbf{I}} = \frac{250}{200 / 36.87^\circ} = 1.25 / -36.87^\circ = (1 - j0.75) \Omega$$

Therefore  $R = 1 \Omega, \quad X_C = -0.75 \Omega$

Parallel circuit derivation

$$P = \frac{(250)^2}{R}; \quad \text{therefore} \quad R = \frac{(250)^2}{40,000} = 1.5625 \Omega$$

$$Q = \frac{(250)^2}{X_C}; \quad \text{therefore} \quad X_C = \frac{(250)^2}{-30,000} = -2.083 \Omega$$

AP 10.6

$$S_1 = 15,000(0.6) + j15,000(0.8) = 9000 + j12,000 \text{ VA}$$

$$S_2 = 6000(0.8) - j6000(0.6) = 4800 - j3600 \text{ VA}$$


$$S_T = S_1 + S_2 = 13,800 + j8400 \text{ VA}$$

$$S_T = 200\mathbf{I}^*; \quad \text{therefore} \quad \mathbf{I}^* = 69 + j42 \quad \mathbf{I} = 69 - j42 \text{ A}$$


$$\mathbf{V}_s = 200 + j\mathbf{I} = 200 + j69 + 42 = 242 + j69 = 251.64/\underline{15.91^\circ} \text{ V(rms)}$$

AP 10.7 [a] The phasor domain equivalent circuit and the Thévenin equivalent are shown below:

Phasor domain equivalent circuit:

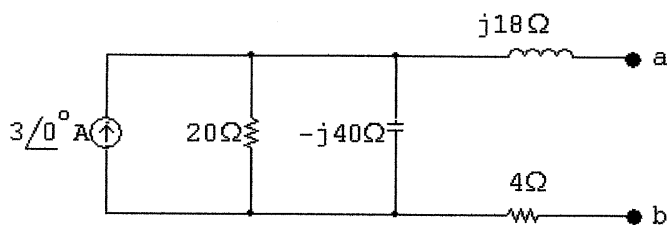

Thévenin equivalent:

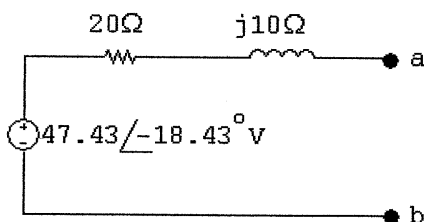

$$\mathbf{V}_{Th} = 3 \frac{-j800}{20 - j40} = 48 - j24 = 53.67/\underline{-26.57^\circ} \text{ V}$$

$$\mathbf{Z}_{Th} = 4 + j18 + \frac{-j800}{20 - j40} = 20 + j10 = 22.36/\underline{26.57^\circ} \Omega$$

For maximum power transfer,  $\mathbf{Z}_L = (20 - j10) \Omega$

$$[b] \mathbf{I} = \frac{53.67 / -26.57^\circ}{40} = 1.34 / -26.57^\circ \text{ A}$$


$$\text{Therefore } P = \left( \frac{1.34}{\sqrt{2}} \right)^2 20 = 17.96 \text{ W}$$

$$[c] R_L = |Z_{Th}| = 22.36 \Omega$$

$$[d] \mathbf{I} = \frac{53.67 / -26.57^\circ}{42.36 + j10} = 1.23 / -39.85^\circ \text{ A}$$

$$\text{Therefore } P = \left( \frac{1.23}{\sqrt{2}} \right)^2 (22.36) = 17 \text{ W}$$

AP 10.8

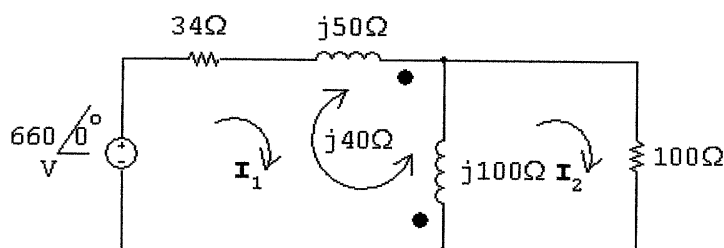

Mesh current equations:


$$660 = (34 + j50)\mathbf{I}_1 + j100(\mathbf{I}_1 - \mathbf{I}_2) + j40\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = j100(\mathbf{I}_2 - \mathbf{I}_1) - j40\mathbf{I}_1 + 100\mathbf{I}_2$$

Solving,

$$\mathbf{I}_2 = 3.5 / 0^\circ \text{ A}; \quad \therefore P = \frac{1}{2}(3.5)^2(100) = 612.50 \text{ W}$$

AP 10.9 [a]

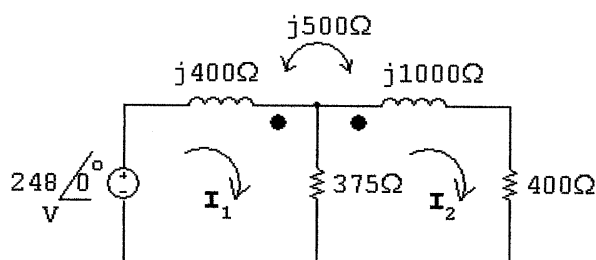

$$248 = j400\mathbf{I}_1 - j500\mathbf{I}_2 + 375(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 375(\mathbf{I}_2 - \mathbf{I}_1) + j1000\mathbf{I}_2 - j500\mathbf{I}_1 + 400\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 0.80 - j0.62 \text{ A}; \quad \mathbf{I}_2 = 0.4 - j0.3 = 0.5 / -36.87^\circ$$

$$\therefore P = \frac{1}{2}(0.25)(400) = 50 \text{ W}$$

$$[b] \mathbf{I}_1 - \mathbf{I}_2 = 0.4 - j0.32 \text{ A}$$

$$P_{375} = \frac{1}{2} |\mathbf{I}_1 - \mathbf{I}_2|^2 (375) = 49.20 \text{ W}$$

$$[c] P_g = \frac{1}{2} (248)(0.8) = 99.20 \text{ W}$$

$$\sum P_{\text{abs}} = 50 + 49.2 = 99.20 \text{ W} \quad (\text{checks})$$

AP 10.10 [a]  $V_{\text{Th}} = 210 \text{ V}; \quad \mathbf{V}_2 = \frac{1}{4} \mathbf{V}_1; \quad \mathbf{I}_1 = \frac{1}{4} \mathbf{I}_2$   
Short circuit equations:

$$840 = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2$$

$$\therefore \mathbf{I}_2 = 14 \text{ A}; \quad R_{\text{Th}} = \frac{210}{14} = 15 \Omega$$

$$[b] P_{\text{max}} = \left( \frac{210}{30} \right)^2 15 = 735 \text{ W}$$

AP 10.11 [a]  $\mathbf{V}_{\text{Th}} = -4(146/\underline{0^\circ}) = -584/\underline{0^\circ} \text{ V(rms)}$

$$\mathbf{V}_2 = 4\mathbf{V}_1; \quad \mathbf{I}_1 = -4\mathbf{I}_2$$

Short circuit equations:

$$146/\underline{0^\circ} = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2$$


$$\therefore \mathbf{I}_2 = -146/365 = -0.40 \text{ A}; \quad R_{\text{Th}} = \frac{-584}{-0.4} = 1460 \Omega$$

$$[b] P = \left( \frac{-584}{2920} \right)^2 1460 = 58.40 \text{ W}$$
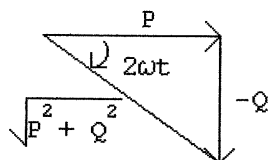
## Problems

P 10.1  $p = P + P \cos 2\omega t - Q \sin 2\omega t; \quad \frac{dp}{dt} = -2\omega P \sin 2\omega t - 2\omega Q \cos 2\omega t$

$$\frac{dp}{dt} = 0 \quad \text{when} \quad -2\omega P \sin 2\omega t = 2\omega Q \cos 2\omega t \quad \text{or} \quad \tan 2\omega t = -\frac{Q}{P}$$



$$\cos 2\omega t = \frac{P}{\sqrt{P^2 + Q^2}}; \quad \sin 2\omega t = -\frac{Q}{\sqrt{P^2 + Q^2}}$$

Let  $\theta = \tan^{-1}(-Q/P)$ , then  $p$  is maximum when  $2\omega t = \theta$  and  $p$  is minimum when  $2\omega t = (\theta + \pi)$ .

$$\text{Therefore } p_{\max} = P + P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - \frac{Q(-Q)}{\sqrt{P^2 + Q^2}} = P + \sqrt{P^2 + Q^2}$$

$$\text{and } p_{\min} = P - P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - Q \cdot \frac{Q}{\sqrt{P^2 + Q^2}} = P - \sqrt{P^2 + Q^2}$$

P 10.2 [a]  $P = \frac{1}{2}(340)(20) \cos(60 - 15) = 3400 \cos 45^\circ = 2404.16 \text{ W (abs)}$

$$Q = 3400 \sin 45^\circ = 2404.16 \text{ VAR (abs)}$$

[b]  $P = \frac{1}{2}(16)(75) \cos(-15 - 60) = 600 \cos(-75^\circ) = 155.29 \text{ W (abs)}$

$$Q = 600 \sin(-75^\circ) = -579.56 \text{ VAR (del)}$$

[c]  $P = \frac{1}{2}(625)(4) \cos(40 - 150) = 1250 \cos(-110^\circ) = -427.53 \text{ W (del)}$

$$Q = 1250 \sin(-110^\circ) = -1174.62 \text{ VAR (del)}$$

[d]  $P = \frac{1}{2}(180)(10) \cos(130 - 20) = 900 \cos(110^\circ) = -307.82 \text{ W (del)}$

$$Q = 900 \sin(110^\circ) = 845.72 \text{ VAR (abs)}$$

P 10.3 [a] coffee maker = 1200 W    radio = 71 W  
 television = 145 W    portable heater = 1322 W  
 $\Sigma P = 2738 \text{ W}$

Therefore  $I_{\text{eff}} = \frac{2738}{120} = 22.82 \text{ A}$


Yes, the breaker will trip.

[b]  $\Sigma P = 2738 - 1200 = 1538 \text{ W}; \quad I_{\text{eff}} = \frac{1538}{120} = 12.82 \text{ A}$

Yes, the breaker will not trip if the current is reduced to 12.82 A.

P 10.4  $I_g = 30 \angle 0^\circ \text{ mA}; \quad \frac{1}{j\omega C} = \frac{10^6}{j(25 \times 10^3)(40)} = -j1 \Omega$

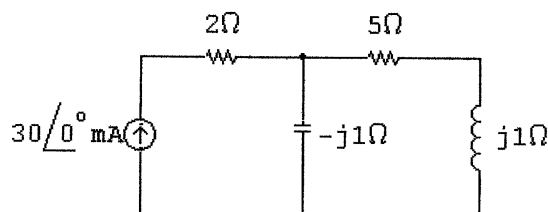$j\omega L = j(25 \times 10^3)(40) \times 10^{-6} = j1 \Omega$



$Z_1 = -j1 \parallel (5 + j1) = 0.2 - j1 \Omega$

$Z_{\text{eq}} = 2 + Z_1 = 2.2 - j1 \Omega$

$P_g = |I_{\text{rms}}|^2 \text{Re}\{Z_{\text{eq}}\} = \left(\frac{30}{\sqrt{2}} \times 10^{-3}\right)^2 (2.2) = 990 \mu\text{W}$

P 10.5  $\frac{1}{\omega C} = \frac{10^9}{(5000)(80)} = 2500 \Omega$

$Z_f = \frac{-j2500(7500)}{7500 - j2500} = 750 - j2250 \Omega$

$Z_i = 1500 \Omega$


$\therefore \frac{Z_f}{Z_i} = \frac{750 - j2250}{1500} = 0.5 - j1.5$

$V_o = -\frac{Z_f}{Z_i} V_g; \quad V_g = 4 \angle 0^\circ \text{ V}$

$$\mathbf{V}_o = (-0.5 + j1.5)(4) = -2 + j6 = 6.32/\underline{108.43^\circ} \text{ V}$$

$$P = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} \frac{(4)(10)}{1000} = 20 \times 10^{-3} = 20 \text{ mW}$$

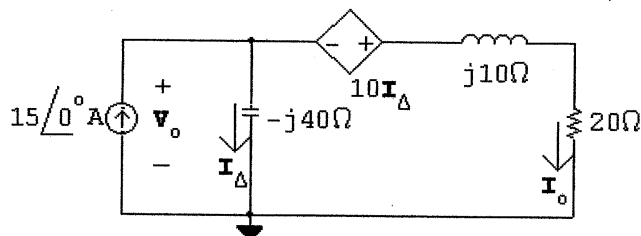P 10.6  $j\omega L = j10,000(10^{-3}) = j10 \Omega$ ;  $\frac{1}{j\omega C} = \frac{10^6}{j10,000(2.5)} = -j40 \Omega$



$$-15 + \frac{\mathbf{V}_o}{-j40} + \frac{\mathbf{V}_o + 10(\mathbf{V}_o / -j40)}{20 + j10} = 0$$

$$\therefore \mathbf{V}_o \left[ \frac{1}{-j40} + \frac{1 + j0.25}{20 + j10} \right] = 15$$

$$\therefore \mathbf{V}_o = 300 - j100 \text{ V}$$


$$\therefore \mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j40} = 2.5 + j7.5 \text{ A}$$

$$\mathbf{I}_o = 15\angle 0^\circ - \mathbf{I}_\Delta = 15 - 2.5 - j7.5 = 12.5 - j7.5 = 14.58/\underline{-30.9^\circ} \text{ A}$$

$$P_{20\Omega} = \frac{1}{2} |\mathbf{I}_o|^2 20 = 2125 \text{ W}$$

P 10.7 [a] line loss = 50,000 - 40,000 = 10 kW

$$\text{line loss} = |\mathbf{I}_g|^2 20 \quad \therefore |\mathbf{I}_g|^2 = 500$$

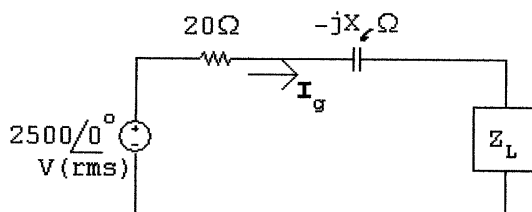


$$|\mathbf{I}_g| = \sqrt{500} \text{ A}$$

$$|\mathbf{I}_g|^2 R_L = 40,000 \quad \therefore R_L = 80 \Omega$$



$$|\mathbf{I}_g|^2 X_L = 30,000 \quad \therefore X_L = 60 \Omega$$

Thus,

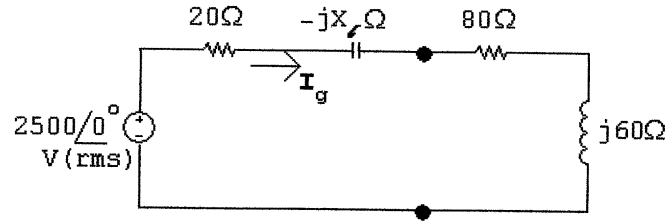

$$|Z| = \sqrt{(100)^2 + (60 - X_\ell)^2} \quad |\mathbf{I}_g| = \frac{2500}{\sqrt{10,000 + (60 - X_\ell)^2}}$$

$$\therefore 10,000 + (60 - X_\ell)^2 = \frac{625 \times 10^4}{500} = 12,500$$

$$\text{Solving,} \quad (60 - X_\ell) = \pm 50.$$

$$\text{Thus, } X_\ell = 10 \Omega \quad \text{or} \quad X_\ell = 110 \Omega$$

[b] If  $X_\ell = 10 \Omega$ :

$$\mathbf{I}_g = \frac{2500}{100 + j50} = 20 - j10 \text{ A}$$

$$S_g = -2500\mathbf{I}_g^* = -50 - j25 \text{ kVA}$$

Thus, the voltage source is delivering 50 KW and 25 magnetizing Kvars.

$$Q_{-j10} = |\mathbf{I}_g|^2 X_\ell = 500(-10) = -5000 \text{ VAR}$$

Therefore the line reactance is generating 5 magnetizing kvars.

$$Q_{j60} = |\mathbf{I}_g|^2 X_L = 500(60) = 30,000 \text{ VAR}$$

Therefore the load reactance is absorbing 30 magnetizing kvars.

$$\sum Q_{\text{gen}} = 25,000 \text{ kVAR} = \sum Q_{\text{abs}}$$

If  $X_\ell = 110 \Omega$ :

$$\mathbf{I}_g = \frac{2500}{100 - j50} = 20 + j10 \text{ A}$$

$$S_g = -2500\mathbf{I}_g^* = -50 + j25 \text{ kVA}$$

Thus, the voltage source is delivering 50 kW and absorbing 25 magnetizing kvars.

$$Q_{-j110} = |\mathbf{I}_g|^2 (-110) = 500(-110) = -55 \text{ kVAR}$$

Therefore the line reactance is generating 55 magnetizing kvars. The load continues to absorb 30 magnetizing kvars.

$$\sum Q_{\text{gen}} = 55 \text{ kVAR} = \sum Q_{\text{abs}}$$

P 10.8 [a]  $P = \frac{1}{2} \frac{(90)^2}{1350} = 3 \text{ W}$

$$Q = \frac{1}{2} \frac{(90)^2}{(1012.5)} = 4 \text{ VAR}$$

$$p_{\max} = P + \sqrt{P^2 + Q^2} = 3 + \sqrt{(3)^2 + (4)^2} = 8 \text{ W (del)}$$

[b]  $p_{\min} = 3 - 5 = -2 \text{ W (abs)}$

[c]  $P = 4 \text{ W}$  from (a)

[d]  $Q = 4 \text{ VAR}$  from (a)

[e] absorb, because  $Q > 0$


[f]  $\text{pf} = \cos(\theta_v - \theta_i)$

$$\mathbf{I} = \frac{90}{1350} + \frac{90}{j1012.5} = 0.0667 - j0.08889 = 111.11 \angle -53.13^\circ \text{ mA}$$

$$\therefore \text{pf} = \cos(0 + 53.13^\circ) = 0.6 \text{ lagging}$$

[g]  $\text{rf} = \sin(53.13^\circ) = 0.8$

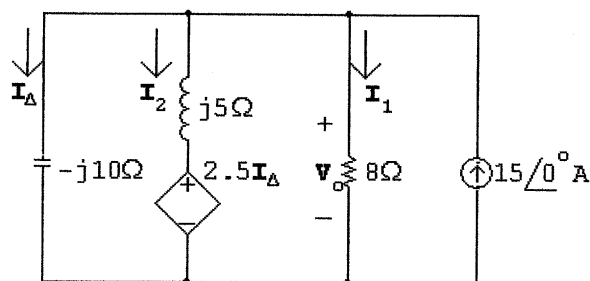P 10.9 [a] From the solution to Problem 9.56 we have:



$$\mathbf{V}_o = 72 + j96 = 120 \angle 53.13^\circ \text{ V}$$

$$S_g = -\frac{1}{2} \mathbf{V}_o \mathbf{I}_g^* = -\frac{1}{2} (72 + j96)(15) = -540 - j720 \text{ VA}$$

Therefore, the independent current source is delivering 540 W and 720 magnetizing vars.

$$\mathbf{I}_1 = \frac{\mathbf{V}_o}{8} = 15 \angle 53.13^\circ \text{ A}$$

$$P_{8\Omega} = \frac{1}{2} (15)^2 (8) = 900 \text{ W}$$

Therefore, the  $8\Omega$  resistor is absorbing 900 W.

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j10} = -9.6 + j7.2 = 12 \angle 143.13^\circ \text{ A}$$

$$Q_{\text{cap}} = \frac{1}{2}(12)^2(-10) = -720 \text{ VAR}$$

Therefore, the  $-j10 \Omega$  capacitor is delivering 720 magnetizing vars.

$$2.5\mathbf{I}_{\Delta} = -24 + j18 \text{ V}$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_o - 2.5\mathbf{I}_{\Delta}}{j5} = \frac{72 + j96 + 24 - j18}{j5}$$

$$= 15.6 - j19.2 \text{ A} = 24.72 \angle -50.91^\circ \text{ A}$$

$$Q_{j5} = \frac{1}{2}|\mathbf{I}_2|^2(5) = 1530 \text{ VAR}$$

Therefore, the  $j5 \Omega$  inductor is absorbing 1530 magnetizing vars.


$$\begin{aligned} S_{2.5\mathbf{I}_{\Delta}} &= \frac{1}{2}(2.5\mathbf{I}_{\Delta})\mathbf{I}_2^* = \frac{1}{2}(-24 + j18)(15.6 + j19.2) \\ &= -360 - j90 \text{ VA} \end{aligned}$$

Thus the dependent source is delivering 360 W and 90 magnetizing vars.

$$[\text{b}] \sum P_{\text{gen}} = 360 + 540 = 900 \text{ W} = \sum P_{\text{abs}}$$

$$[\text{c}] \sum Q_{\text{gen}} = 720 + 90 + 720 = 1530 \text{ VAR} = \sum Q_{\text{abs}}$$

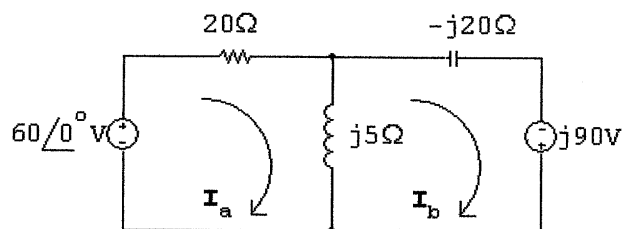P 10.10 [a] From the solution to Problem 9.57 we have



$$\mathbf{I}_a = 2.25 - j2.25 \text{ A}; \quad \mathbf{I}_b = -6.75 + j0.75 \text{ A}; \quad \mathbf{I}_o = 9 - j3 \text{ A}$$

$$S_{60\text{V}} = -\frac{1}{2}(60)\mathbf{I}_a^* = -30(2.25 + j2.25) = -67.5 - j67.5 \text{ VA}$$

Thus, the 60 V source is developing 67.5 W and 67.5 magnetizing vars.

$$\begin{aligned} S_{90\text{V}} &= -\frac{1}{2}(j90)\mathbf{I}_b^* = -j45(-6.75 - j0.75) \\ &= -33.75 + j303.75 \text{ VA} \end{aligned}$$

Thus, the 90 V source is delivering 33.75 W and absorbing 303.75 magnetizing vars.

$$P_{20\Omega} = \frac{1}{2}|\mathbf{I}_a|^2(20) = 101.25 \text{ W}$$

Thus the  $20\Omega$  resistor is absorbing 101.25 W.

$$Q_{-j20\Omega} = \frac{1}{2} |\mathbf{I}_b|^2 (-20) = -461.25 \text{ VAR}$$

Thus the  $-j20\Omega$  capacitor is developing 461.25 magnetizing vars.

$$Q_{j5\Omega} = \frac{1}{2} |\mathbf{I}_o|^2 (5) = 225 \text{ VAR}$$

Thus the  $j5\Omega$  inductor is absorbing 225 magnetizing vars.

$$[\text{b}] \sum P_{\text{dev}} = 67.5 + 33.75 = 101.25 \text{ W} = \sum P_{\text{abs}}$$

$$[\text{c}] \sum Q_{\text{dev}} = 67.5 + 461.25 = 528.75 \text{ VAR}$$

$$\sum Q_{\text{abs}} = 225 + 303.75 = 528.75 \text{ VAR} = \sum Q_{\text{dev}}$$

$$\text{P 10.11 } W_{\text{dc}} = \frac{V_{\text{dc}}^2}{R} T; \quad W_s = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$$

$$\therefore \frac{V_{\text{dc}}^2}{R} T = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$$

$$V_{\text{dc}}^2 = \frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt$$

$$V_{\text{dc}} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt} = V_{\text{rms}} = V_{\text{eff}}$$

$$\text{P 10.12 } [\text{a}] I_{\text{eff}} = 60/110 \cong 0.545 \text{ A}; \quad [\text{b}] I_{\text{eff}} = (60 + 80)/110 \cong 1.273 \text{ A}$$

$$\text{P 10.13 } [\text{a}] \text{ Area under one cycle of } v_g^2:$$

$$\begin{aligned} A &= (400)(4)(20 \times 10^{-6}) + 10,000(2)(20 \times 10^{-6}) \\ &= 21,600(20 \times 10^{-6}) \end{aligned}$$

Mean value of  $v_g^2$ :

$$\text{M.V.} = \frac{A}{120 \times 10^{-6}} = \frac{21,600(20 \times 10^{-6})}{120 \times 10^{-6}} = 3600$$

$$\therefore V_{\text{rms}} = \sqrt{3600} = 60 \text{ V(rms)}$$

$$[\text{b}] P = \frac{V_{\text{rms}}^2}{R} = \frac{3600}{12} = 300 \text{ W}$$

$$\text{P 10.14 } i(t) = \frac{30}{40} \times 10^3 t = 750t \quad 0 \leq t \leq 40 \text{ ms}$$

$$i(t) = M - \frac{30}{10} \times 10^3 t \quad 40 \text{ ms} \leq t \leq 50 \text{ ms}$$

$$i(t) = 0 \text{ when } t = 50 \text{ ms}$$

$$\therefore M = 3000(50 \times 10^{-3}) = 150$$

$$i(t) = 150 - 3000t \quad 40 \text{ ms} \leq t \leq 50 \text{ ms}$$

$$\therefore I_{\text{rms}} = \sqrt{\frac{1000}{50} \left\{ \int_0^{0.04} (750)^2 t^2 dt + \int_{0.04}^{0.05} (150 - 3000t)^2 dt \right\}}$$

$$\int_0^{0.04} (750)^2 t^2 dt = (750)^2 \frac{t^3}{3} \bigg|_0^{0.04} = 12$$

$$(150 - 3000t)^2 = 22,500 - 9 \times 10^5 t + 9 \times 10^6 t^2$$

$$\int_{0.04}^{0.05} 22,500 dt = 225$$

$$\int_{0.04}^{0.05} 9 \times 10^5 t dt = 45 \times 10^4 t^2 \bigg|_{0.04}^{0.05} = 405$$


$$9 \times 10^6 \int_{0.04}^{0.05} t^2 dt = 3 \times 10^6 t^3 \bigg|_{0.04}^{0.05} = 183$$

$$\therefore I_{\text{rms}} = \sqrt{20\{12 + (225 - 405 + 183)\}} = \sqrt{300} = 17.32 \text{ A}$$

$$\text{P 10.15 } P = I_{\text{rms}}^2 R \quad \therefore R = \frac{24 \times 10^3}{300} = 80 \Omega$$

$$\text{P 10.16 } \mathbf{I}_g = 30/\underline{0^\circ} \text{ mA}$$
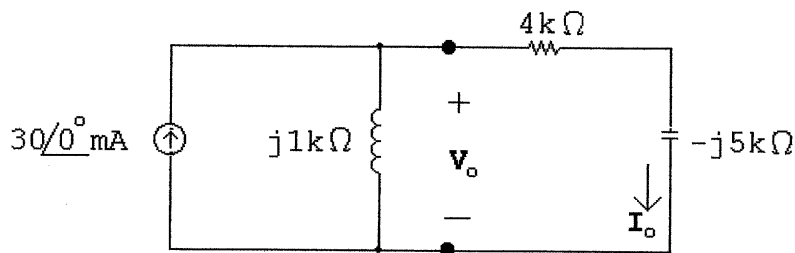
$$j\omega L = j(100)(10) = j1000 \Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j(100)(2)} = -j5000 \Omega$$



$$\mathbf{I}_o = \frac{30/\underline{0^\circ}(j1000)}{4000 - j4000} = 3.75\sqrt{2}/\underline{135^\circ} \text{ mA}$$

$$P = |\mathbf{I}_o|_{\text{rms}}^2 (4000) = (3.75)^2 (4000) = 56.25 \text{ mW}$$


$$Q = |\mathbf{I}_o|_{\text{rms}}^2 (-5000) = -70.3125 \text{ mVAR}$$

$$S = P + jQ = 56.25 - j70.3125 \text{ mVA}$$

$$|S| = 90.044 \text{ mVA}$$

P 10.17 [a]  $\frac{1}{j\omega C} = \frac{10^6}{j10^5} = -j10 \Omega$
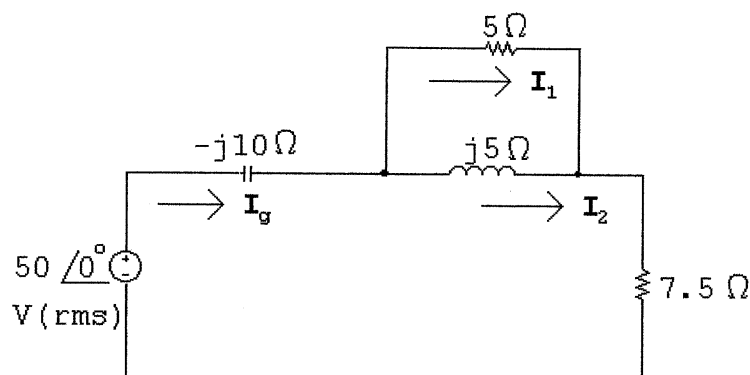
$$j\omega L = j10^5(50 \times 10^{-6}) = j5 \Omega$$



$$Z = -j10 + \frac{(5)(j5)}{5 + j5} + 7.5 = 10 - j7.5 \Omega$$

$$\mathbf{I}_g = \frac{50/0^\circ}{10 - j7.5} = 3.2 + j2.4 \text{ A}$$

$$S_g = -\frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = -25(3.2 - j2.4) = -80 + j60 \text{ VA}$$

$$P = 80 \text{ W (abs)}; \quad Q = 60 \text{ VAR (del)}$$

$$|S| = |S_g| = 100 \text{ VA}$$

[b]  $\mathbf{I}_1 = \frac{\mathbf{I}_g(j5)}{5 + j5} = \frac{1}{2}(3.2 + j2.4)(1 + j1) = 0.4 + j2.8 \text{ A}$

$$P_{5\Omega} = \frac{1}{2} |\mathbf{I}_1|^2 (5) = 20 \text{ W}$$

$$P_{7.5\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (7.5) = 60 \text{ W}$$

$$\sum P_{\text{diss}} = 20 + 60 = 80 \text{ W} = \sum P_{\text{dev}}$$


$$[c] \mathbf{I}_{j5} = \frac{\mathbf{I}_g 5}{5 + j5} = \frac{1}{2}(3.2 + j2.4)(1 - j1) = 2.8 - j0.4 \text{ A}$$

$$Q_{j5\Omega} = \frac{1}{2} |\mathbf{I}_{j5}|^2 (5) = 20 \text{ VAR (abs)}$$

$$Q_{-j10\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (-10) = -80 \text{ VAR (dev)}$$

$$\sum Q_{\text{abs}} = 20 + 60 = 80 \text{ VAR} = \sum Q_{\text{dev}}$$

P 10.18 [a]

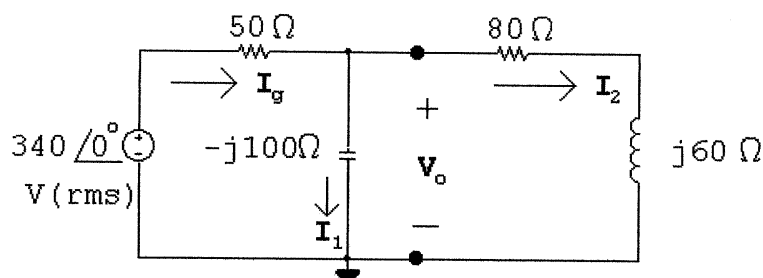

$$\frac{\mathbf{V}_o}{-j100} + \frac{\mathbf{V}_o - 340}{50} + \frac{\mathbf{V}_o}{80 + j60} = 0$$

$$\therefore \mathbf{V}_o = 238 - j34 \text{ V}$$

$$\mathbf{I}_g = \frac{340 - 238 + j34}{50} = 2.04 + j0.68 \text{ A}$$

$$\begin{aligned} S_g &= \mathbf{V}_g \mathbf{I}_g^* = (340)(2.04 - j0.68) \\ &= 693.6 - j231.2 \text{ VA} \end{aligned}$$

[b] Source is delivering 693.6 W.

[c] Source is absorbing 231.2 magnetizing VAR.

$$[d] \mathbf{I}_1 = \frac{\mathbf{V}_o}{-j100} = 0.34 + j2.38 \text{ A}$$

$$\begin{aligned} S_1 &= \mathbf{V}_o \mathbf{I}_1^* = (238 - j34)(0.34 - j2.38) \\ &= 0 - j578 \text{ VA} \end{aligned}$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_o}{80 + j60} = \frac{238 - j34}{80 + j60} = 1.7 - j1.7 \text{ A}$$

$$\begin{aligned} S_2 &= \mathbf{V}_o \mathbf{I}_2^* = (238 - j34)(1.7 + j1.7) \\ &= 462.4 + j346.8 \text{ VA} \end{aligned}$$

$$S_{50\Omega} = |\mathbf{I}_g|^2 (50) + j0 = (2.15)^2 (50) = 231.2 \text{ W}$$

$$[e] \sum P_{\text{del}} = 693.6 \text{ W}$$

$$\sum P_{\text{diss}} = 462.4 + 231.2 = 693.6 \text{ W}$$


$$\therefore \sum P_{\text{del}} = \sum P_{\text{diss}} = 693.6 \text{ W}$$

$$[f] \sum Q_{\text{abs}} = 231.2 + 346.8 = 578 \text{ VAR}$$

$$\sum Q_{\text{dev}} = 578 \text{ VAR}$$

$$\therefore \sum \text{mag VAR dev} = \sum \text{mag VAR abs} = 578$$

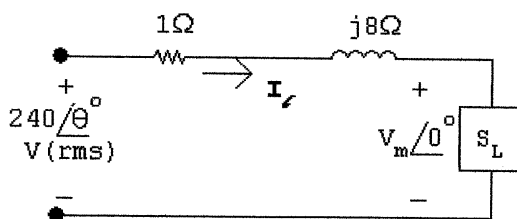P 10.19 [a] Let  $\mathbf{V}_L = V_m \angle 0^\circ$ :



$$S_L = 250(0.6 + j0.8) = 150 + j200 \text{ VA}$$

$$\mathbf{I}_\ell^* = \frac{150}{V_m} + j\frac{200}{V_m}; \quad \mathbf{I}_\ell = \frac{150}{V_m} - j\frac{200}{V_m}$$

$$240\angle\theta = V_m + \left( \frac{150}{V_m} - j\frac{200}{V_m} \right) (1 + j8)$$

$$240V_m\angle\theta = V_m^2 + (150 - j200)(1 + j8) = V_m^2 + 1750 + j1000$$

$$240V_m \cos \theta = V_m^2 + 1750; \quad 240V_m \sin \theta = 1000$$

$$(240)^2 V_m^2 = (V_m^2 + 1750)^2 + 1000^2$$

$$57,600V_m^2 = V_m^4 + 3500V_m^2 + (3.0625 + 1) \times 10^6$$

or

$$V_m^4 - 54,100V_m^2 + 4,062,500 = 0$$

Solving,

$$V_m^2 = 27,050 \pm 26,974.8; \quad V_m = 232.43 \text{ V and } V_m = 8.67 \text{ V}$$

If  $V_m = 232.43 \text{ V}$ :



$$\sin \theta = \frac{1000}{(232.43)(240)} = 0.0179; \quad \therefore \theta = 1.03^\circ$$

If  $V_m = 8.67 \text{ V}$ :

$$\sin \theta = \frac{1000}{(8.67)(240)} = 0.4805; \quad \therefore \theta = 28.72^\circ$$



[b]

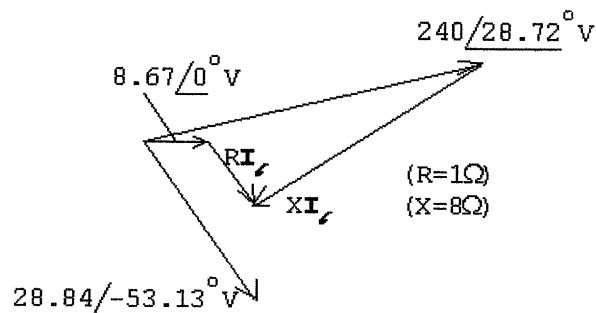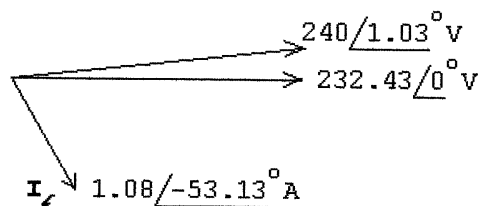

$$\text{P 10.20 } S_T = 52,800 - j\frac{52,800}{0.8}(0.6) = 52,800 - j39,600 \text{ VA}$$

$$S_1 = 40,000(0.96 + j0.28) = 38,400 + j11,200 \text{ VA}$$

$$S_2 = S_T - S_1 = 14,400 - j50,800 = 52,801.52\angle -74.17^\circ \text{ VA}$$

$$\text{rf} = \sin(-74.17^\circ) = -0.9621$$

$$\text{pf} = \cos(-74.17^\circ) = 0.2727 \text{ leading}$$

$$\text{P 10.21 [a] } Z_1 = 12 + j(2\pi)(60)(15 \times 10^{-3}) = 13.27\angle 25.23^\circ \Omega$$

$$\text{pf} = \cos(25.23^\circ) = 0.9 \text{ lagging}$$

$$\text{rf} = \sin(25.23^\circ) = 0.43$$

$$Z_2 = 80 - \frac{j}{2\pi(60)(16 \times 10^{-6})} = 184.08\angle -64.24^\circ \Omega$$

$$\text{pf} = \cos(-64.24^\circ) = 0.43 \text{ leading}$$

$$\text{rf} = \sin(-64.24^\circ) = -0.9$$

$$Z_3 = 400 + Z_p$$

$$Z_p = \frac{j\omega L(1/j\omega C)}{j\omega L + 1/j\omega C} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$= \frac{j(120\pi)(20)}{1 - (120\pi)^2(20)(5 \times 10^{-6})} = -j570.67 \Omega$$

$$\therefore Z_3 = 400 - j570.67 = 696.90 / -54.97^\circ \Omega$$

$$\text{pf} = \cos(-54.97^\circ) = 0.57 \text{ leading}$$

$$\text{rf} = \sin(-54.97^\circ) = -0.82$$

$$[\text{b}] Y = Y_1 + Y_2 + Y_3$$

$$Y_1 = \frac{1}{13.27 / 25.23^\circ}; \quad Y_2 = \frac{1}{184.08 / -64.24^\circ}; \quad Y_3 = \frac{1}{696.90 / -54.97^\circ}$$

$$Y = 71.35 - j26.05 \text{ mS}$$

$$Z = \frac{1}{Y} = 13.16 / 20.06^\circ \Omega$$

$$\text{pf} = \cos(20.06^\circ) = 0.94 \text{ lagging}$$

$$\text{rf} = \sin(20.06^\circ) = 0.343$$

$$\text{P 10.22 } [\text{a}] S_1 = 18 + j24 \text{ kVA}; \quad S_2 = 36 - j48 \text{ kVA}; \quad S_3 = 18 + j0 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 72 - j24 \text{ kVA}$$

$$2400\mathbf{I}^* = (72 - j24) \times 10^3; \quad \therefore \mathbf{I} = 30 + j10 \text{ A}$$

$$Z = \frac{2400}{30 + j10} = 72 - j24 \Omega = 75.89 / -18.43^\circ \Omega$$

$$[\text{b}] \text{ pf} = \cos(-18.43^\circ) = 0.9487 \text{ leading}$$

$$\text{P 10.23 } [\text{a}] \text{ From the solution to Problem 10.22 we have}$$

$$\mathbf{I}_L = 30 + j10 \text{ A(rms)}$$

$$\begin{aligned} \therefore \mathbf{V}_s &= 2400 / 0^\circ + (30 + j10)(0.2 + j1.6) = 2390 + j50 \\ &= 2390.52 / 1.20^\circ \text{ V(rms)} \end{aligned}$$


$$[\text{b}] |\mathbf{I}_L| = \sqrt{1000}$$

$$P_\ell = (1000)(0.2) = 200 \text{ W} \quad Q_\ell = (1000)(1.6) = 1600 \text{ VAR}$$

$$[\text{c}] P_s = 72,000 + 200 = 72.2 \text{ kW} \quad Q_s = -24,000 + 1600 = -22.4 \text{ kVAR}$$

$$[\text{d}] \eta = \frac{72}{72.2}(100) = 99.72\%$$

P 10.24

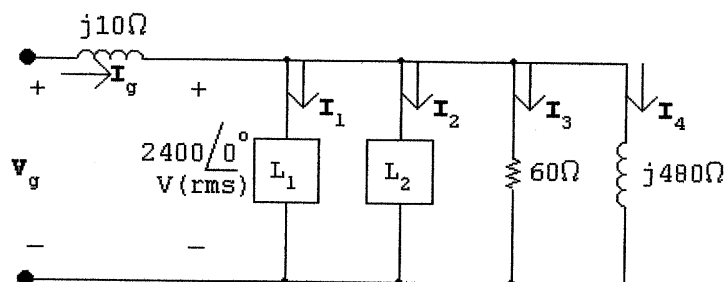

$$2400\mathbf{I}_1^* = 24,000 + j18,000$$

$$\mathbf{I}_1^* = 10 + j7.5; \quad \therefore \mathbf{I}_1 = 10 - j7.5 \text{ A(rms)}$$

$$2400\mathbf{I}_2^* = 48,000 - j30,000$$

$$\mathbf{I}_2^* = 20 - j12.5; \quad \therefore \mathbf{I}_2 = 20 + j12.5 \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{2400\angle 0^\circ}{60} = 40 + j0 \text{ A}; \quad \mathbf{I}_4 = \frac{2400\angle 0^\circ}{j480} = 0 - j5 \text{ A}$$

$$\mathbf{I}_g = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 + \mathbf{I}_4 = 70 \text{ A}$$

$$\mathbf{V}_g = 2400 + (70)(j10) = 2400 + j700 = 2500\angle 16.26^\circ \text{ V(rms)}$$

P 10.25 [a]  $S_1 = 24,960 + j47,040 \text{ VA}$ 

$$S_2 = \frac{|\mathbf{V}_L|^2}{Z_2^*} = \frac{(480)^2}{5 + j5} = 23,040 - j23,040 \text{ VA}$$

$$S_1 + S_2 = 48,000 + j24,000 \text{ VA}$$

$$480\mathbf{I}_L^* = 48,000 + j24,000; \quad \therefore \mathbf{I}_L = 100 - j50 \text{ A(rms)}$$


$$\begin{aligned} \mathbf{V}_g &= \mathbf{V}_L + \mathbf{I}_L(0.02 + j0.20) = 480 + (100 - j50)(0.02 + j0.20) \\ &= 492 + j19 = 492.37\angle 2.21^\circ \text{ Vrms} \end{aligned}$$

$$|\mathbf{V}_g| = 492.37 \text{ Vrms}$$


$$[b] T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$$

$$\frac{2.21^\circ}{360^\circ} = \frac{t}{16.67 \text{ ms}}; \quad \therefore t = 102.39 \mu\text{s}$$

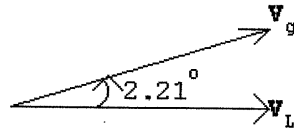[c]  $V_L$  lags  $V_g$  by  $2.21^\circ$  or  $102.31 \mu s$



P 10.26 [a]

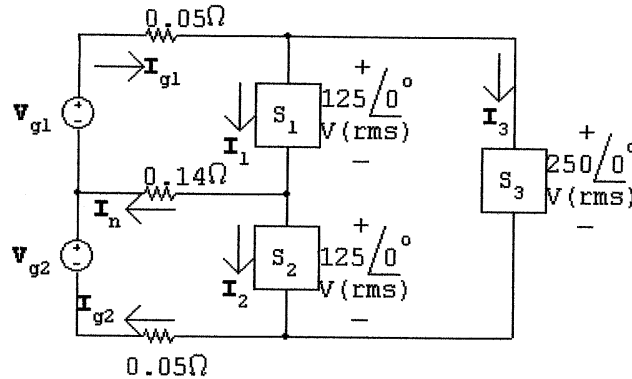

$$I_1 = \frac{5000 - j2000}{125} = 40 - j16 \text{ A (rms)}$$

$$I_2 = \frac{3750 - j1500}{125} = 30 - j12 \text{ A (rms)}$$

$$I_3 = \frac{8000 + j0}{250} = 32 + j0 \text{ A (rms)}$$

$$\therefore I_{g1} = 72 - j16 \text{ A (rms)}$$

$$I_n = I_1 - I_2 = 10 - j4 \text{ A (rms)}$$

$$I_{g2} = 62 - j12 \text{ A}$$

$$V_{g1} = 0.05I_{g1} + 125 + j0 + 0.14I_n = 130 - j1.36 \text{ V(rms)}$$

$$V_{g2} = -0.14I_n + 125 + j0 + 0.05I_{g2} = 126.7 - j0.04 \text{ V(rms)}$$

$$S_{g1} = [(130 - j1.36)(72 + j16)] = [9381.76 + j1982.08] \text{ VA}$$

$$S_{g2} = [(126.7 - j0.04)(62 + j12)] = [7855.88 + j1517.92] \text{ VA}$$

Note: Both sources are delivering average power and magnetizing VAR to the circuit.

[b]  $P_{0.05} = |I_{g1}|^2(0.05) = 272 \text{ W}$

$$P_{0.15} = |I_n|^2(0.14) = 16.24 \text{ W}$$

$$P_{0.05} = |I_{g2}|^2(0.05) = 199.4 \text{ W}$$


$$\sum P_{\text{dis}} = 272 + 16.24 + 199.4 + 5000 + 3750 + 8000 = 17,237.64 \text{ W}$$

$$\sum P_{\text{dev}} = 9381.76 + 7855.88 = 17,237.64 \text{ W} = \sum P_{\text{dis}}$$

$$\sum Q_{\text{abs}} = 2000 + 1500 = 3500 \text{ VAR}$$

$$\sum Q_{\text{del}} = 1982.08 + 1517.92 = 3500 \text{ VAR} = \sum Q_{\text{abs}}$$

P 10.27 [a]

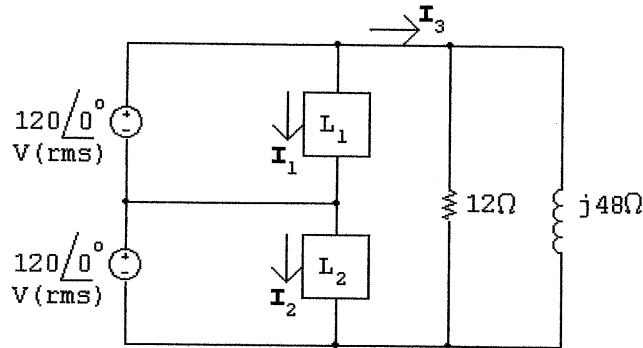

$$120\mathbf{I}_1^* = 1800 + j600; \quad \therefore \mathbf{I}_1 = 15 - j5 \text{ A(rms)}$$

$$120\mathbf{I}_2^* = 1200 - j900; \quad \therefore \mathbf{I}_2 = 10 + j7.5 \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{240}{12} + \frac{240}{j48} = 20 - j5 \text{ A(rms)}$$

$$\mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 35 - j10 \text{ A}$$

$$S_{g1} = 120(35 + j10) = 4200 + j1200 \text{ VA}$$

Thus the  $\mathbf{V}_{g1}$  source is delivering 4200 W and 1200 magnetizing vars.

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 30 + j2.5 \text{ A(rms)}$$

$$S_{g2} = 120(30 - j2.5) = 3600 - j300 \text{ VA}$$

Thus the  $\mathbf{V}_{g2}$  source is delivering 3600 W and absorbing 300 magnetizing vars.

[b]  $\sum P_{\text{gen}} = 4200 + 3600 = 7800 \text{ W}$

$$\sum P_{\text{abs}} = 1800 + 1200 + \frac{(240)^2}{12} = 7800 \text{ W} = \sum P_{\text{gen}}$$

$$\sum Q_{\text{del}} = 1200 + 900 = 2100 \text{ VAR}$$

$$\sum Q_{\text{abs}} = 300 + 600 + \frac{(240)^2}{48} = 2100 \text{ VAR} = \sum Q_{\text{del}}$$

$$P 10.28 \quad S_1 = 1200 + 1196 + 516 + j0 = 2912 + j0 \text{ VA}$$

$$\therefore I_1 = \frac{2912}{120} + j0 = 24.27 + j0 \text{ A}$$

$$S_2 = 600 + 279 + 88 + 512 + j0 = 1479 + j0 \text{ VA}$$

$$\therefore I_2 = \frac{1479}{120} + j0 = 12.33 + j0 \text{ A}$$

$$S_3 = 4474 + 12,200 + j0 = 16,674 + j0 \text{ VA}$$


$$\therefore I_3 = \frac{16,674}{240} + j0 = 69.48 + j0 \text{ A}$$

$$I_{g1} = I_1 + I_3 = 93.75 + j0 \text{ A}$$

$$I_{g2} = I_2 + I_3 = 81.81 + j0 \text{ A}$$

Breakers will not trip since both feeder currents are less than 100 A.

P 10.29

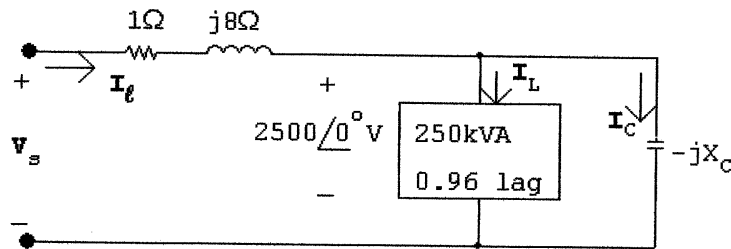

$$I_L = \frac{240,000 - j70,000}{2500} = 96 - j28 \text{ A (rms)}$$

$$I_C = \frac{2500}{-jX_C} = j \frac{2500}{X_C} = jI_C$$

$$I_t = 96 - j28 + jI_C = 96 + j(I_C - 28)$$

$$\begin{aligned} V_s &= 2500 + (1 + j8)[96 + j(I_C - 28)] \\ &= (2820 - 8I_C) + j(740 + I_C) \end{aligned}$$

$$|V_s|^2 = (2820 - 8I_C)^2 + (740 + I_C)^2 = (2500)^2$$

$$\therefore 65I_C^2 - 43,640I_C + 2,250,000 = 0$$

$$I_C = \frac{43,640 \pm \sqrt{(43,640)^2 - 4(65)(2,250,000)}}{2(65)}$$

$$= 335.69 \pm 279.42 = 56.27 \text{ A(rms)}^*$$

\*Select the smaller value of  $I_C$  to minimize the magnitude of  $I_\ell$ .

$$\therefore X_C = -\frac{2500}{56.27} = -44.43$$

$$\therefore C = \frac{1}{(44.43)(120\pi)} = 59.7 \mu\text{F}$$

P 10.30 [a]  $\mathbf{I} = \frac{7200/0^\circ}{140 + j480} = 14.4/-73.74^\circ \text{ A(rms)}$

$$P = (14.4)^2(2) = 414.72 \text{ W}$$

[b]  $Y_L = \frac{1}{138 + j460} = \frac{138 - j460}{230,644}$

$$\therefore -j\omega C = -j\frac{460}{230,644} \quad \therefore X_C = \frac{-230,644}{460} = -501.40 \Omega$$

[c]  $Z_L = \frac{230,644}{138} = 1671.33 \Omega$

[d]  $\mathbf{I} = \frac{7200}{1673.33 + j20} = 4.30/-0.68^\circ \text{ A}$

$$P = (4.30)^2(2) = 37.02 \text{ W}$$

[e]  $\% = \frac{37.02}{414.72}(100) = 8.93\%$

Thus the power loss after the capacitor is added is 8.93% of the power loss before the capacitor is added.

P 10.31 [a]  $S_L = 24 + j7 \text{ kVA}$

$$125\mathbf{I}_L^* = (24 + j7) \times 10^3; \quad \mathbf{I}_L^* = 192 + j56 \text{ A(rms)}$$

$$\therefore \mathbf{I}_L = 192 - j56 \text{ A(rms)}$$

$$\mathbf{V}_s = 125 + (192 - j56)(0.006 + j0.048) = 128.84 + j8.88$$

$$= 129.15/3.94^\circ \text{ V(rms)}$$

$$|\mathbf{V}_s| = 129.15 \text{ V(rms)}$$

[b]  $P_\ell = |\mathbf{I}_\ell|^2(0.006) = (200)^2(0.006) = 240 \text{ W}$

$$[c] \frac{(125)^2}{X_C} = -7000; \quad X_C = -2.23 \Omega$$

$$-\frac{1}{\omega C} = -2.23; \quad C = \frac{1}{(2.23)(120\pi)} = 1188.36 \mu\text{F}$$

$$[d] \mathbf{I}_\ell = 192 + j0 \text{ A(rms)}$$

$$\mathbf{V}_s = 125 + 192(0.006 + j0.048) = 126.152 + j9.216$$

$$= 126.49/\underline{4.18^\circ} \text{ V(rms)}$$

$$|\mathbf{V}_s| = 126.49 \text{ V(rms)}$$

$$[e] P_\ell = (192)^2(0.006) = 221.184 \text{ W}$$

P 10.32 [a]  $S_o = \text{original load} = 1800 + j\frac{1800}{0.6}(0.8) = 1800 + j2400 \text{ kVA}$

$$S_f = \text{final load} = 2400 + j\frac{2400}{0.96}(0.28) = 2400 + j700 \text{ kVA}$$

$$\therefore Q_{\text{added}} = 700 - 2400 = -1700 \text{ kVAR}$$

[b] deliver

[c]  $S_a = \text{added load} = 600 - j1700 = 1802.78/\underline{-70.56^\circ} \text{ kVA}$

$$\text{pf} = \cos(-70.56) = 0.3328 \text{ leading}$$

[d]  $\mathbf{I}_L^* = \frac{(1800 + j2400) \times 10^3}{4800} = 375 + j500 \text{ A}$

$$\mathbf{I}_L = 375 - j500 = 625/\underline{53.13^\circ} \text{ A(rms)}$$

$$|\mathbf{I}_L| = 625 \text{ A(rms)}$$

[e]  $\mathbf{I}_L^* = \frac{(2400 + j700) \times 10^3}{4800} = 500 + j145.83$

$$\mathbf{I}_L = 500 - j145.83 = 520.83/\underline{-16.26^\circ} \text{ A(rms)}$$

$$|\mathbf{I}_L| = 520.83 \text{ A(rms)}$$

P 10.33 [a]  $P_{\text{before}} = (625)^2(0.02) = 7812.50 \text{ W}$

$$P_{\text{after}} = (520.83)^2(0.02) = 5425.35 \text{ W}$$



$$\begin{aligned} \text{[b]} \quad \mathbf{V}_s(\text{before}) &= 4800 + (375 - j500)(0.02 + j0.16) = 4887.5 + j50 \\ &= 4887.5/\underline{0.59^\circ} \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s(\text{before})| = 4887.76 \text{ V(rms)}$$

$$\begin{aligned} \mathbf{V}_s(\text{after}) &= 4800 + (500 - j145.83)(0.02 + j0.16) \\ &= 4833.33 + j77.08 = 4833.95/\underline{0.91^\circ} \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s(\text{after})| = 4833.95 \text{ V(rms)}$$

$$\text{P 10.34 [a]} \quad \mathbf{I}_1 = \frac{125/\underline{0^\circ}}{20 + j34 + 5 + j16} = \frac{125}{25 + j50} = 1 - j2 \text{ A}$$

$$\begin{aligned} \mathbf{I}_2 &= \frac{j\omega M}{Z_{22}} \mathbf{I}_1 = \frac{j50}{200 + j150} (1 - j2) \\ &= 0.44 - j0.08 = 0.45/\underline{-10.30^\circ} \text{ A} \end{aligned}$$

$$\begin{aligned} \mathbf{V}_L &= (150 - j100)(0.44 - j0.08) = 58 - j56 \\ &= 80.62/\underline{-43.99^\circ} \text{ V} \end{aligned}$$

$$|\mathbf{V}_L| = 80.62 \text{ V}$$


$$\text{[b]} \quad P_g(\text{ideal}) = 125(1) = 125 \text{ W}$$

$$P_g(\text{practical}) = 125 - |\mathbf{I}_1|^2(5) = 125 - 25 = 100 \text{ W}$$

$$P_L = |\mathbf{I}_2|^2(150) = 30 \text{ W}$$

$$\% \text{ delivered} = \frac{30}{100}(100) = 30\%$$

P 10.35 [a]

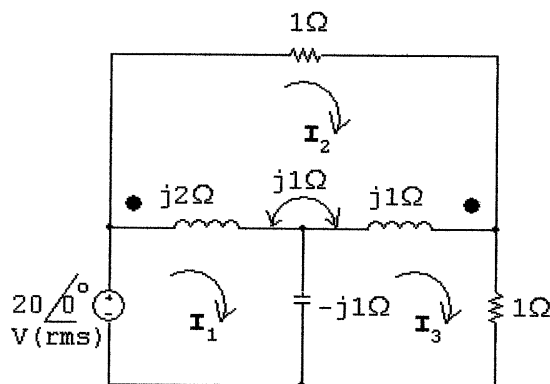

$$20 = j2(\mathbf{I}_1 - \mathbf{I}_2) + j1(\mathbf{I}_2 - \mathbf{I}_3) - j1(\mathbf{I}_1 - \mathbf{I}_3)$$

$$0 = 1\mathbf{I}_2 + j1(\mathbf{I}_2 - \mathbf{I}_3) + j1(\mathbf{I}_1 - \mathbf{I}_2) + j2(\mathbf{I}_2 - \mathbf{I}_1) - j1(\mathbf{I}_2 - \mathbf{I}_3)$$

$$0 = -j1(\mathbf{I}_3 - \mathbf{I}_1) + j1(\mathbf{I}_3 - \mathbf{I}_2) - j1(\mathbf{I}_1 - \mathbf{I}_2) + 1\mathbf{I}_3$$

Solving,


$$\mathbf{I}_1 = 20 - j20 \text{ A(rms)}; \quad \mathbf{I}_2 = 20 + j0 \text{ A(rms)}; \quad \mathbf{I}_3 = 0 \text{ A(rms)}$$

$$\mathbf{I}_a = \mathbf{I}_1 = 20 - j20 \text{ A} \quad \mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_2 = -j20 \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_2 = 20 \text{ A} \quad \mathbf{I}_d = \mathbf{I}_3 - \mathbf{I}_2 = -20 \text{ A}$$

$$\mathbf{I}_e = \mathbf{I}_1 - \mathbf{I}_3 = 20 - j20 \text{ A} \quad \mathbf{I}_f = \mathbf{I}_3 = 0 \text{ A}$$

[b]

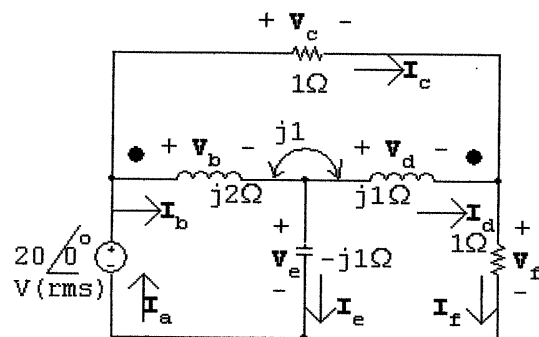

$$\mathbf{V}_a = 20 + j0 \text{ V}$$

$$\mathbf{V}_b = j2\mathbf{I}_b - j1\mathbf{I}_d = 40 + j20 \text{ V}$$

$$\mathbf{V}_c = 1\mathbf{I}_c = 20 + j0 \text{ V}$$

$$\mathbf{V}_d = j1\mathbf{I}_d - j1\mathbf{I}_b = -20 - j20 \text{ V}$$

$$\mathbf{V}_e = -j1\mathbf{I}_e = -20 - j20 \text{ V}$$

$$\mathbf{V}_f = 1\mathbf{I}_f = 0 \text{ V}$$

$$S_a = -20\mathbf{I}_a^* = -400 - j400 \text{ VA}$$

$$S_b = \mathbf{V}_b\mathbf{I}_b^* = -400 + j800 \text{ VA}$$

$$S_c = \mathbf{V}_c\mathbf{I}_c^* = 400 + j0 \text{ VA}$$

$$S_d = \mathbf{V}_d\mathbf{I}_d^* = 400 + j400 \text{ VA}$$

$$S_e = \mathbf{V}_e\mathbf{I}_e^* = 0 - j800 \text{ VA}$$

$$S_f = \mathbf{V}_f\mathbf{I}_f^* = 0 + j0 \text{ VA}$$

[c]  $\sum P_{\text{dev}} = 400 \text{ W}$

$$\sum P_{\text{abs}} = -400 + 400 + 400 = 400 \text{ W}$$

Note that the total power absorbed by the coupled coils is zero:

$$-400 + 400 = 0 = P_b + P_d$$


$$[d] \sum Q_{\text{dev}} = 400 + 800 = 1200 \text{ VAR}$$

Both the source and the capacitor are developing magnetizing vars.

$$\sum Q_{\text{abs}} = 400 + 800 = 1200 \text{ VAR}$$

$\sum Q$  absorbed by the coupled coils is  $Q_b + Q_d$

P 10.36 [a]

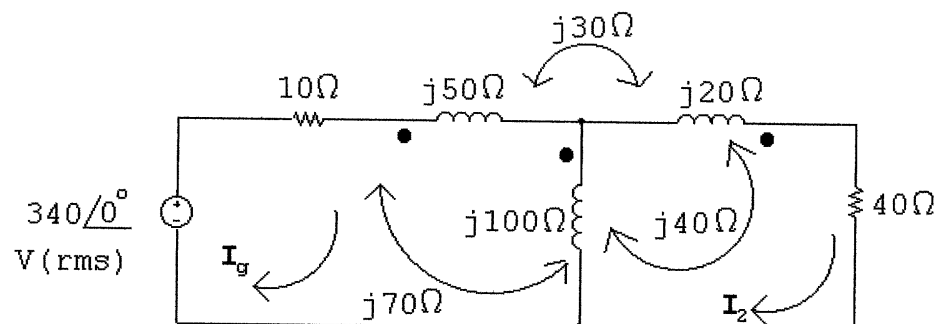

$$\begin{aligned} 340\angle 0^\circ &= 10\mathbf{I}_g + j50\mathbf{I}_g + j70(\mathbf{I}_g - \mathbf{I}_2) - j30\mathbf{I}_2 \\ &\quad + j70\mathbf{I}_g - j40\mathbf{I}_2 + j100(\mathbf{I}_g - \mathbf{I}_2) \\ 0 &= j100(\mathbf{I}_2 - \mathbf{I}_g) - j70\mathbf{I}_g + j40\mathbf{I}_2 + j20\mathbf{I}_2 \\ &\quad + j40(\mathbf{I}_2 - \mathbf{I}_g) - j30\mathbf{I}_g + 40\mathbf{I}_2 \end{aligned}$$

Solving,

$$\mathbf{I}_g = 5 - j1 \text{ A(rms)}; \quad \mathbf{I}_2 = 6\angle 0^\circ \text{ A(rms)}$$

$$P_{40\Omega} = (6)^2(40) = 1440 \text{ W}$$


$$[b] P_g(\text{developed}) = (340)(5) = 1700 \text{ W}$$

$$[c] Z_{\text{ab}} = \frac{\mathbf{V}_g}{\mathbf{I}_g} - 10 = \frac{340}{5 - j} - 10 = 55.38 + j13.08 = 56.91\angle 13.28^\circ \Omega$$

$$[d] P_{10\Omega} = |\mathbf{I}_g|^2(10) = 260 \text{ W}$$

$$\sum P_{\text{diss}} = 1440 + 260 = 1700 \text{ W} = \sum P_{\text{dev}}$$

P 10.37 [a]

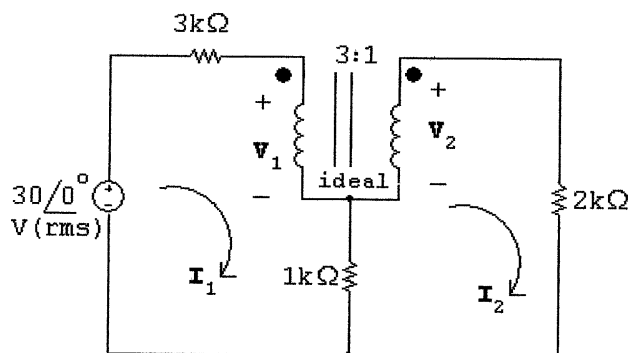

$$30 = 3000\mathbf{I}_1 + \mathbf{V}_1 + 1000(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 1000(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2 + 2000\mathbf{I}_2$$

$$\mathbf{V}_2 = \frac{1}{3}\mathbf{V}_1; \quad \mathbf{I}_2 = 3\mathbf{I}_1$$

Solving,

$$\mathbf{V}_1 = 28.8 \text{ V(rms)}; \quad \mathbf{V}_2 = 9.6 \text{ V(rms)}$$

$$\mathbf{I}_1 = 1.2 \text{ mA(rms)}; \quad \mathbf{I}_2 = 3.6 \text{ mA(rms)}$$

$$\mathbf{V}_{10\text{mA}} = \mathbf{V}_1 + 1000(\mathbf{I}_1 - \mathbf{I}_2) = 26.4 \text{ V(rms)}$$

$$\therefore P = -(26.4)(10 \times 10^{-3}) = -264 \text{ mW}$$

Thus 264 mW is delivered by the current source to the circuit.

[b]  $\mathbf{I}_{1k\Omega} = \mathbf{I}_1 - \mathbf{I}_2 = -2.4 \text{ mA(rms)}$

$$\therefore P_{1k\Omega} = (-0.0024)^2(1000) = 5.76 \text{ mW}$$

P 10.38 [a]  $Z_{ab} = \left(1 + \frac{N_1}{N_2}\right)^2 (4 - j8) = 36 - j72 \Omega$

$$\therefore \mathbf{I}_1 = \frac{250/0^\circ}{4 + j42 + 36 - j72} = 5/36.87^\circ \text{ A}$$

$$P_{4(\text{left})} = |\mathbf{I}_1|^2(4) = (5)^2(4) = 100 \text{ W}$$

$$\mathbf{I}_2 = \frac{N_1}{N_2}\mathbf{I}_1 = 10/36.87^\circ \text{ A}$$


$$\therefore \mathbf{I}_L = 15/36.87^\circ \text{ A(rms)}$$

$$P_{4(\text{right})} = (225)(4) = 900 \text{ W}$$

[b]  $P_g = (250)(5) \cos(36.87^\circ) = 1000 \text{ W(developed)}$

$$\sum P_{\text{abs}} = (5)^2(4) + 900 = 1000 \text{ W} = \sum P_{\text{dev}}$$

P 10.39 [a]

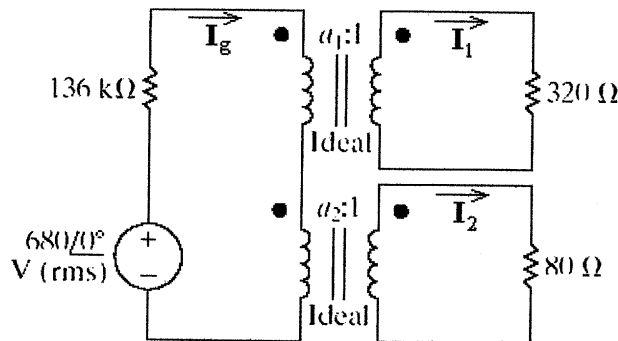

$$a_1 \mathbf{I}_g = \mathbf{I}_1; \quad a_2 \mathbf{I}_g = \mathbf{I}_2; \quad \text{so} \quad \frac{a_1}{a_2} = \frac{\mathbf{I}_1}{\mathbf{I}_2}$$

$$P_{320} = |\mathbf{I}_1|^2(320); \quad P_{80} = |\mathbf{I}_2|^2(80); \quad P_{80} = 16P_{320}$$

$$\therefore |\mathbf{I}_2|^2(80) = 16[|\mathbf{I}_1|^2(320)] \quad \text{thus} \quad \frac{a_1}{a_2} = \frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{1}{8}$$

The load impedances are matched to the source impedance:

$$a_1^2(320) + a_2^2(80) = 136,000 \quad \text{so} \quad a_1^2(320) + (8a_1)^2(80) = 136,000$$

$$\therefore a_1^2 = 25 \quad \text{so} \quad a_1 = 5 \quad \text{and} \quad a_2 = 8a_1 = 40$$

$$[\mathbf{b}] \quad \mathbf{I}_g = \frac{680/\underline{0^\circ}}{(136 + 136)10^3} = 2.5/\underline{0^\circ} \text{ mA(rms)}$$

$$\mathbf{I}_2 = 40\mathbf{I}_g = 100 \text{ mA(rms)}$$

$$\therefore P_{80\Omega} = (0.1)^2(80) = 800 \text{ mW}$$

$$[\mathbf{c}] \quad \mathbf{I}_1 = 5\mathbf{I}_g = 12.5/\underline{0^\circ} \text{ mA(rms)}$$

$$\mathbf{V}_{320} = (12.5 \times 10^{-3})(320) = 4 \text{ V(rms)}$$

P 10.40  $Z_L = |Z_L|/\underline{\theta^\circ} = |Z_L| \cos \theta^\circ + j|Z_L| \sin \theta^\circ$

$$\text{Thus} \quad |\mathbf{I}| = \frac{|\mathbf{V}_{Th}|}{\sqrt{(R_{Th} + |Z_L| \cos \theta)^2 + (X_{Th} + |Z_L| \sin \theta)^2}}$$

$$\text{Therefore} \quad P = \frac{0.5|\mathbf{V}_{Th}|^2|Z_L| \cos \theta}{(R_{Th} + |Z_L| \cos \theta)^2 + (X_{Th} + |Z_L| \sin \theta)^2}$$

Let  $D$  = demoninator in the expression for  $P$ , then

$$\frac{dP}{d|Z_L|} = \frac{(0.5|\mathbf{V}_{Th}|^2 \cos \theta)(D \cdot 1 - |Z_L|dD/d|Z_L|)}{D^2}$$

$$\frac{dD}{d|Z_L|} = 2(R_{Th} + |Z_L| \cos \theta) \cos \theta + 2(X_{Th} + |Z_L| \sin \theta) \sin \theta$$


$$\frac{dP}{d|Z_L|} = 0 \quad \text{when} \quad D = |Z_L| \left( \frac{dD}{d|Z_L|} \right)$$

Substituting the expressions for  $D$  and  $(dD/d|Z_L|)$  into this equation gives us the relationship  $R_{Th}^2 + X_{Th}^2 = |Z_L|^2$  or  $|Z_{Th}| = |Z_L|$ .

P 10.41  $[\mathbf{a}] \quad Z_{Th} = \frac{1}{j\omega C} + \frac{(60)(j60)}{60 + j60} = -j40 + 30 + j30 = 30 - j10 \text{ k}\Omega$

$$\therefore Z_L = Z_{Th}^* = 30 + j10 \text{ k}\Omega$$
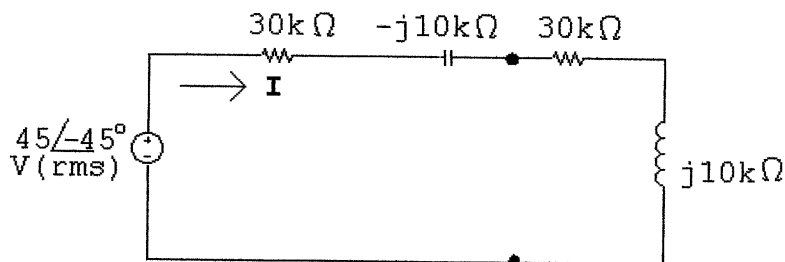
$$[b] \quad V_{Th} = \frac{90/0^\circ(60)}{60 + j60} = 45(1 - j1) = 45\sqrt{2}/-45^\circ \text{ V}$$



$$I = \frac{45\sqrt{2}/-45^\circ}{60 \times 10^3} = 0.75\sqrt{2}/-45^\circ \text{ mA}$$

$$|I_{rms}| = 0.75 \text{ mA}$$

$$P_{load} = (0.75)^2 \times 10^{-6} (30 \times 10^3) = 16.875 \text{ mW}$$

$$P \ 10.42 \ [a] \quad \frac{240 - j80 - 480}{Z_{Th}} + \frac{240 - j80}{100} = 0$$


$$\therefore Z_{Th} = \frac{-100(240 + j80)}{-(240 - j80)} = 80 + j60 \Omega$$

$$\therefore Z_L = 80 - j60 \Omega$$

$$[b] \quad I = \frac{480/0^\circ}{160/0^\circ} = 3/0^\circ \text{ A (rms)}$$

$$P = (9)(80) = 720 \text{ W}$$

P 10.43 [a]

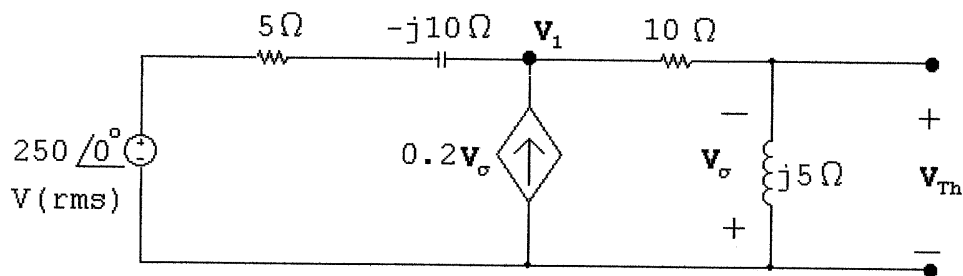

$$\frac{V_1 - 250}{5 - j10} - 0.2V_\sigma + \frac{V_1}{10 + j5} = 0$$

$$V_\sigma = \frac{-j5V_1}{10 + j5} = \frac{-jV_1}{2 + j1}$$


$$-0.2V_\sigma = \frac{j0.2V_1}{2 + j1}$$

$$\therefore V_1 \left[ \frac{1}{5 - j10} + \frac{j0.2}{2 + j1} + \frac{1}{10 + j5} \right] = \frac{250}{5 - j10}$$

Thus,  $\mathbf{V}_1 = 10(10 + j5)$


$$\mathbf{V}_{Th} = \frac{j5}{10 + j5} \mathbf{V}_1 = j50 = 50 \angle 90^\circ \text{ V(rms)}$$

Short circuit current:

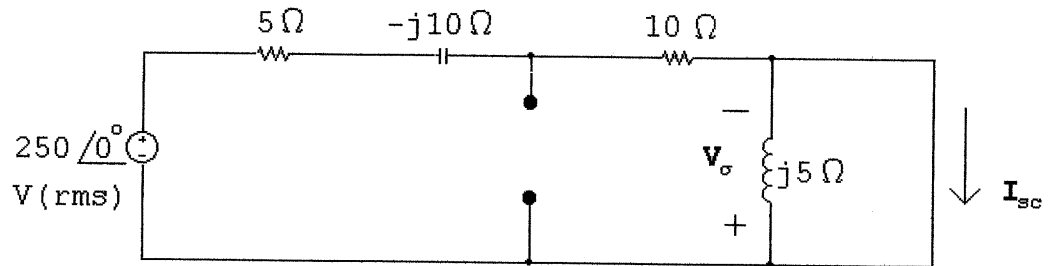

$$\mathbf{I}_{sc} = \frac{250 \angle 0^\circ}{15 - j10} = \frac{50}{3 - j2} \text{ A(rms)}$$

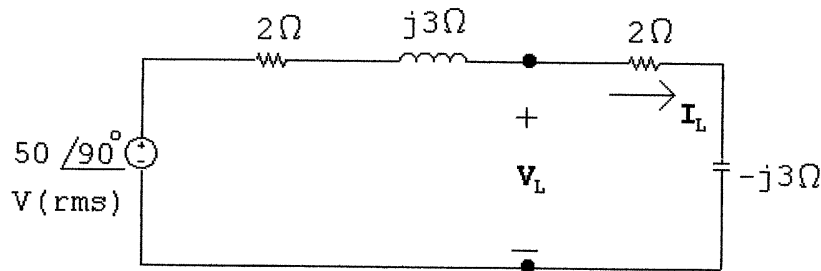
$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{j50}{50} (3 - j2) = 2 + j3 \Omega$$



$$\mathbf{I}_L = \frac{50 \angle 90^\circ}{4} = 12.5 \angle 90^\circ \text{ A(rms)}$$

$$P = (12.5)^2(2) = 312.50 \text{ W}$$

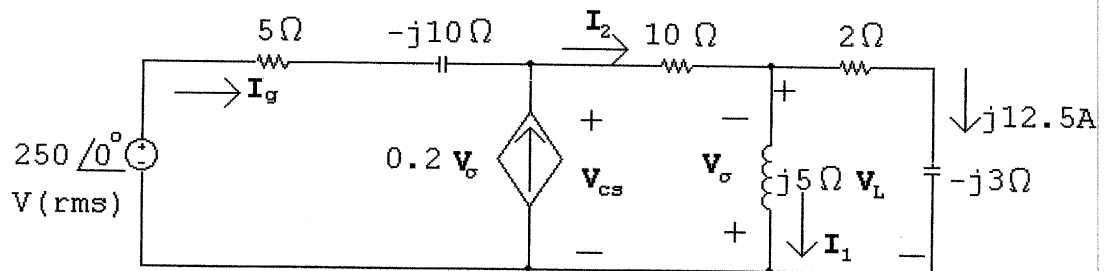[b]  $\mathbf{V}_L = (2 - j3)(j12.5) = 37.5 + j25 \text{ V(rms)}$



$$\mathbf{I}_1 = \frac{\mathbf{V}_L}{j5} = \frac{37.5 + j25}{j5} = 5 - j7.5 \text{ A(rms)}$$

$$\mathbf{I}_2 = \mathbf{I}_1 + \mathbf{I}_L = 5 - j7.5 + j12.5 = 5 + j5 \text{ A(rms)}$$

$$\mathbf{V}_{cs} = \mathbf{V}_L + 10\mathbf{I}_2 = 37.5 + j25 + 50 + j50 = 87.5 + j75 \text{ V(rms)}$$

$$\mathbf{V}_\sigma = -\mathbf{V}_L = -37.5 - j25$$

$$0.2\mathbf{V}_\sigma = -7.5 - j5$$

$$S_{cs} = -\mathbf{V}_{cs}\mathbf{I}_{cs}^* = -(87.5 + j75)(-7.5 + j5) = 1031.25 + j125 \text{ VA}$$

Therefore, the dependent source is absorbing 1031.25 W and 125 magnetizing vars. Only the independent voltage source is developing power.

$$\mathbf{I}_g = -0.2\mathbf{V}_\sigma + \mathbf{I}_2 = 7.5 + j5 + 5 + j5 = 12.5 + j10 \text{ A}$$

$$S_g = -250\mathbf{I}_g^* = -3125 + j2500 \text{ VA}$$

$$\therefore P_{dev} = 3125 \text{ W}$$

$$\% \text{ delivered} = \frac{312.5}{3125}(100) = 10\%$$

Thus, 10% of the developed power is delivered to the load.

Checks:

$$P_{10\Omega} = (5\sqrt{2})^2 10 = 500 \text{ W}$$

$$P_{2\Omega} = 312.5 \text{ W}$$

$$P_{5\Omega} = (\sqrt{256.25})^2 5 = 1281.25 \text{ W}$$

$$\therefore \sum P_{dev} = \sum P_{abs} = 500 + 312.5 + 1281.25 + 1031.25 = 3125 \text{ W}$$


VAR Check:

The 250 V source is absorbing 2500 vars; the dependent current source is absorbing 125 vars; the  $j5\Omega$  inductor is absorbing  $|37.5 + j25|^2/5 = 406.25$  vars. Thus,

$$\sum Q_{abs} = 2625 + 406.25 = 3031.25 \text{ VAR}$$

$$\sum Q_{dev} = (12.5)^2(3) + 256.25(10) = 3031.25 \text{ VAR} = \sum Q_{abs}$$

P 10.44 [a]

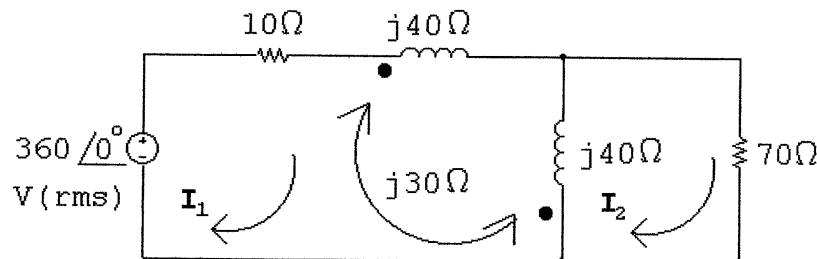

$$360\angle 0^\circ = 10\mathbf{I}_1 + j40\mathbf{I}_1 + j30(\mathbf{I}_2 - \mathbf{I}_1) - j30\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2)$$



$$0 = j40(\mathbf{I}_2 - \mathbf{I}_1) + j30\mathbf{I}_1 + 70\mathbf{I}_2$$

Solving,

$$\mathbf{I}_2 = 2/\underline{0^\circ} \text{ A(rms)}; \quad \therefore \mathbf{V}_o = (2/\underline{0^\circ})(70) = 140/\underline{0^\circ} \text{ V(rms)}$$


$$[\text{b}] \quad P = 70|\mathbf{I}_2|^2 = 70(4) = 280 \text{ W}$$

$$[\text{c}] \quad 360/\underline{0^\circ} = (10 + j20)\mathbf{I}_1 - j10(2 + j0); \quad \therefore \mathbf{I}_1 = 8 - j14 \text{ A}$$

$$P_g = (360)(8) = 2880 \text{ W}$$

$$\% \text{ delivered} = \frac{280}{2880}(100) = 9.72\%$$


P 10.45 [a]

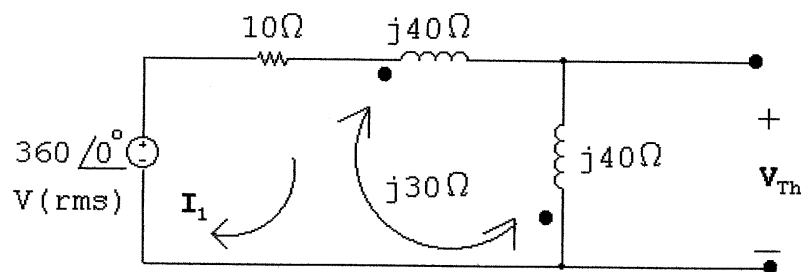

$$360 = 10\mathbf{I}_1 + j40\mathbf{I}_1 - j30\mathbf{I}_1 + j40\mathbf{I}_1 - j30\mathbf{I}_1$$

$$\therefore \mathbf{I}_1 = 7.2 - j14.4 \text{ A(rms)}$$
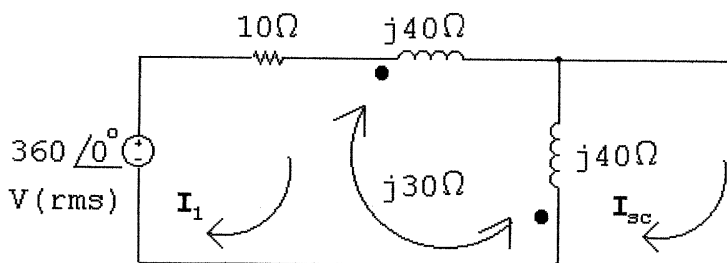
$$\mathbf{V}_{\text{Th}} = j40\mathbf{I}_1 - j30\mathbf{I}_1 = j10\mathbf{I}_1 = 144 + j72 \text{ V}$$




$$360 = (10 + j20)\mathbf{I}_1 - j10\mathbf{I}_{\text{sc}}$$

$$0 = -j10\mathbf{I}_1 + j40\mathbf{I}_{\text{sc}}$$

Solving,

$$\mathbf{I}_{\text{sc}} = 2.215 - j3.877 \text{ A}$$
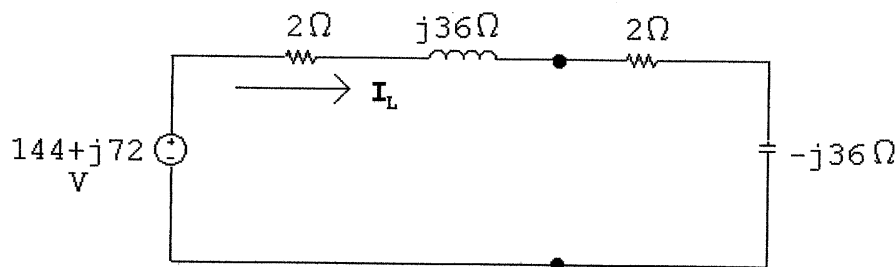
$$Z_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{144 + j72}{2.215 - j3.877} = 2 + j36 \Omega$$




$$\mathbf{I}_L = \frac{144 + j72}{4} = 36 + j18 \text{ A}; \quad \therefore |\mathbf{I}_L| = 18\sqrt{5} \text{ A}$$

$$P_L = (18)^2(5)(2) = 3240 \text{ W}$$


[b]  $360 = (10 + j20)\mathbf{I}_1 - j10(36 + j18); \quad \therefore \mathbf{I}_1 = 18/0^\circ \text{ A}$

$$\therefore P_g = (360)(18) = 6480 \text{ W}$$

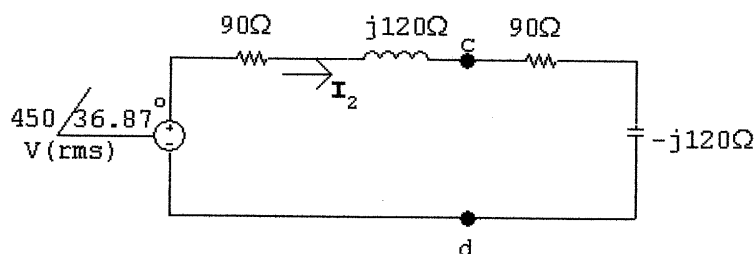P 10.46 [a] From Problem 9.74,  $Z_{Th} = 90 + j120 \Omega$  and  $\mathbf{V}_{Th} = 450/36.87^\circ \text{ V}$ . Thus, for maximum power transfer,  $Z_L = Z_{Th}^* = 90 - j120 \Omega$ :


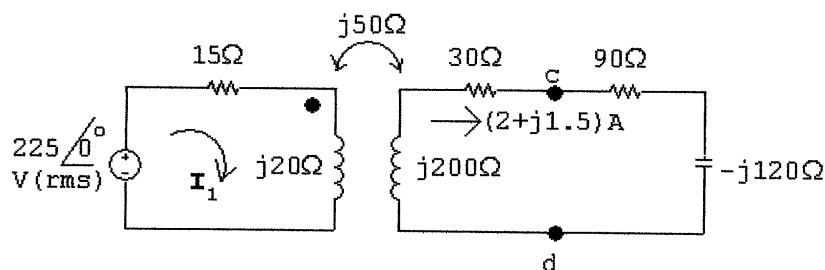
$$\mathbf{I}_2 = \frac{450/36.87^\circ}{180} = 2.5/36.87^\circ = 2 + j1.5 \text{ A}$$



$$225/0^\circ = (15 + j20)\mathbf{I}_1 - j50(2 + j1.5)$$

$$\therefore \mathbf{I}_1 = \frac{150 + j100}{15 + j20} = 6.8 - j2.4 \text{ A}$$

$$S_g(\text{del}) = 225(6.8 + j2.4) = 1530 + j540 \text{ VA}$$

$$P_g = 1530 \text{ W}$$


$$[b] P_{\text{loss}} = |\mathbf{I}_1|^2(15) + |\mathbf{I}_2|^2(30) = 780 + 187.5 = 967.5 \text{ W}$$

$$\% \text{ loss} = \frac{967.50}{1530}(100) = 63.24\%$$

$$\text{P 10.47 [a]} Z_{\text{Th}} = 8 + j15 + \frac{(-j24)(18 + j6)}{18 - j18} = 24 + j7 = 25 \angle 16.26^\circ \Omega$$

$$\therefore R = |Z_{\text{Th}}| = 25 \Omega$$

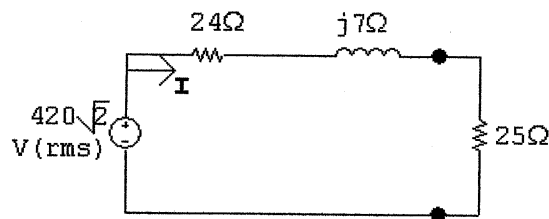
$$[b] \mathbf{V}_{\text{Th}} = \frac{-j24}{18 + j6 - j24}(630 \angle 0^\circ) = 420 - j420 = 420\sqrt{2} \angle -45^\circ \text{ V(rms)}$$



$$\mathbf{I} = \frac{420\sqrt{2} \angle 0^\circ}{49 + j7}; \quad |\mathbf{I}| = \frac{60\sqrt{2}}{\sqrt{50}}$$

$$P = \frac{(3600)(2)}{50}(25) = 3600 \text{ W} = 3.6 \text{ kW}$$

P 10.48 [a]

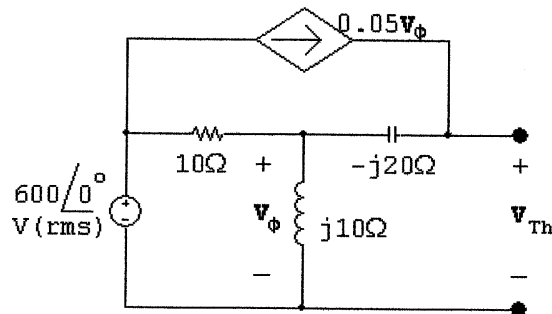


$$\frac{\mathbf{V}_\phi - 600}{10} + \frac{\mathbf{V}_\phi}{j10} - 0.05\mathbf{V}_\phi = 0$$

$$\therefore \mathbf{V}_\phi = 240 + j480 \text{ V(rms)}$$

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_\phi + 0.05\mathbf{V}_\phi(-j20) = \mathbf{V}_\phi(1 - j1) = 720 + j240 \text{ V(rms)}$$

Short circuit current:

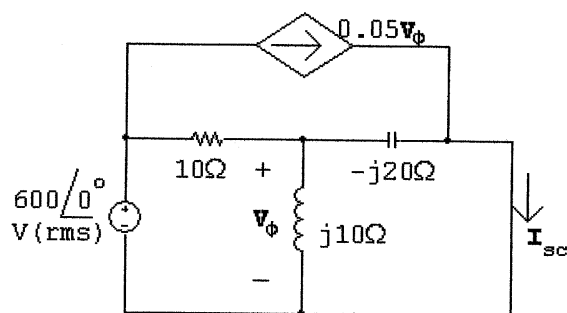

$$I_{sc} = 0.05V_{\phi} + \frac{V_{\phi}}{-j20} = (0.05 + j0.05)V_{\phi}$$

$$\frac{V_{\phi} - 600}{10} + \frac{V_{\phi}}{j10} + \frac{V_{\phi}}{-j20} = 0$$


$$\therefore V_{\phi} = 480 + j240 \text{ V(rms)}$$

$$I_{sc} = (0.05 + j0.05)(480 + j240) = 12 + j36 \text{ A(rms)}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{720 + j240}{12 + j36} = 12 - j16 = 20 \angle -53.13^{\circ} \Omega$$

$$\therefore R_o = 20 \Omega$$


[b]

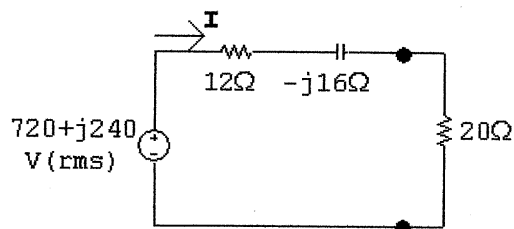

$$I = \frac{720 + j240}{32 - j16} = 15 + j15 = 15\sqrt{2} \angle 45^{\circ} \text{ A(rms)}$$

$$P = (15\sqrt{2})^2(20) = 9000 \text{ W} = 9 \text{ kW}$$


[c]

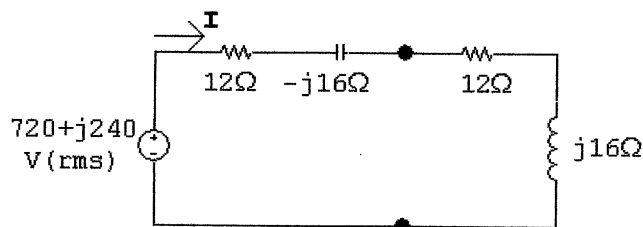

$$I = \frac{720 + j240}{24} = 30 + j10 \text{ A(rms)}$$

$$P = (\sqrt{1000})^2(12) = 12 \text{ kW}$$

[d]

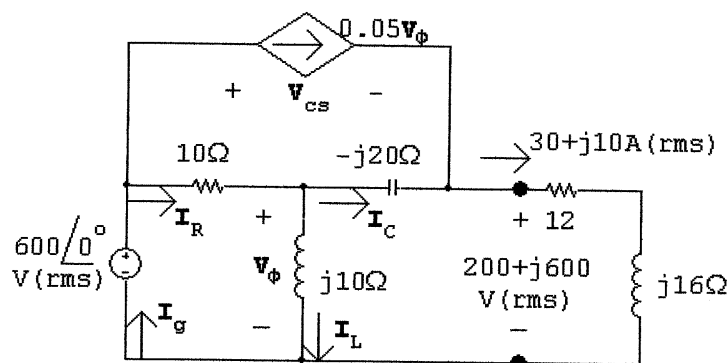

$$\frac{V_\phi - 600}{10} + \frac{V_\phi}{j10} + \frac{V_\phi - 200 - j600}{-j20} = 0$$

$$\therefore V_\phi = 200 + j200 \text{ V}$$

$$0.05V_\phi = 10 + j10 \text{ A}$$

$$10 + j10 + I_C = 30 + j10; \quad \therefore I_C = 20 + j0 \text{ A}$$

$$I_L = \frac{V_\phi}{j10} = 20 - j20 \text{ A}$$

$$I_R = I_C + I_L = 40 - j20 \text{ A}$$

$$I_g = I_R + 0.05V_\phi = 50 - j10 \text{ A (rms)}$$

$$S_g = -600I_g^* = -30,000 - j6000 \text{ VA}$$

$$600 = V_{cs} + 200 + j600; \quad V_{cs} = 400 - j600 \text{ V}$$

$$S_{cs} = (400 - j600)(10 - j10) = -2000 - j10,000 \text{ VA}$$

$$\sum P_{dev} = 30,000 + 2000 = 32,000 \text{ W} = 32 \text{ kW}$$

$$\% \text{ delivered to } Z_o = \frac{12}{32}(100) = 37.50\%$$

Check:

$$\sum P_{abs} = 12,000 + I_R^2(10) = 32 \text{ kW} = \sum P_{dev}$$

$$\sum Q_{dev} = 6000 + 10,000 + |I_C|^2(20) = 24 \text{ kVAR}$$

$$\sum Q_{abs} = |I_L|^2(10) + |I_o|^2(16) = 24 \text{ kVAR} = \sum Q_{dev}$$


P 10.49 [a] First find the Thévenin equivalent:

$$\frac{1}{j\omega C} = \frac{10^6}{j10^4} = -j100 \Omega$$

$$Z_{Th} = \frac{300(-j100)}{300 - j100} = 30 - j90 \Omega$$

$$V_{Th} = \frac{150(-j100)}{300 - j100} = 15 - j45 \text{ V(rms)}$$
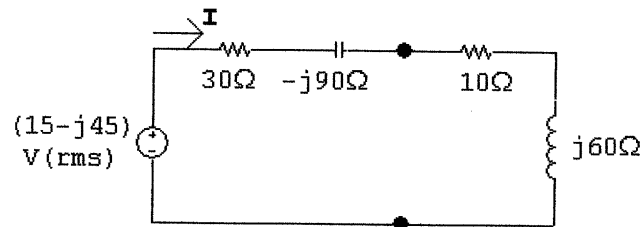
$$j\omega L = j10^4(6 \times 10^{-3}) = j60 \Omega$$



$$I = \frac{15 - j45}{40 - j30} = \frac{1.5}{25}(13 - j9) \text{ A(rms)}$$

$$|I| = \frac{1.5}{25} \sqrt{250} \text{ A(rms)}$$

$$P = \frac{2.25}{625} (250)(10) = 9 \text{ W}$$

[b] Set  $L_o = 8 \text{ mH}$ ; Set  $R_o$  as close as possible to

$$R_o = \sqrt{(30)^2 + (10)^2} = \sqrt{1000} = 31.62 \Omega$$

$$\therefore R_o = 20 \Omega$$

$$[c] I = \frac{15 - j45}{50 - j10} = \frac{3 - j9}{10 - j2} \text{ A(rms)}$$

$$\therefore |I| = \frac{\sqrt{90}}{104}$$

$$P = |I|^2(20) = \frac{(90)(20)}{104} = 17.31 \text{ W}$$

Yes;  $17.31 \text{ W} > 9 \text{ W}$

$$[d] I = \frac{15 - j45}{60} = \frac{1 - j3}{4} \text{ A(rms)}$$

$$P = \left( \frac{\sqrt{10}}{4} \right)^2 30 = 18.75 \text{ W}$$

[e]  $R_o = 30 \Omega$ ;  $L_o = 9 \text{ mH}$

[f] Yes;  $18.75 \text{ W} > 17.31 \text{ W}$

P 10.50 [a]  $L_o = 8 \text{ mH}; \quad R_o = \sqrt{30^2 + 10^2} = 31.62 \Omega$

$$\mathbf{I} = \frac{15(1 - j3)}{61.62 - j10} = \frac{15\sqrt{10}}{62.43} \angle -62.35^\circ \text{ A(rms)}$$

$$P = \left( \frac{15\sqrt{10}}{62.43} \right)^2 (31.62) = 18.26 \text{ W}$$

[b] Yes;  $18.26 \text{ W} > 17.31 \text{ W}$

[c] Yes;  $18.26 \text{ W} < 18.75 \text{ W}$

P 10.51 [a]  $\frac{1}{\omega C} = 240 \Omega; \quad C = \frac{1}{(240)(120\pi)} = 11.05 \mu\text{F}$

[b]  $\mathbf{I}_{\text{wo}} = \frac{4800}{160} + \frac{4800}{j240} = 30 - j20 \text{ A(rms)}$

$$\begin{aligned} \mathbf{V}_{\text{sw}} &= 4800 + (30 - j20)(1 + j8) = 4990 + j220 \\ &= 4994.85 \angle 2.52^\circ \text{ V(rms)} \end{aligned}$$

$$\mathbf{I}_w = \frac{4800}{160} + \frac{4800}{j240} + \frac{4800}{-j240} = 30 + j0 \text{ A(rms)}$$

$$\mathbf{V}_{\text{sw}} = 4800 + 30(1 + j8) = 4830 + j240 = 4835.96 \angle 2.84^\circ \text{ V(rms)}$$


$$\% \text{ increase} = \left( \frac{4994.85}{4835.96} - 1 \right) (100) = 3.29\%$$

[c]  $P_{\ell\text{wo}} = |30 - j20|^2 1 = 1300 \text{ W}$

$$P_{\ell w} = 30^2 (1) = 900 \text{ W}$$

$$\% \text{ increase} = \left( \frac{1300}{900} - 1 \right) (100) = 44.44\%$$

P 10.52 [a]

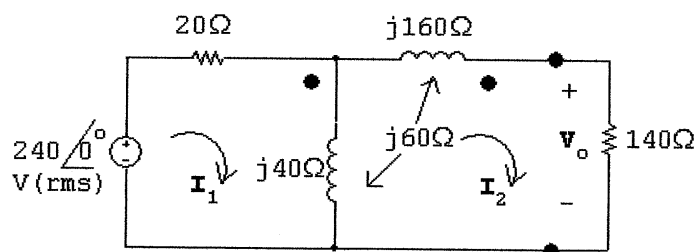

$$240 = 20\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2) - j60\mathbf{I}_2$$

$$0 = j40(\mathbf{I}_2 - \mathbf{I}_1) + j60\mathbf{I}_2 + j160\mathbf{I}_2 + j60(\mathbf{I}_2 - \mathbf{I}_1) + 140\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 6.4 - j2.8 \text{ A(rms);} \quad \mathbf{I}_2 = 2 \angle 0^\circ \text{ A(rms)}$$


$$\mathbf{V}_o = 140\mathbf{I}_2 = 280 \angle 0^\circ \text{ V(rms)}$$

[b]  $P = |\mathbf{I}_2|^2(140) = 560 \text{ W}$

[c]  $P_g = (240)(6.4) = 1536 \text{ W}$

$$\% \text{ delivered} = \frac{560}{1536}(100) = 36.46\%$$

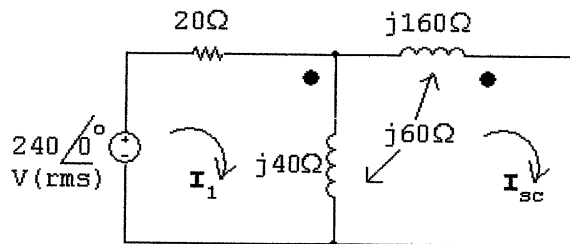P 10.53 [a]  $\mathbf{V}_{\text{Th}} = \frac{240/0^\circ}{20 + j40}(j40) + \frac{240/0^\circ}{20 + j40}(j60) = 480 + j240 \text{ V(rms)}$



From the solution to Problem 10.49 we can write

$$240 = (20 + j40)\mathbf{I}_1 - j100\mathbf{I}_{\text{sc}}$$

$$0 = -j100\mathbf{I}_1 + j320\mathbf{I}_{\text{sc}}$$


Solving,

$$\mathbf{I}_{\text{sc}} = 3.15 - j1.377$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{480 + j240}{3.15 - j1.377} = 100 + j120 = 156.20/50.19^\circ \Omega$$

$$\therefore R_L = 156.20 \Omega$$

[b]

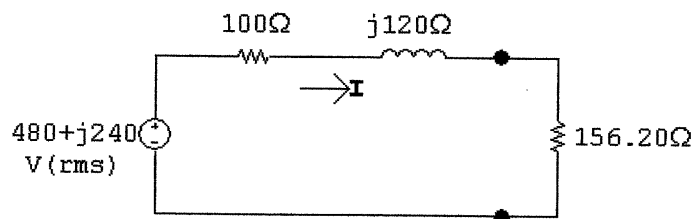


$$\mathbf{I} = \frac{536.66/26.57^\circ}{282.92/25.10^\circ} = 1.90/1.47^\circ$$

$$P = |\mathbf{I}|^2(156.20) = 562.05 \text{ W}$$



P 10.54 [a]

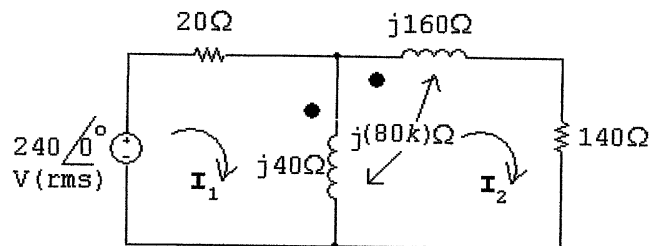

$$240 = 20\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2) + j80k\mathbf{I}_2$$

$$0 = j40(\mathbf{I}_2 - \mathbf{I}_1) - j80k\mathbf{I}_2 + j160\mathbf{I}_2 + j80k(\mathbf{I}_1 - \mathbf{I}_2) + 140\mathbf{I}_2$$

or

$$12 = (1 + j2)\mathbf{I}_1 + j(4k - 2)\mathbf{I}_2$$

$$0 = j(4k - 2)\mathbf{I}_1 + [7 + j(10 - 8k)]\mathbf{I}_2$$

$$N_2 = -j(4k - 2)(12); \quad \mathbf{I}_2 = 0 \text{ when } N_2 = 0$$

$$\mathbf{V}_o = 0 \text{ when } \mathbf{I}_2 = 0$$

$$\therefore k = 0.5$$

[b] When  $\mathbf{I}_2 = 0$ 

$$\mathbf{I}_1 = \frac{12}{1 + j2} = 2.4 - j4.8 \text{ A(rms)}$$

$$P_g = (240)(2.4) = 576 \text{ W}$$

Check:

$$P_{\text{loss}} = |\mathbf{I}_1|^2(20) = 576 \text{ W}$$


$$\text{P 10.55 [a] } \mathbf{V}_{\text{Th}} = \frac{760/0^\circ}{28 + j96}(j50) = 380/16.26^\circ \text{ V}$$

$$Z_{\text{Th}} = 31 + j100 + \left(\frac{50}{100}\right)^2 (28 - j96) = 38 + j76 \Omega$$

$$\therefore Z_L = 38 - j76 \Omega$$

$$\mathbf{I}_L = \frac{380/16.26^\circ}{76} = 4.8 + j1.4 = 5/16.26^\circ \text{ A(rms)}$$

$$P_L = |\mathbf{I}_L|^2(38) = 950 \text{ W}$$

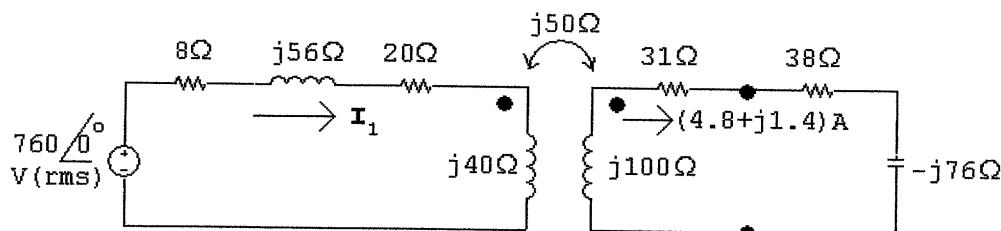

$$760\angle 0^\circ = \mathbf{I}_1(28 + j96) - j50(4.8 + j1.4)$$

$$\therefore \mathbf{I}_1 = \frac{690 + j240}{100\angle 73.74^\circ} = 7.31\angle -54.56^\circ = 4.24 - j5.95 \text{ A}$$

$$S_g(\text{delivered}) = 760(4.24 + j5.95) = 3219.36 + j4523.52 \text{ VA}$$


$$P_{\text{loss}} = |\mathbf{I}_1|^2(8) = 426.96 \text{ W}$$

$$P_{\text{in}}(\text{transformer}) = 3219.36 - 426.96 = 2792.40 \text{ W}$$

$$\% \text{ delivered to } Z_L = \frac{950}{2792.4}(100) = 34.02\%$$

P 10.56 [a]  $j\omega L_1 = j(5000)(2 \times 10^{-3}) = j10 \Omega$
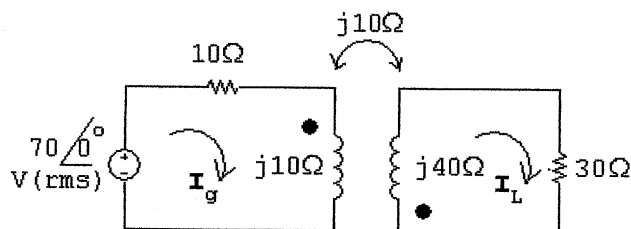
$$j\omega L_2 = j(5000)(8 \times 10^{-3}) = j40 \Omega$$



$$70 = (10 + j10)\mathbf{I}_g + j10\mathbf{I}_L$$

$$0 = j10\mathbf{I}_g + (30 + j40)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 4 - j3 \text{ A}; \quad \mathbf{I}_L = -1 \text{ A}$$

Thus,

$$i_g = 5 \cos(5000t - 36.87^\circ) \text{ A}$$

$$i_L = 1 \cos(5000t - 180^\circ) \text{ A}$$

[b]  $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2}{\sqrt{16}} = 0.5$

[c] When  $t = 100\pi \mu\text{s}$ :

$$5000t = (5000)(100\pi) \times 10^{-6} = 0.5\pi \text{ rad} = 90^\circ$$

$$i_g(100\pi \mu\text{s}) = 5 \cos(53.15^\circ) = 3 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 1 \cos(-90^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(2 \times 10^{-3})(9) + 0 + 0 = 9 \text{ mJ}$$

When  $t = 200\pi \mu\text{s}$ :

$$5000t = \pi \text{ rad} = 180^\circ$$

$$i_g(200\pi \mu\text{s}) = 5 \cos(180 - 36.87^\circ) = -4 \text{ A}$$

$$i_L(200\pi \mu\text{s}) = 1 \cos(180 - 180^\circ) = 1 \text{ A}$$

$$w = \frac{1}{2}(2 \times 10^{-3})(16) + \frac{1}{2}(8 \times 10^{-3})(1) + 2 \times 10^{-3}(-4)(1) = 12 \text{ mJ}$$

[d] From (a),  $I_m = 1 \text{ A}$ ,


$$\therefore P = \frac{1}{2}(1)^2(30) = 15 \text{ W}$$

[e]  $V_{\text{Th}} = \frac{70}{10 + j10}(j10) = 35\sqrt{2}/45^\circ \text{ V}$

$$Z_{\text{Th}} = j40 + \left( \frac{10}{10\sqrt{2}} \right)^2 (10 - j10) = 5 + j35 = \sqrt{1250}/81.78^\circ \Omega$$

$$\therefore R_L = 25\sqrt{2} \Omega$$

[f]

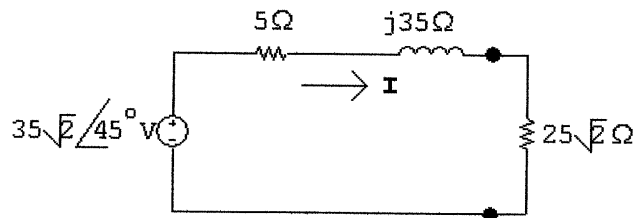

$$I = \frac{35\sqrt{2}/45^\circ}{(5 + 25\sqrt{2}) + j35} = 0.93/4.07^\circ \text{ A}$$


$$P = \frac{1}{2}(0.93)^2(25\sqrt{2}) = 15.18 \text{ W}$$

[g]  $Z_L = Z_{\text{Th}}^* = 5 - j35 \Omega$


$$[h] \mathbf{I} = \frac{35\sqrt{2}/45^\circ}{10} = 3.5\sqrt{2}/45^\circ$$

$$P = \frac{1}{2}(3.5\sqrt{2})^2(5) = 61.25 \text{ W}$$

P 10.57

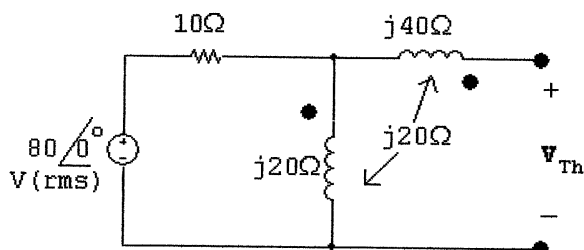
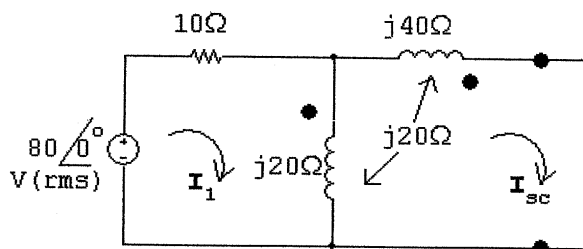
$$\mathbf{V}_{Th} = \frac{80}{10 + j20}(j20) + \frac{80}{10 + j20}(j20) = 128 + j64 \text{ V(rms)}$$




$$80 = 10\mathbf{I}_1 + j20(\mathbf{I}_1 - \mathbf{I}_{sc}) - j20\mathbf{I}_{sc}$$

$$0 = j20(\mathbf{I}_{sc} - \mathbf{I}_1) + j20\mathbf{I}_{sc} + j40\mathbf{I}_{sc} - j20(\mathbf{I}_1 - \mathbf{I}_{sc})$$

Solving,

$$\mathbf{I}_{sc} = 2.76 - j1.10 \text{ A}; \quad \mathbf{Z}_{Th} = \frac{128 + j64}{2.76 - j1.10} = 32 + j36 \Omega$$
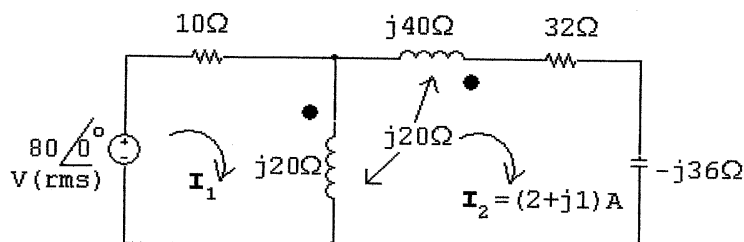
$$\therefore \mathbf{I}_L = \frac{128 + j64}{64} = 2 + j1 \text{ A}$$



$$80 = 10\mathbf{I}_1 + j20(\mathbf{I}_1 - \mathbf{I}_2) - j20\mathbf{I}_2$$


$$\mathbf{I}_2 = 2 + j1 \text{ A}$$

Solving,

$$I_1 = 4/\underline{0^\circ} \text{ A}$$

$$Z_g = 80/4 = 20 + j0 \Omega$$

P 10.58

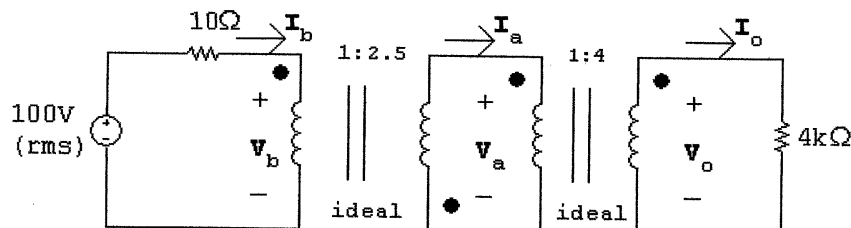


$$V_o = 4V_a; \quad 4I_o = I_a; \quad \text{therefore} \quad \frac{V_a}{I_a} = 250 \Omega$$

$$\frac{V_b}{1} = \frac{-V_a}{2.5}; \quad I_b = -2.5I_a; \quad \text{therefore} \quad \frac{V_b}{I_b} = \frac{250}{6.25} = 40 \Omega$$

Therefore  $I_b = [100/(10 + 40)] = 2 \text{ A (rms)}$ ; since the ideal transformers are lossless,  $P_{4k\Omega} = P_{40\Omega}$ , and the power delivered to the  $4 \text{ k}\Omega$  resistor is  $2^2(40)$  or  $160 \text{ W}$ .

P 10.59 [a]

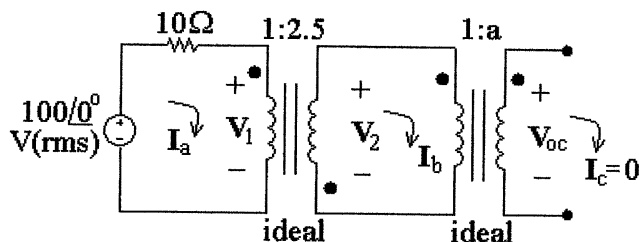


$$10I_a + V_1 = 100; \quad I_a = -2.5I_b; \quad V_1 = -V_2/2.5$$

$$\therefore 10(-2.5I_b) - V_2/2.5 = 100$$

$$I_b = aI_c = 0; \quad V_2 = V_{oc}/a; \quad 10[-2.5(0)] - V_{oc}/2.5a = 100$$

$$\therefore V_{oc} = -250a$$

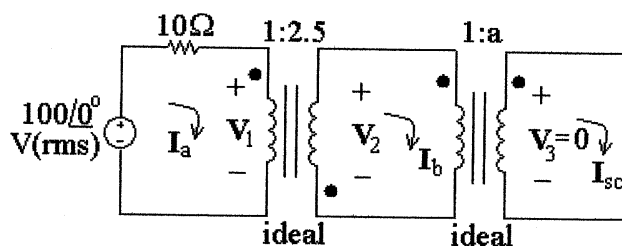

$$10\mathbf{I}_a + \mathbf{V}_1 = 100; \quad \mathbf{I}_a = -2.5\mathbf{I}_b; \quad \mathbf{V}_1 = -\mathbf{V}_2/2.5$$

$$\therefore 10(-2.5\mathbf{I}_b) - \mathbf{V}_2/2.5 = 100$$

$$\mathbf{V}_2 = \mathbf{V}_3/a = 0; \quad \mathbf{I}_b = a\mathbf{I}_{sc}; \quad 10[-2.5(a\mathbf{I}_{sc})] - 0 = 100$$

$$\therefore \mathbf{I}_{sc} = 100/(-2.5a) = -4/a$$


Thus,

$$Z_{Th} = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{-250a}{-4/a} = 62.5a^2$$

For maximum power to the 4 kΩ load,

$$4000 = Z_{Th} = 62.5a^2; \quad \text{so} \quad a = 8$$

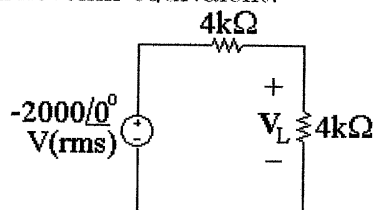- [b] The circuit, with everything to the left of the 4 kΩ load resistor replaced by its Thevenin equivalent:



$$P_L = \frac{V_L^2}{4000} = \frac{(-1000)^2}{4000} = 250 \text{ W}$$

P 10.60 [a]  $Z_{Th} = 32 + j124 + \left(\frac{20}{5}\right)^2 (3 - j4) = 80 + j60 = 100\angle 36.87^\circ \Omega$

$$\therefore Z_{ab} = 100 \Omega$$


$$Z_{ab} = \frac{Z_L}{(1 + N_1/N_2)^2}$$

$$(1 + N_1/N_2)^2 = 3600/100 = 36$$

$$\therefore N_1/N_2 = 5 \quad \text{or} \quad N_2 = N_1/5$$

$$\therefore N_2 = 300 \text{ turns}$$
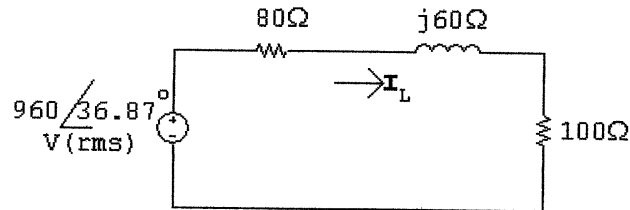
$$[b] \mathbf{V}_{Th} = \frac{240/0^\circ}{3 + j4}(j20) = 960/36.87^\circ \text{ V}$$




$$\mathbf{I} = \frac{960/36.87^\circ}{180 + j60} = 1.6\sqrt{10}/18.43^\circ \text{ A(rms)}$$

$$|\mathbf{I}| = 1.6\sqrt{10} \text{ A(rms)}$$

$$P = |\mathbf{I}|^2(100) = 2560 \text{ W}$$

[c]

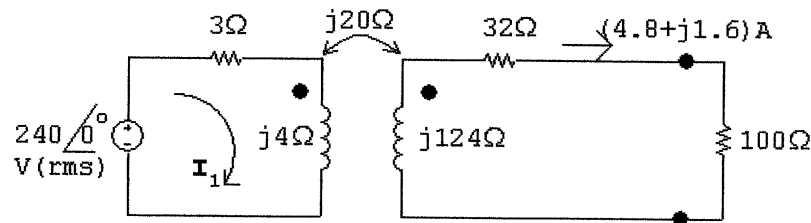

$$240/0^\circ = (3 + j4)\mathbf{I}_1 - j20(4.8 + j1.6)$$


$$\therefore \mathbf{I}_1 = 40.32 - j21.76 \text{ A(rms)}$$

$$P_{\text{gen}} = (240)(40.32) = 9676.80 \text{ W}$$

$$P_{\text{diss}} = 9676.80 - 2560 = 7116.80 \text{ W}$$

$$\% \text{ dissipated} = \frac{7116.80}{9676.80}(100) = 73.54\%$$

P 10.61 [a]

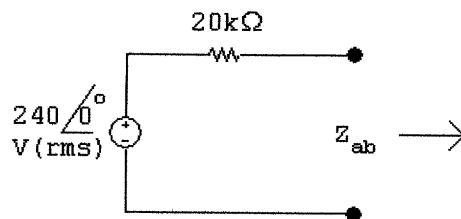

For maximum power transfer,  $Z_{ab} = 20 \text{ k}\Omega$

$$Z_{ab} = \left(1 - \frac{N_1}{N_2}\right)^2 Z_L$$


$$\therefore \left(1 - \frac{N_1}{N_2}\right)^2 = \frac{20,000}{50} = 400$$

$$1 - \frac{N_1}{N_2} = \pm 20; \quad \frac{N_1}{N_2} = 1 \mp 20$$

$$\frac{N_1}{N_2} > 0 \quad \therefore \frac{N_1}{N_2} = 21$$


$$N_2 = \frac{N_1}{21} = \frac{2520}{21} = 120 \text{ turns}$$

[b]

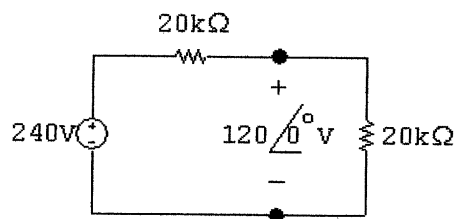

$$P_{50\Omega} = P_{20k\Omega} = \frac{(120)^2}{20} \times 10^{-3} = 720 \text{ mW}$$

[c]

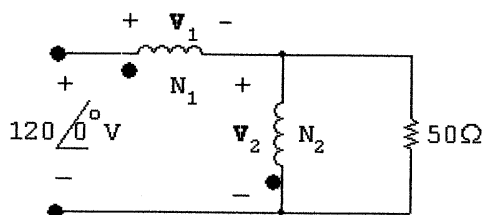

$$V_1 + V_2 = 120; \quad \frac{V_1}{N_1} = -\frac{V_2}{N_2}$$

$$V_2 = -\frac{N_2}{N_1} V_1 = -\frac{V_1}{21}$$


$$V_1 - \frac{V_1}{21} = 120; \quad \therefore V_1 = 126 \text{ V}$$

$$\therefore V_2 = -6 \text{ V}$$

Check the power calculation:

$$P_{50\Omega} = \frac{36}{50} = 0.72 \text{ W} = 720 \text{ mW}$$

[d]

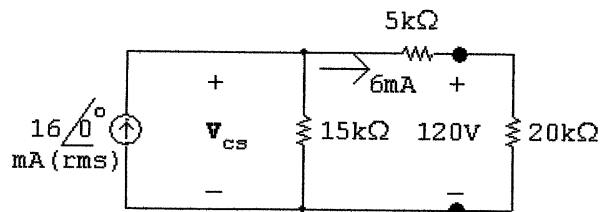


$$V_{cs} = 120 + (6)(5) = 150 \text{ V}$$



$$P_{cs}(\text{del}) = (150)(16) = 2400 \text{ mW}$$

$$\% \text{ delivered} = \frac{720}{2400}(100) = 30\%$$

P 10.62 [a]

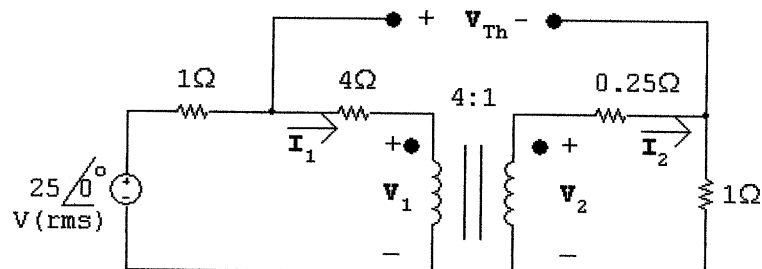


$$V_2 = \frac{1}{4}V_1; \quad I_2 = 4I_1$$

$$25 = 5I_1 + V_1$$

$$0 = -V_2 + 1.25I_2$$

$$\therefore I_1 = 1 \text{ A}; \quad I_2 = 4 \text{ A}$$
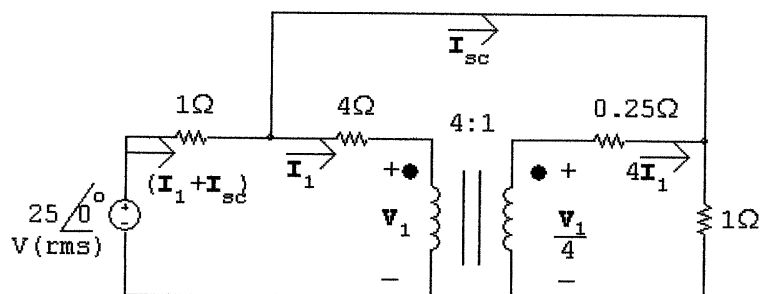
$$25 = (1)I_1 + V_{Th} + (1)I_2; \quad \therefore V_{Th} = 20 \text{ V}$$



$$25 = (I_{sc} + I_1)(1) + 4I_1 + V_1$$


$$25 = (I_{sc} + I_1)(1) + (I_{sc} + 4I_1)(1)$$

$$\frac{V_1}{4} = 4I_1(0.25) + (I_{sc} + 4I_1)(1)$$

Solving,


$$I_{sc} = 20 \text{ A}$$
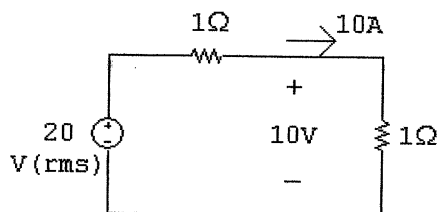
$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{20}{20} = 1 \Omega$$



$$P = (10)^2(1) = 100 \text{ W}$$

[b]

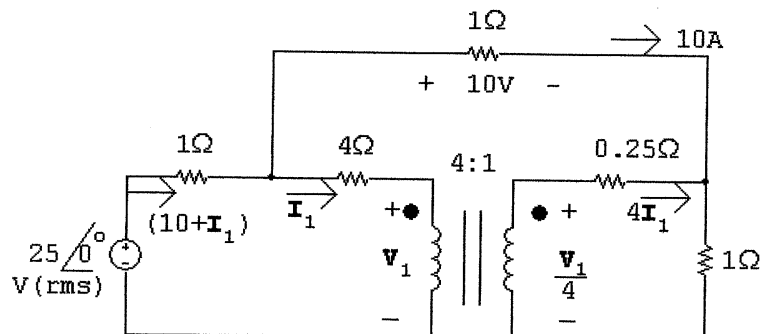

$$25 = (10 + I_1)(1) + 4I_1 + V_1$$

$$\frac{V_1}{4} = 4I_1(0.25) + (4I_1 + 10)(1)$$

Solving,

$$I_1 = -1 \text{ A}$$

$$\therefore P_{\text{source}} = (25)(10 - 1) = 225 \text{ W}$$

$$\% \text{ delivered} = \frac{100}{225}(100) = 44.44\%$$

$$[c] P_{\text{dev}} = 25(10 - 1) = 225 \text{ W}$$


$$P_{1\Omega} = (9)^2(1) = 81 \text{ W}; \quad P_{4\Omega} = (-1)^2(4) = 4 \text{ W}$$

$$P_{1\Omega} = (10)^2(1) = 100 \text{ W}; \quad P_{0.25\Omega} = (-4)^2(0.25) = 4 \text{ W}$$

$$P_{1\Omega} = (10 - 4)^2(1) = 36 \text{ W}$$

$$\sum P_{\text{abs}} = 81 + 4 + 100 + 4 + 36 = 225 \text{ W} = \sum P_{\text{dev}}$$

P 10.63 [a] Open circuit voltage:

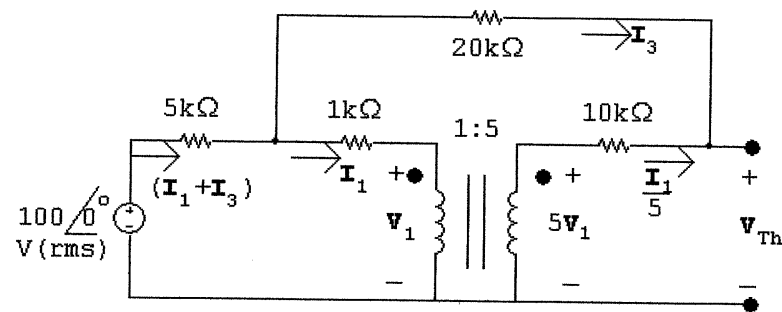

$$100\angle 0^\circ = 5000(\mathbf{I}_1 + \mathbf{I}_3) + 20,000\mathbf{I}_3 + \mathbf{V}_{Th}$$


$$\mathbf{I}_1 = -5\mathbf{I}_3$$

$$\therefore 100 = 5000(-5\mathbf{I}_3 + \mathbf{I}_3) + 20,000\mathbf{I}_3 + \mathbf{V}_{Th}$$

Solving,

$$\mathbf{V}_{Th} = 100\angle 0^\circ \text{ V}$$

Short circuit current:

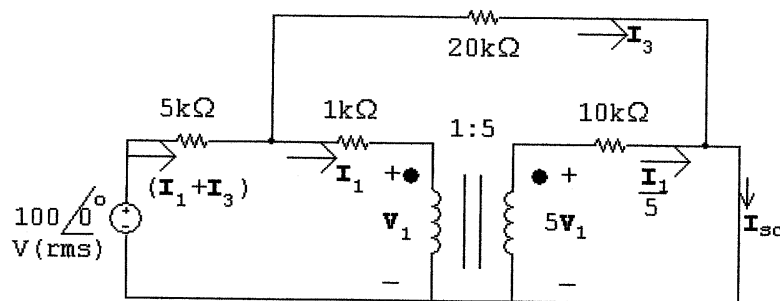

$$100\angle 0^\circ = 5000\mathbf{I}_1 + 5000\mathbf{I}_3 + 1000\mathbf{I}_1 + \mathbf{V}_1$$

$$5\mathbf{V}_1 = 25,000(\mathbf{I}_1/5); \quad \therefore \mathbf{V}_1 = 1000\mathbf{I}_1$$

$$\therefore 100\angle 0^\circ = 7000\mathbf{I}_1 + 5000\mathbf{I}_3$$


Also,

$$100\angle 0^\circ = 5000(\mathbf{I}_1 + \mathbf{I}_3) + 20,000\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 13.33 \text{ mA}; \quad \mathbf{I}_3 = 1.33 \text{ mA}; \quad \mathbf{I}_{sc} = \mathbf{I}_1/5 + \mathbf{I}_3 = 4 \text{ mA}$$

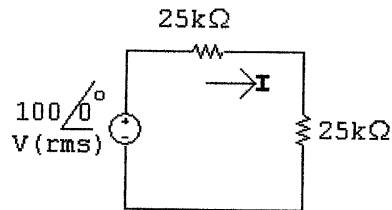
$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{100}{0.004} = 25 \text{ k}\Omega$$



$$I = \frac{100/0^\circ}{50,000} = 2/0^\circ \text{ mA(rms)}$$

$$P = (0.002)^2(25,000) = 100 \text{ mW}$$

[b]

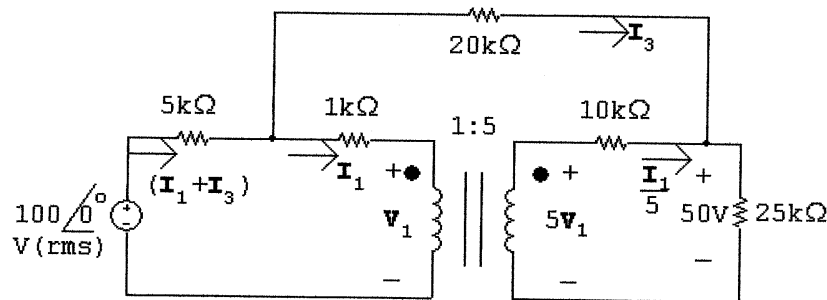

$$100 = 5000(I_1 + I_3) + 20,000I_3 + 50$$

$$5V_1 = 10,000 \left( \frac{I_1}{5} \right) + 50$$

$$100 = 5000(I_1 + I_3) + 1000I_1 + V_1$$

$$\therefore I_1 = 14.82 \text{ mA}; \quad I_3 = -0.963 \text{ mA}; \quad I_1 + I_3 = 13.857/0^\circ \text{ mA}$$

$$P_{100V}(\text{developed}) = 100(13.857 \text{ m}) = 1386 \text{ mW}$$

$$\therefore \% \text{ delivered} = \frac{100}{1386}(100) = 7.22\%$$

$$[c] P_{RL} = 100 \text{ mW}; \quad P_{10k\Omega} = (2.96 \text{ m})^2(10 \text{ k}) = 87.9 \text{ mW}$$

$$P_{20k\Omega} = (0.963 \text{ m})^2(20 \text{ k}) = 18.6 \text{ mW}; \quad P_{5k\Omega} = (13.857 \text{ m})^2(5000) = 960.1 \text{ mW}$$

$$P_{1k\Omega} = (14.82 \text{ m})^2(1000) = 219.6 \text{ mW}$$

$$\sum P_{abs} = 100 + 87.9 + 18.6 + 960.1 + 219.6 = 1386 \text{ mW} = \sum P_{dev}$$


P 10.64 [a] Replace the circuit to the left of the primary winding with a Thévenin equivalent:

$$\mathbf{V}_{\text{Th}} = \frac{250/0^\circ}{25 + j50}(j50) = 200 + j100 \text{ mV}$$

$$\mathbf{Z}_{\text{Th}} = 20 + \frac{(25)(j50)}{25 + j50} = 40 + j10 \Omega$$

Transfer the secondary impedance to the primary side:
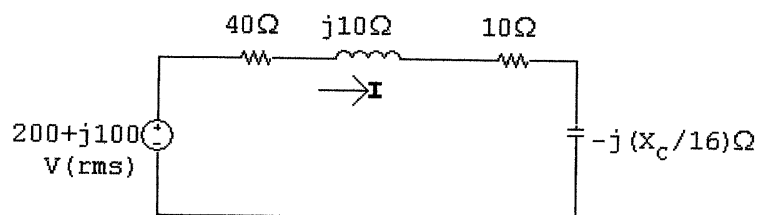
$$\mathbf{Z}_p = \frac{1}{16}(160 - jX_C) = 10 - j\frac{X_C}{16} \Omega$$



Now maximize  $\mathbf{I}$  by setting  $(X_C/16) = 10 \Omega$ :

$$\therefore C = \frac{10^{-3}}{(160)(50)} = 125 \text{ nF}$$

$$[\text{b}] \mathbf{I} = \frac{200 + j100}{50} = 4 + j2 \text{ mA}$$

$$|\mathbf{I}| = \sqrt{20} \text{ mA}$$

$$P = (20 \times 10^{-6})(10) = 200 \mu\text{W}$$

$$[\text{c}] \frac{R_o}{16} = 40 \Omega; \quad \therefore R_o = 640 \Omega$$


$$[\text{d}] \mathbf{I} = \frac{200 + j100}{80} = 2.5 + j1.25 \text{ mA}$$

$$P = |\mathbf{I}|^2(40) = 312.50 \mu\text{W}$$


$$\text{P 10.65 [a]} \mathbf{Z}_{\text{ab}} = 30,000 - j10,000 = \left(1 - \frac{N_1}{N_2}\right)^2 \mathbf{Z}_L$$

$$\therefore \mathbf{Z}_L = \frac{1}{4}(30,000 - j10,000) = 7500 - j2500 \Omega$$

[b]

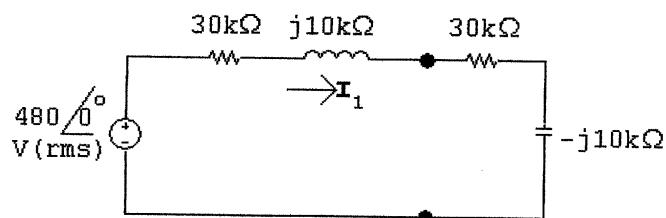
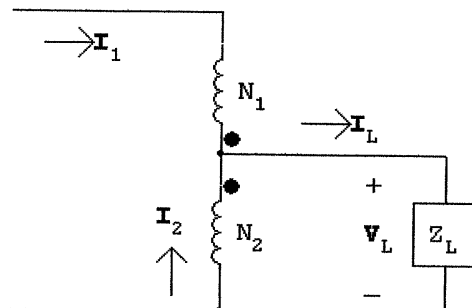
$$I_1 = \frac{480}{60} \times 10^{-3} = 8\angle 0^\circ \text{ mA}$$



$$N_1 I_1 = -N_2 I_2$$

$$I_2 = -3I_1 = -24\angle 0^\circ \text{ mA}$$

$$I_L = I_1 + I_2 = -16\angle 0^\circ \text{ mA}$$

$$V_L = (7500 - j2500)I_L = -120 + j40 = 126.49\angle 161.57^\circ \text{ V(rms)}$$

P 10.66 [a] Begin with the MEDIUM setting, as shown in Fig. 10.31, as it involves only the resistor  $R_2$ . Then,

$$P_{\text{med}} = 500 \text{ W} = \frac{V^2}{R_2} = \frac{120^2}{R_2}$$

Thus,

$$R_2 = \frac{120^2}{500} = 28.8 \Omega$$

[b] Now move to the LOW setting, as shown in Fig. 10.30, which involves the resistors  $R_1$  and  $R_2$  connected in series:

$$P_{\text{low}} = \frac{V^2}{R_1 + R_2} = \frac{V^2}{R_1 + 28.8} = 250 \text{ W}$$

Thus,

$$R_1 = \frac{120^2}{250} - 28.8 = 28.8 \Omega$$

[c] Note that the HIGH setting has  $R_1$  and  $R_2$  in parallel:

$$P_{\text{high}} = \frac{V^2}{R_1 \parallel R_2} = \frac{120^2}{28.8 \parallel 28.8} = 1000 \text{ W}$$

If the HIGH setting has required power other than 1000 W, this problem could not have been solved. In other words, the HIGH power setting was chosen in such a way that it would be satisfied once the two resistor values were calculated to satisfy the LOW and MEDIUM power settings.

$$\text{P 10.67 [a]} \quad P_L = \frac{V^2}{R_1 + R_2}; \quad R_1 + R_2 = \frac{V^2}{P_L}$$

$$P_M = \frac{V^2}{R_2}; \quad R_2 = \frac{V^2}{P_M}$$

$$P_H = \frac{V^2(R_1 + R_2)}{R_1 R_2}$$

$$R_1 + R_2 = \frac{V^2}{P_L}; \quad R_1 = \frac{V^2}{P_L} - \frac{V^2}{P_M}$$

$$P_H = \frac{V^2 V^2 / P_L}{\left(\frac{V^2}{P_L} - \frac{V^2}{P_M}\right) \left(\frac{V^2}{P_M}\right)} = \frac{P_M P_L P_M}{P_L (P_M - P_L)}$$

$$P_H = \frac{P_M^2}{P_M - P_L}$$

$$\text{[b]} \quad P_H = \frac{(750)^2}{(750 - 250)} = 1125 \text{ W}$$

P 10.68 First solve the expression derived in P10.67 for  $P_M$  as a function of  $P_L$  and  $P_H$ . Thus

$$P_M - P_L = \frac{P_M^2}{P_H} \quad \text{or} \quad \frac{P_M^2}{P_H} - P_M + P_L = 0$$

$$P_M^2 - P_M P_H + P_L P_H = 0$$

$$\begin{aligned} \therefore P_M &= \frac{P_H}{2} \pm \sqrt{\left(\frac{P_H}{2}\right)^2 - P_L P_H} \\ &= \frac{P_H}{2} \pm P_H \sqrt{\frac{1}{4} - \left(\frac{P_L}{P_H}\right)} \end{aligned}$$

For the specified values of  $P_L$  and  $P_H$

$$P_M = 500 \pm 1000\sqrt{0.25 - 0.24} = 500 \pm 100$$

$$\therefore P_{M1} = 600 \text{ W}; \quad P_{M2} = 400 \text{ W}$$

Note in this case we design for two medium power ratings

If  $P_{M1} = 600 \text{ W}$

$$R_2 = \frac{(120)^2}{600} = 24 \Omega$$

$$R_1 + R_2 = \frac{(120)^2}{240} = 60 \Omega$$

$$R_1 = 60 - 24 = 36 \Omega$$

$$\text{CHECK: } P_H = \frac{(120)^2(60)}{(36)(24)} = 1000 \text{ W}$$

If  $P_{M2} = 400 \text{ W}$

$$R_2 = \frac{(120)^2}{400} = 36 \Omega$$

$$R_1 + R_2 = 60 \Omega \quad (\text{as before})$$

$$R_1 = 24 \Omega$$

CHECK:  $P_H = 1000 \text{ W}$

$$\text{P 10.69 } R_1 + R_2 + R_3 = \frac{(120)^2}{600} = 24 \Omega$$

$$R_2 + R_3 = \frac{(120)^2}{900} = 16 \Omega$$

$$\therefore R_1 = 24 - 16 = 8 \Omega$$

$$R_3 + R_1 \parallel R_2 = \frac{(120)^2}{1200} = 12 \Omega$$

$$\therefore 16 - R_2 + \frac{8R_2}{8 + R_2} = 12$$

$$R_2 - \frac{8R_2}{8 + R_2} = 4$$

$$8R_2 + R_2^2 - 8R_2 = 32 + 4R_2$$

$$R_2^2 - 4R_2 - 32 = 0$$

$$R_2 = 2 \pm \sqrt{4 + 32} = 2 \pm 6$$

$$\therefore R_2 = 8 \Omega; \quad \therefore R_3 = 8 \Omega$$



$$\text{P 10.70 } R_2 = \frac{(220)^2}{500} = 96.8 \, \Omega$$

$$R_1 + R_2 = \frac{(220)^2}{250} = 193.6 \, \Omega$$

$$\therefore R_1 = 96.8 \, \Omega$$

$$\text{CHECK: } R_1 \parallel R_2 = 48.4 \, \Omega$$

$$P_H = \frac{(220)^2}{48.4} = 1000 \, \text{W}$$