

# The Fourier Transform

## Assessment Problems

$$\begin{aligned}
 \text{AP 17.1 [a]} \quad F(\omega) &= \int_{-\tau/2}^0 (-Ae^{-j\omega t}) dt + \int_0^{\tau/2} Ae^{-j\omega t} dt \\
 &= \frac{A}{j\omega} [2 - e^{j\omega\tau/2} - e^{-j\omega\tau/2}] \\
 &= \frac{2A}{j\omega} \left[ 1 - \frac{e^{j\omega\tau/2} - e^{-j\omega\tau/2}}{2} \right] \\
 &= \frac{-j2A}{\omega} \left[ 1 - \frac{\cos \omega\tau}{2} \right]
 \end{aligned}$$

$$\text{[b]} \quad F(\omega) = \int_0^{\infty} te^{-at}e^{-j\omega t} dt = \int_0^{\infty} te^{-(a+j\omega)t} dt = \frac{1}{(a+j\omega)^2}$$

AP 17.2

$$\begin{aligned}
 f(t) &= \frac{1}{2\pi} \left\{ \int_{-3}^{-2} 4e^{jtw} d\omega + \int_{-2}^2 e^{jtw} d\omega + \int_2^3 4e^{jtw} d\omega \right\} \\
 &= \frac{1}{j2\pi t} \{ 4e^{-j2t} - 4e^{-j3t} + e^{j2t} - e^{-j2t} + 4e^{j3t} - 4e^{j2t} \} \\
 &= \frac{1}{\pi t} \left[ \frac{3e^{-j2t} - 3e^{j2t}}{j2} + \frac{4e^{j3t} - 4e^{-j3t}}{j2} \right] \\
 &= \frac{1}{\pi t} (4 \sin 3t - 3 \sin 2t)
 \end{aligned}$$

$$\text{AP 17.3 [a]} \quad F(\omega) = F(s) \big|_{s=j\omega} = \mathcal{L}\{e^{-at} \sin \omega_0 t\} \big|_{s=j\omega}$$

$$= \frac{\omega_0}{(s+a)^2 + \omega_0^2} \bigg|_{s=j\omega} = \frac{\omega_0}{(a+j\omega)^2 + \omega_0^2}$$

$$\text{[b]} \quad F(\omega) = \mathcal{L}\{f^-(t)\} \big|_{s=-j\omega} = \left[ \frac{1}{(s+a)^2} \right]_{s=-j\omega} = \frac{1}{(a-j\omega)^2}$$

$$[c] \quad f^+(t) = te^{-at}, \quad f^-(t) = -te^{-at}$$

$$\mathcal{L}\{f^+(t)\} = \frac{1}{(s+a)^2}, \quad \mathcal{L}\{f^-(t)\} = \frac{-1}{(s+a)^2}$$

$$\text{Therefore} \quad F(\omega) = \frac{1}{(a+j\omega)^2} - \frac{1}{(a-j\omega)^2} = \frac{-j4a\omega}{(a^2+\omega^2)^2}$$

$$\text{AP 17.4 [a]} \quad f'(t) = \frac{2A}{\tau}, \quad -\frac{\tau}{2} < t < 0; \quad f'(t) = \frac{-2A}{\tau}, \quad 0 < t < \frac{\tau}{2}$$

$$\begin{aligned} \therefore f'(t) &= \frac{2A}{\tau}[u(t+\tau/2) - u(t)] - \frac{2A}{\tau}[u(t) - u(t-\tau/2)] \\ &= \frac{2A}{\tau}u(t+\tau/2) - \frac{4A}{\tau}u(t) + \frac{2A}{\tau}u(t-\tau/2) \end{aligned}$$

$$\therefore f''(t) = \frac{2A}{\tau}\delta\left(t+\frac{\tau}{2}\right) - \frac{4A}{\tau} + \frac{2A}{\tau}\delta\left(t-\frac{\tau}{2}\right)$$

$$\begin{aligned} [b] \quad \mathcal{F}\{f''(t)\} &= \left[ \frac{2A}{\tau}e^{j\omega\tau/2} - \frac{4A}{\tau} + \frac{2A}{\tau}e^{-j\omega\tau/2} \right] \\ &= \frac{4A}{\tau} \left[ \frac{e^{j\omega\tau/2} + e^{-j\omega\tau/2}}{2} - 1 \right] = \frac{4A}{\tau} \left[ \cos\left(\frac{\omega\tau}{2}\right) - 1 \right] \end{aligned}$$

$$[c] \quad \mathcal{F}\{f''(t)\} = (j\omega)^2 F(\omega) = -\omega^2 F(\omega); \quad \text{therefore} \quad F(\omega) = -\frac{1}{\omega^2} \mathcal{F}\{f''(t)\}$$

$$\text{Thus we have} \quad F(\omega) = -\frac{1}{\omega^2} \left\{ \frac{4A}{\tau} \left[ \cos\left(\frac{\omega\tau}{2}\right) - 1 \right] \right\}$$

AP 17.5

$$v(t) = V_m \left[ u\left(t + \frac{\tau}{2}\right) - u\left(t - \frac{\tau}{2}\right) \right]$$

$$\mathcal{F}\left\{u\left(t + \frac{\tau}{2}\right)\right\} = \left[ \pi\delta(\omega) + \frac{1}{j\omega} \right] e^{j\omega\tau/2}$$

$$\mathcal{F}\left\{u\left(t - \frac{\tau}{2}\right)\right\} = \left[ \pi\delta(\omega) + \frac{1}{j\omega} \right] e^{-j\omega\tau/2}$$

$$\begin{aligned} \text{Therefore} \quad V(\omega) &= V_m \left[ \pi\delta(\omega) + \frac{1}{j\omega} \right] [e^{j\omega\tau/2} - e^{-j\omega\tau/2}] \\ &= j2V_m\pi\delta(\omega) \sin\left(\frac{\omega\tau}{2}\right) + \frac{2V_m}{\omega} \sin\left(\frac{\omega\tau}{2}\right) \\ &= \frac{(V_m\tau) \sin(\omega\tau/2)}{\omega\tau/2} \end{aligned}$$

AP 17.6 [a]  $I_g(\omega) = \mathcal{F}\{10\text{sgn } t\} = \frac{20}{j\omega}$

[b]  $H(s) = \frac{V_o}{I_g}$

Using current division and Ohm's law,

$$V_o = -I_2 s = -\left[\frac{4}{4+1+s}\right](-I_g)s = \frac{4s}{5+s}I_g$$

$$H(s) = \frac{4s}{s+5}, \quad H(j\omega) = \frac{j4\omega}{5+j\omega}$$

[c]  $V_o(\omega) = H(j\omega) \cdot I_g(\omega) = \left(\frac{j4\omega}{5+j\omega}\right) \left(\frac{20}{j\omega}\right) = \frac{80}{5+j\omega}$

[d]  $v_o(t) = 80e^{-5t}u(t) \text{ V}$

[e] Using current division,

$$i_1(0^-) = \frac{1}{5}i_g = \frac{1}{5}(-10) = -2 \text{ A}$$

[f]  $i_1(0^+) = i_g + i_2(0^+) = 10 + i_2(0^-) = 10 + 8 = 18 \text{ A}$

[g] Using current division,

$$i_2(0^-) = \frac{4}{5}(10) = 8 \text{ A}$$

[h] Since the current in an inductor must be continuous,

$$i_2(0^+) = i_2(0^-) = 8 \text{ A}$$

[i] Since the inductor behaves as a short circuit for  $t < 0$ ,

$$v_o(0^-) = 0 \text{ V}$$

[j]  $v_o(0^+) = 1i_2(0^+) + 4i_1(0^+) = 80 \text{ V}$

AP 17.7 [a]  $V_g(\omega) = \frac{1}{1-j\omega} + \pi\delta(\omega) + \frac{1}{j\omega}$

$$H(s) = \frac{V_a}{V_g} = \frac{0.5\|(1/s)}{1+0.5\|(1/s)} = \frac{1}{s+3}, \quad H(j\omega) = \frac{1}{3+j\omega}$$

$$V_a(\omega) = H(j\omega)V_g(j\omega)$$

$$\begin{aligned} &= \frac{1}{(1-j\omega)(3+j\omega)} + \frac{1}{j\omega(3+j\omega)} + \frac{\pi\delta(\omega)}{3+j\omega} \\ &= \frac{1/4}{1-j\omega} + \frac{1/4}{3+j\omega} + \frac{1/3}{j\omega} - \frac{1/3}{3+j\omega} + \frac{\pi\delta(\omega)}{3+j\omega} \\ &= \frac{1/4}{1-j\omega} + \frac{1/3}{j\omega} - \frac{1/12}{3+j\omega} + \frac{\pi\delta(\omega)}{3+j\omega} \end{aligned}$$

Therefore  $v_a(t) = \left[\frac{1}{4}e^tu(-t) + \frac{1}{6}\text{sgn } t - \frac{1}{12}e^{-3t}u(t) + \frac{1}{6}\right] \text{ V}$

$$[\mathbf{b}] \quad v_a(0^-) = \frac{1}{4} - \frac{1}{6} + 0 + \frac{1}{6} = \frac{1}{4} \text{ V}$$

$$v_a(0^+) = 0 + \frac{1}{6} - \frac{1}{12} + \frac{1}{6} = \frac{1}{4} \text{ V}$$

$$v_a(\infty) = 0 + \frac{1}{6} + 0 + \frac{1}{6} = \frac{1}{3} \text{ V}$$

AP 17.8

$$v(t) = 4te^{-t}u(t); \quad V(\omega) = \frac{4}{(1 + j\omega)^2}$$

$$\text{Therefore } |V(\omega)| = \frac{4}{1 + \omega^2}$$

$$\begin{aligned} W_{1\Omega} &= \frac{1}{\pi} \int_0^{\sqrt{3}} \left[ \frac{4}{(1 + \omega^2)} \right]^2 d\omega \\ &= \frac{16}{\pi} \left\{ \frac{1}{2} \left[ \frac{\omega}{\omega^2 + 1} + \tan^{-1} \frac{\omega}{1} \right]_0^{\sqrt{3}} \right\} \\ &= 16 \left[ \frac{\sqrt{3}}{8\pi} + \frac{1}{6} \right] = 3.769 \text{ J} \end{aligned}$$

$$W_{1\Omega}(\text{total}) = \frac{8}{\pi} \left[ \frac{\omega}{\omega^2 + 1} + \tan^{-1} \frac{\omega}{1} \right]_0^{\infty} = \frac{8}{\pi} \left[ 0 + \frac{\pi}{2} \right] = 4 \text{ J}$$

$$\text{Therefore } \% = \frac{3.769}{4}(100) = 94.23\%$$

AP 17.9

$$|V(\omega)| = 6 - \left( \frac{6}{2000\pi} \right) \omega, \quad 0 \leq \omega \leq 2000\pi$$

$$|V(\omega)|^2 = 36 - \left( \frac{72}{2000\pi} \right) \omega + \left( \frac{36}{4\pi^2 \times 10^6} \right) \omega^2$$

$$\begin{aligned} W_{1\Omega} &= \frac{1}{\pi} \int_0^{2000\pi} \left[ 36 - \frac{72\omega}{2000\pi} + \frac{36 \times 10^{-6}}{4\pi^2} \omega^2 \right] d\omega \\ &= \frac{1}{\pi} \left[ 36\omega - \frac{72\omega^2}{4000\pi} + \frac{36 \times 10^{-6}\omega^3}{12\pi^2} \right]_0^{2000\pi} \\ &= \frac{1}{\pi} \left[ 36(2000\pi) - \frac{72}{4000\pi}(2000\pi)^2 + \frac{36 \times 10^{-6}(2000\pi)^3}{12\pi^2} \right] \end{aligned}$$

$$= 36(2000) - \frac{72(2000)^2}{4000} + \frac{36 \times 10^{-6}(2000)^3}{12}$$

$$= 24 \text{ kJ}$$

$$W_{6\text{k}\Omega} = \frac{24 \times 10^3}{6 \times 10^3} = 4 \text{ J}$$

## Problems

$$\text{P 17.1 [a]} \quad F(\omega) = \int_{-2}^2 \left[ A \sin\left(\frac{\pi}{2}t\right) \right] e^{-j\omega t} dt = \frac{-j4\pi A}{\pi^2 - 4\omega^2} \sin 2\omega$$

$$\begin{aligned} \text{[b]} \quad F(\omega) &= \int_{-\tau/2}^0 \left( \frac{2A}{\tau}t + A \right) e^{-j\omega t} dt + \int_0^{\tau/2} \left( \frac{-2A}{\tau}t + A \right) e^{-j\omega t} dt \\ &= \frac{4A}{\omega^2\tau} \left[ 1 - \cos\left(\frac{\omega\tau}{2}\right) \right] \end{aligned}$$

$$\begin{aligned} \text{P 17.2 [a]} \quad F(\omega) &= \int_{-\infty}^{\infty} f(t)e^{-j\omega t} dt \\ &= \int_{-\tau/2}^0 \frac{-2A}{\tau}te^{-j\omega t} dt + \int_0^{\tau/2} \frac{2A}{\tau}te^{-j\omega t} dt \end{aligned}$$

$$= \text{Int1} + \text{Int2}$$

$$\begin{aligned} \text{Int1} &= \frac{-2A}{\tau} \int_{-\tau/2}^0 te^{-j\omega t} dt \\ &= \frac{-2A}{\tau} \left\{ \frac{e^{-j\omega t}}{-\omega^2} (-j\omega t - 1) \right\} \Big|_{-\tau/2}^0 \\ &= \frac{-2A}{\omega^2\tau} \left\{ 1 - [e^{j\omega\tau/2}(-j\omega\tau/2 + 1)] \right\} \\ &= \frac{2A}{\omega^2\tau} \left\{ e^{j\omega\tau/2}(1 - j\omega\tau/2) - 1 \right\} \end{aligned}$$


$$\begin{aligned} \text{Int2} &= \frac{2A}{\tau} \int_0^{\tau/2} te^{-j\omega t} dt \\ &= \frac{2A}{\tau} \left\{ \frac{e^{-j\omega t}}{-\omega^2} (-j\omega t - 1) \right\} \Big|_0^{\tau/2} \\ &= \frac{2A}{\omega^2\tau} \left\{ e^{j\omega\tau/2}(j\omega\tau/2 + 1) - 1 \right\} \end{aligned}$$

$$\begin{aligned} F(\omega) &= \text{Int1} + \text{Int2} \\ &= \frac{2A}{\omega^2\tau} \left\{ 2 \cos \frac{\omega\tau}{2} + \omega\tau \sin \frac{\omega\tau}{2} - 2 \right\} \end{aligned}$$

[b] After using L'Hopital's rule we have

$$F(0) = \lim_{\omega \rightarrow 0} \frac{2A\tau \cos(\omega\tau/2)}{4} = \frac{A\tau}{2}$$

[c]

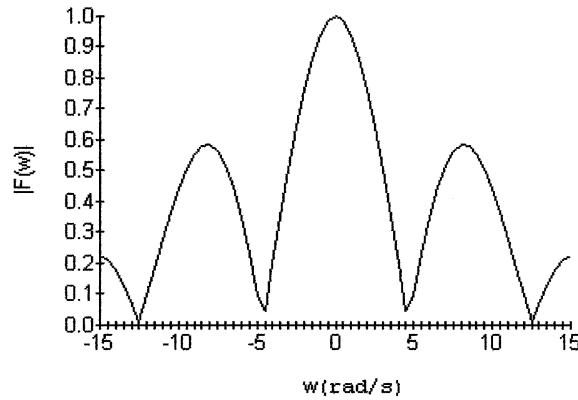

P 17.3 [a]  $F(\omega) = j \frac{2A}{\omega_o} \omega \quad -\frac{\omega_o}{2} \leq \omega \leq \frac{\omega_o}{2}$

$$\begin{aligned} f(t) &= \frac{1}{2\pi} \int_{-\omega_o/2}^{\omega_o/2} \frac{j2A}{\omega_o} \omega e^{j\omega t} d\omega \\ &= \frac{jA}{\pi\omega_o} \left[ \frac{e^{j\omega t}}{-t^2} (jt\omega - 1) \right]_{-\omega_o/2}^{\omega_o/2} \\ &= \frac{A}{\pi\omega_o t^2} [\omega_o t \cos(\omega_o t/2) - 2 \sin(\omega_o t/2)] \end{aligned}$$


[b]  $f(t) = \frac{A}{\pi\omega_o} \left[ \frac{\omega_o t \cos(\omega_o t/2) - 2 \sin(\omega_o t/2)}{t^2} \right]$

$$\begin{aligned} f(0) &= \lim_{t \rightarrow 0} \left\{ \frac{A}{\pi\omega_o} \left[ \frac{\omega_o t \left( -\frac{\omega_o}{2} \sin \frac{\omega_o t}{2} \right) + \omega_o \cos \frac{\omega_o t}{2} - \omega_o \cos \frac{\omega_o t}{2} }{2t} \right] \right\} \\ &= \lim_{t \rightarrow 0} \left\{ \frac{A}{\pi\omega_o} \left[ \frac{-\omega_o^2}{4} \sin \left( \frac{\omega_o t}{2} \right) \right] \right\} = 0 \end{aligned}$$

[c] When  $A = 2\pi$  and  $\omega_o = 2$  rad/s

$$f(t) = \frac{1}{t^2} [2t \cos t - 2 \sin t]$$
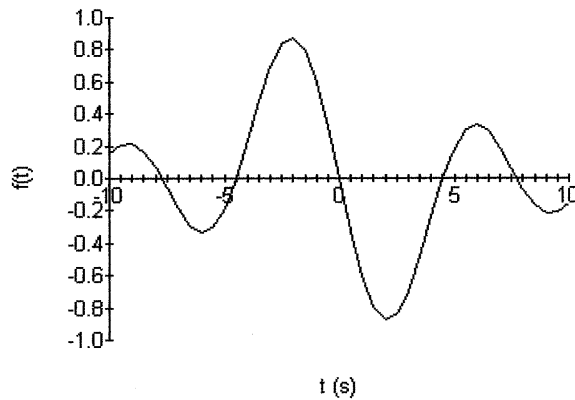
$$f(-t) = -f(t) \quad \text{odd function}$$



P 17.4 [a]  $F(s) = \mathcal{L}\{te^{-at}\} = \frac{1}{(s+a)^2}$

$$F(\omega) = F(s) \Big|_{s=j\omega} + F(s) \Big|_{s=-j\omega}$$

$$\begin{aligned} F(\omega) &= \left[ \frac{1}{(a+j\omega)^2} \right] + \left[ \frac{1}{(a-j\omega)^2} \right] \\ &= \frac{2(a^2 - \omega^2)}{(a^2 - \omega^2)^2 + 4a^2\omega^2} = \frac{2(a^2 - \omega^2)}{(a^2 + \omega^2)^2} \end{aligned}$$

[b]  $F(s) = \mathcal{L}\{t^3 e^{-at}\} = \frac{-6}{(s+a)^4}$

$$F(\omega) = F(s) \Big|_{s=j\omega} + F(s) \Big|_{s=-j\omega}$$

$$F(\omega) = \frac{-6}{(a+j\omega)^4} + \frac{-6}{(a-j\omega)^4} = -j48a\omega \frac{a^2 - \omega^2}{(a^2 + \omega^2)^4}$$

[c]  $F(s) = \mathcal{L}\{e^{-at} \cos \omega_0 t\} = \frac{s+a}{(s+a)^2 + \omega_0^2} = \frac{0.5}{(s+a) - j\omega_0} + \frac{0.5}{(s+a) + j\omega_0}$

$$F(\omega) = F(s) \Big|_{s=j\omega} + F(s) \Big|_{s=-j\omega}$$

$$\begin{aligned} F(\omega) &= \frac{0.5}{(a+j\omega) - j\omega_0} + \frac{0.5}{(a+j\omega) + j\omega_0} \\ &\quad + \frac{0.5}{(a-j\omega) - j\omega_0} + \frac{0.5}{(a-j\omega) + j\omega_0} \\ &= \frac{a}{a^2 + (\omega - \omega_0)^2} + \frac{a}{a^2 + (\omega + \omega_0)^2} \end{aligned}$$



$$[d] \quad F(s) = \mathcal{L}\{e^{-at} \sin \omega_0 t\} = \frac{\omega_0}{(s+a)^2 + \omega_0^2} = \frac{-j0.5}{(s+a) - j\omega_0} + \frac{j0.5}{(s+a) + j\omega_0}$$

$$F(\omega) = F(s) \Big|_{s=j\omega} + F(s) \Big|_{s=-j\omega}$$

$$F(\omega) = \frac{-(\omega - \omega_0)}{a^2 + (\omega - \omega_0)^2} + \frac{(\omega + \omega_0)}{a^2 + (\omega + \omega_0)^2}$$

$$[e] \quad F(\omega) = \int_{-\infty}^{\infty} \delta(t - t_0) e^{-j\omega t} dt = e^{-j\omega t_0}$$

(Use the sifting property of the Dirac delta function.)

$$\begin{aligned} \text{P 17.5} \quad \mathcal{F}\{\sin \omega_0 t\} &= \mathcal{F}\left\{\frac{e^{j\omega_0 t}}{2j}\right\} - \mathcal{F}\left\{\frac{e^{-j\omega_0 t}}{2j}\right\} \\ &= \frac{1}{2j} [2\pi\delta(\omega - \omega_0) - 2\pi\delta(\omega + \omega_0)] \\ &= j\pi [\delta(\omega + \omega_0) - \delta(\omega - \omega_0)] \end{aligned}$$

$$\begin{aligned} \text{P 17.6} \quad f(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} [A(\omega) + jB(\omega)] [\cos t\omega + j \sin t\omega] d\omega \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} [A(\omega) \cos t\omega - B(\omega) \sin t\omega] d\omega \\ &\quad + \frac{j}{2\pi} \int_{-\infty}^{\infty} [A(\omega) \sin t\omega + B(\omega) \cos t\omega] d\omega \end{aligned}$$

But  $f(t)$  is real, therefore the second integral in the sum is zero.

P 17.7 By hypothesis,  $f(t) = -f(-t)$ . From Problem 17.6, we have

$$f(-t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} [A(\omega) \cos t\omega + B(\omega) \sin t\omega] d\omega$$

For  $f(t) = -f(-t)$ , the integral  $\int_{-\infty}^{\infty} A(\omega) \cos t\omega d\omega$  must be zero. Therefore, if  $f(t)$  is real and odd, we have

$$f(t) = \frac{-1}{2\pi} \int_{-\infty}^{\infty} B(\omega) \sin t\omega d\omega$$

$$\text{P 17.8} \quad F(\omega) = \frac{-j2}{\omega}; \quad \text{therefore} \quad B(\omega) = \frac{-2}{\omega}; \quad \text{thus we have}$$

$$f(t) = -\frac{1}{2\pi} \int_{-\infty}^{\infty} \left(\frac{-2}{\omega}\right) \sin t\omega d\omega = \frac{1}{\pi} \int_{-\infty}^{\infty} \frac{\sin t\omega}{\omega} d\omega$$

$$\text{But} \quad \frac{\sin t\omega}{\omega} \quad \text{is even;} \quad \text{therefore} \quad f(t) = \frac{2}{\pi} \int_0^{\infty} \frac{\sin t\omega}{\omega} d\omega$$

Therefore,

$$\left. \begin{aligned} f(t) &= \frac{2}{\pi} \cdot \frac{\pi}{2} = 1 & t > 0 \\ f(t) &= \frac{2}{\pi} \cdot \left(\frac{-\pi}{2}\right) = -1 & t < 0 \end{aligned} \right\} \text{from a table of definite integrals}$$

Therefore  $f(t) = \operatorname{sgn} t$

P 17.9 From Problem 17.4[c] we have

$$F(\omega) = \frac{\epsilon}{\epsilon^2 + (\omega - \omega_0)^2} + \frac{\epsilon}{\epsilon^2 + (\omega + \omega_0)^2}$$

Note that as  $\epsilon \rightarrow 0$ ,  $F(\omega) \rightarrow 0$  everywhere except at  $\omega = \pm\omega_0$ . At  $\omega = \pm\omega_0$ ,  $F(\omega) = 1/\epsilon$ , therefore  $F(\omega) \rightarrow \infty$  at  $\omega = \pm\omega_0$  as  $\epsilon \rightarrow 0$ . The area under each bell-shaped curve is independent of  $\epsilon$ , that is

$$\int_{-\infty}^{\infty} \frac{\epsilon d\omega}{\epsilon^2 + (\omega - \omega_0)^2} = \int_{-\infty}^{\infty} \frac{\epsilon d\omega}{\epsilon^2 + (\omega + \omega_0)^2} = \pi$$

Therefore as  $\epsilon \rightarrow 0$ ,  $F(\omega) \rightarrow \pi\delta(\omega - \omega_0) + \pi\delta(\omega + \omega_0)$

P 17.10  $A(\omega) = \int_{-\infty}^{\infty} f(t) \cos \omega t dt$

$$\begin{aligned} &= \int_{-\infty}^0 f(t) \cos \omega t dt + \int_0^{\infty} f(t) \cos \omega t dt \\ &= 2 \int_0^{\infty} f(t) \cos \omega t dt, \quad \text{since } f(t) \cos \omega t \text{ is also even.} \end{aligned}$$

$B(\omega) = 0$ , since  $f(t) \sin \omega t$  is an odd function and

$$\int_{-\infty}^0 f(t) \sin \omega t dt = - \int_0^{\infty} f(t) \sin \omega t dt$$

P 17.11  $A(\omega) = \int_{-\infty}^0 f(t) \cos \omega t dt + \int_0^{\infty} f(t) \cos \omega t dt = 0$

since  $f(t) \cos \omega t$  is an odd function.

$$B(\omega) = -2 \int_0^{\infty} f(t) \sin \omega t dt, \quad \text{since } f(t) \sin \omega t \text{ is an even function.}$$

P 17.12 [a]  $\mathcal{F} \left\{ \frac{df(t)}{dt} \right\} = \int_{-\infty}^{\infty} \frac{df(t)}{dt} e^{-j\omega t} dt$

Let  $u = e^{-j\omega t}$ , then  $du = -j\omega e^{-j\omega t} dt$ ; let  $dv = [df(t)/dt] dt$ , then  $v = f(t)$ .

$$\begin{aligned}\text{Therefore } \mathcal{F}\left\{\frac{df(t)}{dt}\right\} &= f(t)e^{-j\omega t} \Big|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} f(t)[-j\omega e^{-j\omega t} dt] \\ &= 0 + j\omega F(\omega)\end{aligned}$$

[b] Fourier transform of  $f(t)$  exists, i.e.,  $f(\infty) = f(-\infty) = 0$ .

[c] To find  $\mathcal{F}\left\{\frac{d^2 f(t)}{dt^2}\right\}$ , let  $g(t) = \frac{df(t)}{dt}$

$$\text{Then } \mathcal{F}\left\{\frac{d^2 f(t)}{dt^2}\right\} = \mathcal{F}\left\{\frac{dg(t)}{dt}\right\} = j\omega G(\omega)$$

$$\text{But } G(\omega) = \mathcal{F}\left\{\frac{df(t)}{dt}\right\} = j\omega F(\omega)$$

$$\text{Therefore we have } \mathcal{F}\left\{\frac{d^2 f(t)}{dt^2}\right\} = (j\omega)^2 F(\omega)$$

Repeated application of this thought process gives

$$\mathcal{F}\left\{\frac{d^n f(t)}{dt^n}\right\} = (j\omega)^n F(\omega)$$

$$\text{P 17.13 [a] } \mathcal{F}\left\{\int_{-\infty}^t f(x) dx\right\} = \int_{-\infty}^{\infty} \left[\int_{-\infty}^t f(x) dx\right] e^{-j\omega t} dt$$

$$\text{Now let } u = \int_{-\infty}^t f(x) dx, \quad \text{then } du = f(t) dt$$

$$\text{Let } dv = e^{-j\omega t} dt, \quad \text{then } v = \frac{e^{-j\omega t}}{-j\omega}$$

Therefore,

$$\begin{aligned}\mathcal{F}\left\{\int_{-\infty}^t f(x) dx\right\} &= \frac{e^{-j\omega t}}{-j\omega} \int_{-\infty}^t f(x) dx \Big|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} \left[\frac{e^{-j\omega t}}{-j\omega}\right] f(t) dt \\ &= 0 + \frac{F(\omega)}{j\omega}\end{aligned}$$

$$\text{[b] We require } \int_{-\infty}^{\infty} f(x) dx = 0$$

$$\text{[c] No, because } \int_{-\infty}^{\infty} e^{-ax} u(x) dx = \frac{1}{a} \neq 0$$

$$\text{P 17.14 [a]} \quad \mathcal{F}\{f(at)\} = \int_{-\infty}^{\infty} f(at)e^{-j\omega t} dt$$

$$\text{Let } u = at, \quad du = a dt, \quad u = \pm\infty \quad \text{when } t = \pm\infty$$

Therefore,



$$\mathcal{F}\{f(at)\} = \int_{-\infty}^{\infty} f(u)e^{-j\omega u/a} \left(\frac{du}{a}\right) = \frac{1}{a} F\left(\frac{\omega}{a}\right), \quad a > 0$$

$$\text{[b]} \quad \mathcal{F}\{e^{-|t|}\} = \frac{1}{1+j\omega} + \frac{1}{1-j\omega} = \frac{2}{1+\omega^2}$$

$$\text{Therefore } \mathcal{F}\{e^{-a|t|}\} = \frac{(1/a)2}{(\omega/a)^2 + 1}$$

$$\text{Therefore } \mathcal{F}\{e^{-0.5|t|}\} = \frac{4}{4\omega^2 + 1}, \quad \mathcal{F}\{e^{-|t|}\} = \frac{2}{\omega^2 + 1}$$

$\mathcal{F}\{e^{-2|t|}\} = 1/[0.25\omega^2 + 1]$ , yes as “ $a$ ” increases, the sketches show that  $f(t)$  approaches zero faster and  $F(\omega)$  flattens out over the frequency spectrum.

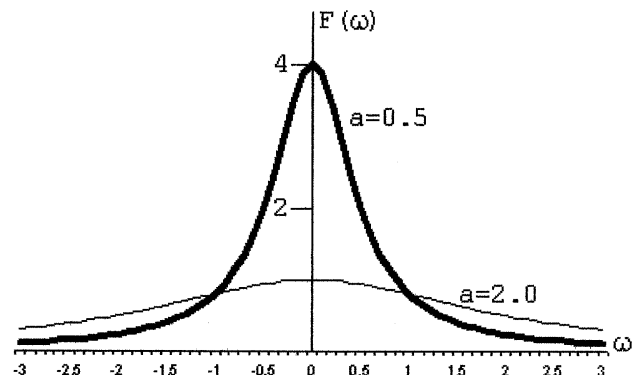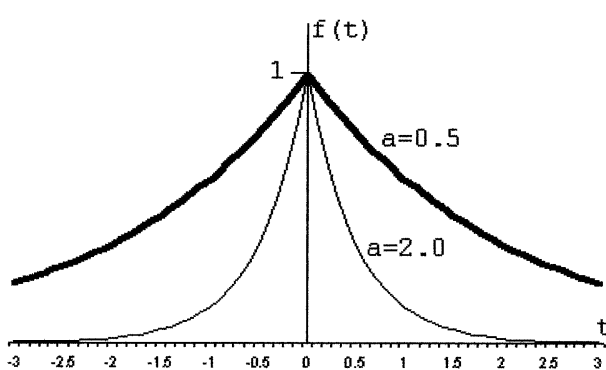

$$\text{P 17.15 [a]} \quad \mathcal{F}\{f(t-a)\} = \int_{-\infty}^{\infty} f(t-a)e^{-j\omega t} dt$$

$$\text{Let } u = t - a, \text{ then } du = dt, \quad t = u + a, \text{ and } u = \pm\infty \text{ when } t = \pm\infty.$$

Therefore,

$$\begin{aligned} \mathcal{F}\{f(t-a)\} &= \int_{-\infty}^{\infty} f(u)e^{-j\omega(u+a)} du \\ &= e^{-j\omega a} \int_{-\infty}^{\infty} f(u)e^{-j\omega u} du = e^{-j\omega a} F(\omega) \end{aligned}$$

$$\text{[b]} \quad \mathcal{F}\{e^{j\omega_0 t} f(t)\} = \int_{-\infty}^{\infty} f(t)e^{-j(\omega-\omega_0)t} dt = F(\omega - \omega_0)$$

$$\begin{aligned} \text{[c]} \quad \mathcal{F}\{f(t) \cos \omega_0 t\} &= \mathcal{F}\left\{f(t) \left[\frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2}\right]\right\} \\ &= \frac{1}{2} F(\omega - \omega_0) + \frac{1}{2} F(\omega + \omega_0) \end{aligned}$$

$$\text{P 17.16 } Y(\omega) = \int_{-\infty}^{\infty} \left[ \int_{-\infty}^{\infty} x(\lambda) h(t - \lambda) d\lambda \right] e^{-j\omega t} dt$$

$$= \int_{-\infty}^{\infty} x(\lambda) \left[ \int_{-\infty}^{\infty} h(t - \lambda) e^{-j\omega t} dt \right] d\lambda$$

Let  $u = t - \lambda$ ,  $du = dt$ , and  $u = \pm\infty$ , when  $t = \pm\infty$ .

$$\begin{aligned} \text{Therefore } Y(\omega) &= \int_{-\infty}^{\infty} x(\lambda) \left[ \int_{-\infty}^{\infty} h(u) e^{-j\omega(u+\lambda)} du \right] d\lambda \\ &= \int_{-\infty}^{\infty} x(\lambda) \left[ e^{-j\omega\lambda} \int_{-\infty}^{\infty} h(u) e^{-j\omega u} du \right] d\lambda \\ &= \int_{-\infty}^{\infty} x(\lambda) e^{-j\omega\lambda} H(\omega) d\lambda = H(\omega) X(\omega) \end{aligned}$$

$$\text{P 17.17 } \mathcal{F}\{f_1(t)f_2(t)\} = \int_{-\infty}^{\infty} \left[ \frac{1}{2\pi} \int_{-\infty}^{\infty} F_1(u) e^{jtu} du \right] f_2(t) e^{-j\omega t} dt$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \left[ \int_{-\infty}^{\infty} F_1(u) f_2(t) e^{-j\omega t} e^{jtu} du \right] dt$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \left[ F_1(u) \int_{-\infty}^{\infty} f_2(t) e^{-j(\omega-u)t} dt \right] du$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} F_1(u) F_2(\omega - u) du$$

$$\text{P 17.18 [a] } F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$\frac{dF}{d\omega} = \int_{-\infty}^{\infty} \frac{d}{d\omega} [f(t) e^{-j\omega t}] dt = -j \int_{-\infty}^{\infty} t f(t) e^{-j\omega t} dt = -j \mathcal{F}\{t f(t)\}$$

$$\text{Therefore } j \frac{dF(\omega)}{d\omega} = \mathcal{F}\{t f(t)\}$$

$$\frac{d^2 F(\omega)}{d\omega^2} = \int_{-\infty}^{\infty} (-jt)(-jt) f(t) e^{-j\omega t} dt = (-j)^2 \mathcal{F}\{t^2 f(t)\}$$

$$\text{Note that } (-j)^n = \frac{1}{j^n}$$

$$\text{Thus we have } j^n \left[ \frac{d^n F(\omega)}{d\omega^n} \right] = \mathcal{F}\{t^n f(t)\}$$

$$\text{[b] (i) } \mathcal{F}\{e^{-at} u(t)\} = \frac{1}{a + j\omega} = F(\omega); \quad \frac{dF(\omega)}{d\omega} = \frac{-j}{(a + j\omega)^2}$$

$$\text{Therefore } j \left[ \frac{dF(\omega)}{d\omega} \right] = \frac{1}{(a + j\omega)^2}$$

Therefore  $\mathcal{F}\{te^{-at}u(t)\} = \frac{1}{(a + j\omega)^2}$

(ii)  $\mathcal{F}\{|t|e^{-a|t|}\} = \mathcal{F}\{te^{-at}u(t)\} - \mathcal{F}\{te^{at}u(-t)\}$

$$\begin{aligned} &= \frac{1}{(a + j\omega)^2} - j \frac{d}{d\omega} \left( \frac{1}{a - j\omega} \right) \\ &= \frac{1}{(a + j\omega)^2} + \frac{1}{(a - j\omega)^2} \end{aligned}$$

(iii)  $\mathcal{F}\{te^{-a|t|}\} = \mathcal{F}\{te^{-at}u(t)\} + \mathcal{F}\{te^{at}u(-t)\}$

$$\begin{aligned} &= \frac{1}{(a + j\omega)^2} + j \frac{d}{d\omega} \left( \frac{1}{a - j\omega} \right) \\ &= \frac{1}{(a + j\omega)^2} - \frac{1}{(a - j\omega)^2} \end{aligned}$$

P 17.19 [a]  $f_1(t) = \cos \omega_0 t$ ,  $F_1(u) = \pi[\delta(u + \omega_0) + \delta(u - \omega_0)]$

$f_2(t) = 1$ ,  $-\tau/2 < t < \tau/2$ , and  $f_2(t) = 0$  elsewhere

Thus  $F_2(u) = \frac{\tau \sin(u\tau/2)}{u\tau/2}$

Using convolution,

$$\begin{aligned} F(\omega) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} F_1(u) F_2(\omega - u) du \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} \pi[\delta(u + \omega_0) + \delta(u - \omega_0)] \tau \frac{\sin[(\omega - u)\tau/2]}{(\omega - u)(\tau/2)} du \\ &= \frac{\tau}{2} \int_{-\infty}^{\infty} \delta(u + \omega_0) \frac{\sin[(\omega - u)\tau/2]}{(\omega - u)(\tau/2)} du \\ &\quad + \frac{\tau}{2} \int_{-\infty}^{\infty} \delta(u - \omega_0) \frac{\sin[(\omega - u)\tau/2]}{(\omega - u)(\tau/2)} du \\ &= \frac{\tau}{2} \cdot \frac{\sin[(\omega + \omega_0)\tau/2]}{(\omega + \omega_0)(\tau/2)} + \frac{\tau}{2} \cdot \frac{\sin[(\omega - \omega_0)\tau/2]}{(\omega - \omega_0)\tau/2} \end{aligned}$$

[b] As  $\tau$  increases, the amplitude of  $F(\omega)$  increases at  $\omega = \pm\omega_0$  and at the same time the duration of  $F(\omega)$  approaches zero as  $\omega$  deviates from  $\pm\omega_0$ . The area under the  $[\sin x]/x$  function is independent of  $\tau$ , that is


$$\frac{\tau}{2} \int_{-\infty}^{\infty} \frac{\sin[(\omega - \omega_0)(\tau/2)]}{(\omega - \omega_0)(\tau/2)} d\omega = \int_{-\infty}^{\infty} \frac{\sin[(\omega - \omega_0)(\tau/2)]}{(\omega - \omega_0)(\tau/2)} [(\tau/2) d\omega] = \pi$$

Therefore as  $t \rightarrow \infty$ ,

$$f_1(t)f_2(t) \rightarrow \cos \omega_0 t \quad \text{and} \quad F(\omega) \rightarrow \pi[\delta(\omega - \omega_0) + \delta(\omega + \omega_0)]$$

P 17.20 [a] Find the Thévenin equivalent with respect to the terminals of the inductor. Thus,
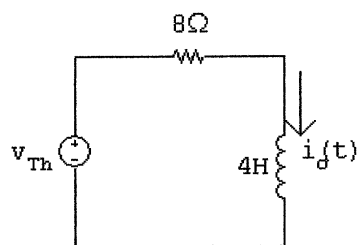
$$v_{\text{Th}} = \frac{40}{50}v_g = 0.8v_g; \quad R_{\text{Th}} = 10 \parallel 40 = 8 \Omega$$



$$I_o = \frac{0.8V_g}{8 + 4s} = \frac{0.2V_g}{s + 2}$$

$$H(s) = \frac{I_o}{V_g} = \frac{0.2}{s + 2}$$

$$H(j\omega) = \frac{0.2}{j\omega + 2}$$

$$V_g(\omega) = 125 \left( \pi\delta(\omega) + \frac{1}{j\omega} \right)$$

$$\begin{aligned} I_o(\omega) &= V_g(\omega)H(j\omega) \\ &= \frac{25}{j\omega + 2} \left( \pi\delta(\omega) + \frac{1}{j\omega} \right) \\ &= \frac{25\pi\delta(\omega)}{j\omega + 2} + \frac{25}{j\omega(2 + j\omega)} \\ &= I_1(\omega) + I_2(\omega) \end{aligned}$$

$$i_1(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \frac{25\pi\delta(\omega)e^{j\omega t}}{2 + j\omega} dt = 6.25 \text{ A}$$


$$I_2(\omega) = \frac{12.5}{j\omega} - \frac{12.5}{j\omega + 2}$$

$$i_2(t) = 6.25\text{sgn}(t) - 12.5e^{-2t}u(t) \text{ A}$$

$$i_o = i_1 + i_2 = 6.25 + 6.25\text{sgn}(t) - 12.5e^{-2t}u(t) \text{ A}$$

$$i_o(t) = 12.5u(t) - 12.5e^{-2t}u(t) \text{ A}$$

[b]

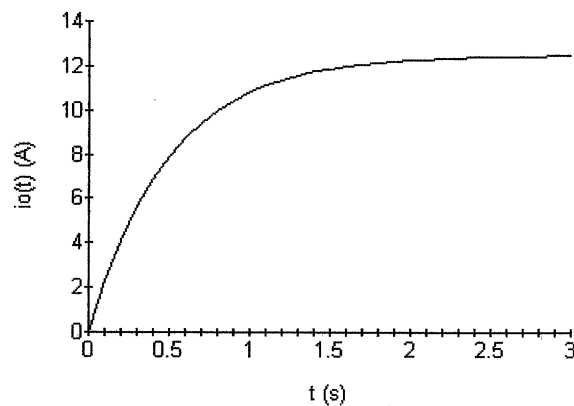

P 17.21 [a] From the solution to Problem 17.20 we have

$$H(s) = \frac{I_o}{V_g} = \frac{0.2}{s+2}$$


$$H(j\omega) = \frac{0.2}{j\omega + 2}$$

$$v_g = 125\text{sgn}(t) \text{ V}; \quad V_g(\omega) = \frac{250}{j\omega}$$

$$I_o = V_g H(j\omega) = \frac{50}{j\omega(j\omega + 2)} = \frac{25}{j\omega} - \frac{25}{j\omega + 2}$$

$$\therefore i_o(t) = 12.5\text{sgn}(t) - 25e^{-2t}u(t) \text{ A}$$

[b]

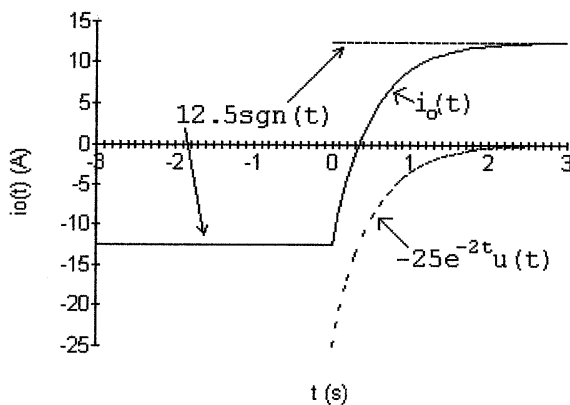

P 17.22 [a]  $H(s) = \frac{1/sC}{R + 1/sC} = \frac{1/RC}{s + 1/RC} = \frac{50}{s + 50}$

$$H(\omega) = \frac{50}{j\omega + 50}$$

$$V_g(\omega) = \frac{40}{j\omega}$$



$$V_o(\omega) = \left(\frac{40}{j\omega}\right) \left(\frac{50}{j\omega + 50}\right) = \frac{2000}{j\omega(j\omega + 50)}$$

$$= \frac{40}{j\omega} - \frac{40}{j\omega + 50}$$

$$v_o(t) = 20\text{sgn}(t) - 40e^{-50t}u(t) \text{ V}$$

- [b]  $v_o(0^-) = -20 \text{ V}$ . This makes sense because the capacitor will be charged to  $-20 \text{ V}$  when  $t < 0$ .  
 $v_o(0^+) = 20 - 40 = -20 \text{ V}$ . This makes sense because there cannot be an instantaneous change in the voltage drop across the capacitor.  
 $v(\infty) = 20 \text{ V}$ . This makes sense because the capacitor will charge to  $20 \text{ V}$  after the signal voltage reverses polarity.  
The circuit is a first-order circuit with a time constant of  $RC$  or  $0.02 \text{ s}$ .  
Therefore,  $1/\tau = 50$ . We would expect the transition from  $-20 \text{ V}$  to  $+20 \text{ V}$  to be exponential with a time constant of  $0.02 \text{ s}$ .

P 17.23 [a]  $H(s) = \frac{I_o}{V_g} = \frac{1}{R + 1/sC} = \frac{(1/R)s}{s + 1/RC}$

$$H(s) = \frac{25 \times 10^{-6}s}{s + 50}; \quad H(\omega) = \frac{25 \times 10^{-6}j\omega}{j\omega + 50}$$

$$\therefore I_o(\omega) = \frac{25 \times 10^{-6}j\omega}{j\omega + 50} \frac{40}{j\omega} = \frac{10^{-3}}{j\omega + 50}$$

$$i_o(t) = 10^{-3}e^{-50t}u(t) = e^{-50t}u(t) \text{ mA}$$

[b]  $i_o(0^-) = 0$

This makes sense because  $v_g$  and  $v_o$  equal;  $-20 \text{ V}$  at  $t = 0$ .

$$i_o(0^+) = 1 \text{ mA}$$

This makes sense because  $v_o = -20 \text{ V}$  and  $v_g = +20 \text{ V}$  at  $t = 0^+$ . Thus,

$$i_o(0^+) = [20 - (-20)]/(40 \times 10^3) = 1 \text{ mA}$$

$$i_o(\infty) = 0$$

This makes sense because at  $t = \infty$ ,  $v_g = v_o = 20 \text{ V}$ .

We have a first-order circuit with a time constant of  $0.02 \text{ s}$  and therefore we expect  $i_o(t)$  to decay exponentially with an exponent of  $-t/\tau$  or  $-50t$ .

P 17.24 [a]  $H(s) = \frac{1/RC}{s + 1/RC} = \frac{100}{s + 100}$

$$H(\omega) = \frac{100}{j\omega + 100}; \quad V_g(\omega) = \frac{30}{j\omega}$$

$$V_o(\omega) = \left(\frac{30}{j\omega}\right) \left(\frac{100}{j\omega + 100}\right) = \frac{3000}{j\omega(j\omega + 100)}$$


$$= \frac{30}{j\omega} - \frac{30}{j\omega + 100}$$

$$\therefore v_o(t) = 15\text{sgn}(t) - 30e^{-100t}u(t) \text{ V}$$

[b]  $v_o(0^-) = -15 \text{ V}$

[c]  $v_o(0^+) = 15 - 30 = -15 \text{ V}$

[d]

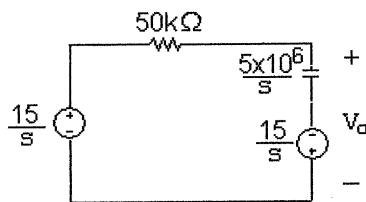

$$\frac{V_o - 15/s}{50,000} + \frac{(V_o + 15/s)s}{5 \times 10^6} = 0$$

$$100V_o - \frac{1500}{s} + V_oss + 15 = 0$$

$$\therefore V_o = \frac{15(100 - s)}{s(s + 100)} = \frac{K_1}{s} + \frac{K_2}{s + 100}$$

$$K_1 = \frac{15(100)}{100} = 15; \quad K_2 = \frac{15(200)}{-100} = -30$$

$$v_o(t) = (15 - 30e^{-100t})u(t) \text{ V}$$

[e] Yes, they agree. The solution from part (a) for  $t > 0$  is

$$v_o(t) = (15 - 30e^{-100t})u(t) \text{ V}$$

P 17.25 [a]  $H(s) = \frac{I_o}{V_g} = \frac{(1/R)s}{s + 1/RC}$

$$H(s) = \frac{20 \times 10^{-6}s}{s + 100}; \quad H(\omega) = \frac{20 \times 10^{-6}(j\omega)}{j\omega + 100}$$


$$I_o(\omega) = \frac{20 \times 10^{-6}(j\omega)}{j\omega + 100} \cdot \frac{30}{j\omega} = \frac{600 \times 10^{-6}}{j\omega + 100}$$

$$i_o(t) = 600e^{-100t}u(t) \mu\text{A}$$

[b]  $i_o(0^-) = 0$

[c]  $i_o(0^+) = 600 \mu\text{A}$

[d]

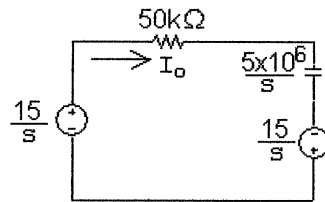


$$I_o = \frac{30/s}{50,000 + (5 \times 10^6/s)} = \frac{30}{50,000s + 5 \times 10^6}$$

$$= \frac{600 \times 10^{-6}}{s + 100}$$

$$i_o(t) = 600e^{-100t}u(t) \mu\text{A}$$

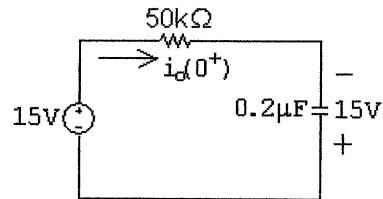
[e] Yes they agree. Also note that at  $t = 0^+$  the circuit is



$$i_o(0^+) = \frac{30}{50,000} = 600 \mu\text{A}$$

which agrees with our solution.

P 17.26 [a]

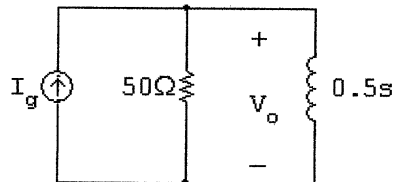

$$\frac{V_o}{50} + \frac{2V_o}{s} = I_g$$

$$V_o \left[ \frac{1}{50} + \frac{2}{s} \right] = I_g$$

$$\frac{V_o}{I_g} = H(s) = \frac{50s}{s + 100}$$


$$H(j\omega) = \frac{j\omega 50}{j\omega + 100}$$

$$I_g(\omega) = \frac{4}{j\omega}$$


$$V_o(\omega) = \frac{4}{j\omega} \cdot \frac{50(j\omega)}{j + 100} = \frac{200}{j\omega + 100}$$

$$\therefore v_o(t) = 200e^{-100t}u(t) \text{ V}$$

[b] At  $t = 0^-$  the circuit is

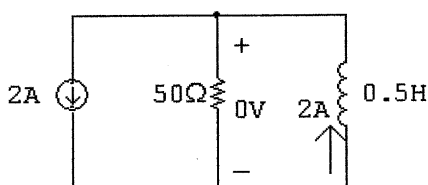

At  $t = 0^+$  the circuit is

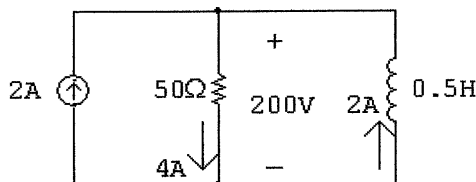

From the circuit

$$v_o(0^+) = (4)(50) = 200 \text{ V}$$

which agrees with our solution.

At  $t = \infty$

$$v_o(\infty) = 0$$

since the inductor short-circuits the dc current source. This is also in agreement with our solution.

$$\tau = L/R = 0.5/50 = 1/100; \quad \therefore 1/\tau = 100$$

which agrees with our solution.

P 17.27 [a] 
$$I_o = \frac{V_o}{0.5s} = \frac{2}{s} \left( \frac{50sI_g}{s + 100} \right)$$

$$\frac{I_o}{I_g} = H(s) = \frac{100}{s + 100}$$

$$H(j\omega) = \frac{100}{j\omega + 100}$$

$$I_g(\omega) = \frac{4}{j\omega}$$

$$I_o(\omega) = \frac{400}{j\omega(j\omega + 100)} = \frac{4}{j\omega} - \frac{4}{j\omega + 100}$$

$$\therefore i_o(t) = 2\text{sgn}(t) - 4e^{-100t}u(t) \text{ A}$$

- [b] • From the solution to Problem 17.21(b) we note  $i_o(0^-) = -2 \text{ A}$  and  $i_o(0^+) = -2 \text{ A}$ . Our solution agrees with these results.
- From the circuit,  $i_o(\infty) = 2 \text{ A}$ . Our solution agrees with this value.
- From the circuit,  $\tau = 0.01 \text{ s}$  which agrees with our solution.

P 17.28 [a]  $V_o = \frac{V_g(1/sC)}{R + (1/sC)} = \frac{V_g}{RCs + 1}$

$$\frac{V_o}{V_g} = H(s) = \frac{1/RC}{s + (1/RC)} = \frac{1}{s + 1}$$

$$H(j\omega) = \frac{1}{j\omega + 1}$$

$$V_g(\omega) = \frac{30}{-j\omega + 5} + \frac{30}{j\omega + 5}$$

$$\begin{aligned} V_o(\omega) &= \frac{30}{(-j\omega + 5)(j\omega + 1)} + \frac{30}{(j\omega + 5)(j\omega + 1)} \\ &= \frac{K_1}{-j\omega + 5} + \frac{K_2}{j\omega + 1} + \frac{K_3}{j\omega + 5} + \frac{K_4}{j\omega + 1} \end{aligned}$$

$$K_1 = \frac{30}{6} = 5; \quad K_2 = \frac{30}{6} = 5; \quad K_3 = \frac{30}{-4} = -7.5; \quad K_4 = \frac{30}{4} = 7.5$$


$$V_o(\omega) = \frac{5}{-j\omega + 5} + \frac{12.5}{j\omega + 1} - \frac{7.5}{j\omega + 5}$$

$$v_o(t) = 5e^{5t}u(-t) + (12.5e^{-t} - 7.5e^{-5t})u(t) \text{ V}$$

[b]  $v_o(0^-) = 5 \text{ V}$

[c]  $v_o(0^+) = 12.5 - 7.5 = 5 \text{ V}$

[d]

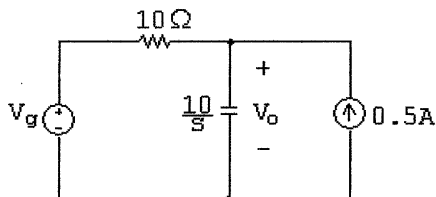

$$\frac{V_o - V_g}{10} + \frac{V_o s}{10} - 0.5 = 0$$

$$V_o - V_g + V_o s - 5 = 0$$

$$V_o(s + 1) = 5 + V_g$$

$$V_g = \frac{30}{s + 5}$$

$$\therefore V_o = \frac{5}{s + 1} + \frac{30}{(s + 1)(s + 5)} = \frac{5}{s + 1} + \frac{7.5}{s + 1} - \frac{7.5}{s + 5} = \frac{12.5}{s + 1} - \frac{7.5}{s + 5}$$

$$v_o(t) = (12.5e^{-t} - 7.5e^{-5t})u(t) \text{ V}$$

[e] Yes, for  $t \geq 0^+$  the solution in part (a) is also

$$v_o(t) = (12.5e^{-t} - 7.5e^{-5t})u(t) \text{ V}$$

P 17.29 [a]  $I_o = \frac{V_g}{10 + 10/s} = \frac{V_g s}{10s + 10}$

$$H(s) = \frac{I_o}{V_g} = \frac{0.1}{s + 1}$$

$$H(j\omega) = \frac{0.1}{j\omega + 1}$$

$$V_g(\omega) = \frac{30}{-j\omega + 5} + \frac{30}{j\omega + 5}$$

$$I_o(\omega) = H(j\omega)V_g(j\omega) = \frac{0.1j\omega}{j\omega + 1} \left[ \frac{30}{-j\omega + 5} + \frac{30}{j\omega + 5} \right]$$

$$= \frac{3j\omega}{(j\omega + 1)(-j\omega + 5)} + \frac{3j\omega}{(j\omega + 1)(j\omega + 5)}$$

$$= \frac{K_1}{j\omega + 1} + \frac{K_2}{-j\omega + 5} + \frac{K_3}{j\omega + 1} + \frac{K_4}{j\omega + 5}$$

$$K_1 = \frac{3(-1)}{6} = -0.5; \quad K_2 = \frac{3(5)}{6} = 2.5$$

$$K_3 = \frac{3(-1)}{4} = -0.75; \quad K_4 = \frac{3(-5)}{-4} = 3.75$$


$$\therefore I_o(\omega) = \frac{-1.25}{j\omega + 1} + \frac{2.5}{-j\omega + 5} + \frac{3.75}{j\omega + 5}$$

$$i_o(t) = 2.5e^{5t}u(-t) + [-1.25e^{-t} + 3.75e^{-5t}]u(t) \text{ A}$$

[b]  $i_o(0^-) = 2.5 \text{ V}$

[c]  $i_o(0^+) = 2.5 \text{ V}$

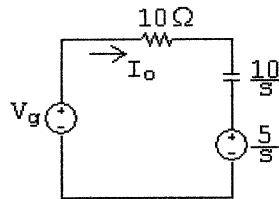[d] Note – since  $i_o(0^+) = 2.5 \text{ A}$ ,  $v_o(0^+) = 30 - 25 = 5 \text{ V}$ .



$$I_o = \frac{V_g - (5/s)}{10 + (10/s)} = \frac{sV_g - 5}{10s + 10}; \quad V_g = \frac{30}{s + 5}$$

$$\therefore I_o = \frac{25s - 25}{10(s + 1)(s + 5)} = \frac{2.5(s - 1)}{(s + 1)(s + 5)} = \frac{-1.25}{s + 1} + \frac{3.75}{s + 5}$$


$$i_o(t) = (-1.25e^{-t} + 3.75e^{-5t})u(t) \text{ A}$$

[e] Yes, for  $t \geq 0^+$  the solution in part (a) is also

$$i_o(t) = (-1.25e^{-t} + 3.75e^{-5t})u(t) \text{ A}$$

P 17.30 [a]  $v_g = 125 \cos 75t$
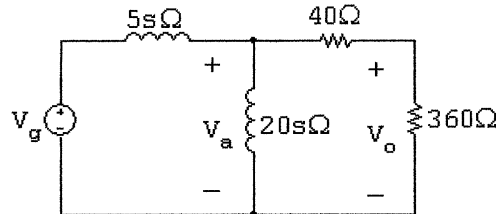
$$V_g(\omega) = 125\pi[\delta(\omega + 75) + \delta(\omega - 75)]$$



$$\frac{V_a}{20s} + \frac{V_a - V_g}{5s} + \frac{V_a}{400} = 0$$

$$V_a \left[ \frac{1}{20s} + \frac{1}{5s} + \frac{1}{400} \right] = \frac{V_g}{5s}$$

$$V_a[20 + 80 + s] = 80V_g$$

$$V_a = \frac{80V_g}{s+100}; \quad V_o = \frac{V_a}{400}(360) = 0.9V_a$$

$$H(s) = \frac{V_o}{V_g} = \frac{72}{s+100}$$


$$H(\omega) = \frac{72}{j\omega + 100}$$

$$V_o(\omega) = V_g(\omega)H(\omega) = \frac{9000\pi[\delta(\omega + 75) + \delta(\omega - 75)]}{j\omega + 100}$$

$$\begin{aligned} v_o(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} V_o(\omega) e^{j\omega t} d\omega \\ &= 4500 \left[ \frac{e^{j75t}}{100 + j75} + \frac{e^{-j75t}}{100 - j75} \right] \\ &= 180 \left[ \frac{e^{j75t}}{4 + j3} + \frac{e^{-j75t}}{4 - j3} \right] \\ &= 36[e^{j75t}e^{-j36.87^\circ} + e^{-j75t}e^{j36.87^\circ}] \\ &= 36[e^{j(75t-36.87^\circ)} + e^{-j(75t+36.87^\circ)}] \end{aligned}$$

$$v_o(t) = 72 \cos(75t - 36.87^\circ) \text{ V}$$

[b] In the phasor domain:

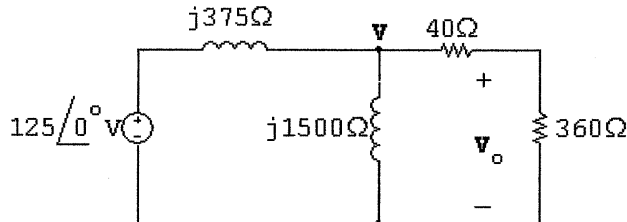

$$\frac{V - 125}{j375} + \frac{V}{j1500} + \frac{V}{400} = 0$$

$$V \left[ \frac{1}{j375} + \frac{1}{j1500} + \frac{1}{400} \right] = \frac{125}{j375}$$


$$V = \frac{(144 + j192)(125)}{j375} = 64 - j48 = 80 \angle -36.87^\circ \text{ V}$$

$$V_o = \frac{360}{400}(V) = 72 \angle -36.87^\circ \text{ V}$$

$$v_o(t) = 72 \cos(75t - 36.87^\circ) \text{ V}$$



P 17.31 [a]

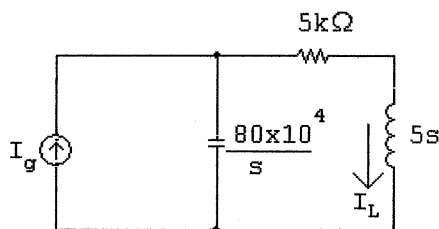

$$I_L = \frac{80 \times 10^4 / s}{5000 + 5s + 80 \times 10^4 / s} I_g = \frac{80 \times 10^4}{5s^2 + 5000s + 80 \times 10^4} I_g$$

$$\frac{I_L}{I_g} = H(s) = \frac{16 \times 10^4}{s^2 + 1000s + 16 \times 10^4} = \frac{16 \times 10^4}{(s + 200)(s + 800)}$$

$$H(j\omega) = \frac{16 \times 10^4}{(j\omega + 200)(j\omega + 800)}$$

$$I_g(\omega) = \frac{-45}{(-j\omega + 400)} + \frac{45}{(j\omega + 400)}$$

$$I_L(\omega) = \frac{-45(16 \times 10^4)}{(j\omega + 200)(j\omega + 800)(-j\omega + 400)} + \frac{45(16 \times 10^4)}{(j\omega + 200)(j\omega + 800)(j\omega + 400)}$$

$$= I_{L1} + I_{L2}$$

 $I_{L1}$ :

$$K_1 = \frac{-45(16 \times 10^4)}{(600)(600)} = -20$$

$$K_2 = \frac{-45(16 \times 10^4)}{(-600)(1200)} = 10$$

$$K_3 = \frac{-45(16 \times 10^4)}{(600)(1200)} = -10$$

$$I_{L1} = \frac{-20}{j\omega + 200} + \frac{10}{j\omega + 800} - \frac{10}{-j\omega + 400}$$

 $I_{L2}$ :

$$K_1 = \frac{45(16 \times 10^4)}{(200)(600)} = 60$$

$$K_2 = \frac{45(16 \times 10^4)}{(-600)(-400)} = 30$$

$$K_3 = \frac{45(16 \times 10^4)}{(-200)(400)} = -90$$

$$I_{L2} = \frac{60}{j\omega + 200} + \frac{30}{j\omega + 800} - \frac{90}{j\omega + 400}$$

$$\therefore I_L = \frac{40}{j\omega + 200} + \frac{40}{j\omega + 800} - \frac{10}{-j\omega + 400} - \frac{90}{j\omega + 400}$$

$$i_L(t) = (40e^{-200t} + 40e^{-800t} - 90e^{-400t})u(t) - 10e^{400t}u(-t) \text{ A}$$


[b]  $i_L(0^-) = -10e^{400(0^-)}u(0^-) = -10 \text{ A}$

[c]  $i_L(0^+) = (40e^{-200(0^+)} + 40e^{-800(0^+)} - 90e^{-400(0^+)}) = -10 \text{ A}$

[d] Yes, there cannot be an instantaneous change in the inductor current,

$$\therefore i_L(0^-) = i_L(0^+)$$

P 17.32

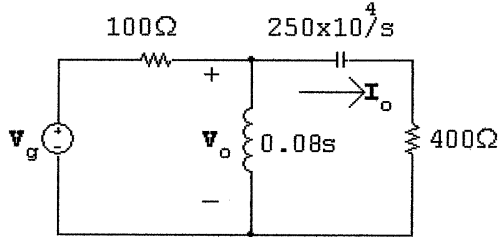

$$\frac{V_o - V_g}{100} + \frac{V_o}{0.08s} + \frac{V_o s}{400s + 250 \times 10^4} = 0$$

$$\therefore V_o = \frac{32s(s + 6250)V_g}{40(s^2 + 6000s + 625 \times 10^4)}$$

$$I_o = \frac{sV_o}{400(s + 6250)}$$

$$H(s) = \frac{I_o}{V_g} = \frac{2 \times 10^{-3}s^2}{s^2 + 6000s + 625 \times 10^4}$$

$$H(j\omega) = \frac{-2 \times 10^{-3}\omega^2}{(625 \times 10^4 - \omega^2) + j6000\omega}$$


$$V_g(\omega) = 200\pi[\delta(\omega + 2500) + \delta(\omega - 2500)]$$

$$I_o(\omega) = H(j\omega)V_g(\omega) = \frac{-0.4\pi\omega^2[\delta(\omega + 2500) + \delta(\omega - 2500)]}{(625 \times 10^4 - \omega^2) + j6000\omega}$$

$$\begin{aligned}
i_o(t) &= \frac{-0.4\pi}{2\pi} \int_{-\infty}^{\infty} \frac{\omega^2 [\delta(\omega + 2500) + \delta(\omega - 2500)]}{(625 \times 10^4 - \omega^2) + j6000\omega} e^{j\omega t} d\omega \\
&= -0.2 \left\{ \frac{625 \times 10^4 e^{-j2500t}}{-j(6000)(2500)} + \frac{625 \times 10^4 e^{j2500t}}{j(6000)(2500)} \right\} \\
&= \frac{1}{12} \left\{ \frac{e^{-j2500t}}{-j} + \frac{e^{j2500t}}{j} \right\} \\
&= 0.0833 [e^{-j(2500t+90^\circ)} + e^{j(2500t+90^\circ)}]
\end{aligned}$$

$$i_o(t) = 166.67 \cos(2500t + 90^\circ) \text{ mA}$$

P 17.33 [a]

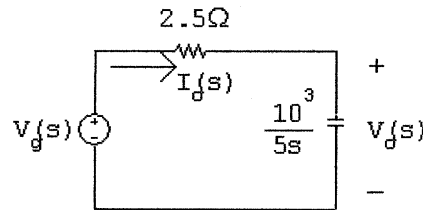

$$v_g(t) = 18e^{4t}u(-t) - 12u(t); \quad \therefore V_g(\omega) = \frac{18}{4 - j\omega} - 12\pi\delta(\omega) - \frac{12}{j\omega}$$

Using voltage division,

$$V_o(s) = \frac{(10^3/5s)}{(10^3/5s) + 2.5} V_g(s) = \frac{80}{s + 80} V_g$$

$$\therefore H(s) = \frac{V_o(s)}{V_g(s)} = \frac{80}{s + 80}$$

$$\therefore H(j\omega) = \frac{80}{j\omega + 80}$$

$$V_o(j\omega) = H(j\omega) \cdot V_g(\omega)$$

$$= \frac{(80)(18)}{(j\omega + 80)(4 - j\omega)} - \frac{(80)12\pi\delta(\omega)}{j\omega + 80} - \frac{(12)(80)}{j\omega(j\omega + 80)}$$

$$= \frac{(120/7)}{j\omega + 80} + \frac{(120/7)}{4 - j\omega} - \frac{960\pi\delta(\omega)}{j\omega + 80} - \frac{12}{j\omega} + \frac{12}{j\omega + 80}$$

$$v_o(t) = \frac{120}{7} e^{-80t} u(t) + \frac{120}{7} e^{4t} u(-t) - 6 - 6 \operatorname{sgn}(t) + 12e^{-80t} u(t) \text{ V}$$

$$\therefore v_o(0^-) = \frac{120}{7} - 6 + 6 = \frac{120}{7} \text{ V}; \quad v_o(0^+) = \frac{120}{7} - 6 - 6 + 12 = \frac{120}{7} \text{ V}$$

The voltages at  $0^-$  and  $0^+$  must be the same since the voltage cannot change instantaneously across a capacitor.

$$[b] \quad I_o(s) = \frac{V_g(s)}{(10^3/5s) + 2.5} = \frac{0.4s}{s + 80} V_g(s)$$

$$H(s) \frac{I_o(s)}{V_g(s)} = \frac{0.4s}{s + 80}; \quad \therefore H(j\omega) = \frac{0.4j\omega}{j\omega + 80}$$

$$I_o(j\omega) = H(j\omega) \cdot V_g(\omega)$$

$$= \frac{7.2j\omega}{(4 - j\omega)(j\omega + 80)} - \frac{4.8\pi\delta(\omega)j\omega}{j\omega + 80} - \frac{4.8j\omega}{j\omega(j\omega + 80)}$$

$$= \frac{(24/70)}{4 - j\omega} - \frac{(48/7)}{j\omega + 80} - \frac{4.8}{j\omega + 80}$$


$$= \frac{(24/70)}{4 - j\omega} - \frac{(816/70)}{j\omega + 80}$$

$$i_o(t) = \frac{24}{70}e^{4t}u(-t) - \frac{816}{70}e^{-80t}u(t) \text{ A}$$

$$\therefore i_o(0^-) = 24/70 \text{ A}; \quad i_o(0^+) = -816/70 \text{ A}$$

$$[c] \quad v_o(t) = \frac{120}{7}e^{-80t}u(t) + \frac{120}{7}e^{4t}u(-t) - 6 - 6\text{sgn}(t) + 12e^{-80t}u(t) \text{ V}$$

P 17.34 [a]

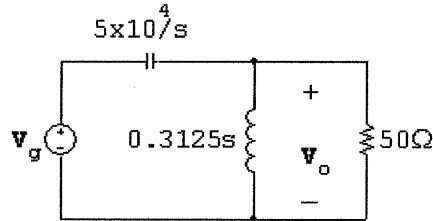

$$\frac{(V_o - V_g)s}{5 \times 10^4} + \frac{V_o}{0.3125s} + \frac{V_o}{50} = 0$$

$$\therefore V_o = \frac{s^2 V_g}{s^2 + 1000s + 16 \times 10^4}$$

$$\frac{V_o}{V_g} = H(s) = \frac{s^2}{(s + 200)(s + 800)}$$

$$H(j\omega) = \frac{(j\omega)^2}{(j\omega + 200)(j\omega + 800)}$$

$$v_g = 90e^{-400|t|}; \quad V_g(\omega) = \frac{72,000}{(j\omega + 400)(-j\omega + 400)}$$

$$\therefore V_o(\omega) = H(j\omega)V_g(\omega) = \frac{72,000(j\omega)^2}{(j\omega + 200)(j\omega + 400)(j\omega + 800)(-j\omega + 400)}$$

$$= \frac{K_1}{j\omega + 200} + \frac{K_2}{j\omega + 400} + \frac{K_3}{j\omega + 800} + \frac{K_4}{-j\omega + 400}$$

$$K_1 = \frac{72,000(-200)^2}{(200)(600)(600)} = 40$$

$$K_2 = \frac{72,000(-400)^2}{(-200)(400)(800)} = -180$$

$$K_3 = \frac{72,000(-800)^2}{(-600)(-400)(1200)} = 160$$

$$K_4 = \frac{72,000(400)^2}{(600)(800)(1200)} = 20$$

$$\therefore v_o(t) = [40e^{-200t} - 180e^{-400t} + 160e^{-800t}]u(t) + 20e^{400t}u(-t) \text{ V}$$

$$[\text{b}] \quad v_o(0^-) = 20 \text{ V}; \quad V_o(0^+) = 40 - 180 + 160 = 20 \text{ V}$$

$$v_o(\infty) = 0 \text{ V}$$

$$[\text{c}] \quad I_L = \frac{V_o}{0.3125s} = \frac{3.2sV_g}{(s+200)(s+800)}$$

$$H(s) = \frac{I_L}{V_o} = \frac{3.2s}{(s+200)(s+800)}$$

$$H(j\omega) = \frac{3.2(j\omega)}{(j\omega+200)(j\omega+800)}$$

$$\begin{aligned} I_L(\omega) &= \frac{3.2(j\omega)(72,000)}{(j\omega+200)(j\omega+400)(j\omega+800)(-j\omega+400)} \\ &= \frac{K_1}{j\omega+200} + \frac{K_2}{j\omega+400} + \frac{K_3}{j\omega+800} + \frac{K_4}{-j\omega+400} \end{aligned}$$

$$K_4 = \frac{(3.2)(400)(72,000)}{(600)(800)(1200)} = 160 \text{ mA}$$

$$i_L(t) = 160e^{400t}u(-t); \quad \therefore i_L(0^-) = 160 \text{ mA}$$

$$K_1 = \frac{(3.2)(-200)(72,000)}{(200)(600)(600)} = -640 \text{ mA}$$

$$K_2 = \frac{(3.2)(-400)(72,000)}{(-200)(400)(800)} = 1440 \text{ mA}$$

$$K_3 = \frac{(3.2)(-800)(72,000)}{(-600)(-400)(1200)} = -640 \text{ mA}$$

$$\therefore i_L(0^+) = K_1 + K_2 + K_3 = -640 + 1440 - 640 = 160 \text{ mA}$$

$$\text{Checks, i.e., } i_L(0^+) = i_L(0^-) = 160 \text{ mA}$$


At  $t = 0^-$ :

$$v_C(0^-) = 90 - 20 = 70 \text{ V}$$

At  $t = 0^+$ :

$$v_C(0^+) = 90 - 20 = 70 \text{ V}$$

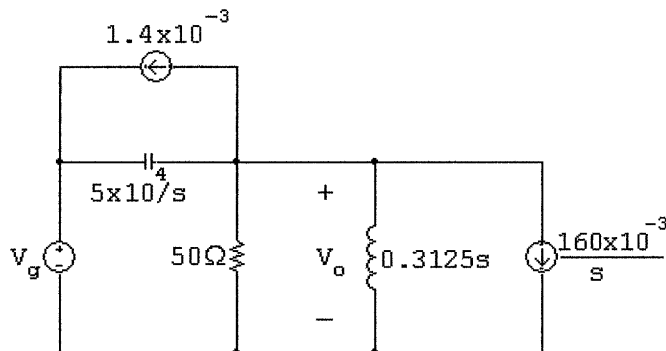[d] We can check the correctness of our solution for  $t \geq 0^+$  by using the Laplace transform. Our circuit becomes



$$\frac{V_o}{50} + \frac{V_o}{0.3125s} + \frac{(V_o - V_g)s}{5 \times 10^4} + 1.4 \times 10^{-3} + \frac{160 \times 10^{-3}}{s} = 0$$

$$\therefore (s^2 + 1000s + 16 \times 10^4)V_o = s^2V_g - (70s + 8000)$$

$$v_g(t) = 90e^{-400t}u(t) \text{ V}; \quad V_g = \frac{90}{s + 400}$$

$$\therefore (s + 200)(s + 800)V_o = \frac{90s^2 - (70s + 8000)(s + 400)}{(s + 400)}$$

$$\begin{aligned} \therefore V_o &= \frac{20s^2 - 36,000s - 320 \times 10^4}{(s + 200)(s + 400)(s + 800)} \\ &= \frac{40}{s + 200} - \frac{180}{s + 400} + \frac{160}{s + 800} \end{aligned}$$

$$\therefore v_o(t) = [40e^{-200t} - 180e^{-400t} + 160e^{-800t}]u(t) \text{ V}$$

This agrees with our solution for  $v_o(t)$  for  $t \geq 0^+$ .

P 17.35 [a]  $V_g(\omega) = \frac{60}{-j\omega + 5} + \frac{900}{(j\omega + 5)^2}$

$$\frac{V_o}{12} + \frac{V_o}{4s + 20} + \frac{sV_o}{300} = 0$$

$$\therefore H(s) = \frac{V_o}{V_g} = \frac{25(s + 5)}{(s + 10)(s + 20)}$$

$$H(\omega) = \frac{25(j\omega + 5)}{(j\omega + 10)(j\omega + 20)}$$

$$V_o(\omega) = V_g(\omega)H(\omega)$$

$$\begin{aligned} &= \frac{1500(j\omega + 5)}{(j\omega + 10)(j\omega + 20)(-j\omega + 5)} + \frac{22,500}{(j\omega + 10)(j\omega + 20)(j\omega + 5)^2} \\ &= V_1(\omega) + V_2(\omega) \end{aligned}$$

$$V_1(\omega) = \frac{K_1}{j\omega + 10} + \frac{K_2}{j\omega + 20} + \frac{K_3}{-j\omega + 5}$$

$$K_1 = \frac{1500(-5)}{(10)(15)} = -50$$

$$K_2 = \frac{1500(-15)}{(-10)(25)} = 90$$

$$K_3 = \frac{1500(10)}{(15)(25)} = 40$$

$$V_2(\omega) = \frac{K_4}{j\omega + 10} + \frac{K_5}{j\omega + 20} + \frac{K_6}{(j\omega + 5)^2} + \frac{K_7}{(j\omega + 5)}$$

$$K_4 = \frac{22,500}{(10)(-5)^2} = 90$$

$$K_5 = \frac{22,500}{(-10)(-15)^2} = -10$$

$$K_6 = \frac{22,500}{(5)(15)} = 300$$

$$K_7 = \frac{-22,500}{(5)^2(15)} + \frac{-22,500}{(5)(15)^2} = -80$$

$$\begin{aligned} V_o(\omega) &= \frac{-50}{j\omega + 10} + \frac{90}{j\omega + 20} + \frac{40}{-j\omega + 5} + \frac{90}{j\omega + 10} \\ &\quad - \frac{10}{j\omega + 20} + \frac{300}{(j\omega + 5)^2} - \frac{80}{j\omega + 5} \end{aligned}$$

$$= \frac{40}{j\omega + 10} + \frac{80}{j\omega + 20} + \frac{40}{-j\omega + 5} + \frac{300}{(j\omega + 5)^2} - \frac{80}{j\omega + 5}$$

$$\therefore v_o(t) = [40e^{-10t} + 80e^{-20t} - 80e^{-5t} + 300te^{-5t}]u(t) + 40e^{5t}u(-t) \text{ V}$$

[b]  $v_o(0^-) = 40 \text{ V}$

[c]  $v_o(0^+) = 40 + 80 - 80 = 40 \text{ V}$

$$\text{P 17.36 } V_o = \frac{60}{s} - \frac{40}{s+5} + \frac{20}{s+20} = \frac{40(s^2 + 20s + 150)}{s(s+5)(s+20)}$$

$$V_i = \frac{8}{s}$$

$$H(s) = \frac{5(s^2 + 20s + 150)}{(s+5)(s+20)}$$

$$H(j\omega) = \frac{5[(j\omega)^2 + 20(j\omega) + 150]}{(j\omega+5)(j\omega+20)}$$

$$V_i(\omega) = \frac{16}{(j\omega)}$$

$$\begin{aligned} V_o(\omega) &= \frac{80[(j\omega)^2 + 20(j\omega) + 150]}{j\omega(j\omega+5)(j\omega+20)} \\ &= \frac{K_1}{j\omega} + \frac{K_2}{j\omega+5} + \frac{K_3}{j\omega+20} \end{aligned}$$

$$K_1 = \frac{(80)(150)}{100} = 120$$

$$K_2 = \frac{(80)(25 - 100 + 150)}{(-5)(15)} = -80$$

$$K_3 = \frac{(80)(150)}{300} = 40$$

$$\therefore v_o(t) = 60\text{sgn}(t) - 80e^{-5t}u(t) + 40e^{-20t}u(t) \text{ V}$$

$$\text{P 17.37 [a] } f(t) = \frac{1}{2\pi} \left\{ \int_{-\infty}^0 e^{\omega} e^{j t \omega} d\omega + \int_0^{\infty} e^{-\omega} e^{j t \omega} d\omega \right\} = \frac{1/\pi}{1+t^2}$$

$$\text{[b] } W = 2 \int_0^{\infty} \frac{(1/\pi)^2}{(1+t^2)^2} dt = \frac{2}{\pi^2} \int_0^{\infty} \frac{dt}{(1+t^2)^2} = \frac{1}{2\pi} \text{ J}$$

$$\text{[c] } W = \frac{1}{\pi} \int_0^{\infty} e^{-2\omega} d\omega = \frac{1}{\pi} \frac{e^{-2\omega}}{-2} \Big|_0^{\infty} = \frac{1}{2\pi} \text{ J}$$

$$\text{[d] } \frac{1}{\pi} \int_0^{\omega_1} e^{-2\omega} d\omega = \frac{0.9}{2\pi}, \quad 1 - e^{-2\omega_1} = 0.9, \quad e^{2\omega_1} = 10$$

$$\omega_1 = (1/2) \ln 10 \cong 1.15 \text{ rad/s}$$



$$\text{P 17.38 } I_o = \frac{I_g(10)}{10 + 0.2s} = \frac{50I_g}{s + 50}$$

$$H(s) = \frac{I_o}{I_g} = \frac{50}{s + 50}$$

$$H(j\omega) = \frac{50}{j\omega + 50}$$

$$I_g(\omega) = \frac{3}{j\omega + 25}$$

$$I_o(\omega) = \frac{150}{(j\omega + 25)(j\omega + 50)}$$

$$|I_o(\omega)| = \frac{150}{\sqrt{(\omega^2 + 625)(\omega^2 + 2500)}}$$

$$|I_o(\omega)|^2 = \frac{22,500}{(\omega^2 + 625)(\omega^2 + 2500)} = \frac{12}{\omega^2 + 625} - \frac{12}{\omega^2 + 2500}$$

$$\begin{aligned} W_o &= \frac{1}{\pi} \int_0^\infty \frac{12d\omega}{\omega^2 + 625} - \frac{1}{\pi} \int_0^\infty \frac{12d\omega}{\omega^2 + 2500} \\ &= \frac{12}{\pi} \cdot \frac{1}{25} \cdot \tan^{-1} \left( \frac{\omega}{25} \right) \Big|_0^\infty - \frac{12}{\pi} \cdot \frac{1}{50} \cdot \tan^{-1} \left( \frac{\omega}{50} \right) \Big|_0^\infty \\ &= \frac{12}{25\pi} \cdot \frac{\pi}{2} - \frac{12}{50\pi} \cdot \frac{\pi}{2} = \frac{12}{50} - \frac{6}{50} = \frac{6}{50} = 120 \text{ mJ} \end{aligned}$$

$$\therefore W_o(\text{total}) = 120 \text{ mJ}$$

$$W_o(10\text{rad/s}) = \frac{12}{\pi} \left( \frac{1}{25} \tan^{-1}(0.4) \right) - \frac{12}{\pi} \left( \frac{1}{50} \tan^{-1}(0.2) \right) = 43.06 \text{ mJ}$$

$$\% = \frac{43.06}{120}(100) = 35.88\%$$

$$\text{P 17.39 [a] } V_g(\omega) = \frac{600}{(j\omega + 5)(-j\omega + 5)}$$


$$H(s) = \frac{V_o}{V_g} = \frac{5}{s + 25}; \quad H(\omega) = \frac{5}{(j\omega + 25)}$$

$$V_o(\omega) = \frac{3000}{(j\omega + 5)(j\omega + 25)(-j\omega + 5)}$$


$$V_o(\omega) = \frac{15}{j\omega + 5} - \frac{5}{j\omega + 25} + \frac{10}{-j\omega + 5}$$

$$v_o(t) = [15e^{-5t} - 5e^{-25t}]u(t) + 10e^{5t}u(-t) \text{ V}$$

$$[\text{b}] \quad |V_g(\omega)| = \frac{600}{(\omega^2 + 25)}$$

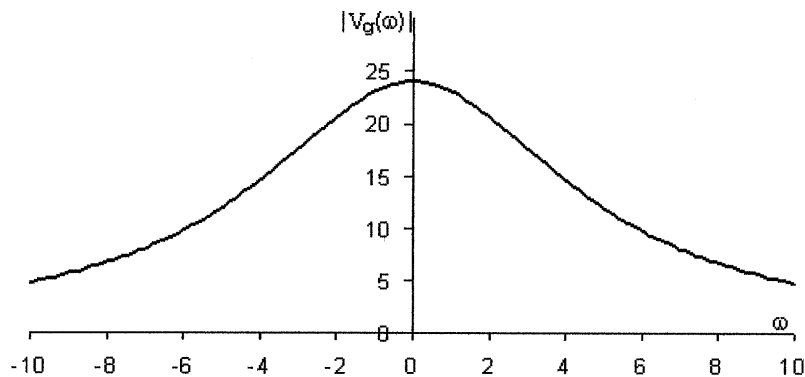

$$[\text{c}] \quad |V_o(\omega)| = \frac{3000}{(\omega^2 + 25)\sqrt{\omega^2 + 625}}$$

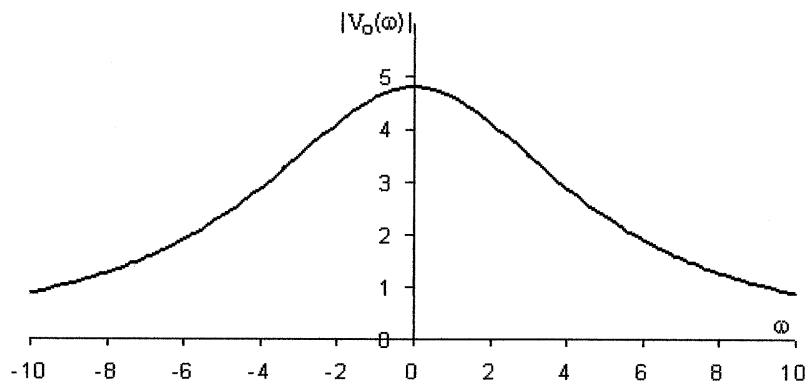

$$[\text{d}] \quad W_i = 2 \int_0^{\infty} 3600e^{-10t} dt = 7200 \left. \frac{e^{-10t}}{-10} \right|_0^{\infty} = 720 \text{ J}$$

$$\begin{aligned}
 [\text{e}] \quad W_o &= \int_{-\infty}^0 100e^{10t} dt + \int_0^{\infty} (15e^{-5t} - 5e^{-25t})^2 dt \\
 &= 10 + \int_0^{\infty} [225e^{-10t} - 150e^{-30t} + 25e^{-50t}] dt \\
 &= 10 + 22.5 - 5 + 0.5 = 28 \text{ J}
 \end{aligned}$$

$$[\mathbf{f}] \quad |V_g(\omega)| = \frac{600}{\omega^2 + 25}, \quad |V_g^2(\omega)| = \frac{36 \times 10^4}{(\omega^2 + 25)^2}$$

$$\begin{aligned} W_g &= \frac{36 \times 10^4}{\pi} \int_0^{10} \frac{d\omega}{(\omega^2 + 25)^2} \\ &= \frac{36 \times 10^4}{\pi} \left\{ \frac{1}{2(25)} \left( \frac{\omega}{\omega^2 + 25} + \frac{1}{5} \tan^{-1} \frac{\omega}{5} \right) \right\}_0^{10} \\ &= \frac{7200}{\pi} \left( \frac{10}{125} + \frac{1}{5} \tan^{-1} 2 \right) = 690.8 \text{ J} \end{aligned}$$

$$\therefore \% = \left( \frac{690.8}{720} \right) \times 100 = 95.95\%$$

$$\begin{aligned} [\mathbf{g}] \quad |V_o(\omega)|^2 &= \frac{9 \times 10^6}{(\omega^2 + 25)^2(\omega^2 + 625)} \\ &= \frac{15,000}{(\omega^2 + 25)^2} - \frac{25}{\omega^2 + 25} + \frac{25}{(\omega^2 + 625)} \end{aligned}$$

$$\begin{aligned} W_o &= \frac{1}{\pi} \left\{ 15,000 \left( \frac{1}{2(25)} \right) \left( \frac{\omega}{\omega^2 + 25} + \frac{1}{5} \tan^{-1} \frac{\omega}{5} \right) \right\}_0^{10} - 25 \left( \frac{1}{5} \right) \tan^{-1} \frac{\omega}{5} \Big|_0^{10} \\ &\quad + 25 \left( \frac{1}{25} \right) \tan^{-1} \frac{\omega}{25} \Big|_0^{10} \Big\} \\ &= \frac{300}{\pi} \left( \frac{10}{125} + \frac{1}{5} \tan^{-1} 2 \right) - \frac{5}{\pi} \tan^{-1} 2 + \frac{1}{\pi} \tan^{-1} 0.4 \\ &= 27.14 \text{ J} \end{aligned}$$

$$\% = \frac{27.14}{28} \times 100 = 96.93\%$$

$$\text{P 17.40} \quad I_g(\omega) = \frac{30 \times 10^{-6}}{j\omega + 2}$$

$$H(s) = \frac{V_o}{I_g} = \frac{1/C}{s + 1/RC} = \frac{800,000}{s + 8}$$

$$H(\omega) = \frac{8 \times 10^5}{j\omega + 8}; \quad V_o(\omega) = I_g(\omega)H(\omega)$$

$$\therefore V_o(\omega) = \frac{24}{(j\omega + 2)(j\omega + 8)}$$

$$|V_o(\omega)| = \frac{24}{\sqrt{\omega^2 + 4} \cdot \sqrt{\omega^2 + 64}}$$


$$|V_o(\omega)|^2 = \frac{576}{(\omega^2 + 4)(\omega^2 + 64)} = \frac{9.6}{\omega^2 + 4} - \frac{9.6}{\omega^2 + 64}$$

$$\begin{aligned} W_o &= \frac{1}{\pi} \int_0^\infty \frac{9.6 d\omega}{\omega^2 + 4} - \frac{1}{\pi} \int_0^\infty \frac{9.6 d\omega}{\omega^2 + 64} \\ &= \frac{9.6}{\pi} \cdot \frac{1}{2} \cdot \frac{\pi}{2} - \frac{9.6}{\pi} \cdot \frac{1}{8} \cdot \frac{\pi}{2} = 1.8 \text{ J TOTAL} \end{aligned}$$

$$W_{\text{to } 4 \text{ rad/s}} = \frac{4.8}{\pi} \tan^{-1} 2 - \frac{1.2}{\pi} \tan^{-1} 0.5 = 1.5145 \text{ J}$$

$$\% = \left( \frac{1.5145}{1.8} \right) 100 = 84.14\%$$

P 17.41 [a]  $|V_i(\omega)|^2 = \frac{4 \times 10^4}{\omega^2}$ ;  $|V_i(100)|^2 = \frac{4 \times 10^4}{100^2} = 4$ ;  $|V_i(200)|^2 = \frac{4 \times 10^4}{200^2} = 1$

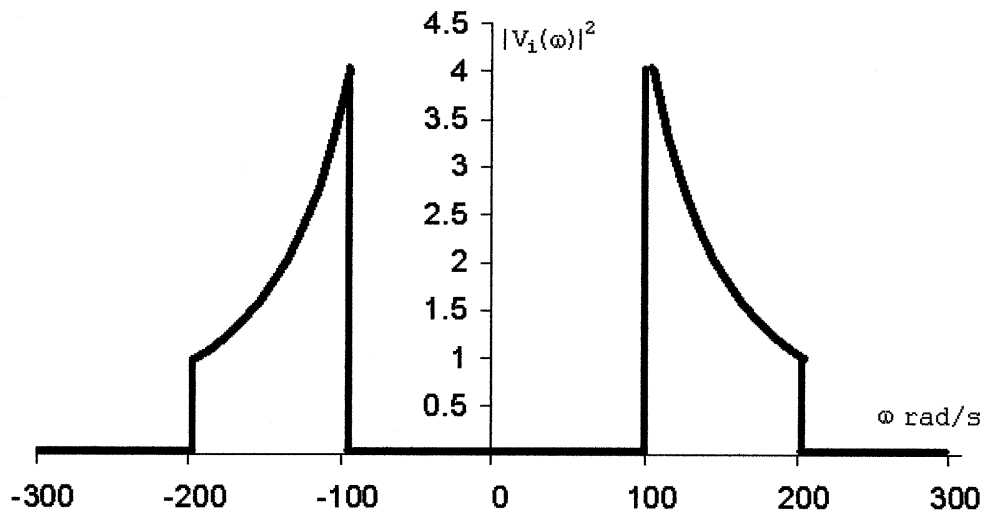

[b]  $V_o = \frac{V_i R}{R + (1/sC)} = \frac{sRCV_i}{RCs + 1}$


$$H(s) = \frac{V_o}{V_i} = \frac{s}{s + (1/RC)}; \quad \frac{1}{RC} = \frac{10^6 10^{-3}}{(0.5)(20)} = \frac{1000}{10} = 100$$

$$H(j\omega) = \frac{j\omega}{j\omega + 100}$$

$$|V_o(\omega)| = \frac{200}{|\omega|} \cdot \frac{|\omega|}{\sqrt{\omega^2 + 10^4}} = \frac{200}{\sqrt{\omega^2 + 10^4}}$$

$$|V_o(\omega)|^2 = \frac{4 \times 10^4}{\omega^2 + 10^4}, \quad 100 \leq \omega \leq 200 \text{ rad/s}; \quad |V_o(\omega)|^2 = 0, \quad \text{elsewhere}$$

$$|V_o(100)|^2 = \frac{4 \times 10^4}{10^4 + 10^4} = 2; \quad |V_o(200)|^2 = \frac{4 \times 10^4}{5 \times 10^4} = 0.8$$

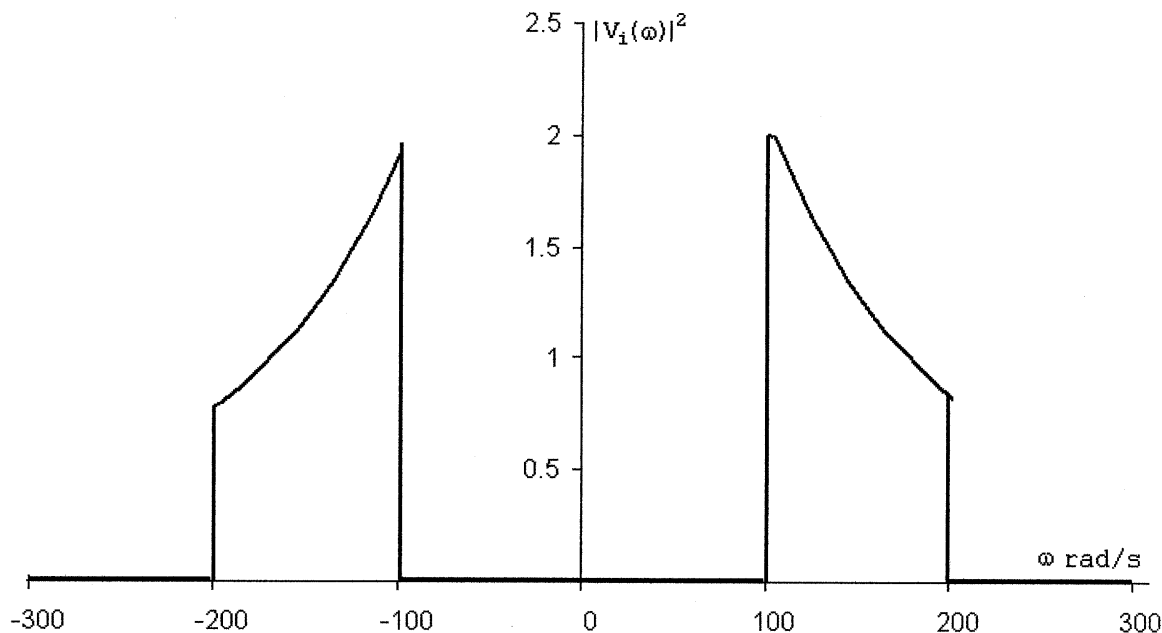

$$\begin{aligned} \text{[c]} \quad W_{1\Omega} &= \frac{1}{\pi} \int_{100}^{200} \frac{4 \times 10^4}{\omega^2} d\omega = \frac{4 \times 10^4}{\pi} \left[ -\frac{1}{\omega} \right]_{100}^{200} \\ &= \frac{4 \times 10^4}{\pi} \left[ \frac{1}{100} - \frac{1}{200} \right] = \frac{200}{\pi} \cong 63.66 \text{ J} \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad W_{1\Omega} &= \frac{1}{\pi} \int_{100}^{200} \frac{4 \times 10^4}{\omega^2 + 10^4} d\omega = \frac{4 \times 10^4}{\pi} \cdot \tan^{-1} \frac{\omega}{100} \Big|_{100}^{200} \\ &= \frac{400}{\pi} [\tan^{-1} 2 - \tan^{-1} 1] \cong 40.97 \text{ J} \end{aligned}$$

P 17.42 [a]  $V_i(\omega) = \frac{A}{a + j\omega}; \quad |V_i(\omega)| = \frac{A}{\sqrt{a^2 + \omega^2}}$

$$H(s) = \frac{s}{s + \alpha}; \quad H(j\omega) = \frac{j\omega}{\alpha + j\omega}; \quad |H(\omega)| = \frac{\omega}{\sqrt{\alpha^2 + \omega^2}}$$

$$\text{Therefore } |V_o(\omega)| = \frac{\omega A}{\sqrt{(a^2 + \omega^2)(\alpha^2 + \omega^2)}}$$

$$\text{Therefore } |V_o(\omega)|^2 = \frac{\omega^2 A^2}{(a^2 + \omega^2)(\alpha^2 + \omega^2)}$$

$$W_{\text{IN}} = \int_0^\infty A^2 e^{-2at} dt = \frac{A^2}{2a}; \quad \text{when } \alpha = a \text{ we have}$$

$$\begin{aligned}
W_{\text{OUT}} &= \frac{A^2}{\pi} \int_0^a \frac{\omega^2 d\omega}{(\omega^2 + a^2)^2} = \frac{A^2}{\pi} \left\{ \int_0^a \frac{d\omega}{a^2 + \omega^2} - \int_0^a \frac{a^2 d\omega}{(a^2 + \omega^2)^2} \right\} \\
&= \frac{A^2}{4a\pi} \left( \frac{\pi}{2} - 1 \right)
\end{aligned}$$

$$W_{\text{OUT}}(\text{total}) = \frac{A^2}{\pi} \int_0^\infty \left[ \frac{\omega^2}{(a^2 + \omega^2)^2} \right] d\omega = \frac{A^2}{4a}$$

$$\text{Therefore } \frac{W_{\text{OUT}}(a)}{W_{\text{OUT}}(\text{total})} = 0.5 - \frac{1}{\pi} = 0.1817 \quad \text{or} \quad 18.17\%$$

[b] When  $\alpha \neq a$  we have

$$\begin{aligned}
W_{\text{OUT}}(\alpha) &= \frac{1}{\pi} \int_0^\alpha \frac{\omega^2 A^2 d\omega}{(a^2 + \omega^2)(\alpha^2 + \omega^2)} \\
&= \frac{A^2}{\pi} \left\{ \int_0^\alpha \left[ \frac{K_1}{a^2 + \omega^2} + \frac{K_2}{\alpha^2 + \omega^2} \right] d\omega \right\}
\end{aligned}$$

$$\text{where } K_1 = \frac{a^2}{a^2 - \alpha^2} \quad \text{and} \quad K_2 = \frac{-\alpha^2}{a^2 - \alpha^2}$$

Therefore

$$W_{\text{OUT}}(\alpha) = \frac{A^2}{\pi(a^2 - \alpha^2)} \left[ a \tan^{-1} \left( \frac{\alpha}{a} \right) - \frac{\alpha\pi}{4} \right]$$

$$W_{\text{OUT}}(\text{total}) = \frac{A^2}{\pi(a^2 - \alpha^2)} \left[ a \frac{\pi}{2} - \alpha \frac{\pi}{2} \right] = \frac{A^2}{2(a + \alpha)}$$

$$\text{Therefore } \frac{W_{\text{OUT}}(\alpha)}{W_{\text{OUT}}(\text{total})} = \frac{2}{\pi(a - \alpha)} \cdot \left[ a \tan^{-1} \left( \frac{\alpha}{a} \right) - \frac{\alpha\pi}{4} \right]$$


For  $\alpha = a\sqrt{3}$ , this ratio is 0.2723, or 27.23% of the output energy lies in the frequency band between 0 and  $a\sqrt{3}$ .

[c] For  $\alpha = a/\sqrt{3}$ , the ratio is 0.1057, or 10.57% of the output energy lies in the frequency band between 0 and  $a/\sqrt{3}$ .

## Two-Port Circuits
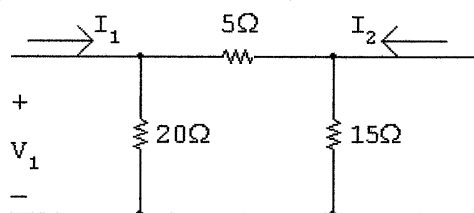
### Assessment Problems

AP 18.1 With port 2 short-circuited, we have




$$I_1 = \frac{V_1}{20} + \frac{V_1}{5}; \quad \frac{I_1}{V_1} = y_{11} = 0.25 \text{ S}; \quad I_2 = \left( \frac{-20}{25} \right) I_1 = -0.8 I_1$$

When  $V_2 = 0$ , we have  $I_1 = y_{11}V_1$  and  $I_2 = y_{21}V_1$

Therefore  $I_2 = -0.8(y_{11}V_1) = -0.8y_{11}V_1$

Thus  $y_{21} = -0.8y_{11} = -0.2 \text{ S}$

With port 1 short-circuited, we have

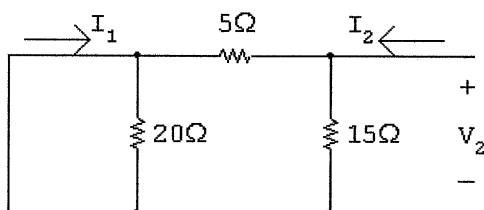

$$I_2 = \frac{V_2}{15} + \frac{V_2}{5}; \quad \frac{I_2}{V_2} = y_{22} = \left( \frac{4}{15} \right) \text{ S}$$

$$I_1 = \left( \frac{-15}{20} \right) I_2 = -0.75 I_2 = -0.75 y_{22} V_2$$

$$\text{Therefore } y_{12} = (-0.75) \frac{4}{15} = -0.2 \text{ S}$$

AP 18.2

$$h_{11} = \left( \frac{V_1}{I_1} \right)_{V_2=0} = 20 \parallel 5 = 4 \Omega$$

$$h_{21} = \left( \frac{I_2}{I_1} \right)_{V_2=0} = \frac{(-20/25)I_1}{I_1} = -0.8$$

$$h_{12} = \left( \frac{V_1}{V_2} \right)_{I_1=0} = \frac{(20/25)V_2}{V_2} = 0.8$$

$$h_{22} = \left( \frac{I_2}{V_2} \right)_{I_1=0} = \frac{1}{15} + \frac{1}{25} = \frac{8}{75} \text{ S}$$

$$g_{11} = \left( \frac{I_1}{V_1} \right)_{I_2=0} = \frac{1}{20} + \frac{1}{20} = 0.1 \text{ S}$$

$$g_{21} = \left( \frac{V_2}{V_1} \right)_{I_2=0} = \frac{(15/20)V_1}{V_1} = 0.75$$

$$g_{12} = \left( \frac{I_1}{I_2} \right)_{V_1=0} = \frac{(-15/20)I_2}{I_2} = -0.75$$

$$g_{22} = \left( \frac{V_2}{I_2} \right)_{V_1=0} = 15 \parallel 5 = \frac{75}{20} = 3.75 \Omega$$

AP 18.3

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} = \frac{5 \times 10^{-6}}{50 \times 10^{-3}} = 0.1 \text{ mS}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} = \frac{200 \times 10^{-3}}{50 \times 10^{-3}} = 4$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} = \frac{2 \times 10^{-6}}{0.5 \times 10^{-6}} = 4$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} = \frac{10 \times 10^{-3}}{0.5 \times 10^{-6}} = 20 \text{ k}\Omega$$



AP 18.4 First calculate the  $b$ -parameters:

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0} = \frac{15}{10} = 1.5 \Omega; \quad b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} = \frac{30}{10} = 3 \text{ S}$$

$$b_{12} = \left. \frac{-V_2}{I_1} \right|_{V_1=0} = \frac{-10}{-5} = 2 \Omega; \quad b_{22} = \left. \frac{-I_2}{I_1} \right|_{V_1=0} = \frac{-4}{-5} = 0.8$$

Now the  $z$ -parameters are calculated:

$$z_{11} = \frac{b_{22}}{b_{21}} = \frac{0.8}{3} = \frac{4}{15} \Omega; \quad z_{12} = \frac{1}{b_{21}} = \frac{1}{3} \Omega$$

$$z_{21} = \frac{\Delta b}{b_{21}} = \frac{(1.5)(0.8) - 6}{3} = -1.6 \Omega; \quad z_{22} = \frac{b_{11}}{b_{21}} = \frac{1.5}{3} = \frac{1}{2} \Omega$$

AP 18.5

$$z_{11} = z_{22}, \quad z_{12} = z_{21}, \quad 95 = z_{11}(5) + z_{12}(0)$$

$$\text{Therefore, } z_{11} = z_{22} = 95/5 = 19 \Omega$$

$$11.52 = 19I_1 - z_{12}(2.72)$$

$$0 = z_{12}I_1 - 19(2.72)$$

Solving these simultaneous equations for  $z_{12}$  yields the quadratic equation

$$z_{12}^2 + \left(\frac{72}{17}\right)z_{12} - \frac{6137}{17} = 0$$

For a purely resistive network, it follows that  $z_{12} = z_{21} = 17 \Omega$ .

$$\begin{aligned} \text{AP 18.6 [a]} \quad I_2 &= \frac{-V_g}{a_{11}Z_L + a_{12} + a_{21}Z_gZ_L + a_{22}Z_g} \\ &= \frac{-50 \times 10^{-3}}{(5 \times 10^{-4})(5 \times 10^3) + 10 + (10^{-6})(100)(5 \times 10^3) + (-3 \times 10^{-2})(100)} \\ &= \frac{-50 \times 10^{-3}}{10} = -5 \text{ mA} \end{aligned}$$

$$P_L = \frac{1}{2}(5 \times 10^{-3})^2(5 \times 10^3) = 62.5 \text{ mW}$$

$$\begin{aligned} \text{[b]} \quad Z_{\text{Th}} &= \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g} = \frac{10 + (-3 \times 10^{-2})(100)}{5 \times 10^{-4} + (10^{-6})(100)} \\ &= \frac{7}{6 \times 10^{-4}} = \frac{70}{6} \text{ k}\Omega \end{aligned}$$

$$[\text{c}] \quad V_{\text{Th}} = \frac{V_g}{a_{11} + a_{21}Z_g} = \frac{50 \times 10^{-3}}{6 \times 10^{-4}} = \frac{500}{6} \text{ V}$$

$$\text{Therefore} \quad V_2 = \frac{250}{6} \text{ V}; \quad P_{\text{max}} = \frac{(1/2)(250/6)^2}{(70/6) \times 10^3} = 74.4 \text{ mW}$$

AP 18.7 [a] For the given bridged-tee circuit, we have

$$a'_{11} = a'_{22} = 1.25, \quad a'_{21} = \frac{1}{20} \text{ S}, \quad a'_{12} = 11.25 \Omega$$

The  $a$ -parameters of the cascaded networks are

$$a_{11} = (1.25)^2 + (11.25)(0.05) = 2.125$$

$$a_{12} = (1.25)(11.25) + (11.25)(1.25) = 28.125 \Omega$$

$$a_{21} = (0.05)(1.25) + (1.25)(0.05) = 0.125 \text{ S}$$

$$a_{22} = a_{11} = 2.125, \quad R_{\text{Th}} = (45.125/3.125) = 14.44 \Omega$$

$$[\text{b}] \quad V_t = \frac{100}{3.125} = 32 \text{ V}; \quad \text{therefore} \quad V_2 = 16 \text{ V}$$

$$[\text{c}] \quad P = \frac{16^2}{14.44} = 17.73 \text{ W}$$

## Problems

$$\text{P 18.1} \quad h_{11} = \left( \frac{V_1}{I_1} \right)_{V_2=0} = 20 \parallel 5 = 4 \Omega$$

$$h_{21} = \left( \frac{I_2}{I_1} \right)_{V_2=0} = \frac{(-20/25)I_1}{I_1} = -0.8$$

$$h_{12} = \left( \frac{V_1}{V_2} \right)_{I_1=0} = \frac{(20/25)V_2}{V_2} = 0.8$$

$$h_{22} = \left( \frac{I_2}{V_2} \right)_{I_1=0} = \frac{1}{15} + \frac{1}{25} = \frac{8}{75} \text{ S}$$


$$g_{11} = \left( \frac{I_1}{V_1} \right)_{I_2=0} = \frac{1}{20} + \frac{1}{20} = 0.1 \text{ S}$$

$$g_{21} = \left( \frac{V_2}{V_1} \right)_{I_2=0} = \frac{(15/20)V_1}{V_1} = 0.75$$

$$g_{12} = \left( \frac{I_1}{I_2} \right)_{V_1=0} = \frac{(-15/20)I_2}{I_2} = -0.75$$

$$g_{22} = \left( \frac{V_2}{I_2} \right)_{V_1=0} = 15 \parallel 5 = \frac{75}{20} = 3.75 \Omega$$

P 18.2

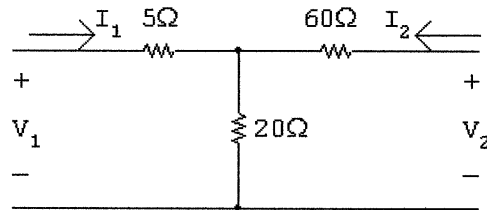

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 5 + 20 = 25 \Omega$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 20 \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = 20 \Omega$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = 60 + 20 = 80 \Omega$$

P 18.3  $\Delta z = (25)(80) - (20)(20) = 1600$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{80}{1600} = \frac{1}{20} \text{ S}$$

$$y_{12} = \frac{-z_{12}}{\Delta z} = \frac{-20}{1600} = \frac{-1}{80} \text{ S}$$

$$y_{21} = \frac{-z_{21}}{\Delta z} = \frac{-20}{1600} = \frac{-1}{80} \text{ S}$$

$$y_{22} = \frac{-z_{11}}{\Delta z} = \frac{25}{1600} = \frac{1}{64} \text{ S}$$

P 18.4  $V_1 = z_{11}I_1 + z_{12}I_2$

$$V_1 = z_{21}I_1 + z_{22}I_2$$

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 5 \parallel 20 + 16 = 20 \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = 16 + (10)(5/25) = 18 \Omega$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 16 + (10/25)(5) = 18 \Omega$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = 10 \parallel 15 + 6 = 22 \Omega$$


Summary:

$$z_{11} = 20 \Omega \quad z_{12} = 18 \Omega \quad z_{21} = 18 \Omega \quad z_{22} = 22 \Omega$$

P 18.5  $V_2 = b_{11}V_1 - b_{12}I_1$

$$I_2 = b_{21}V_1 - b_{22}I_1$$

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0}; \quad b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0}$$

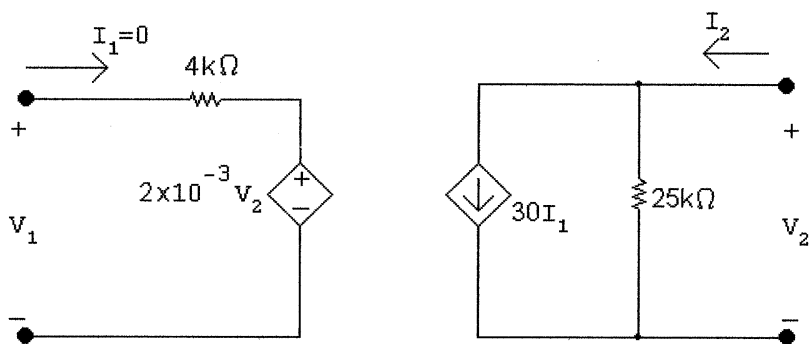


$$V_1 = 2 \times 10^{-3} V_2$$

$$\therefore b_{11} = \frac{1}{2 \times 10^{-3}} = 500$$

$$V_2 = 25,000 I_2; \quad \text{so} \quad V_1 = (2 \times 10^{-3})(25,000) I_2 = 50 I_2$$

$$\therefore b_{21} = \frac{1}{50} = 20 \text{ mS}$$

$$b_{12} = \left. \frac{-V_2}{I_1} \right|_{V_1=0}; \quad b_{22} = \left. \frac{-I_2}{I_1} \right|_{V_1=0}$$

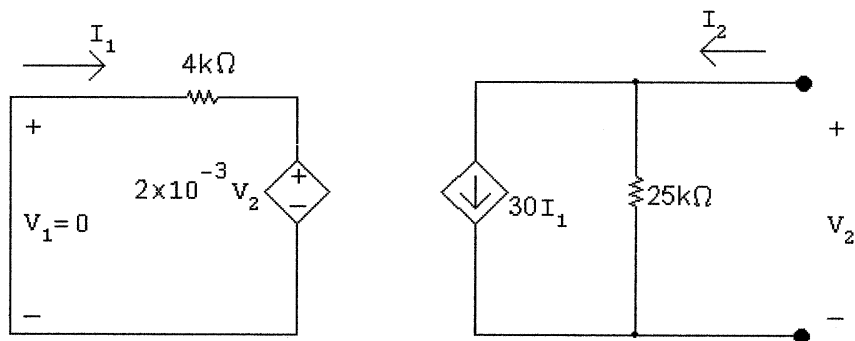

$$I_1 = -\frac{2 \times 10^{-3} V_2}{4000}; \quad \therefore b_{12} = \frac{4000}{2 \times 10^{-3}} = 2 \text{ M}\Omega$$

$$I_2 = 30 I_1 + \frac{V_2}{25,000} = 30 I_1 - \frac{4000}{(2 \times 10^{-3})(25,000)} I_1 = -50 I_1; \quad \therefore b_{22} = 50$$

Summary

$$b_{11} = 500; \quad b_{12} = 2 \text{ M}\Omega; \quad b_{21} = 20 \text{ mS}; \quad b_{22} = 50$$


$$\text{P 18.6} \quad g_{11} = \frac{b_{21}}{b_{22}} = \frac{20 \times 10^{-3}}{50} = 0.4 \text{ mS}$$

$$g_{12} = \frac{-1}{b_{22}} = \frac{-1}{50} = -0.02$$

$$g_{21} = \frac{\Delta b}{b_{22}} = \frac{(500)(50) - (2 \times 10^6)(20 \times 10^{-3})}{50} = -300$$

$$g_{22} = \frac{b_{12}}{b_{22}} = \frac{2 \times 10^6}{50} = 40 \text{ k}\Omega$$

$$\text{P 18.7} \quad h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

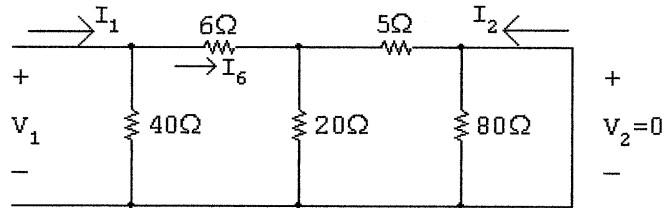


$$\frac{V_1}{I_1} = 40 \parallel [6 + 20 \parallel 5] = 40 \parallel 10 = 8 \Omega \quad \therefore h_{11} = 8 \Omega$$

$$I_6 = \frac{40}{40 + 10} I_1 = 0.8 I_1$$

$$I_2 = \frac{-20}{20 + 5} I_6 = -0.8 I_6 = -0.8(0.8) I_1 = -0.64 I_1 \quad \therefore h_{21} = -0.64$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}; \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

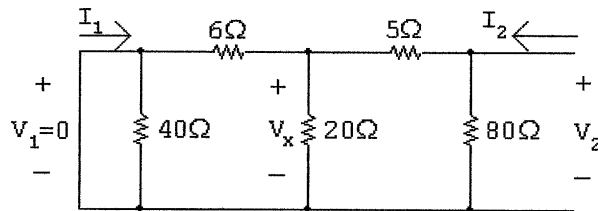

$$\frac{V_2}{I_2} = 80 \parallel [5 + 20 \parallel (40 + 6)] = 15.314 \Omega \quad \therefore h_{22} = \frac{1}{15.314} = 65.3 \text{ mS}$$

$$V_x = \frac{20 \parallel 46}{5 + 20 \parallel 46} V_2$$

$$V_1 = \frac{40}{40 + 6} V_x = \frac{40(20 \parallel 46)}{46(5 + 20 \parallel 46)} V_2 = \frac{557.5758}{871.2121} V_2$$

$$\therefore h_{12} = 0.64$$


Summary:

$$h_{11} = 8 \Omega; \quad h_{12} = 0.64; \quad h_{21} = -0.64; \quad h_{22} = 65.3 \text{ mS}$$

P 18.8  $V_2 = b_{11}V_1 - b_{12}I_1$

$$I_2 = b_{21}V_1 - b_{22}I_1$$

$$b_{12} = \left. \frac{-V_2}{I_1} \right|_{V_1=0}; \quad b_{22} = \left. \frac{-I_2}{I_1} \right|_{V_1=0}$$

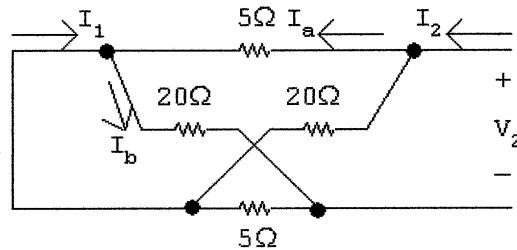

$$5 \parallel 20 = 4 \Omega$$

$$I_2 = \frac{V_2}{4 + 4} = \frac{V_2}{8}; \quad I_1 = I_b - I_a$$


$$I_a = \frac{20}{25} I_2; \quad I_b = \frac{5}{25} I_2$$

$$I_1 = \left( \frac{5}{25} - \frac{20}{25} \right) I_2 = \frac{-15}{25} I_2 = \frac{-3}{5} I_2$$

$$b_{22} = \frac{-I_2}{I_1} = \frac{5}{3}$$

$$b_{12} = \frac{-V_2}{I_1} = \frac{-V_2}{I_2} \left( \frac{I_2}{I_1} \right) = 8 \left( \frac{5}{3} \right) = \frac{40}{3} \Omega$$

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0}; \quad b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0}$$

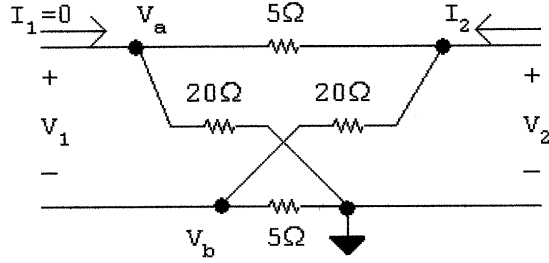

$$V_1 = V_a - V_b; \quad V_a = \frac{20}{25}V_2; \quad V_b = \frac{5}{25}V_2$$

$$V_1 = \frac{20}{25}V_2 - \frac{5}{25}V_2 = \frac{15}{25}V_2 = \frac{3}{5}V_2$$

$$b_{11} = \frac{V_2}{V_1} = \frac{5}{3}$$

$$V_2 = (20 + 5) \parallel (20 + 5) I_2 = 12.5 I_2$$

$$b_{21} = \frac{I_2}{V_1} = \left( \frac{I_2}{V_2} \right) \left( \frac{V_2}{V_1} \right) = \left( \frac{1}{12.5} \right) \left( \frac{5}{3} \right) = \frac{2}{15} \text{ S}$$

P 18.9  $a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}; \quad V_2 = \frac{V_1}{R_1 + R_3} R_3$

$$\therefore a_{11} = \frac{R_1 + R_3}{R_3} = 1 + \frac{R_1}{R_3} = 1.2 \quad \therefore \frac{R_1}{R_3} = 0.2$$

$$\therefore R_1 = 0.2 R_3 \quad (\text{Eq 1})$$


$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0}; \quad V_2 = I_3 R_3 = \frac{R_2}{R_1 + R_2 + R_3} I_1 R_3$$

$$\therefore a_{21} = \frac{R_1 + R_2 + R_3}{R_2 R_3} = 20 \times 10^{-3} \quad (\text{Eq 2})$$

Substitute Eq 1 into Eq 2:
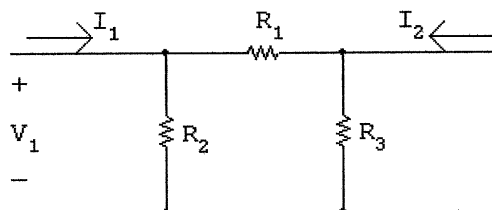
$$\frac{0.2 R_3 + R_2 + R_3}{R_2 R_3} = \frac{R_2 + 1.2 R_3}{R_2 R_3} = 20 \times 10^{-3} \quad (\text{Eq 3})$$





$$a_{22} = -\frac{I_1}{I_2} \Big|_{V_2=0}; \quad I_2 = \frac{-R_2}{R_1 + R_2} I_1; \quad \therefore a_{22} = \frac{R_1 + R_2}{R_2} = 1.4$$

$$\frac{R_1}{R_2} = 0.4; \quad \therefore R_2 = \frac{R_1}{0.4} = \frac{0.2R_3}{0.4} = 0.5R_3 \quad (\text{Eq 4})$$

Substitute Eq 4 into Eq 3:


$$\frac{0.5R_3 + 1.2R_3}{(0.5R_3)R_3} = \frac{3.4}{R_3} = 20 \times 10^{-3} \quad \therefore R_3 = 170 \Omega$$

Therefore,

$$R_1 = 0.2R_3 = 0.2(170) = 34 \Omega; \quad R_2 = 0.5R_3 = 0.5(170) = 85 \Omega$$

**Summary:**  $R_1 = 34 \Omega$ ;  $R_2 = 85 \Omega$ ;  $R_3 = 170 \Omega$

P 18.10  $h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}; \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$

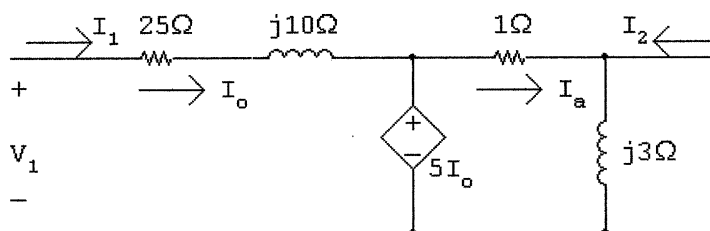


$$I_a = \frac{5I_o}{1} = 5I_1 = -I_2; \quad \therefore h_{21} = -5$$

$$V_1 = (25 + j10)I_1 + 5I_1 = (30 + j10)I_1 = (30 + j10)I_1$$

$$\therefore h_{11} = 30 + j10 \Omega$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}; \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

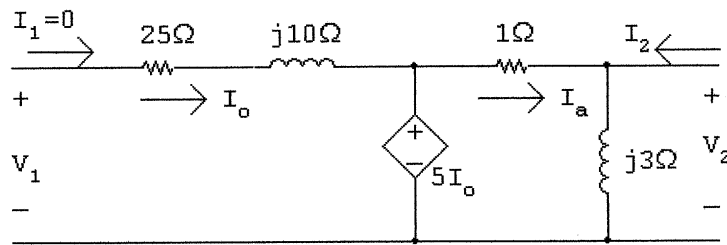

$I_o = 0$  thus  $5I_o = 0$  is a short circuit

$$V_1 = 5I_o = 0; \quad \therefore h_{12} = 0$$

$$h_{22} = \frac{I_2}{V_2} = \frac{1 + j3}{j3} = (1 - j/3) \text{ S}$$

Summary:

$$h_{11} = 30 + j10 \Omega; \quad h_{12} = 0; \quad h_{21} = -5; \quad h_{22} = 1 - j/3 \text{ S}$$

P 18.11  $V_1 = h_{11}I_1 + h_{12}V_2$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$I_1 = 0:$$

$$1 \times 10^{-3} = h_{12}(10); \quad \therefore h_{12} = 1 \times 10^{-4}$$

$$200 \times 10^{-6} = h_{22}(10); \quad \therefore h_{22} = 20 \times 10^{-6} \text{ S}$$

$$V_1 = 0:$$

$$80 \times 10^{-6} = h_{21}(-0.5 \times 10^{-6}) + (20 \times 10^{-6})(5); \quad \therefore h_{21} = 40$$

$$0 = h_{11}(-0.5 \times 10^{-6}) + (1 \times 10^{-4})(5); \quad \therefore h_{11} = 1000 \Omega$$

P 18.12 [a]  $V_1 = a_{11}V_2 - a_{12}I_2$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

$$\text{From } I_1 = 0: \quad 1 \times 10^{-3} = a_{11}(10) - a_{12}(200 \times 10^{-6})$$

$$\text{From } V_1 = 0: \quad 0 = a_{11}(5) - a_{12}(80 \times 10^{-6})$$

Solving simultaneously yields

$$a_{11} = -4 \times 10^{-4}; \quad a_{12} = -25 \Omega$$

$$\text{From } I_1 = 0: \quad 0 = a_{21}(10) - a_{22}(200 \times 10^{-6})$$

$$\text{From } V_1 = 0: \quad -0.5 \times 10^{-6} = a_{21}(5) - a_{22}(80 \times 10^{-6})$$

Solving simultaneously yields

$$a_{21} = -5 \times 10^{-7} \text{ S}; \quad a_{22} = -0.025$$

$$[\text{b}] \quad a_{11} = -\frac{\Delta h}{h_{21}} = \frac{-[(1000)(20 \times 10^{-6}) - (1 \times 10^{-4})(40)]}{40} = -4 \times 10^{-4}$$

$$a_{12} = \frac{-h_{11}}{h_{21}} = \frac{-1000}{40} = -25 \Omega$$


$$a_{21} = \frac{-h_{22}}{h_{21}} = \frac{-20 \times 10^{-6}}{40} = -5 \times 10^{-7} \text{ S}$$

$$a_{22} = \frac{-1}{h_{21}} = \frac{-1}{40} = -0.025$$

Summary:

$$a_{11} = -4 \times 10^{-4}; \quad a_{12} = -25 \Omega; \quad a_{21} = -5 \times 10^{-7} \text{ S}; \quad a_{22} = -0.025$$

$$\text{P 18.13} \quad y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}; \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

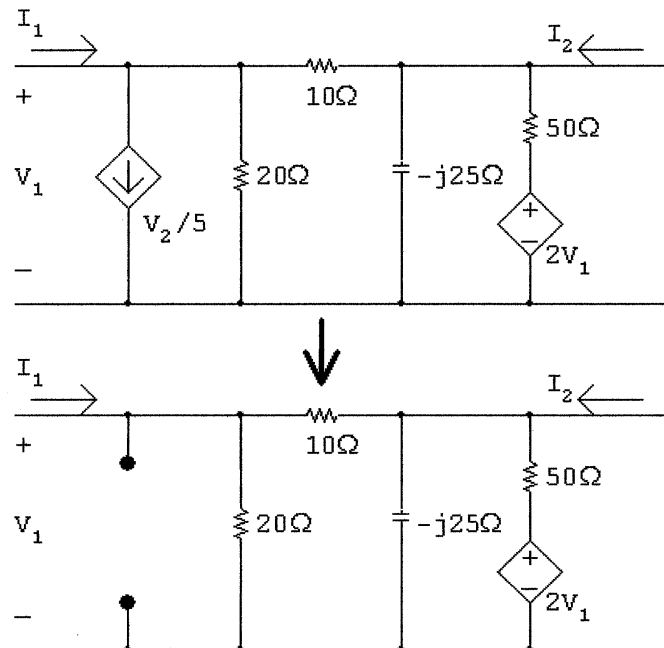


$$I_1 = \frac{V_1}{20} + \frac{V_1}{10} = \frac{3V_1}{20}; \quad \therefore y_{11} = \frac{I_1}{V_1} = \frac{3}{20} = 0.15 \text{ S}$$

$$I_2 = -\frac{2V_1}{50} - (I_1 - V_1/20) = -\frac{V_1}{25} - \frac{3V_1}{20} + \frac{V_1}{20} = -\frac{7V_1}{50}$$

$$\therefore y_{21} = \frac{I_2}{V_1} = -\frac{7}{50} = -0.14 \text{ S}$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}; \quad y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

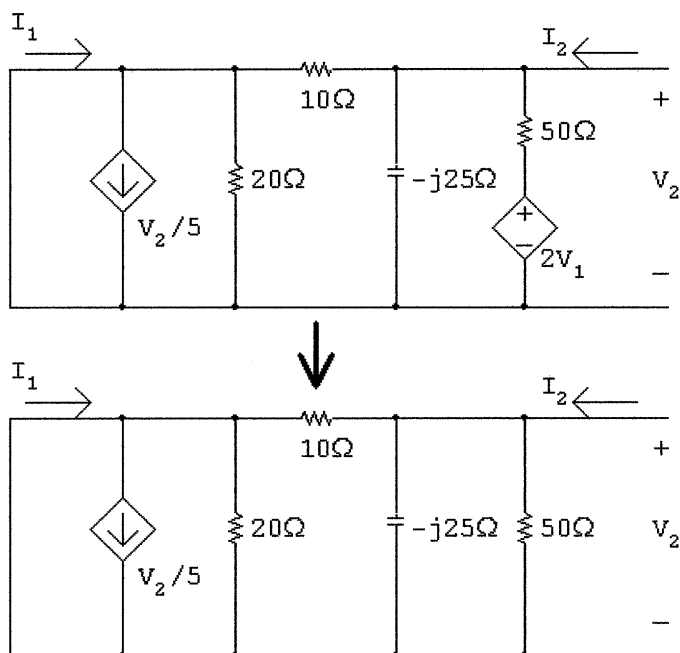

$$I_1 = \frac{V_2}{5} - \frac{V_2}{10} = 0.1V_2; \quad \therefore y_{12} = \frac{I_1}{V_2} = 0.1 \text{ S}$$

$$I_2 = \frac{V_2}{50} + \frac{V_2}{-j25} + \frac{V_2}{10} = \frac{6 + j2}{50} V_2$$

$$\therefore y_{22} = \frac{I_2}{V_2} = \frac{6 + j2}{50} = 0.12 + j0.04 \text{ S}$$

Summary:

$$y_{11} = 0.15 \text{ S}; \quad y_{12} = 0.1 \text{ S}; \quad y_{21} = -0.14 \text{ S}; \quad y_{22} = 0.12 + j0.04 \text{ S}$$


P 18.14  $b_{11} = -\frac{y_{11}}{y_{12}} = \frac{-0.15}{0.1} = -1.5$

$$b_{12} = -\frac{1}{y_{12}} = \frac{-1}{0.1} = -10 \Omega$$

$$b_{21} = -\frac{\Delta y}{y_{12}} = \frac{-[(0.15)(0.12 + j0.04) + (0.1)(0.14)]}{0.1} = -0.32 - j0.06 \text{ S}$$

$$b_{22} = \frac{y_{22}}{y_{12}} = \frac{0.12 + j0.04}{0.1} = 1.2 + j0.4$$

P 18.15  $h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$

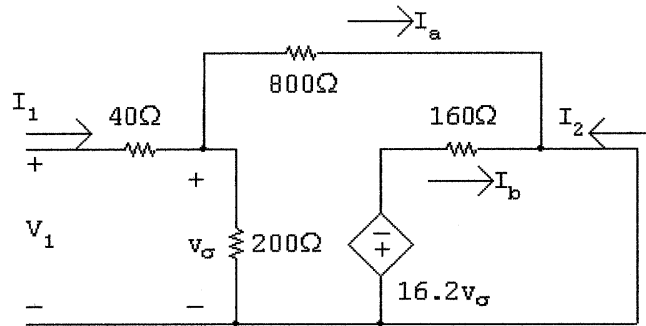

$$\frac{V_1}{I_1} = 40 + \frac{(800)(200)}{1000} = 40 + 160 = 200 \Omega$$

$$\therefore h_{11} = 200 \Omega$$

$$I_a = I_1 \left( \frac{200}{1000} \right) = 0.2I_1$$


$$16.2v_\sigma + 160I_b = 0; \quad v_\sigma = 160I_1$$

$$\therefore 160I_b = -2592I_1; \quad I_b = -16.2I_1$$

$$\therefore I_a + I_b + I_2 = 0; \quad 0.2I_1 - 16.2I_1 + I_2 = 0; \quad I_2 = 16I_1$$

$$\therefore h_{21} = 16$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}; \quad h_{21} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

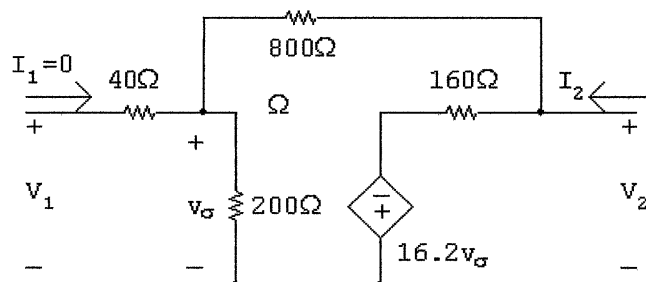

$$I_1 = 0; \quad v_\sigma = V_1$$

$$\frac{V_1}{200} + \frac{V_1 - V_2}{800} = 0; \quad 4V_1 + V_1 - V_2 = 0; \quad 5V_1 = V_2$$

$$\therefore h_{12} = \frac{1}{5} = 0.2$$

$$I_2 = \frac{V_2 + 16.2V_1}{160} + \frac{V_2 - V_1}{800}; \quad 800I_2 = 6V_2 + 80V_1$$

$$800I_2 = 6V_2 + 80(0.2V_2) = 22V_2$$

$$\therefore h_{22} = \frac{I_2}{V_2} = \frac{22}{800} = 27.5 \text{ mS}$$

Summary:

$$h_{11} = 200 \Omega; \quad h_{12} = 0.20; \quad h_{21} = 16; \quad h_{22} = 27.5 \text{ mS}$$

P 18.16  $V_1 = a_{11}V_2 - a_{12}I_2; \quad I_1 = a_{21}V_2 - a_{22}I_2$

$$V_1 = h_{11}I_1 + h_{12}V_2; \quad I_2 = h_{21}I_1 + h_{22}V_2$$

$$V_1 = -a_{12}I_2 + a_{11}V_2; \quad I_2 = \frac{a_{21}V_2 - I_1}{a_{22}}$$

$$\therefore V_1 = -a_{12} \left( \frac{a_{21} - I_1}{a_{22}} \right) + a_{11}V_2$$

$$V_1 = \frac{a_{12}}{a_{22}}I_1 + \left( \frac{a_{11}a_{22} - a_{12}a_{21}}{a_{22}} \right) V_2$$

$$\therefore h_{11} = \frac{a_{12}}{a_{22}}; \quad h_{12} = \frac{\Delta a}{a_{22}}$$

$$I_2 = -\frac{1}{a_{22}}I_1 + \frac{a_{21}}{a_{22}}V_2$$

$$\therefore h_{21} = -\frac{1}{a_{22}}; \quad h_{22} = \frac{a_{21}}{a_{22}}$$

$$\text{P 18.17 } I_1 = y_{11}V_1 + y_{12}V_2; \quad I_2 = y_{21}V_1 + y_{22}V_2$$

$$V_2 = b_{11}V_1 - b_{12}I_1; \quad I_2 = b_{21}V_1 - b_{22}I_1$$

$$I_1 = \frac{b_{11}}{b_{12}}V_1 - \frac{1}{b_{12}}V_2$$

$$\therefore y_{11} = \frac{b_{11}}{b_{12}}; \quad y_{12} = -\frac{1}{b_{12}}$$

$$I_2 = b_{21}V_1 - b_{22} \left[ \frac{b_{11}}{b_{12}}V_1 - \frac{1}{b_{12}}V_2 \right]$$

$$I_2 = \frac{b_{21}b_{12} - b_{11}b_{22}}{b_{12}}V_1 + \frac{b_{22}}{b_{12}}V_2$$

$$\therefore y_{21} = -\frac{\Delta b}{b_{12}}; \quad y_{22} = \frac{b_{22}}{b_{12}}$$

$$\text{P 18.18 } I_1 = g_{11}V_1 + g_{12}I_2; \quad V_2 = g_{21}V_1 + g_{22}I_2$$

$$V_1 = z_{11}I_1 + z_{12}I_2; \quad V_2 = z_{21}I_1 + z_{22}I_2$$

$$I_1 = \frac{V_1}{z_{11}} - \frac{z_{12}}{z_{11}}I_2$$

$$\therefore g_{11} = \frac{1}{z_{11}}; \quad g_{12} = \frac{-z_{12}}{z_{11}}$$

$$V_2 = z_{21} \left( \frac{V_1}{z_{11}} - \frac{z_{12}}{z_{11}}I_2 \right) + z_{22}I_2 = \frac{z_{21}}{z_{11}}V_1 + \left( \frac{z_{11}z_{22} - z_{12}z_{21}}{z_{11}} \right) I_2$$

$$\therefore g_{21} = \frac{z_{21}}{z_{11}}; \quad g_{22} = \frac{\Delta z}{z_{11}}$$

$$\text{P 18.19 } g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}; \quad g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

$$V_1 = 200I_1 + 800I_1 = 1000I_1; \quad \therefore g_{11} = 10^{-3} \text{ S}$$

$$V_- = \frac{1000}{1500}V_2 = V_+; \quad V_+ = \frac{800}{1000}V_1$$


$$\therefore \frac{1000}{1500}V_2 = \frac{800}{1000}V_1; \quad \therefore g_{21} = 1.2$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}; \quad g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

$$I_1 = 0; \quad \therefore g_{12} = 0$$

$$\text{Also, } V_o = 0; \quad \therefore g_{22} = \frac{V_2}{I_2} = 40 \Omega$$

P 18.20  $V_2 = 0$ :

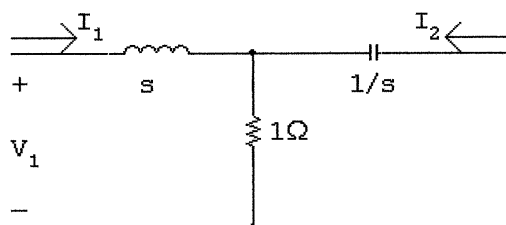


$$\frac{V_1}{I_1} = s + [1 \parallel (1/s)] = \frac{s^2 + s + 1}{s + 1}$$

$$\therefore y_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{s + 1}{s^2 + s + 1}$$

$$I_2 = \frac{-1}{1 + (1/s)} I_1 = \frac{-s}{s + 1} I_1 = \frac{-s}{s + 1} \left( \frac{s + 1}{s^2 + s + 1} \right) V_1$$

$$\therefore y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-s}{s^2 + s + 1}$$

$V_1 = 0$ :

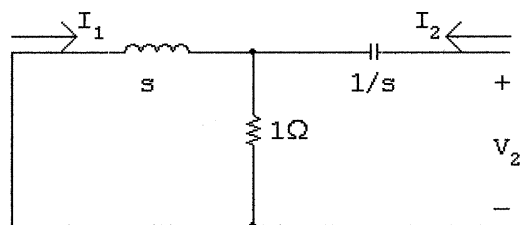

$$\frac{V_2}{I_2} = (1/s) + 1 \parallel s = \frac{1}{s} + \frac{s}{s + 1} = \frac{s^2 + s + 1}{s(s + 1)}$$

$$\therefore y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{s(s + 1)}{s^2 + s + 1}$$



$$I_1 = \frac{-1}{s+1} I_2 = \frac{-1}{s+1} \left[ \frac{s(s+1)}{s^2+s+1} \right] V_2$$


$$\therefore y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{-s}{s^2+s+1}$$

P 18.21 First, find the  $y$  parameters:

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

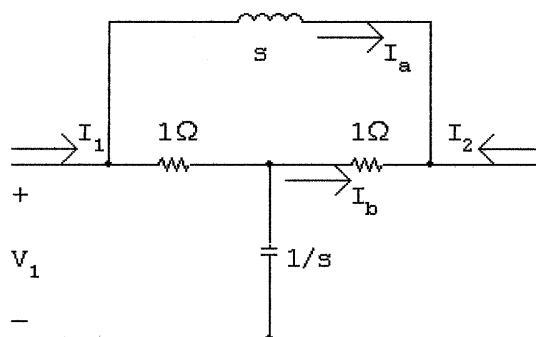Since the two-port is symmetric and reciprocal we only need to calculate two parameters since  $y_{11} = y_{22}$  and  $y_{12} = y_{21}$ .



$$I_1 = \frac{V_1}{s} + \frac{V_1}{1 + \left(\frac{1}{s+1}\right)} = \left[ \frac{1}{s} + \frac{1}{1 + \frac{1}{s+1}} \right] V_1$$

$$\frac{I_1}{V_1} = \frac{s^2 + 2s + 2}{s(s+2)}$$

$$y_{11} = y_{22} = \frac{s^2 + 2s + 2}{s(s+2)}$$

$$I_a = \frac{V_1}{s}$$

$$I_b = \frac{V_1}{1 + \frac{1}{s+1}} \cdot \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{V_1}{s+2}$$

$$I_2 = -(I_a + I_b) = -\left[ \frac{V_1}{s} + \frac{V_1}{s+2} \right]$$

$$\frac{I_2}{V_1} = -\frac{2s+2}{s(s+2)}$$

$$y_{12} = y_{21} = -\frac{2(s+1)}{s(s+2)}$$

Now, transform to the  $a$  parameters:

$$a_{11} = \frac{-y_{22}}{y_{21}} = \frac{s^2 + 2s + 2}{2(s+1)}$$

$$a_{12} = \frac{-1}{y_{21}} = \frac{s(s+2)}{2(s+1)}$$

$$a_{21} = \frac{-\Delta y}{y_{21}} = \frac{-1}{y_{21}} = \frac{s(s+2)}{2(s+1)}$$

$$a_{22} = \frac{-y_{11}}{y_{21}} = \frac{s^2 + 2s + 2}{2(s+1)}$$


P 18.22 First we note that

$$z_{11} = \frac{(Z_b + Z_c)(Z_a + Z_b)}{Z_a + 2Z_b + Z_c} \quad \text{and} \quad z_{22} = \frac{(Z_a + Z_b)(Z_b + Z_c)}{Z_a + 2Z_b + Z_c}$$

Therefore  $z_{11} = z_{22}$ .

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0};$$

Use the circuit below:

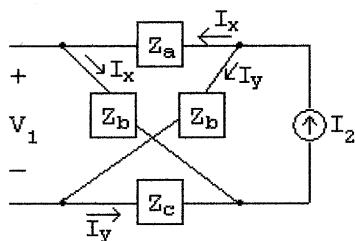


$$V_1 = Z_b I_x - Z_c I_y = Z_b I_x - Z_c (I_2 - I_x) = (Z_b + Z_c) I_x - Z_c I_2$$

$$I_x = \frac{Z_b + Z_c}{Z_a + 2Z_b + Z_c} I_2 \quad \text{so} \quad V_1 = \frac{(Z_b + Z_c)^2}{Z_a + 2Z_b + Z_c} I_2 - Z_c I_2$$

$$\therefore z_{12} = \frac{V_1}{I_2} = \frac{(Z_b + Z_c)^2}{Z_a + 2Z_b + Z_c} - Z_c = \frac{Z_b^2 - Z_a Z_c}{Z_a + 2Z_b + Z_c}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}; \quad \text{Use the circuit below:}$$

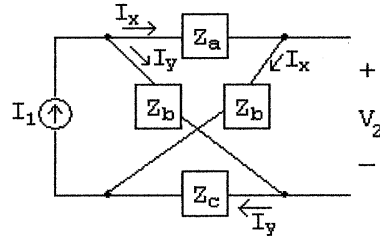


$$V_2 = Z_b I_x - Z_c I_y = Z_b I_x - Z_c (I_1 - I_x) = (Z_b + Z_c) I_x - Z_c I_1$$

$$I_x = \frac{Z_b + Z_c}{Z_a + 2Z_b + Z_c} I_1 \quad \text{so} \quad V_2 = \frac{(Z_b + Z_c)^2}{Z_a + 2Z_b + Z_c} I_1 - Z_c I_1$$

$$\therefore z_{21} = \frac{V_2}{I_1} = \frac{(Z_b + Z_c)^2}{Z_a + 2Z_b + Z_c} - Z_c = \frac{Z_b^2 - Z_a Z_c}{Z_a + 2Z_b + Z_c} = z_{12}$$

Thus the network is symmetrical and reciprocal.

P 18.23 [a]  $h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$

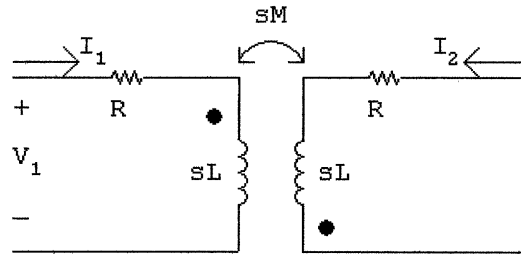

$$V_1 = (R + sL)I_1 - sMI_2$$

$$0 = -sMI_1 + (R + sL)I_2$$


$$\Delta = \begin{vmatrix} (R + sL) & -sM \\ -sM & (R + sL) \end{vmatrix} = (R + sL)^2 - s^2 M^2$$

$$N_1 = \begin{vmatrix} V_1 & -sM \\ 0 & (R + sL) \end{vmatrix} = (R + sL)V_1$$

$$I_1 = \frac{N_1}{\Delta} = \frac{(R + sL)V_1}{(R + sL)^2 - s^2 M^2}; \quad h_{11} = \frac{V_1}{I_1} = \frac{(R + sL)^2 - s^2 M^2}{R + sL}$$

$$0 = -sMI_1 + (R + sL)I_2; \quad \therefore h_{21} = \frac{I_2}{I_1} = \frac{sM}{R + sL}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}; \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

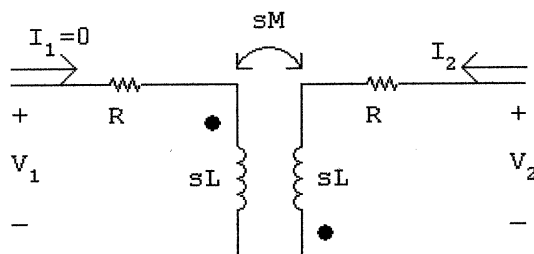

$$V_1 = -sMI_2; \quad I_2 = \frac{V_2}{R + sL}$$

$$V_1 = \frac{-sMV_2}{R + sL}; \quad h_{12} = \frac{V_1}{V_2} = \frac{-sM}{R + sL}$$

$$h_{22} = \frac{I_2}{V_2} = \frac{1}{R + sL}$$


[b]  $h_{12} = -h_{21}$  (reciprocal)

$$h_{11}h_{22} - h_{12}h_{21} = 1 \quad (\text{symmetrical, reciprocal})$$

$$h_{12} = \frac{-sM}{R + sL}; \quad h_{21} = \frac{sM}{R + sL} \quad (\text{checks})$$

$$\begin{aligned} h_{11}h_{22} - h_{12}h_{21} &= \frac{(R + sL)^2 - s^2M^2}{R + sL} \cdot \frac{1}{R + sL} - \frac{(sM)(-sM)}{(R + sL)^2} \\ &= \frac{(R + sL)^2 - s^2M^2 + s^2M^2}{(R + sL)^2} = 1 \quad (\text{checks}) \end{aligned}$$

P 18.24

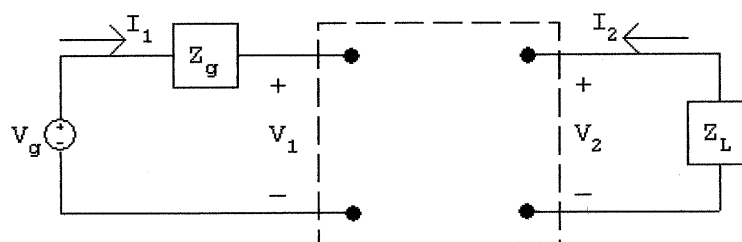

$$V_2 = b_{11}V_1 - b_{12}I_1; \quad V_1 = V_g - I_1Z_g$$

$$I_2 = b_{21}V_1 - b_{22}I_1; \quad V_2 = -Z_L I_2$$

$$I_2 = -\frac{V_2}{Z_L} = \frac{-b_{11}V_1 + b_{12}I_1}{Z_L}$$

$$\frac{-b_{11}V_1 + b_{12}I_1}{Z_L} = b_{21}V_1 - b_{22}I_1$$

$$\therefore V_1 \left( \frac{b_{11}}{Z_L} + b_{21} \right) = \left( b_{22} + \frac{b_{12}}{Z_L} \right) I_1$$

$$\frac{V_1}{I_1} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}} = Z_{\text{in}}$$

P 18.25  $I_1 = g_{11}V_1 + g_{12}I_2; \quad V_1 = V_g - Z_g I_1$

$$V_2 = g_{21}V_1 + g_{22}I_2; \quad V_2 = -Z_L I_2$$

$$-Z_L I_2 = g_{21}V_1 + g_{22}I_2; \quad V_1 = \frac{I_1 - g_{12}I_2}{g_{11}}$$

$$\therefore -Z_L I_2 = \frac{g_{21}}{g_{11}}(I_1 - g_{12}I_2) + g_{22}I_2$$

$$\therefore -Z_L I_2 + \frac{g_{12}g_{21}}{g_{11}}I_2 - g_{22}I_2 = \frac{g_{21}}{g_{11}}I_1$$

$$\therefore (Z_L g_{11} + \Delta g)I_2 = -g_{21}I_1; \quad \therefore \frac{I_2}{I_1} = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$$

P 18.26  $I_1 = y_{11}V_1 + y_{12}V_2; \quad V_1 = V_g - Z_g I_1$

$$I_2 = y_{21}V_1 + y_{22}V_2; \quad V_2 = -Z_L I_2$$

$$\frac{-V_2}{Z_L} = y_{21}V_1 + y_{22}V_2$$

$$\therefore -y_{21}V_1 = \left( \frac{1}{Z_L} + y_{22} \right) V_2; \quad -y_{21}Z_L V_1 = (1 + y_{22}Z_L)V_2$$

$$\therefore \frac{V_2}{V_1} = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$$

$$\text{P 18.27 } V_1 = h_{11}I_1 + h_{12}V_2; \quad V_1 = V_g - Z_g I_1$$

$$I_2 = h_{21}I_1 + h_{22}V_2; \quad V_2 = -Z_L I_2$$

$$\therefore V_g - Z_g I_1 = h_{11}I_1 + h_{12}V_2; \quad V_g = (h_{11} + Z_g)I_1 + h_{12}V_2$$

$$\therefore I_1 = \frac{V_g - h_{12}V_2}{h_{11} + Z_g}$$

$$\therefore -\frac{V_2}{Z_L} = h_{21} \left[ \frac{V_g - h_{12}V_2}{h_{11} + Z_g} \right] + h_{22}V_2$$

$$\frac{-V_2(h_{11} + Z_g)}{Z_L} = h_{21}V_g - h_{12}h_{21}V_2 + h_{22}(h_{11} + Z_g)V_2$$

$$-V_2(h_{11} + Z_g) = h_{21}Z_L V_g - h_{12}h_{21}Z_L V_2 + h_{22}Z_L(h_{11} + Z_g)V_2$$

$$-h_{21}Z_L V_g = (h_{11} + Z_g)[V_2 + h_{22}Z_L V_2] - h_{12}h_{21}Z_L V_2$$

$$\therefore \frac{V_2}{V_g} = \frac{-h_{21}Z_L}{(h_{11} + Z_g)(1 + h_{22}Z_L) - h_{12}h_{21}Z_L}$$

$$\text{P 18.28 } V_1 = z_{11}I_1 + z_{12}I_2; \quad V_1 = V_g - Z_g I_1$$

$$V_2 = z_{21}I_1 + z_{22}I_2; \quad V_2 = -Z_L I_2$$

$$V_{\text{Th}} = V_2 \Big|_{I_2=0}; \quad V_2 = z_{21}I_1; \quad I_1 = \frac{V_1}{z_{11}} = \frac{V_g - I_1 Z_g}{z_{11}}$$

$$\therefore I_1 = \frac{V_g}{z_{11} + Z_g}; \quad \therefore V_2 = \frac{z_{21}V_g}{z_{11} + Z_g} = V_t$$


$$Z_{\text{Th}} = \frac{V_2}{I_2} \Big|_{V_g=0}; \quad V_2 = z_{21}I_1 + z_{22}I_2$$

$$-I_1 Z_g = z_{11}I_1 + z_{12}I_2; \quad I_1 = \frac{-z_{12}I_2}{z_{11} + Z_g}$$

$$\therefore V_2 = z_{21} \left[ \frac{-z_{12}I_2}{z_{11} + Z_g} \right] + z_{22}I_2$$

$$\therefore \frac{V_2}{I_2} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g} = Z_{\text{Th}}$$

P 18.29 [a]  $a_{11} = \frac{V_1}{V_2} \Big|_{I_2=0}; \quad a_{21} = \frac{I_1}{V_2} \Big|_{I_2=0}$

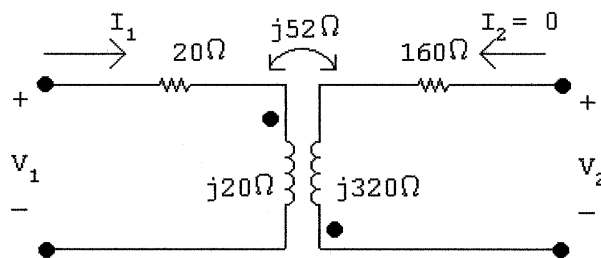


$$V_2 = -j52I_1 = -j52 \frac{V_1}{20 + j20}$$

$$a_{11} = \frac{V_1}{V_2} = \frac{20 + j20}{-j52} = \frac{5}{13}(-1 + j)$$

$$a_{21} = \frac{I_1}{V_2} = \frac{1}{-j52} = \frac{j}{52} \text{ S}$$

$a_{12} = -\frac{V_1}{I_2} \Big|_{V_2=0}; \quad a_{22} = -\frac{I_1}{I_2} \Big|_{V_2=0}$

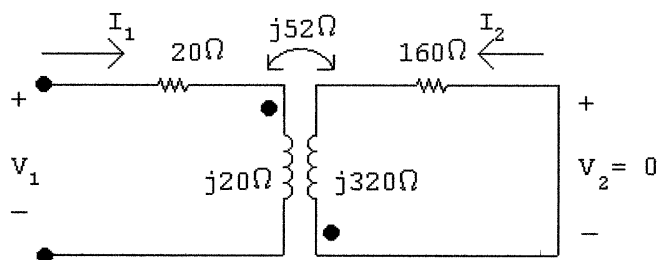

$$V_1 = (20 + j20)I_1 - j52I_2$$

$$0 = -j52I_1 + (160 + j320)I_2$$

$$\Delta = \begin{vmatrix} 20 + j20 & -j52 \\ -j52 & 160 + j320 \end{vmatrix} = -496 + j9600$$

$$N_2 = \begin{vmatrix} 20 + j20 & V_1 \\ -j52 & 0 \end{vmatrix} = j52V_1$$

$$I_2 = \frac{j52V_1}{-496 + j9600} \quad \text{so} \quad \frac{V_1}{I_2} = \frac{-496 + j9600}{j52} = \frac{1}{52}(9600 + j496)$$

$$\therefore a_{12} = -\frac{V_1}{I_2} = \frac{1}{13}(-2400 - j124)$$


$$j52I_1 = (160 + j320)I_2; \quad \therefore a_{22} = -\frac{I_1}{I_2} = \frac{-320 + j160}{52}$$

$$[\text{b}] \quad V_{\text{Th}} = \frac{V_g}{a_{11} + a_{21}Z_g} = \frac{100/0^\circ}{(5/13)(-1 + j) + (j/52)(10)}$$

$$= -80 - j120 = 144.22/-123.69^\circ \text{ V}$$

$$Z_{\text{Th}} = \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g} = \frac{\frac{1}{13}(-2400 - j124) + \frac{-320 + j160}{52}(10)}{(5/13)(-1 + j) + (j/52)(10)}$$
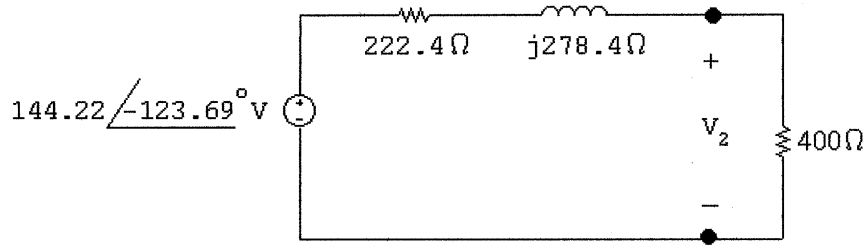
$$= 222.4 + j278.4 = 356.33/51.38^\circ \Omega$$



$$[\text{c}] \quad V_2 = \frac{144.22/-123.69^\circ}{222.4 + j278.4}(400) = 84.607/-147.789^\circ$$

$$v_2(t) = 84.607 \cos(2000t - 147.789^\circ) \text{ V}$$

$$\begin{aligned} \text{P 18.30} \quad I_2 &= \frac{y_{21} \mathbf{V}_g}{1 + y_{22}Z_L + y_{11}Z_g + \Delta y Z_g Z_L} \\ &= \frac{-0.25(1)}{1 + (-0.04)(100) + (0.025)(10) + (-0.00125)(10)(100)} \\ &= 0.0625 \text{ A(rms)} \end{aligned}$$

$$P_o = (I_2)^2 Z_L = (0.0625)^2(100) = 390.625 \text{ mW}$$

$$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta y Z_L} = \frac{-0.25}{0.025 + (-0.00125)(100)} = 2.5$$

$$\therefore I_1 = \frac{I_2}{2.5} = \frac{0.0625}{2.5} = 25 \text{ mA(rms)}$$

$$P_g = (1)(0.025) = 25 \text{ mW}$$

$$\frac{P_o}{P_g} = \frac{390.625}{25} = 15.625$$



P 18.31 [a]  $Z_{Th} = g_{22} - \frac{g_{12}g_{21}Z_g}{1 + g_{11}Z_g}$

$$g_{12}g_{21} = \left(-\frac{1}{2} + j\frac{1}{2}\right) \left(\frac{1}{2} - j\frac{1}{2}\right) = j\frac{1}{2}$$

$$1 + g_{11}Z_g = 1 + 1 - j1 = 2 - j1$$

$$\therefore Z_{Th} = 1.5 + j2.5 - \frac{j3}{2 - j1} = 2.1 + j1.3 \Omega$$

$$\therefore Z_L = 2.1 - j1.3 \Omega$$

$$\frac{V_2}{V_g} = \frac{g_{21}Z_L}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$

$$g_{21}Z_L = \left(\frac{1}{2} - j\frac{1}{2}\right) (2.1 - j1.3) = 0.4 - j1.7$$

$$1 + g_{11}Z_g = 1 + 1 - j1 = 2 - j1$$

$$g_{22} + Z_L = 1.5 + j2.5 + 2.1 - j1.3 = 3.6 + j1.2$$

$$g_{12}g_{21}Z_g = j3$$

$$\frac{V_2}{V_g} = \frac{0.4 - j1.7}{(2 - j1)(3.6 + j1.2) - j3} = \frac{0.4 - j1.7}{8.4 - j4.2}$$

$$V_2 = \frac{0.4 - j1.7}{8.4 - j4.2} (42 \angle 0^\circ) = 5 - j6 \text{ V(rms)} = 7.81 \angle -50.19^\circ \text{ V(rms)}$$

The rms value of  $V_2$  is 7.81 V.

[b]  $I_2 = \frac{-V_2}{Z_L} = \frac{-5 + j6}{2.1 - j1.3} = -3 + j1 \text{ A(rms)}$

$$P = |I_2|^2 (2.1) = 21 \text{ W}$$

[c]  $\frac{I_2}{I_1} = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$

$$\begin{aligned} \Delta g &= \left(\frac{1}{6} - j\frac{1}{6}\right) \left(\frac{3}{2} + j\frac{5}{2}\right) - \left(\frac{1}{2} - j\frac{1}{2}\right) \left(-\frac{1}{2} + j\frac{1}{2}\right) \\ &= \frac{3}{12} + j\frac{5}{12} - j\frac{3}{12} + \frac{5}{12} - j\frac{1}{2} = \frac{2}{3} - j\frac{1}{3} \end{aligned}$$

$$g_{11}Z_L = \left(\frac{1}{6} - j\frac{1}{6}\right) (2.1 - j1.3) = \frac{0.8}{6} - j\frac{3.4}{6}$$

$$\therefore g_{11}Z_L + \Delta g = \frac{0.8}{6} - j\frac{3.4}{6} + \frac{4}{6} - j\frac{2}{6} = 0.8 - j0.9$$

P 18.33 [a]  $Z_{Th} = \frac{1 + y_{11}Z_g}{y_{22} + \Delta y Z_g}$

From the solution to Problem 18.32

$$1 + y_{11}Z_g = 1 + (2 \times 10^{-3})(2500) = 6$$

$$y_{22} + \Delta y Z_g = -50 \times 10^{-6} + 10^{-7}(2500) = 200 \times 10^{-6}$$

$$Z_{Th} = \frac{6}{200} \times 10^6 = 30,000 \Omega$$

$$Z_L = Z_{Th}^* = 30,000 \Omega$$

[b]  $y_{21}Z_L = (100 \times 10^{-3})(30,000) = 3000$

$$y_{12}y_{21}Z_gZ_L = (-2 \times 10^{-6})(100 \times 10^{-3})(2500)(30,000) = -15$$

$$1 + y_{11}Z_g = 6$$

$$1 + y_{22}Z_L = 1 + (-50 \times 10^{-6})(30 \times 10^3) = -0.5$$

$$\frac{V_2}{V_g} = \frac{3000}{-15 - 6(-0.5)} = \frac{3000}{-12} = -250$$

$$V_2 = -250(80 \times 10^{-3}) = -20 = 20/\underline{180^\circ} \text{ V(rms)}$$

$$P = \frac{|V_2|^2}{30,000} = \frac{400}{30} \times 10^{-3} = 13.33 \text{ mW}$$


[c]  $I_2 = \frac{-V_2}{30,000} = \frac{20/\underline{0^\circ}}{30,000} = \frac{2}{3} \text{ mA}$

$$\frac{I_2}{I_1} = \frac{100 \times 10^{-3}}{2 \times 10^{-3} + 10^{-7}(30,000)} = \frac{100 \times 10^{-3}}{5 \times 10^{-3}} = 20$$

$$I_1 = \frac{I_2}{20} = \frac{2 \times 10^{-3}}{3(20)} = \frac{1}{30} \text{ mA(rms)}$$

$$P_g(\text{developed}) = (80 \times 10^{-3}) \left( \frac{1}{30} \times 10^{-3} \right) = \frac{8}{3} \mu\text{W}$$

P 18.34 [a]  $h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$

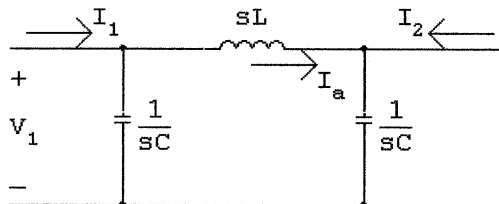

$$h_{11} = \frac{(1/sC)(sL)}{(1/sC) + sL} = \frac{(1/C)s}{s^2 + (1/LC)}$$

$$I_2 = -I_a; \quad I_a = \frac{I_1(1/sC)}{sL + (1/sC)}$$

$$I_2 = \frac{-I_1}{s^2LC + 1}$$

$$h_{21} = \frac{I_2}{I_1} = \frac{-(1/LC)}{s^2 + (1/LC)}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}; \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

$$V_1 = \frac{V_2(1/sC)}{sL + (1/sC)} = \frac{V_2}{s^2LC + 1}$$

$$\frac{V_1}{V_2} = h_{12} = \frac{1/LC}{s^2 + (1/LC)}$$

$$\frac{V_2}{I_2} = \frac{(1/sC)[sL + (1/sC)]}{sL + (2/sC)} = \frac{s^2 + (1/LC)}{sC[s^2 + (2/LC)]}$$

$$\frac{I_2}{V_2} = h_{22} = \frac{Cs[s^2 + (2/LC)]}{s^2 + (1/LC)}$$

$$[b] \quad \frac{1}{LC} = \frac{10^9}{(0.1)(400)} = 25 \times 10^6$$

$$h_{11} = \frac{10^7 s}{s^2 + 25 \times 10^6}$$

$$h_{12} = \frac{25 \times 10^6}{s^2 + 25 \times 10^6}$$

$$h_{21} = \frac{-25 \times 10^6}{s^2 + 25 \times 10^6}$$

$$h_{22} = \frac{10^{-7}s(s^2 + 50 \times 10^6)}{(s^2 + 25 \times 10^6)}$$

$$\frac{V_2}{V_1} = \frac{-h_{21}Z_L}{h_{11} + \Delta h Z_L} = \frac{-h_{21}Z_L}{h_{11} + Z_L} = \frac{\left(\frac{25 \times 10^6}{s^2 + 25 \times 10^6}\right) 800}{\frac{10^7 s}{(s^2 + 25 \times 10^6)} + 800}$$

$$\frac{V_2}{V_1} = \frac{25 \times 10^6}{s^2 + 12,500s + 25 \times 10^6} = \frac{25 \times 10^6}{(s + 2500)(s + 10,000)}$$

$$V_1 = \frac{45}{s}$$

$$V_2 = \frac{1125 \times 10^6}{s(s + 2500)(s + 10,000)} = \frac{45}{s} - \frac{60}{s + 2500} + \frac{15}{s + 10,000}$$

$$v_2 = [45 - 60e^{-2500t} + 15e^{-10,000t}]u(t) \quad \text{V}$$

P 18.35 [a]  $V_1 = z_{11}I_1 + z_{12}I_2$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = s + \frac{1}{s} = \frac{s^2 + 1}{s}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{1}{s}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{1}{s}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = s + \frac{1}{s} = \frac{s^2 + 1}{s}$$

$$\begin{aligned} \text{[b]} \quad \frac{V_2}{V_g} &= \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}} \\ &= \frac{z_{21}}{(z_{11} + 1)(z_{22} + 1) - z_{12}z_{21}} \\ &= \frac{1/s}{\left(\frac{s^2+1}{s} + 1\right)\left(\frac{s^2+1}{s} + 1\right) - \frac{1}{s^2}} \\ &= \frac{s}{(s^2 + s + 1)^2 - 1} \\ &= \frac{s}{s^4 + 2s^3 + 3s^2 + 2s + 1 - 1} \\ &= \frac{1}{s^3 + 2s^2 + 3s + 2} \\ &= \frac{1}{(s+1)(s^2 + s + 2)} \end{aligned}$$

$$\therefore V_2 = \frac{50}{s(s+1)(s^2 + s + 2)}$$

$$s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{7}}{2}$$

$$V_2 = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s + \frac{1}{2} - j\frac{\sqrt{7}}{2}} + \frac{K_3^*}{s + \frac{1}{2} + j\frac{\sqrt{7}}{2}}$$

$$K_1 = 25; \quad K_2 = -25; \quad K_3 = 9.45 \angle 90^\circ$$

$$\therefore v_2(t) = [25 - 25e^{-t} + 18.90e^{-0.5t} \cos(1.32t + 90^\circ)]u(t) \text{ V}$$

CHECK

$$v_2(0) = 25 - 25 + 18.90 \cos 90^\circ = 0$$

$$v_2(\infty) = 25 + 0 + 0 = 25 \text{ V}$$

$$\text{P 18.36 } z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{100}{1.125} = \frac{800}{9} \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{104}{1.125} = \frac{832}{9} \Omega$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{20}{0.25} = 80 \Omega$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{24}{0.25} = 96 \Omega$$

$$Z_{\text{Th}} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g} = 96 - \frac{(80)(832/9)}{(800/9) + 0} = 12.8 \Omega$$

$$\therefore Z_L = 12.8 \Omega$$

$$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$$

$$\Delta z = \left( \frac{800}{9} \right) 96 - 80 \left( \frac{832}{9} \right) = \frac{10,240}{9}$$

$$\frac{V_2}{V_1} = \frac{(832/9)(12.8)}{(800/9)(12.8) + (10,240/9)} = \frac{10,649.60}{20,480} = 0.52$$

$$V_2 = (0.52)(160) = 83.20 \text{ V}$$

$$P = \frac{(83.2)^2}{12.8} = 540.80 \text{ W}$$

$$\text{P 18.37 } h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = 25 \Omega; \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = -0.5$$

From the second set of measurements we have

$$41 = 25(1) + h_{12}(20); \quad \therefore h_{12} = \frac{41 - 25}{20} = 0.80$$

$$0 = -0.5(1) + h_{22}(20); \quad \therefore h_{22} = \frac{0.5}{20} = 0.025 \text{ V}$$

$$R_{\text{Th}} = \frac{23 + 25}{23(0.025) + \Delta h}; \quad \Delta h = 25(0.025) - (-0.5)(0.8) = 1.025$$

$$\therefore R_{\text{Th}} = \frac{48}{1.6} = 30 \Omega; \quad \therefore R_o = 30 \Omega$$

$$\frac{V_2}{V_g} = \frac{-(-0.5)(30)}{(48)(1.75) + (0.4)(30)} = \frac{15}{96}$$

$$V_2 = 15 \text{ V}; \quad P = \frac{(15)^2}{30} = 7.5 \text{ W}$$

$$\text{P 18.38 } a'_{11} = -\frac{\Delta h}{h_{21}} = \frac{-0.01}{-0.1} = 0.1$$

$$a'_{12} = -\frac{h_{11}}{h_{21}} = \frac{-150}{-0.1} = 1500$$

$$a'_{21} = -\frac{h_{22}}{h_{21}} = \frac{-10^{-4}}{-0.1} = 10^{-3}$$

$$a'_{22} = -\frac{1}{h_{21}} = \frac{-1}{-0.1} = 10$$

$$a''_{11} = \frac{1}{g_{21}} = \frac{1}{20} = 0.05$$

$$a''_{12} = \frac{g_{22}}{g_{21}} = \frac{24 \times 10^3}{20} = 1200$$

$$a''_{21} = \frac{g_{11}}{g_{21}} = \frac{0.01}{20} = 5 \times 10^{-4}$$

$$a''_{22} = \frac{\Delta g}{g_{21}} = \frac{320}{20} = 16$$

$$a_{11} = a'_{11}a''_{11} + a'_{12}a''_{21} = (0.1)(0.05) + (1500)(5 \times 10^{-4}) = 0.755$$

$$a_{12} = a'_{11}a''_{12} + a'_{12}a''_{22} = (0.1)(1200) + (1500)(16) = 24,120$$

$$a_{21} = a'_{21}a''_{11} + a'_{22}a''_{21} = (10^{-3})(0.05) + (10)(5 \times 10^{-4}) = 5.05 \times 10^{-3}$$

$$a_{22} = a'_{21}a''_{12} + a'_{22}a''_{22} = (10^{-3})(1200) + (10)(16) = 161.2$$

$$\begin{aligned} V_2 &= \frac{Z_L V_g}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g} \\ &= \frac{(1000)(109.5)}{[0.755 + (5.05 \times 10^{-3})(20)](1000) + 24,120 + (161.2)(20)} = 3.88 \text{ V} \end{aligned}$$

P 18.39 The  $a$  parameters of the first two port are

$$a'_{11} = \frac{z_{11}}{z_{21}} = \frac{200}{-1.6 \times 10^6} = -125 \times 10^{-6}$$

$$a'_{12} = \frac{\Delta z}{z_{21}} = \frac{40 \times 10^6}{-1.6 \times 10^6} = -25 \Omega$$

$$a'_{21} = \frac{1}{z_{21}} = \frac{1}{-1.6 \times 10^6} = -625 \times 10^{-9} \text{ S}$$

$$a'_{22} = \frac{z_{22}}{z_{21}} = \frac{40,000}{-1.6 \times 10^6} = -25 \times 10^{-3}$$

The  $a$  parameters of the second two port are

$$a''_{11} = \frac{5}{4}; \quad a''_{12} = \frac{3R}{4}; \quad a''_{21} = \frac{3}{4R}; \quad a''_{22} = \frac{5}{4}$$

$$\text{or } a''_{11} = 1.25; \quad a''_{12} = 6 \text{ k}\Omega; \quad a''_{21} = 93.75 \mu\text{S}; \quad a''_{22} = 1.25$$

The  $a$  parameters of the cascade connection are

$$a_{11} = -125 \times 10^{-6}(1.25) + (-25)(93.75 \times 10^{-6}) = -2.5 \times 10^{-3}$$

$$a_{12} = -125 \times 10^{-6}(6000) + (-25)(1.25) = -32 \Omega$$

$$a_{21} = -625 \times 10^{-9}(1.25) + (-25 \times 10^{-3})(93.75 \times 10^{-6}) = -3.125 \times 10^{-6} \text{ S}$$

$$a_{22} = -625 \times 10^{-9}(6000) + (-25 \times 10^{-3})(1.25) = -35 \times 10^{-3}$$

$$\frac{V_o}{V_g} = \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g}$$

$$a_{21}Z_g = (-3.125 \times 10^{-6})(500) = -1.5625 \times 10^{-3}$$

$$a_{11} + a_{21}Z_g = -2.5 \times 10^{-3} - 1.5625 \times 10^{-3} = -4.0625 \times 10^{-3}$$

$$(a_{11} + a_{21}Z_g)Z_L = (-4.0625 \times 10^{-3})(8000) = -32.5$$

$$a_{22}Z_g = (-35 \times 10^{-3})(500) = -17.5$$


$$\frac{V_o}{V_g} = \frac{8000}{-32.5 - 32.25 - 17.5} = -97.26$$

$$v_o = V_o = -97.26V_g = -1.46 \text{ V}$$

P 18.40 [a] From reciprocity and symmetry

$$a'_{11} = a'_{22}, \quad \Delta a' = 1; \quad \therefore 16 - 5a'_{21} = 1, \quad a'_{21} = 3 \text{ S}$$

For network B

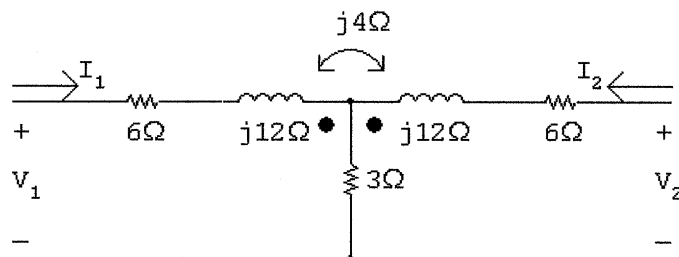

$$a''_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$V_1 = (6 + j12 + 3)I_1 = (9 + j12)I_1$$

$$V_2 = 3I_1 + j4I_1 = (3 + j4)I_1$$

$$a''_{11} = \frac{9 + j12}{3 + j4} = 3$$

$$a''_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{3 + j4} = 0.12 - j0.16 \text{ S}$$

$$a''_{22} = a''_{11} = 3$$

$$\Delta a'' = 1 = (3)(3) - (0.12 - j0.16)a''_{12}$$

$$\therefore a''_{12} = \frac{8}{0.12 - j0.16} = 24 + j32 \Omega$$



$$[b] \quad a_{11} = a'_{11}a''_{11} + a'_{12}a''_{21} = 12 + 5(0.12 - j0.16) = 12.6 - j0.8$$


$$a_{12} = a'_{11}a''_{12} + a'_{12}a''_{22} = (4)(24 + j32) + (5)(3) = 111 + j128 \Omega$$

$$a_{21} = a'_{21}a''_{11} + a'_{22}a''_{21} = (3)(3) + (4)(0.12 - j0.16) = 9.48 - j0.64 S$$

$$a_{22} = a'_{21}a''_{12} + a'_{22}a''_{22} = (3)(24 + j32) + (4)(3) = 84 + j96$$

$$\left. \frac{V_2}{V_1} \right|_{I_2=0} = \frac{1}{a_{11}} = \frac{1}{12.6 - j0.8} = 0.079 + j0.005$$

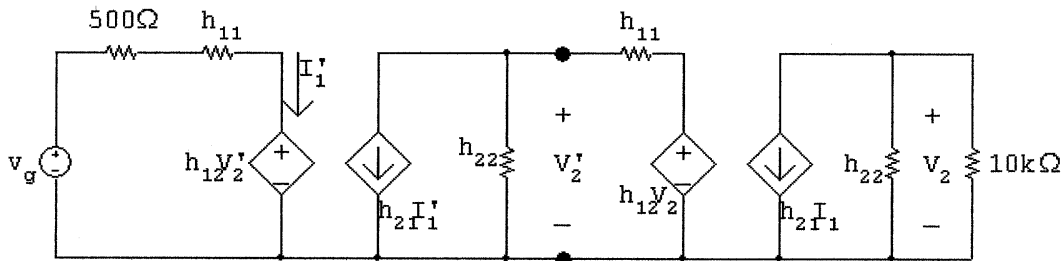- P 18.41 [a] At the input port:  $V_1 = h_{11}I_1 + h_{12}V_2$ ;  
At the output port:  $I_2 = h_{21}I_1 + h_{22}V_2$



$$[b] \quad \frac{V_2}{10^4} + (100 \times 10^{-6}V_2) + 100I_1 = 0$$

$$\text{therefore } I_1 = -2 \times 10^{-6}V_2$$

$$V'_2 = 1000I_1 + 15 \times 10^{-4}V_2 = -5 \times 10^{-4}V_2$$

$$100I'_1 + 10^{-4}V'_2 + (-2 \times 10^{-6})V_2 = 0$$

$$\text{therefore } I'_1 = 205 \times 10^{-10}V_2$$

$$V_g = 1500I'_1 + 15 \times 10^{-4}V'_2 = 3000 \times 10^{-8}V_2$$

$$\frac{V_2}{V_g} = \frac{10^5}{3} = 33,333$$

- P 18.42 [a]  $V_1 = I_2(z_{12} - z_{21}) + I_1(z_{11} - z_{21}) + z_{21}(I_1 + I_2)$   
 $= I_2z_{12} - I_2z_{21} + I_1z_{11} - I_1z_{21} + z_{21}I_1 + z_{21}I_2 = z_{11}I_1 + z_{12}I_2$   
 $V_2 = I_2(z_{22} - z_{21}) + z_{21}(I_1 + I_2) = z_{21}I_1 + z_{22}I_2$


- [b] Short circuit  $V_g$  and apply a test current source to port 2 as shown. Note that  $I_T = I_2$ . We have

$$\frac{V}{z_{21}} - I_T + \frac{V + I_T(z_{12} - z_{21})}{Z_g + z_{11} - z_{21}} = 0$$

Therefore

$$V = \left[ \frac{z_{21}(Z_g + z_{11} - z_{12})}{Z_g + z_{11}} \right] I_T \quad \text{and} \quad V_T = V + I_T(z_{22} - z_{21})$$
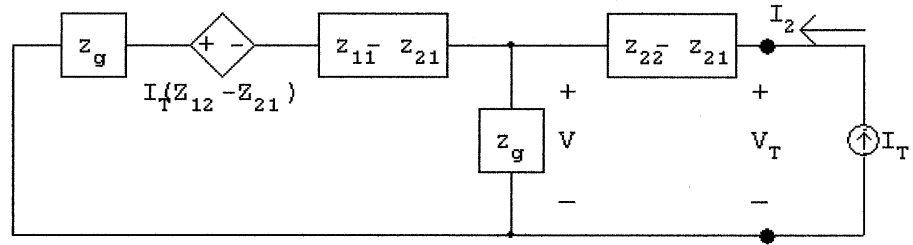
$$\text{Thus} \quad \frac{V_T}{I_T} = Z_{Th} = z_{22} - \left( \frac{z_{12}z_{21}}{Z_g + z_{11}} \right) \Omega$$



For  $V_{Th}$  note that  $V_{oc} = \frac{z_{21}}{z_g + z_{11}} V_g$  since  $I_2 = 0$ .

P 18.43 [a]  $V_1 = (z_{11} - z_{12})I_1 + z_{12}(I_1 + I_2) = z_{11}I_1 + z_{12}I_2$

$$V_2 = (z_{21} - z_{12})I_1 + (z_{22} - z_{12})I_2 + z_{12}(I_2 + I_1) = z_{21}I_1 + z_{22}I_2$$

[b] With port 2 terminated in an impedance  $Z_L$ , the two mesh equations are

$$V_1 = (z_{11} - z_{12})I_1 + z_{12}(I_1 + I_2)$$

$$0 = Z_L I_2 + (z_{21} - z_{12})I_1 + (z_{22} - z_{12})I_2 + z_{12}(I_1 + I_2)$$


Solving for  $I_1$ :

$$I_1 = \frac{V_1(z_{22} + Z_L)}{z_{11}(Z_L + z_{22}) - z_{12}z_{21}}$$


Therefore

$$Z_{in} = \frac{V_1}{I_1} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$$

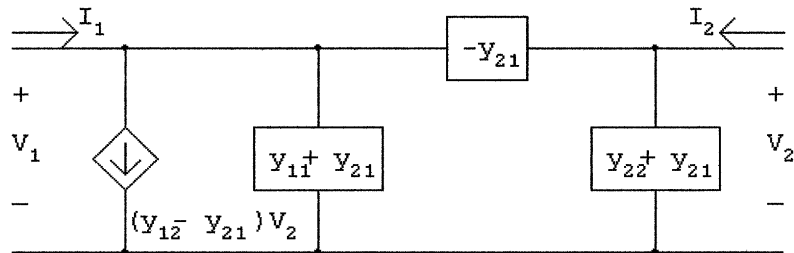
P 18.44 [a]  $I_1 = y_{11}V_1 + y_{21}V_2 + (y_{12} - y_{21})V_2; \quad I_2 = y_{21}V_1 + y_{22}V_2$


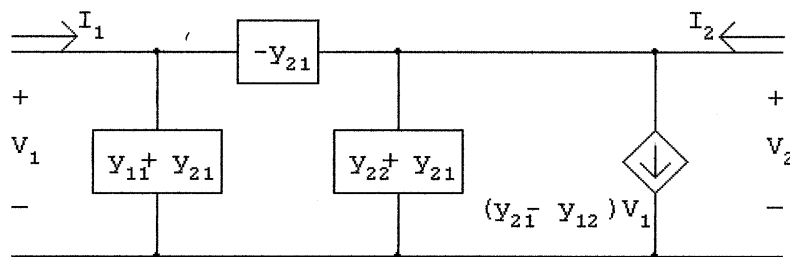
$$I_1 = y_{11}V_1 + y_{12}V_2; \quad I_2 = y_{12}V_1 + y_{22}V_2 + (y_{21} - y_{12})V_1$$



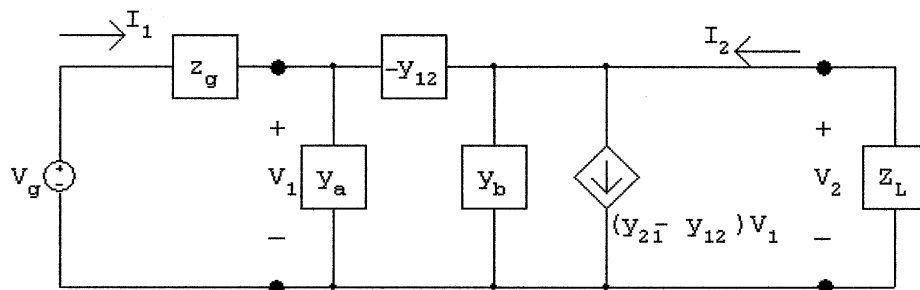[b] Using the second circuit derived in part [a], we have



where  $y_a = (y_{11} + y_{12})$  and  $y_b = (y_{22} + y_{12})$

At the input port we have

$$I_1 = y_a V_1 - y_{12}(V_1 - V_2) = y_{11} V_1 + y_{12} V_2$$

At the output port we have

$$\frac{V_2}{Z_L} + (y_{21} - y_{12})V_1 + y_b V_2 - y_{12}(V_2 - V_1) = 0$$

Solving for  $V_1$  gives


$$V_1 = \left( \frac{1 + y_{22} Z_L}{-y_{21} Z_L} \right) V_2$$

Substituting Eq. (18.2) into (18.1) and at the same time using

$V_2 = -Z_L I_2$ , we get

$$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta y Z_L}$$

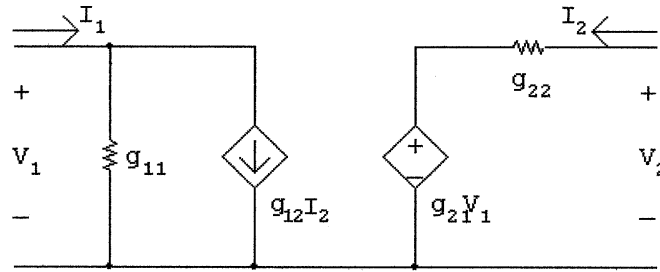- P 18.45 [a] The  $g$ -parameter equations are  $I_1 = g_{11}V_1 + g_{12}I_2$  and  $V_2 = g_{21}V_1 + g_{22}I_2$ . These equations are satisfied by the following circuit:



- [b] The  $g$  parameters for the first two port in Fig P 18.39(a) are


$$g_{11} = \frac{1}{z_{11}} = \frac{1}{200} = 5 \times 10^{-3} \text{ S}$$

$$g_{12} = \frac{-z_{12}}{z_{11}} = \frac{-20}{200} = -0.10$$

$$g_{21} = \frac{z_{21}}{z_{11}} = \frac{-1.6 \times 10^6}{200} = -8000$$

$$g_{22} = \frac{\Delta z}{z_{11}} = \frac{40 \times 10^6}{200} = 200 \text{ k}\Omega$$

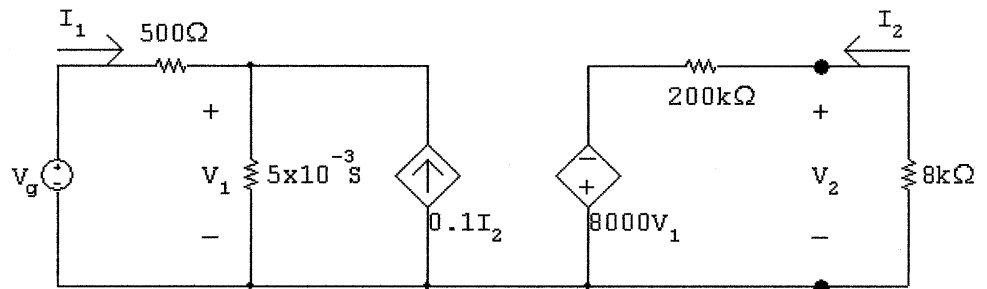From Problem 3.64, since the load resistor and all resistors in the attenuator pad of the second two-port are equal to  $8 \text{ k}\Omega$ ,  $R_{cd} = 8 \text{ k}\Omega$ , hence our circuit reduces to



$$V_2 = \frac{8000}{8000 + 200,000}(-8000V_1)$$

$$I_2 = \frac{-V_2}{8000} = \frac{8000}{208,000}V_1 = \frac{8}{208}V_1$$

$$v_g = 15 \text{ mV}$$

$$\frac{V_1 - 15 \times 10^{-3}}{500} + V_1(5 \times 10^{-3}) - 0.1 \frac{8V_1}{208} = 0$$

$$V_1 \left( \frac{1}{500} + 5 \times 10^{-3} - \frac{0.8}{208} \right) = \frac{15 \times 10^{-3}}{500}$$

$$\therefore V_1 = 9.512 \times 10^{-3}$$

$$V_2 = \frac{-(8000)^2}{208,000} (9.512 \times 10^{-3}) = -2.927 \text{ V}$$

Again, from the results of analyzing the attenuator pad in Problem 3.64

$$\frac{V_o}{V_2} = 0.5; \quad \therefore V_o = (0.5)(-2.927) = -1.46 \text{ V}$$

This result matches the solution to Problem 18.38.