

6

Inductance, Capacitance, and Mutual Inductance

Assessment Problems

AP 6.1 [a] $i_g = 8e^{-300t} - 8e^{-1200t} \text{ A}$

$$v = L \frac{di_g}{dt} = -9.6e^{-300t} + 38.4e^{-1200t} \text{ V}, \quad t > 0^+$$

$$v(0^+) = -9.6 + 38.4 = 28.8 \text{ V}$$

[b] $v = 0$ when $38.4e^{-1200t} = 9.6e^{-300t}$ or $t = (\ln 4)/900 = 1.54 \text{ ms}$

[c] $p = vi = 384e^{-1500t} - 76.8e^{-600t} - 307.2e^{-2400t} \text{ W}$

[d] $\frac{dp}{dt} = 0$ when $e^{1800t} - 12.5e^{900t} + 16 = 0$

Let $x = e^{900t}$ and solve the quadratic $x^2 - 12.5x + 16 = 0$

$$x = 1.44766, \quad t = \frac{\ln 1.45}{900} = 411.05 \mu\text{s}$$

$$x = 11.0523, \quad t = \frac{\ln 11.05}{900} = 2.67 \text{ ms}$$

p is maximum at $t = 411.05 \mu\text{s}$

[e] $p_{\max} = 384e^{-1.5(0.41105)} - 76.8e^{-0.6(0.41105)} - 307.2e^{-2.4(0.41105)} = 32.72 \text{ W}$

[f] W is max when i is max, i is max when di/dt is zero.

When $di/dt = 0$, $v = 0$, therefore $t = 1.54 \text{ ms}$.

[g] $i_{\max} = 8[e^{-0.3(1.54)} - e^{-1.2(1.54)}] = 3.78 \text{ A}$

$$w_{\max} = (1/2)(4 \times 10^{-3})(3.78)^2 = 28.6 \text{ mJ}$$

$$\begin{aligned}\text{AP 6.2 [a]} \quad i &= C \frac{dv}{dt} = 24 \times 10^{-6} \frac{d}{dt} [e^{-15,000t} \sin 30,000t] \\ &= [0.72 \cos 30,000t - 0.36 \sin 30,000t] e^{-15,000t} \text{ A}, \quad i(0^+) = 0.72 \text{ A}\end{aligned}$$

$$\text{[b]} \quad i\left(\frac{\pi}{80} \text{ ms}\right) = -31.66 \text{ mA}, \quad v\left(\frac{\pi}{80} \text{ ms}\right) = 20.505 \text{ V},$$

$$p = vi = -649.23 \text{ mW}$$

$$\text{[c]} \quad w = \left(\frac{1}{2}\right) C v^2 = 126.13 \mu\text{J}$$

$$\begin{aligned}\text{AP 6.3 [a]} \quad v &= \left(\frac{1}{C}\right) \int_{0^-}^t i \, dx + v(0^-) \\ &= \frac{1}{0.6 \times 10^{-6}} \int_{0^-}^t 3 \cos 50,000x \, dx = 100 \sin 50,000t \text{ V}\end{aligned}$$

$$\begin{aligned}\text{[b]} \quad p(t) &= vi = [300 \cos 50,000t] \sin 50,000t \\ &= 150 \sin 100,000t \text{ W}, \quad p_{(\max)} = 150 \text{ W}\end{aligned}$$

$$\text{[c]} \quad w_{(\max)} = \left(\frac{1}{2}\right) C v_{\max}^2 = 0.30(100)^2 = 3000 \mu\text{J} = 3 \text{ mJ}$$

$$\text{AP 6.4 [a]} \quad L_{\text{eq}} = \frac{60(240)}{300} = 48 \text{ mH}$$

$$\text{[b]} \quad i(0^+) = 3 + -5 = -2 \text{ A}$$

$$\text{[c]} \quad i = \frac{125}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 2 = 0.125e^{-5t} - 2.125 \text{ A}$$

$$\text{[d]} \quad i_1 = \frac{50}{3} \int_{0^+}^t (-0.03e^{-5x}) \, dx + 3 = 0.1e^{-5t} + 2.9 \text{ A}$$

$$i_2 = \frac{25}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 5 = 0.025e^{-5t} - 5.025 \text{ A}$$

$$i_1 + i_2 = i$$

$$\text{AP 6.5} \quad v_1 = 0.5 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 10 = -12e^{-10t} + 2 \text{ V}$$

$$v_2 = 0.125 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 5 = -3e^{-10t} - 2 \text{ V}$$

$$v_1(\infty) = 2 \text{ V}, \quad v_2(\infty) = -2 \text{ V}$$

$$W = \left[\frac{1}{2}(2)(4) + \frac{1}{2}(8)(4) \right] \times 10^{-6} = 20 \mu\text{J}$$

AP 6.6 [a] Summing the voltages around mesh 1 yields

$$4\frac{di_1}{dt} + 8\frac{d(i_2 + i_g)}{dt} + 20(i_1 - i_2) + 5(i_1 + i_g) = 0$$

or

$$4\frac{di_1}{dt} + 25i_1 + 8\frac{di_2}{dt} - 20i_2 = -\left(5i_g + 8\frac{di_g}{dt}\right)$$

Summing the voltages around mesh 2 yields

$$16\frac{d(i_2 + i_g)}{dt} + 8\frac{di_1}{dt} + 20(i_2 - i_1) + 780i_2 = 0$$

or

$$8\frac{di_1}{dt} - 20i_1 + 16\frac{di_2}{dt} + 800i_2 = -16\frac{di_g}{dt}$$


[b] From the solutions given in part (b)

$$i_1(0) = -0.4 - 11.6 + 12 = 0; \quad i_2(0) = -0.01 - 0.99 + 1 = 0$$

These values agree with zero initial energy in the circuit. At infinity,

$$i_1(\infty) = -0.4\text{A}; \quad i_2(\infty) = -0.01\text{A}$$

When $t = \infty$ the circuit reduces to

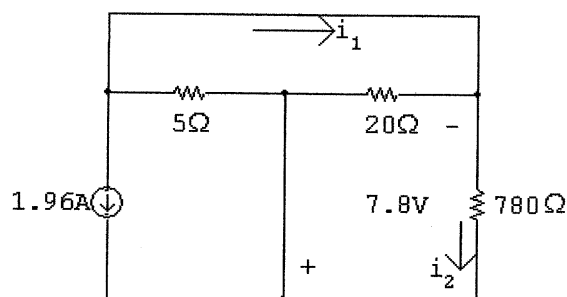

$$\therefore i_1(\infty) = -\left(\frac{7.8}{20} + \frac{7.8}{780}\right) = -0.4\text{A}; \quad i_2(\infty) = -\frac{7.8}{780} = -0.01\text{A}$$

From the solutions for i_1 and i_2 we have

$$\frac{di_1}{dt} = 46.40e^{-4t} - 60e^{-5t}$$

$$\frac{di_2}{dt} = 3.96e^{-4t} - 5e^{-5t}$$

$$\text{Also, } \frac{di_g}{dt} = 7.84e^{-4t}$$

Thus

$$4\frac{di_1}{dt} = 185.60e^{-4t} - 240e^{-5t}$$

$$25i_1 = -10 - 290e^{-4t} + 300e^{-5t}$$

$$8\frac{di_2}{dt} = 31.68e^{-4t} - 40e^{-5t}$$

$$20i_2 = -0.20 - 19.80e^{-4t} + 20e^{-5t}$$

$$5i_g = 9.8 - 9.8e^{-4t}$$

$$8\frac{di_g}{dt} = 62.72e^{-4t}$$

Test:

$$185.60e^{-4t} - 240e^{-5t} - 10 - 290e^{-4t} + 300e^{-5t} + 31.68e^{-4t} - 40e^{-5t}$$

$$+ 0.20 + 19.80e^{-4t} - 20e^{-5t} \stackrel{?}{=} -[9.8 - 9.8e^{-4t} + 62.72e^{-4t}]$$

$$-9.8 + (300 - 240 - 40 - 20)e^{-5t}$$

$$+ (185.60 - 290 + 31.68 + 19.80)e^{-4t} \stackrel{?}{=} -(9.8 + 52.92e^{-4t})$$

$$-9.8 + 0e^{-5t} + (237.08 - 290)e^{-4t} \stackrel{?}{=} -9.8 - 52.92e^{-4t}$$

$$-9.8 - 52.92e^{-4t} = -9.8 - 52.92e^{-4t} \quad (\text{OK})$$

Also,

$$8\frac{di_1}{dt} = 371.20e^{-4t} - 480e^{-5t}$$

$$20i_1 = -8 - 232e^{-4t} + 240e^{-5t}$$

$$16\frac{di_2}{dt} = 63.36e^{-4t} - 80e^{-5t}$$

$$800i_2 = -8 - 792e^{-4t} + 800e^{-5t}$$

$$16\frac{di_g}{dt} = 125.44e^{-4t}$$

Test:

$$371.20e^{-4t} - 480e^{-5t} + 8 + 232e^{-4t} - 240e^{-5t} + 63.36e^{-4t} - 80e^{-5t}$$

$$-8 - 792e^{-4t} + 800e^{-5t} \stackrel{?}{=} -125.44e^{-4t}$$

$$(8 - 8) + (800 - 480 - 240 - 80)e^{-5t}$$

$$+ (371.20 + 232 + 63.36 - 792)e^{-4t} \stackrel{?}{=} -125.44e^{-4t}$$

$$(800 - 800)e^{-5t} + (666.56 - 792)e^{-4t} \stackrel{?}{=} -125.44e^{-4t}$$

$$-125.44e^{-4t} = -125.44e^{-4t} \quad (\text{OK})$$

Problems

P 6.1 [a] $i = 0 \quad t < 0$
 $i = 16t \text{ A} \quad 0 \leq t \leq 25 \text{ ms}$
 $i = 0.8 - 16t \text{ A} \quad 25 \leq t \leq 50 \text{ ms}$
 $i = 0 \quad 50 \text{ ms} < t$

[b] $v = L \frac{di}{dt} = 375 \times 10^{-3}(16) = 6 \text{ V} \quad 0 \leq t \leq 25 \text{ ms}$
 $v = 375 \times 10^{-3}(-16) = -6 \text{ V} \quad 25 \leq t \leq 50 \text{ ms}$

$v = 0 \quad t < 0$
 $v = 6 \text{ V} \quad 0 < t < 25 \text{ ms}$
 $v = -6 \text{ V} \quad 25 < t < 50 \text{ ms}$
 $v = 0 \quad 50 \text{ ms} < t$

$p = vi$

$p = 0 \quad t < 0$
 $p = 96t \text{ W} \quad 0 < t < 25 \text{ ms}$
 $p = 96t - 4.8 \text{ W} \quad 25 < t < 50 \text{ ms}$
 $p = 0 \quad 50 \text{ ms} < t$

$w = \frac{1}{2}Li^2$

$w = 0 \quad t < 0$
 $w = 48t^2 \text{ J} \quad 0 < t < 25 \text{ ms}$
 $w = 48t^2 - 4.8t + 0.12 \text{ J} \quad 25 < t < 50 \text{ ms}$
 $w = 0 \quad 50 \text{ ms} < t$

P 6.2 [a] $0 \leq t \leq 1 \text{ ms} :$

$$i = \frac{1}{L} \int_0^t v_s dx + i(0) = \frac{10^6}{300} \int_0^t 6 \times 10^{-3} dx + 0$$

$$= 20x \Big|_0^t = 20t \text{ A}$$

$$1 \text{ ms} \leq t \leq 2 \text{ ms} :$$


$$i = \frac{10^6}{300} \int_{10^{-3}}^t (12 \times 10^{-3} - 6x) dx + 20 \times 10^{-3}$$

$$\therefore i = 40t - 10,000t^2 - 10 \times 10^{-3} \text{ A}$$

$$2 \text{ ms} \leq t \leq \infty :$$

$$i = \frac{10^6}{300} \int_{2 \times 10^{-3}}^t (0) dx + 30 \times 10^{-3} = 30 \text{ mA}$$



[b]

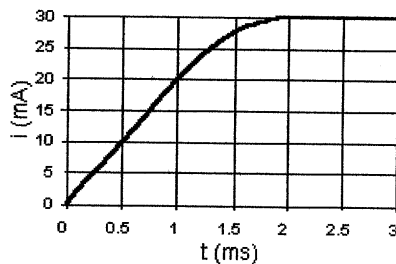

P 6.3 $0 \leq t < \infty$

$$i_L = \frac{10^3}{4} \int_0^t 30 \times 10^{-3} e^{-3x} dx + 2.5 = 7.5 \frac{e^{-3x}}{-3} \Big|_0^t + 2.5$$
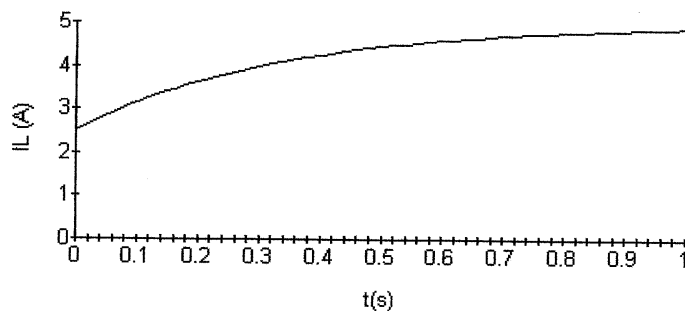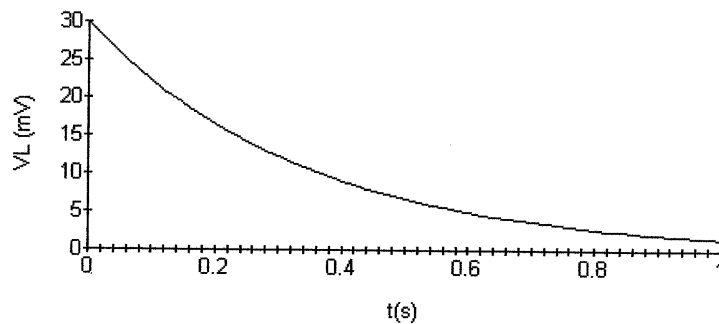
$$= 5 - 2.5e^{-3t} \text{ A}, \quad 0 \leq t \leq \infty$$



P 6.4 [a] $v = L \frac{di}{dt}$

$$\frac{di}{dt} = 20[e^{-5t} - 5te^{-5t}] = 20e^{-5t}(1 - 5t)$$

$$v = (100 \times 10^{-6})(20)e^{-5t}(1 - 5t) \\ = 2e^{-5t}(1 - 5t) \text{ mV}, \quad t > 0$$

[b] $p = vi = 0.04te^{-10t}(1 - 5t)$

$$p(100 \text{ ms}) = 0.04(0.1)e^{-1}(1 - 0.5) = 735.76 \mu\text{W}$$

[c] absorbing

[d] $i(100 \text{ ms}) = 20(0.1)e^{-0.5} = 2e^{-0.5}$

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(100 \times 10^{-6})(2e^{-0.5})^2 = 73.58 \mu\text{J}$$

[e] The energy is a maximum where the current is a maximum:

$$\frac{di_L}{dt} = 0 \quad \text{when} \quad 1 - 5t = 0 \quad \text{or} \quad t = 0.2 \text{ s}$$

$$i_{\max} = 20(0.2)e^{-1} = 4e^{-1} \text{ A}$$

$$w_{\max} = \frac{1}{2}(100 \times 10^{-6})(4e^{-1})^2 = 108.27 \mu\text{J}$$

P 6.5 [a] $0 \leq t \leq 2 \text{ s} :$

$$v = -25t$$

$$i = \frac{1}{2.5} \int_0^t -25x \, dx + 0 = -10 \frac{x^2}{2} \Big|_0^t$$

$$i = -5t^2 \text{ A}$$

$$2 \text{ s} \leq t \leq 6 \text{ s} :$$

$$v = -100 + 25t$$

$$i(2) = -20 \text{ A}$$

$$\therefore i = \frac{1}{2.5} \int_2^t (25x - 100) \, dx - 20$$

$$= 10 \int_2^t x \, dx - 40 \int_2^t dx - 20$$

$$= 5(t^2 - 4) - 40(t - 2) - 20$$

$$= 5t^2 - 40t + 40 \text{ A}$$

$$6 \text{ s} \leq t \leq 10 \text{ s} :$$

$$v = 200 - 25t$$

$$i(6) = 5(36) - 240 + 40 = -20 \text{ A}$$

$$\begin{aligned} i &= \frac{1}{2.5} \int_6^t (200 - 25x) dx - 20 \\ &= 80 \int_6^t dx - 10 \int_6^t x dx - 20 \\ &= 80(t - 6) - 10(t^2 - 36)/2 - 20 = 80t - 5t^2 - 320 \text{ A} \end{aligned}$$

$$10 \text{ s} \leq t \leq 12 \text{ s} :$$

$$v = 25t - 300$$

$$i(10) = 800 - 500 - 320 = -20 \text{ A}$$

$$\begin{aligned} i &= \frac{1}{2.5} \int_{10}^t (25x - 300) dx - 20 \quad t \geq 12 \text{ s} : \\ &= 10 \int_{10}^t x dx - 120 \int_{10}^t dx - 20 \\ &= 5(t^2 - 100) - 120(t - 10) - 20 \\ &= 5t^2 - 120t + 680 \text{ A} \end{aligned}$$

$$v = 0$$

$$i(12) = 5(12)^2 - 120(12) + 680 = -40 \text{ A}$$

$$\begin{aligned} i &= \frac{1}{2.5} \int_{12}^t 0 dx - 40 \\ &= -40 \text{ A} \end{aligned}$$

[b] For $0 \leq t \leq 2 \text{ s}$, $v = -25t \text{ V}$; $i = -5t^2 \text{ A}$

$$v = 0 \quad \text{when} \quad t = 0 \quad \text{so} \quad i = 0 \text{ A}$$

$$\text{For } 2 \leq t \leq 6 \text{ s}, \quad v = -100 + 25t \text{ V}; \quad i = 5t^2 - 40t + 40 \text{ A}$$

$$v = 0 \quad \text{when} \quad t = 4 \text{ s} \quad \text{so} \quad i = 5(4)^2 - 40(4) + 40 = -40 \text{ A}$$


$$\text{For } 6 \leq t \leq 10 \text{ s}, \quad v = 200 - 25t \text{ V}; \quad i = -5t^2 + 80t - 320 \text{ A}$$

$$v = 0 \quad \text{when} \quad t = 8 \text{ s} \quad \text{so} \quad i = -5(8)^2 + 80(8) - 320 = 0 \text{ A}$$

$$\text{For } 10 \leq t \leq 12 \text{ s}, \quad v = 25t - 300 \text{ V}; \quad i = 5t^2 - 120t + 680 \text{ A}$$

$$v = 0 \quad \text{when} \quad t = 12 \text{ s} \quad \text{so} \quad i = 5(12)^2 - 120(12) + 680 = -40 \text{ A}$$
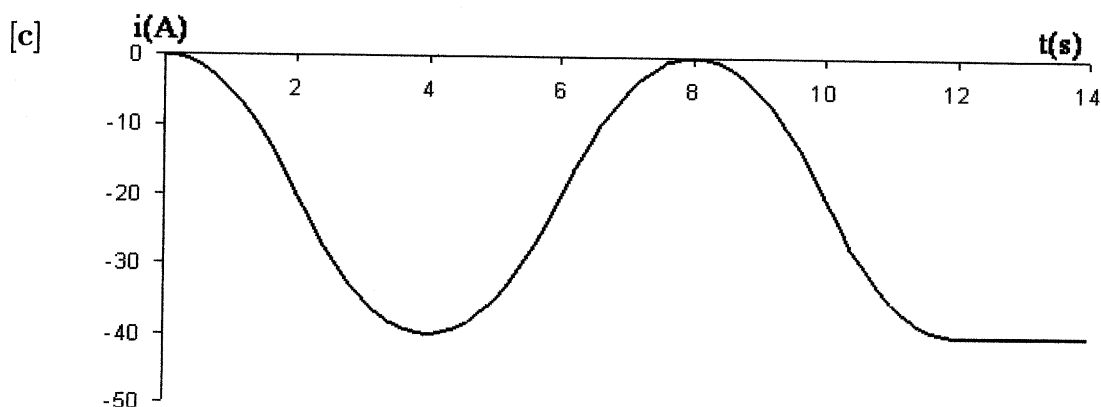
$$\text{For } t \geq 12 \text{ s}, \quad v = 0; \quad i = -40 \text{ A}$$



P 6.6 [a] $v_L = L \frac{di}{dt} = [56 \cos 140t + 92 \sin 140t]e^{-20t} \text{ mV}$

$$\therefore \frac{dv_L}{dt} = [11,760 \cos 140t - 9680 \sin 140t]e^{-20t} \text{ mV/s}$$

$$\frac{dv_L}{dt} = 0 \quad \text{when} \quad \tan 140t = \frac{11,760}{9680} = 1.21$$

$$\therefore t = 6.30 \text{ ms}$$

Also $140t = 0.8821 + \pi$ etc.

Because of the decaying exponential v_L will be maximum the first time the derivative is zero.

[b] $v_L(\text{max}) = [56 \cos 0.8821 + 92 \sin 0.8821]e^{-0.12602} = 93.997 \text{ mV}$

$$v_L \text{ max} \approx 94 \text{ mV}$$

Note: When $t = \frac{0.8821 + \pi}{140}$; $v_L = -60 \text{ mV}$

P 6.7 [a] $i = \frac{1000}{50} \int_0^t 250 \sin 1000x \, dx - 5$

$$= 5000 \int_0^t \sin 1000x \, dx - 5$$

$$= 5000 \left[\frac{-\cos 1000x}{1000} \right]_0^t - 5$$

$$= 5(1 - \cos 1000t) - 5$$

$$i = -5 \cos 1000t \text{ A}$$

$$[b] \quad p = vi = (250 \sin 1000t)(-5 \cos 1000t)$$

$$= -1250 \sin 1000t \cos 1000t$$





$$p = -625 \sin 2000t \text{ W}$$

$$w = \frac{1}{2} Li^2$$

$$= \frac{1}{2} (50 \times 10^{-3}) 25 \cos^2 1000t$$

$$= 625 \cos^2 1000t \text{ mJ}$$
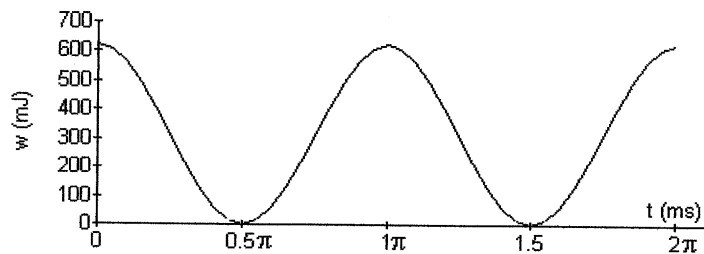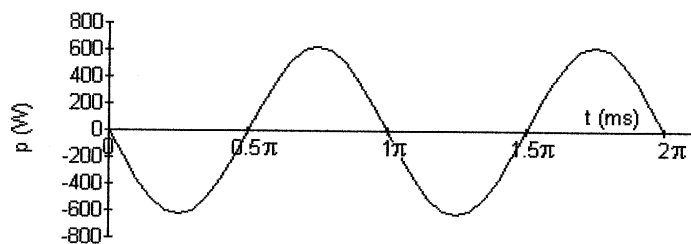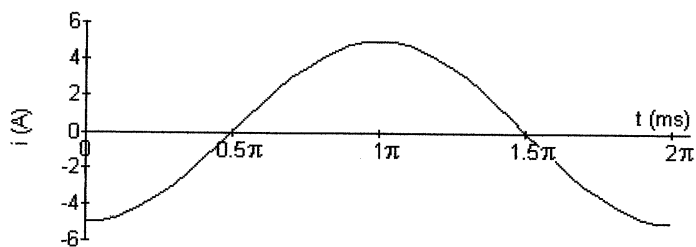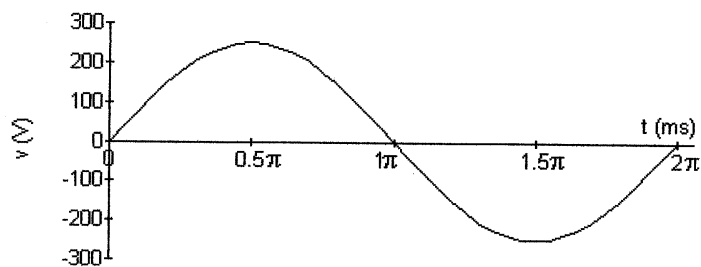
$$w = [312.5 + 312.5 \cos 2000t] \text{ mJ.}$$



[c] Absorbing power: Delivering power:

$$0.5\pi \leq t \leq \pi \text{ ms} \quad 0 \leq t \leq 0.5\pi \text{ ms}$$

$$1.5\pi \leq t \leq 2\pi \text{ ms} \quad \pi \leq t \leq 1.5\pi \text{ ms}$$

P 6.8 [a] $i(0) = A_1 + A_2 = 1$

$$\frac{di}{dt} = -2000A_1e^{-2000t} - 8000A_2e^{-8000t}$$

$$v = -30A_1e^{-2000t} - 120A_2e^{-8000t} \text{ V}$$

$$v(0) = -30A_1 - 120A_2 = 60$$

$$\text{Solving, } A_1 = 2 \quad \text{and } A_2 = -1$$

Thus,

$$i_1 = (2e^{-2000t} - e^{-8000t}) \text{ A} \quad t \geq 0$$

$$v = -60e^{-2000t} + 120e^{-8000t} \text{ V}, \quad t \geq 0$$

[b] $p = vi = 300e^{-10,000t} - 120e^{-4000t} - 120e^{-16,000t}$

$$p = 0 \quad \text{when} \quad 300e^{6000t} - 120e^{12,000t} - 120 = 0$$

$$\text{Let } x = e^{6000t}; \quad \text{then} \quad 300x - 120x^2 - 120 = 0$$

$$\text{Thus } x^2 - 2.5x + 1 = 0 \quad \text{so} \quad x = 0.5 \text{ and } x = 2$$

If $x = e^{6000t} = 0.5$, t will be negative. Hence, the solution for $t > 0$ must be $x = 2$:

$$e^{6000t} = 2 \quad \text{so} \quad 6000t = \ln 2$$

$$\text{Thus, } t = \frac{\ln 2}{6000} = 115.52 \mu\text{s}$$

P 6.9 [a] From Problem 6.8 we have

$$i = A_1e^{-2000t} + A_2e^{-8000t} \text{ A}$$

$$v = -30A_1e^{-2000t} - 120A_2e^{-8000t} \text{ V}$$

$$i(0) = A_1 + A_2 = 1$$

$$v(0) = -30A_1 - 120A_2 = -300$$

$$\text{Solving, } A_1 = -2; \quad A_2 = 3$$

Thus,

$$i = -2e^{-2000t} + 3e^{-8000t} \text{ A} \quad t \geq 0$$

$$v = 60e^{-2000t} - 360e^{-8000t} \text{ V} \quad t \geq 0$$

[b] $i = 0$ when $3e^{-8000t} = 2e^{-2000t}$

$$\therefore e^{6000t} = 1.5 \quad \text{so} \quad t = (\ln 1.5)/6000 = 67.58 \mu\text{s}$$

Thus,

$$i > 0 \quad \text{for} \quad 0 \leq t \leq 67.58 \mu\text{s} \quad \text{and} \quad i < 0 \quad \text{for} \quad 67.58 \mu\text{s} \leq t < \infty$$

$$v = 0 \quad \text{when} \quad 60e^{-2000t} = 3600e^{-8000t}$$

$$\therefore t = (\ln 6)/6000 = 298.63 \mu\text{s}$$

Thus,

$$v < 0 \quad \text{for} \quad 0 \leq t \leq 298.63 \mu\text{s} \quad \text{and} \quad v > 0 \quad \text{for} \quad 298.63 \mu\text{s} \leq t < \infty$$

Therefore,

$$p < 0 \quad \text{for} \quad 0 \leq t \leq 67.58 \mu\text{s} \quad \text{and} \quad 298.63 \mu\text{s} \leq t < \infty$$

(inductor delivers energy)

$$p > 0 \quad \text{for} \quad 67.58 \mu\text{s} \leq t \leq 298.63 \mu\text{s} \quad (\text{inductor stores energy})$$

[c] $p = vi = 900e^{-10,000t} - 120e^{-4000t} - 1080e^{-16,000t} \text{ W}$

$$\therefore w_{\text{stored}} = \int_{t_2}^{t_1} p dx + w(0)$$

$$\begin{aligned} w_{\text{stored}} &= 10^{-3} \left[-90e^{-10,000x} \Big|_{t_1}^{t_2} + 30e^{-4000x} \Big|_{t_1}^{t_2} + 67.5e^{-16,000x} \Big|_{t_1}^{t_2} \right] + 7.5 \times 10^{-3} \\ &= 30e^{-4000t_2} + 67.5e^{-16,000t_2} - 90e^{-10,000t_2} + 90e^{-10,000t_1} - 30e^{-4000t_1} \\ &\quad - 67.5e^{-16,000t_1} + 7.5 \text{ mJ} \end{aligned}$$

$$\text{where } t_1 = 67.58 \mu\text{s} \quad \text{and} \quad t_2 = 298.63 \mu\text{s}$$

$$\therefore w_{\text{stored}} = 5.11 + 7.5 = 12.61 \text{ mJ}$$

$$\begin{aligned} w_{\text{extracted}} &= \int_0^{t_1} p dt + \int_{t_2}^{\infty} p dt \\ &= \int_0^{t_1} [900e^{-10,000x} - 120e^{-4000x} - 1080e^{-16,000x}] dx \\ &\quad + \int_{t_2}^{\infty} [900e^{-10,000x} - 120e^{-4000x} - 1080e^{-16,000x}] dx \\ &= 10^{-3} \left(-90e^{-10,000x} \Big|_0^{t_1} + 30e^{-4000x} \Big|_0^{t_1} + 67.5e^{-16,000x} \Big|_0^{t_1} \right) \\ &\quad - 10^{-3} \left(90e^{-10,000x} \Big|_{t_2}^{\infty} + 30e^{-4000x} \Big|_{t_2}^{\infty} + 67.5e^{-16,000x} \Big|_{t_2}^{\infty} \right) \end{aligned}$$

$$= 90e^{-10,000t_2} - 30e^{-4000t_2} - 67.5e^{-16,000t_2} + 30e^{-4000t_1} \\ + 67.5e^{-16,000t_1} - 90e^{-10,000t_1} - 7.5 \text{ mJ}$$

$$\text{where } t_1 = 67.58 \mu\text{s} \quad \text{and} \quad t_2 = 298.63 \mu\text{s}$$

$$\therefore w_{\text{extracted}} = -12.61 \text{ mJ}$$

Thus, the energy stored equals the energy extracted.

P 6.10 $i = (B_1 \cos 5t + B_2 \sin 5t)e^{-t}$

$$i(0) = B_1 = 25 \text{ A}$$

$$\frac{di}{dt} = (B_1 \cos 5t + B_2 \sin 5t)(-e^{-t}) + e^{-t}(-5B_1 \sin 5t + 5B_2 \cos 5t)$$

$$= [(5B_2 - B_1) \cos 5t - (5B_1 + B_2) \sin 5t]e^{-t}$$

$$v = 2 \frac{di}{dt} = [(10B_2 - 2B_1) \cos 5t - (10B_1 + 2B_2) \sin 5t]e^{-t}$$

$$v(0) = 100 = 10B_2 - 2B_1 = 10B_2 - 50 \quad \therefore B_2 = 150/10 = 15 \text{ A}$$

Thus,

$$i = (25 \cos 5t + 15 \sin 5t)e^{-t} \text{ A}, \quad t \geq 0$$

$$v = (100 \cos 5t - 280 \sin 5t)e^{-t} \text{ V}, \quad t \geq 0$$

$$i(0.5) = -6.70 \text{ A}; \quad v(0.5) = -150.23 \text{ V}$$

$$p(0.5) = (-6.70)(-150.23) = 1007.00 \text{ W absorbing}$$

P 6.11 For $0 \leq t \leq 1.2 \text{ s}$:

$$i_L = \frac{1}{20} \int_0^t 14 \times 10^{-3} dx + 0 = 0.7 \times 10^{-3} t$$

$$i_L(1.2 \text{ s}) = (0.7 \times 10^{-3})(1.2) = 0.84 \text{ mA}$$

$$R_m = (25)(1000) = 25 \text{ k}\Omega$$

$$v_m(1.2 \text{ s}) = (0.84 \times 10^{-3})(25 \times 10^3) = 21 \text{ V}$$

P 6.12 $p = vi = 40t[e^{-10t} - 10te^{-20t} - e^{-20t}]$

$$W = \int_0^{\infty} p dx = \int_0^{\infty} 40x[e^{-10x} - 10xe^{-20x} - e^{-20x}] dx = 0.2 \text{ J}$$

This is energy stored in the inductor at $t = \infty$.

P 6.13 [a] $v(20 \mu\text{s}) = 12.5 \times 10^9 (20 \times 10^{-6})^2 = 5 \text{ V}$ (end of first interval)

$$\begin{aligned} v(20 \mu\text{s}) &= 10^6 (20 \times 10^{-6}) - (12.5)(400) \times 10^{-3} - 10 \\ &= 5 \text{ V (start of second interval)} \end{aligned}$$

$$\begin{aligned} v(40 \mu\text{s}) &= 10^6 (40 \times 10^{-6}) - (12.5)(1600) \times 10^{-3} - 10 \\ &= 10 \text{ V (end of second interval)} \end{aligned}$$

[b] $p(10 \mu\text{s}) = 62.5 \times 10^{12} (10^{-5})^3 = 62.5 \text{ mW}$, $v(10 \mu\text{s}) = 1.25 \text{ V}$,

$$i(10 \mu\text{s}) = 50 \text{ mA}, \quad p(10 \mu\text{s}) = vi = (1.25)(50 \text{ m}) = 62.5 \text{ mW (checks)}$$

$$p(30 \mu\text{s}) = 437.50 \text{ mW}, \quad v(30 \mu\text{s}) = 8.75 \text{ V}, \quad i(30 \mu\text{s}) = 0.05 \text{ A}$$

$$p(30 \mu\text{s}) = vi = (8.75)(0.05) = 62.5 \text{ mW (checks)}$$

[c] $w(10 \mu\text{s}) = 15.625 \times 10^{12} (10 \times 10^{-6})^4 = 0.15625 \mu\text{J}$

$$w = 0.5Cv^2 = 0.5(0.2 \times 10^{-6})(1.25)^2 = 0.15625 \mu\text{J}$$


$$w(30 \mu\text{s}) = 7.65625 \mu\text{J}$$

$$w(30 \mu\text{s}) = 0.5(0.2 \times 10^{-6})(8.75)^2 = 7.65625 \mu\text{J}$$

P 6.14 $i_C = C(dv/dt)$

$$0 < t < 1: \quad i_C = 0.5 \times 10^{-6} (120)t^2 = 60t^2 \mu\text{A}$$
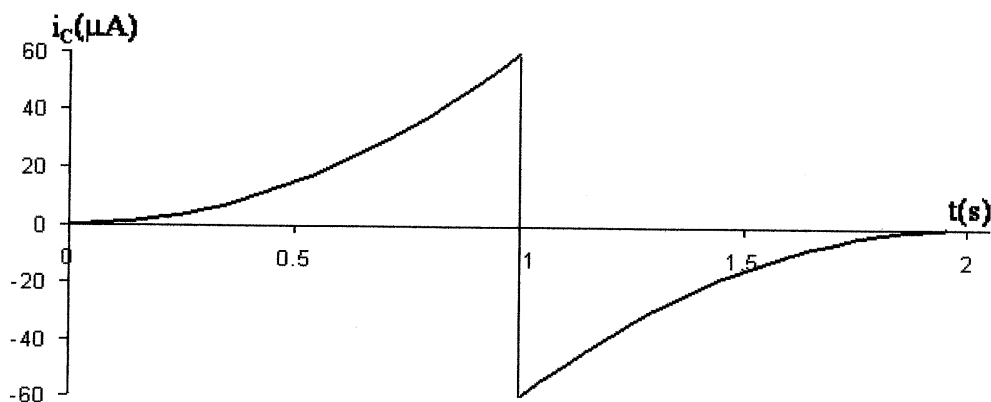
$$1 < t < 2: \quad i_C = 0.5 \times 10^{-6} (120)(2-t)^2(-1) = -60(2-t)^2 \mu\text{A}$$



P 6.15 [a] $0 \leq t \leq 100 \mu s$

$$C = 0.2 \mu F \quad \frac{1}{C} = 5 \times 10^6$$

$$v = 5 \times 10^6 \int_0^t -0.04 dx + 40$$

$$v = -200 \times 10^3 t + 40 \text{ V} \quad 0 \leq t \leq 100 \mu s$$

$$v(100 \mu s) = -20 + 40 = 20 \text{ V}$$

[b] $100 \mu s \leq t \leq 300 \mu s$

$$v = 5 \times 10^6 \int_{100 \times 10^{-6}}^t 0.08 dx + 20 = 4 \times 10^5 t - 40 + 20$$

$$v = 4 \times 10^5 t - 20 \text{ V} \quad 100 \leq t \leq 300 \mu s$$


$$v(300 \mu s) = 4 \times 10^5 (300 \times 10^{-6}) - 20 = 100 \text{ V}$$

[c] $300 \mu s \leq t < \infty$

$$v = 5 \times 10^6 \int_{300 \times 10^{-6}}^t 0 dx + 100 = 100$$

$$v = 100 \text{ V}, \quad 300 \mu s \leq t < \infty$$

[d]

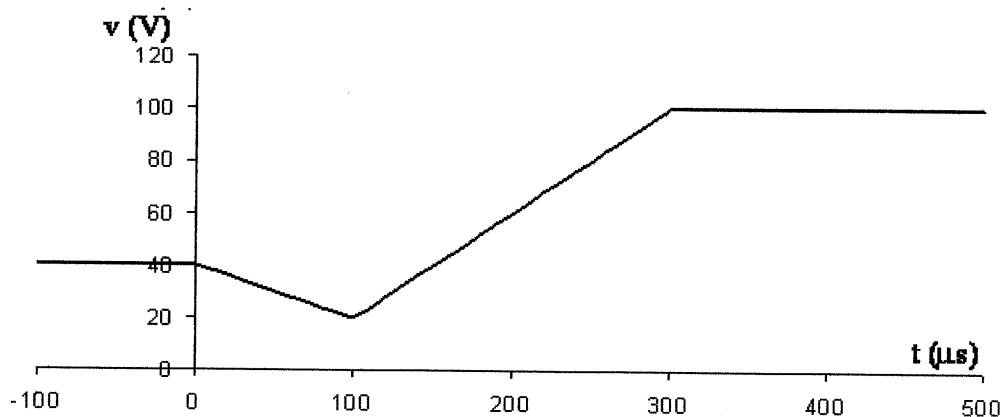P 6.16 [a] $i = C \frac{dv}{dt} = 0, \quad t < 0$ [b] $i = C \frac{dv}{dt} = 5e^{-1000t} [\cos 3000t + 13 \sin 3000t] \text{ mA}, \quad t \geq 0$ [c] no, $v(0^-) = -30 \text{ V}$
 $v(0^+) = 10 - 40 = -30 \text{ V}$ [d] yes, $i(0^-) = 0 \text{ A}$
 $i(0^+) = 5 \text{ mA}$

$$[e] \quad v(\infty) = 10 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.5 \times 10^{-6}) (10)^2 = 25 \mu\text{J}$$

$$\text{P 6.17} \quad [a] \quad i = \frac{50 \times 10^{-3}}{10 \times 10^{-6}} t = 5 \times 10^3 t \quad 0 \leq t \leq 10 \mu\text{s}$$

$$i = 50 \times 10^{-3} \quad 10 \leq t \leq 30 \mu\text{s}$$

$$q = \int_0^{10 \times 10^{-6}} 5 \times 10^3 t \, dt + \int_{10 \times 10^{-6}}^{30 \times 10^{-6}} 50 \times 10^{-3} \, dt$$

$$= 5 \times 10^3 \frac{t^2}{2} \Big|_0^{10 \times 10^{-6}} + 50 \times 10^{-3} (20 \times 10^{-6})$$

$$= 5 \times 10^3 \left(\frac{1}{2}\right) (100 \times 10^{-12}) + 1000 \times 10^{-3} \times 10^{-6}$$

$$= 1.25 \mu\text{C}$$

$$[b] \quad i = 200 \times 10^{-3} - 5 \times 10^{-3} t \quad 30 \mu\text{s} \leq t \leq 50 \mu\text{s}$$

$$q = 1.25 \times 10^{-6} + \int_{30 \times 10^{-6}}^{50 \times 10^{-6}} [200 \times 10^{-3} - 5 \times 10^3 t] \, dt$$

$$= 1.25 \times 10^{-6} + 200 \times 10^{-3} (20 \times 10^{-6}) - 5 \times 10^3 \frac{t^2}{2} \Big|_{30 \times 10^{-6}}^{50 \times 10^{-6}}$$

$$= 1.25 \times 10^{-6} + 4000 \times 10^{-9} - 5 \times 10^3 \left[\frac{2500 - 900}{2} \right] 10^{-12}$$

$$= 1.25 \mu\text{C}$$

$$\text{Since } q = vC, \quad \therefore v = 1.25/0.25 = 5 \text{ V.}$$

$$[c] \quad i = -300 \times 10^{-3} + 5 \times 10^{-3} t \quad 50 \mu\text{s} \leq t \leq 60 \mu\text{s}$$

$$q = 1.25 \times 10^{-6} + \int_{50 \times 10^{-6}}^{60 \times 10^{-6}} [-300 \times 10^{-3} + 5 \times 10^3 t] \, dt$$

$$= 1.25 \times 10^{-6} - 300 \times 10^{-3} (10 \times 10^{-6})$$

$$+ 5 \times 10^3 \left[\frac{3600 - 2500}{2} \right] 10^{-12}$$

$$= 1 \mu\text{C}$$

$$v = \frac{1 \times 10^{-6}}{0.25 \times 10^{-6}} = 4 \text{ V}$$

$$w = \frac{C}{2} v^2 = \frac{1}{2} (0.25) \times 10^{-6} (16) = 2 \mu\text{J}$$

$$\text{P 6.18 [a]} \quad v = 5 \times 10^6 \int_0^{250 \times 10^{-6}} 100 \times 10^{-3} e^{-1000t} dt - 60.6$$

$$= 500 \times 10^3 \left. \frac{e^{-1000t}}{-1000} \right|_0^{250 \times 10^{-6}} - 60.6$$

$$= 500(1 - e^{-0.25}) - 60.6 = 50 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.2) (10^{-6}) (50)^2 = 250 \mu\text{J}$$

$$\text{[b]} \quad v = 500 - 60.6 = 439.40 \text{ V}$$

$$w = \frac{1}{2} (0.2) \times 10^{-6} (439.40)^2 = 19.31 \text{ mJ} = 19,307.24 \mu\text{J}$$

$$\text{P 6.19 [a]} \quad w(0) = \frac{1}{2} C [v(0)]^2 = \frac{1}{2} (0.40) \times 10^{-6} (25)^2 = 125 \mu\text{J}$$

$$\text{[b]} \quad v = (A_1 t + A_2) e^{-1500t}$$

$$v(0) = A_2 = 25 \text{ V}$$

$$\frac{dv}{dt} = -1500 e^{-1500t} (A_1 t + A_2) + e^{-1500t} (A_1)$$

$$= (-1500 A_1 t - 1500 A_2 + A_1) e^{-1500t}$$

$$\frac{dv}{dt}(0) = A_1 - 1500 A_2$$

$$i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{90 \times 10^{-3}}{0.40 \times 10^{-6}} = 225 \times 10^3$$

$$\therefore 225 \times 10^3 = A_1 - 1500(25)$$

$$\text{Thus, } A_1 = 2.25 \times 10^5 + 3.75 \times 10^4 = 262,500 \frac{\text{V}}{\text{s}}$$

$$\text{[c]} \quad v = (262,500t + 25) e^{-1500t}$$

$$i = C \frac{dv}{dt} = 0.40 \times 10^{-6} \frac{d}{dt} (262,500t + 25) e^{-1500t}$$

$$i = \frac{d}{dt} [(0.105t + 10 \times 10^{-6}) e^{-1500t}]$$

$$= (0.105t + 10 \times 10^{-6}) (-1500) e^{-1500t} + e^{-1500t} (0.105)$$

$$= (-157.5t - 15 \times 10^{-3} + 0.105) e^{-1500t}$$

$$= (0.09 - 157.5t) e^{-1500t} \text{ A}, \quad t \geq 0$$

$$= (90 - 157,500t) e^{-1500t} \text{ mA}, \quad t \geq 0$$

$$\text{P 6.20} \quad 10 \parallel (15 + 25) = 8 \text{ H}$$

$$8 \parallel 12 = 4.8 \text{ H}$$

$$44 \parallel (1.2 + 4.8) = 5.28 \text{ H}$$

$$21 \parallel 4 = 3.36 \text{ H}$$

$$5.28 + 3.36 = 8.64 \text{ H}$$

$$\text{P 6.21} \quad 6 \parallel 14 = 4.2 \text{ H}$$

$$15.8 + 4.2 = 20 \text{ H}$$

$$20 \parallel 60 = 15 \text{ H}$$

$$15 + 5 = 20 \text{ H}$$


$$20 \parallel 80 = 16 \text{ H}$$

$$16 + 24 = 40 \text{ H}$$

$$40 \parallel 10 = 8 \text{ H}$$

$$L_{ab} = 12 + 8 = 20 \text{ H}$$

$$\text{P 6.22} \quad [\mathbf{a}]$$

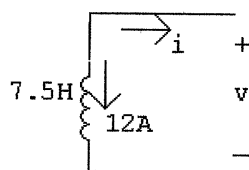

$$i(t) = -\frac{1}{7.5} \int_0^t -1800e^{-20x} dx - 12$$

$$= 240 \frac{e^{-20x}}{-20} \bigg|_0^t - 12$$

$$= -12(e^{-20t} - 1) - 12$$

$$i(t) = -12e^{-20t} \text{ A}$$

$$[\mathbf{b}] \quad i_1(t) = -\frac{1}{10} \int_0^t -1800e^{-20x} dx + 4$$

$$= 180 \frac{e^{-20x}}{-20} \Big|_0^t + 4$$

$$= -9(e^{-20t} - 1) + 4$$

$$i_1(t) = -9e^{-20t} + 13 \text{ A}$$

$$[\mathbf{c}] \quad i_2(t) = -\frac{1}{30} \int_0^t -1800e^{-20x} dx - 16$$

$$= 60 \frac{e^{-20x}}{-20} \Big|_0^t - 16$$

$$= -3(e^{-20t} - 1) - 16$$

$$i_2(t) = -3e^{-20t} - 13 \text{ A}$$

$$[\mathbf{d}] \quad p = vi = (-1800e^{-20t})(-12e^{-20t}) = 21,600e^{-40t} \text{ W}$$

$$w = \int_0^\infty p dt = \int_0^\infty 21,600e^{-40t} dt$$

$$= 21,600 \frac{e^{-40t}}{-40} \Big|_0^\infty$$

$$= 540 \text{ J}$$


$$[\mathbf{e}] \quad w = \frac{1}{2}(10)(16) + \frac{1}{2}(30)(256) = 3920 \text{ J}$$

$$[\mathbf{f}] \quad w_{\text{trapped}} = w_{\text{initial}} - w_{\text{delivered}} = 3920 - 540 = 3380 \text{ J}$$

$$[\mathbf{g}] \quad w_{\text{trapped}} = \frac{1}{2}(10)(13)^2 + \frac{1}{2}(30)(13)^2 = 3380 \text{ J} \quad \text{checks}$$

P 6.23 [a] $i_o(0) = i_1(0) + i_2(0) = 5 \text{ A}$


[b]

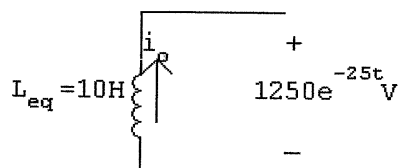

$$i_o = -\frac{1}{10} \int_0^t 1250e^{-25x} dx + 5 = -125 \left[\frac{e^{-25x}}{-25} \right]_0^t + 5$$

$$= 5(e^{-25t} - 1) + 5 = 5e^{-25t} \text{ A}, \quad t \geq 0$$

[c]

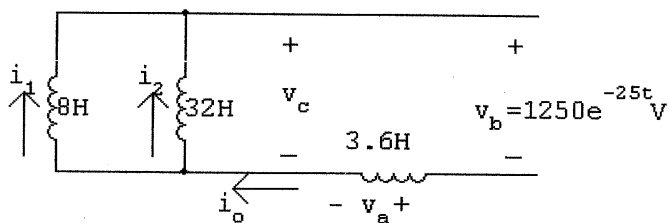

$$v_a = 3.6 \frac{d}{dt}(5e^{-25t}) = -450e^{-25t} \text{ V}$$

$$\begin{aligned} v_c &= v_a + v_b = -450e^{-25t} + 1250e^{-25t} \\ &= 800e^{-25t} \text{ V} \end{aligned}$$

$$i_1 = -\frac{1}{8} \int_0^t 800e^{-25x} dx + 10$$

$$= 4e^{-25t} - 4 + 10$$

$$i_1 = 4e^{-25t} + 6 \text{ A} \quad t \geq 0$$

$$[\text{d}] \quad i_2 = -\frac{1}{32} \int_0^t 800e^{-25x} dx - 5$$

$$= e^{-25t} - 1 - 5$$

$$i_2 = e^{-25t} - 6 \text{ A}, \quad t \geq 0$$

$$[\text{e}] \quad w(0) = \frac{1}{2}(8)(100) + \frac{1}{2}(32)(25) + \frac{1}{2}(3.6)(25) = 845 \text{ J}$$

$$[\text{f}] \quad w_{\text{del}} = \frac{1}{2}(10)(25) = 125 \text{ J}$$

$$[\text{g}] \quad w_{\text{trapped}} = 845 - 125 = 720 \text{ J}$$

P 6.24 $v_b = 1250e^{-25t} \text{ V}$

$$i_o = 5e^{-25t} \text{ A}$$

$$p = 6250e^{-50t} \text{ W}$$

$$w = \int_0^t 6250e^{-50x} dx = 6250 \frac{e^{-50x}}{-50} \Big|_0^t = 125(1 - e^{-50t}) \text{ W}$$

$$w_{\text{total}} = 125 \text{ J}$$

$$80\% w_{\text{total}} = 100 \text{ J}$$



Thus,

$$125 - 125e^{-50t} = 100; \quad e^{50t} = 5; \quad \therefore t = 32.19 \text{ ms}$$

$$\text{P 6.25} \quad \frac{1}{21} + \frac{1}{28} = \frac{7}{84} \quad \therefore C_{\text{eq}} = 12 \mu\text{F}$$

$$-10 \text{ V} - 5 \text{ V} = -15 \text{ V}$$



$$24 + 12 = 36 \mu\text{F}$$

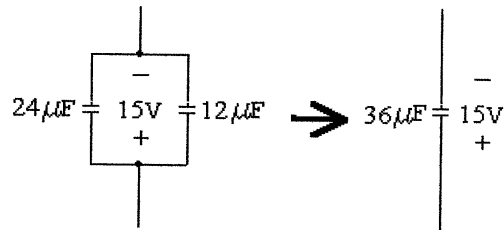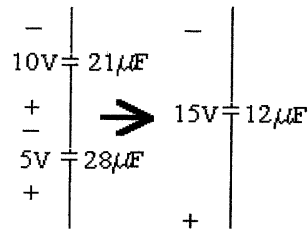

$$\frac{1}{36} + \frac{1}{36} = \frac{2}{36} \quad \therefore C_{\text{eq}} = 18 \mu\text{F}$$

$$-15 \text{ V} + 2 \text{ V} = -13 \text{ V}$$



$$12 + 20 = 32 \mu\text{F}$$

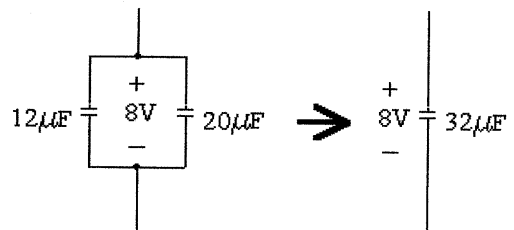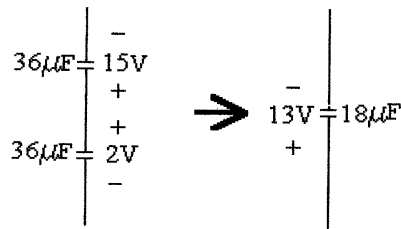

$$18 + 14 = 32 \mu\text{F}$$

$$\frac{1}{32} + \frac{1}{32} = \frac{2}{32} \quad \therefore C_{\text{eq}} = 16 \mu\text{F}$$
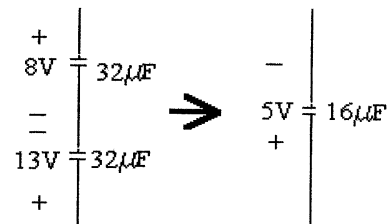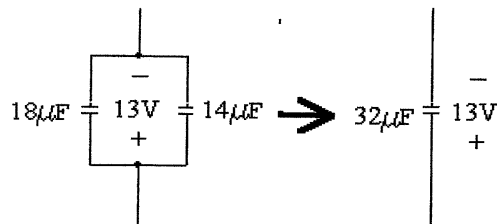
$$8 \text{ V} - 13 \text{ V} = -5 \text{ V}$$






P 6.26 $\frac{1}{C_1} = \frac{1}{8} + \frac{1}{32} = \frac{5}{32}; \quad C_1 = 6.4 \text{ nF}$

$$C_2 = 5.6 + 6.4 = 12 \text{ nF}$$

$$\frac{1}{C_3} = \frac{1}{18} + \frac{1}{12} = \frac{10}{72}; \quad C_3 = 7.2 \text{ nF}$$


$$C_4 = 12.8 + 7.2 = 20 \text{ nF}$$
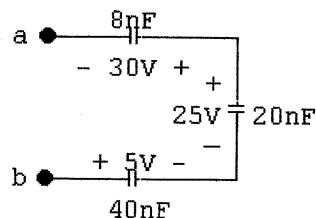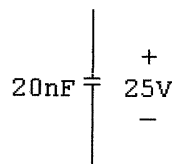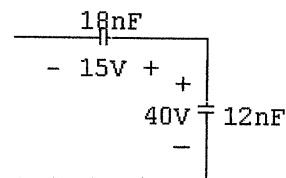
$$\frac{1}{C_5} = \frac{1}{8} + \frac{1}{20} + \frac{1}{40} = \frac{1}{5}; \quad C_5 = 5 \text{ nF}$$



Equivalent capacitance is 5 nF with an initial voltage drop of -10 V.

P 6.27 [a]

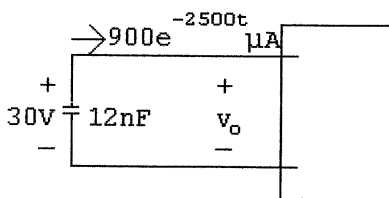

$$v_o = -\frac{10^9}{12} \int_0^t 900 \times 10^{-6} e^{-2500x} dx + 30$$

$$= -75,000 \frac{e^{-2500x}}{-2500} \Big|_0^t + 30$$

$$= 30e^{-2500t} \text{ V}, \quad t \geq 0$$

[b] $v_1 = -\frac{10^9}{20} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t + 45$

$$= 18e^{-2500t} + 27 \text{ V}, \quad t \geq 0$$

[c] $v_2 = -\frac{10^9}{30} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t - 15$

$$= 12e^{-2500t} - 27 \text{ V}, \quad t \geq 0$$

$$[d] \quad p = vi = (30e^{-2500t})(900 \times 10^{-6})e^{-2500t}$$

$$= 27 \times 10^{-3} e^{-5000t}$$

$$w = \int_0^{\infty} 27 \times 10^{-3} e^{-5000t} dt$$

$$= 27 \times 10^{-3} \left. \frac{e^{-5000t}}{-5000} \right|_0^{\infty}$$

$$= -5.4 \times 10^{-6}(0 - 1) = 5.4 \mu\text{J}$$

$$[e] \quad w = \frac{1}{2}(20 \times 10^{-9})(45)^2 + \frac{1}{2}(30 \times 10^{-9})(15)^2$$

$$= 20.25 \times 10^{-6} + 3.375 \times 10^{-6}$$

$$= 23.625 \mu\text{J}$$

$$[f] \quad w_{\text{trapped}} = w_{\text{initial}} - w_{\text{delivered}} = 23.625 - 5.4 = 18.225 \mu\text{J}$$

$$[g] \quad w_{\text{trapped}} = \frac{1}{2}(20 \times 10^{-9})(27)^2 + \frac{1}{2}(30 \times 10^{-9})(27)^2$$

$$= (10 + 15)(27)^2 \times 10^{-9}$$

$$= 18.225 \mu\text{J}$$

$$\text{CHECK: } 18.225 + 5.4 = 23.625 \mu\text{J}$$


$$\text{P 6.28} \quad C_1 = 1 + 1.5 = 2.5 \text{ nF}$$

$$\frac{1}{C_2} = \frac{1}{2.5} + \frac{1}{12.5} + \frac{1}{50} = \frac{1}{2}$$

$$\therefore C_2 = 2 \text{ nF}$$

$$v_d(0) + v_a(0) - v_c(0) = 40 + 15 + 45 = 100 \text{ V}$$

[a]

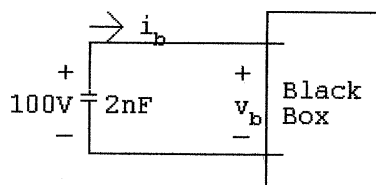

$$v_b = -\frac{10^9}{2} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 100$$

$$= -25,000 \left. \frac{e^{-250x}}{-250} \right|_0^t + 100$$

$$= 100(e^{-250t} - 1) + 100$$

$$= 100e^{-250t} \text{ V}$$

$$\begin{aligned}
[\text{b}] \quad v_a &= -\frac{10^9}{12.5} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 15 \\
&= -4000 \frac{e^{-250x}}{-250} \Big|_0^t + 15 \\
&= 16(e^{-250t} - 1) + 15 \\
&= 16e^{-250t} - 1 \text{ V}
\end{aligned}$$

$$\begin{aligned}
[\text{c}] \quad v_c &= \frac{10^9}{50} \int_0^t 50 \times 10^{-6} e^{-250x} dx - 45 \\
&= 1000 \frac{e^{-250x}}{-250} \Big|_0^t - 45 \\
&= -4(e^{-250t} - 1) - 45 \\
&= -4e^{-250t} - 41 \text{ V}
\end{aligned}$$

$$\begin{aligned}
[\text{d}] \quad v_d &= -\frac{10^9}{2.5} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 40 \\
&= -20,000 \frac{e^{-250x}}{-250} \Big|_0^t + 40 \\
&= 80(e^{-250t} - 1) + 40 \\
&= 80e^{-250t} - 40 \text{ V}
\end{aligned}$$

$$\begin{aligned}
\text{CHECK: } v_b &= v_d + v_a - v_c \\
&= 80e^{-250t} - 40 + 16e^{-250t} - 1 + 4e^{-250t} + 41 \\
&= 100e^{-250t} \text{ V (checks)}
\end{aligned}$$

$$\begin{aligned}
[\text{e}] \quad i_1 &= -10^{-9} \frac{d}{dt} [80e^{-250t} - 40] \\
&= -10^{-9} (-20,000e^{-250t}) \\
&= 20e^{-250t} \mu\text{A}
\end{aligned}$$

$$\begin{aligned}
[\text{f}] \quad i_2 &= -1.5 \times 10^{-9} \frac{d}{dt} [80e^{-250t} - 40] \\
&= -1.5 \times 10^{-9} (-20,000e^{-250t}) \\
&= 30e^{-250t} \mu\text{A}
\end{aligned}$$

$$\text{CHECK: } i_1 + i_2 = 50e^{-250t} \mu\text{A} = i_b$$

$$\begin{aligned}\text{P 6.29 [a]} \quad w(0) &= \left[\frac{1}{2}(2.5)(40)^2 + \frac{1}{2}(12.5)(15)^2 + \frac{1}{2}(50)(45)^2 \right] \times 10^{-9} \\ &= 54,031.25 \text{ nJ}\end{aligned}$$

$$\text{[b]} \quad v_a(\infty) = -1 \text{ V}$$

$$v_c(\infty) = -41 \text{ V}$$

$$v_d(\infty) = -40 \text{ V}$$

$$\begin{aligned}w(\infty) &= \left[\frac{1}{2}(2.5)(40)^2 + \frac{1}{2}(12.5)(1)^2 + \frac{1}{2}(50)(41)^2 \right] \times 10^{-9} \\ &= 44,031.25 \text{ nJ}\end{aligned}$$

$$\text{[c]} \quad w = \int_0^\infty (100e^{-250t})(50e^{-250t}) \times 10^{-6} dt = 10,000 \text{ nJ}$$

$$\text{CHECK: } 54,031.25 - 44,031.25 = 10,000$$

$$\text{[d]} \quad \% \text{ delivered} = \frac{10,000}{54,031.25} \times 100 = 18.51\%$$

$$\text{[e]} \quad w = 5 \times 10^{-3} \int_0^t e^{-500x} dx$$

$$= 10^4(1 - e^{-500t}) \text{ nJ}$$

$$\therefore 10^4(1 - e^{-500t}) = 5000; \quad e^{-500t} = 0.5$$

$$\text{Thus, } t = \frac{\ln 2}{500} = 1.39 \text{ ms.}$$

P 6.30 From Figure 6.17(a) we have

$$v = \frac{1}{C_1} \int_0^t i + v_1(0) + \frac{1}{C_2} \int_0^t i dx + v_2(0) + \dots$$

$$v = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots \right] \int_0^t i dx + v_1(0) + v_2(0) + \dots$$

$$\text{Therefore } \frac{1}{C_{\text{eq}}} = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots \right], \quad v_{\text{eq}}(0) = v_1(0) + v_2(0) + \dots$$

P 6.31 From Fig. 6.18(a)

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots = [C_1 + C_2 + \dots] \frac{dv}{dt}$$

Therefore $C_{\text{eq}} = C_1 + C_2 + \dots$. Because the capacitors are in parallel, the initial voltage on every capacitor must be the same. This initial voltage would appear on C_{eq} .

P 6.32

$$\begin{aligned}
 v_2(t) &= 20 \times 10^{-3} \frac{di_o}{dt} \\
 &= (20 \times 10^{-3})(50 \times 10^{-3}) \{e^{-8000t}[-6000 \sin 6000t + 12,000 \cos 6000t] \\
 &\quad + (-8000e^{-8000t})[\cos 6000t + 2 \sin 6000t]\} \\
 &= e^{-8000t} \{4 \cos 6000t - 22 \sin 6000t\} \text{ V}
 \end{aligned}$$

$$\therefore v_2(0) = 4 \text{ V}$$

$$i_o(0) = 50 \text{ mA}$$

$$v_R(0) = 320(50 \times 10^{-3}) = 16 \text{ V}$$

$$v_1(0) = 16 + 4 = 20 \text{ V}$$

$$\text{P 6.33} \quad v_c = \frac{-10^6}{20} \int_0^t e^{-80x} \sin 60x \, dx - 300$$

$$= 5e^{-80t} [80 \sin 60t + 60 \cos 60t] + 300 - 300$$

$$= 400e^{-80t} \sin 60t + 300e^{-80t} \cos 60t \text{ V}$$

$$v_L = 5 \frac{di_o}{dt}$$

$$= 5[-80e^{-80t} \sin 60t + 60e^{-80t} \cos 60t]$$

$$= -400e^{-80t} \sin 60t + 300e^{-80t} \cos 60t \text{ V}$$

$$v_o = v_c - v_L$$

$$= (300e^{-80t} \cos 60t - 300e^{-80t} \cos 60t + 400e^{-80t} \sin 60t + 400e^{-80t} \sin 60t)$$

$$= 800e^{-80t} \sin 60t \text{ V}$$

$$\text{P 6.34} \quad [\text{a}] \quad 5 \frac{di_g}{dt} + 40 \frac{di_2}{dt} + 90i_2 = 0$$

$$40 \frac{di_2}{dt} + 90i_2 = -5 \frac{di_g}{dt}$$

$$[\text{b}] \quad i_2 = e^{-t} - 5e^{-2.25t} \text{ A}$$

$$\frac{di_2}{dt} = -e^{-t} + 11.25e^{-2.25t} \text{ A/s}$$

$$i_g = 10e^{-t} - 10 \text{ A}$$

$$\begin{aligned}
 \text{[c]} \quad p_{\text{dev}} &= v_g i_g \\
 &= 960 + 92,480e^{-4t} - 94,400e^{-5t} - 92,480e^{-9t} + \\
 &\quad 93,440e^{-10t} \text{ W}
 \end{aligned}$$

$$\text{[d]} \quad p_{\text{dev}}(\infty) = 960 \text{ W}$$

$$\text{[e]} \quad i_1(\infty) = 4 \text{ A}; \quad i_2(\infty) = 1 \text{ A}; \quad i_g(\infty) = 16 \text{ A};$$

$$p_{5\Omega} = (16 - 4)^2(5) = 720 \text{ W}$$

$$p_{20\Omega} = 3^2(20) = 180 \text{ W}$$

$$p_{60\Omega} = 1^2(60) = 60 \text{ W}$$

$$\sum p_{\text{abs}} = 720 + 180 + 60 = 960 \text{ W}$$

$$\therefore \sum p_{\text{dev}} = \sum p_{\text{abs}} = 960 \text{ W}$$

P 6.37 [a] Rearrange by organizing the equations by di_1/dt , i_1 , di_2/dt , i_2 and transfer the i_g terms to the right hand side of the equations. We get

$$4 \frac{di_1}{dt} + 25i_1 - 8 \frac{di_2}{dt} - 20i_2 = 5i_g - 8 \frac{di_g}{dt}$$

$$-8 \frac{di_1}{dt} - 20i_1 + 16 \frac{di_2}{dt} + 80i_2 = 16 \frac{di_g}{dt}$$

[b] From the given solutions we have

$$\frac{di_1}{dt} = -320e^{-5t} + 272e^{-4t}$$

$$\frac{di_2}{dt} = 260e^{-5t} - 204e^{-4t}$$

Thus,

$$4 \frac{di_1}{dt} = -1280e^{-5t} + 1088e^{-4t}$$

$$25i_1 = 100 + 1600e^{-5t} - 1700e^{-4t}$$

$$8 \frac{di_2}{dt} = 2080e^{-5t} - 1632e^{-4t}$$

$$20i_2 = 20 - 1040e^{-5t} + 1020e^{-4t}$$

$$5i_g = 80 - 80e^{-5t}$$

$$8 \frac{di_g}{dt} = 640e^{-5t}$$

Thus,

$$-1280e^{-5t} + 1088e^{-4t} + 100 + 1600e^{-5t} - 1700e^{-4t} - 2080e^{-5t} \\ + 1632e^{-4t} - 20 + 1040e^{-5t} - 1020e^{-4t} \stackrel{?}{=} 80 - 80e^{-5t} - 640e^{-5t}$$

$$80 + (1088 - 1700 + 1632 - 1020)e^{-4t}$$

$$+ (1600 - 1280 - 2080 + 1040)e^{-5t} \stackrel{?}{=} 80 - 720e^{-5t}$$

$$80 + (2720 - 2720)e^{-4t} + (2640 - 3360)e^{-5t} = 80 - 720e^{-5t} \quad (\text{OK})$$

$$8 \frac{di_1}{dt} = -2560e^{-5t} + 2176e^{-4t}$$

$$20i_1 = 80 + 1280e^{-5t} - 1360e^{-4t}$$

$$16 \frac{di_2}{dt} = 4160e^{-5t} - 3264e^{-4t}$$

$$80i_2 = 80 - 4160e^{-5t} + 4080e^{-4t}$$

$$16 \frac{di_g}{dt} = 1280e^{-5t}$$

$$2560e^{-5t} - 2176e^{-4t} - 80 - 1280e^{-5t} + 1360e^{-4t} + 4160e^{-5t} - 3264e^{-4t} \\ + 80 - 4160e^{-5t} + 4080e^{-4t} \stackrel{?}{=} 1280e^{-5t}$$

$$(-80 + 80) + (2560 - 1280 + 4160 - 4160)e^{-5t}$$

$$+ (1360 - 2176 - 3264 + 4080)e^{-4t} \stackrel{?}{=} 1280e^{-5t}$$

$$0 + 1280e^{-5t} + 0e^{-4t} = 1280e^{-5t} \quad (\text{OK})$$

- P 6.38 [a] Dot terminal 2; with current entering terminal 2, the flux is right-to-left coil 1-2. Assign the current into terminal 4; the flux is left-to-right in coil 3-4. The flux is in the same direction, due to the topology of the core, so dot terminal 4. Hence, 2 and 4 or 1 and 3.
- [b] Dot terminal 1; with current entering terminal 1 the flux is down in coil 1-2. Assign the current into terminal 4; the flux is right-to-left in coil 3-4. Therefore the flux is in the same direction, due to the topology of the core, so dot terminal 4. Hence, 1 and 4 or 2 and 3.
- [c] Dot terminal 1; with current entering terminal 1 the flux is up in coil 1-2. Assign the current into terminal 4; the flux is left-to-right in coil 3-4. Therefore the flux is in the same direction, due to the topology of the core, so dot terminal 4. Hence, 1 and 4 or 2 and 3.

- [d] Dot terminal 2; with current entering terminal 2, the flux is down in coil 1-2. Assign the current into terminal 4; the flux is down in coil 3-4. Therefore, the flux is in the same direction, so dot terminal 4. Hence, 2 and 4 or 1 and 3.

P 6.39 When the switch is closed, the induced voltage in the coil connected to the source is negative at the dotted terminal. Since the dc voltmeter kicks up-scale, the induced voltage in the coil connected to the voltmeter is positive at the lower terminal. Therefore, dot the upper terminal of the coil connected to the voltmeter.

P 6.40 [a] $v_{ab} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt} + M \frac{di}{dt} = (L_1 + L_2 + 2M) \frac{di}{dt}$

It follows that $L_{ab} = (L_1 + L_2 + 2M)$

[b] $v_{ab} = L_1 \frac{di}{dt} - M \frac{di}{dt} + L_2 \frac{di}{dt} - M \frac{di}{dt} = (L_1 + L_2 - 2M) \frac{di}{dt}$

Therefore $L_{ab} = (L_1 + L_2 - 2M)$

P 6.41 [a] $v_{ab} = L_1 \frac{d(i_1 - i_2)}{dt} + M \frac{di_2}{dt}$

$$0 = L_1 \frac{d(i_2 - i_1)}{dt} - M \frac{di_2}{dt} + M \frac{d(i_1 - i_2)}{dt} + L_2 \frac{di_2}{dt}$$

Collecting coefficients of $[di_1/dt]$ and $[di_2/dt]$, the two mesh-current equations become

$$v_{ab} = L_1 \frac{di_1}{dt} + (M - L_1) \frac{di_2}{dt}$$

and

$$0 = (M - L_1) \frac{di_1}{dt} + (L_1 + L_2 - 2M) \frac{di_2}{dt}$$

Solving for $[di_1/dt]$ gives

$$\frac{di_1}{dt} = \frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2} v_{ab}$$

from which we have

$$v_{ab} = \left(\frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \right) \left(\frac{di_1}{dt} \right)$$

$$\therefore L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

- [b] If the magnetic polarity of coil 2 is reversed, the sign of M reverses, therefore

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

$$\text{P 6.42 [a]} \quad L_2 = \left(\frac{M^2}{k^2 L_1} \right) = \frac{(0.1)^2}{(0.5)^2 (0.250)} = 160 \text{ mH}$$

$$\frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} = \sqrt{\frac{250}{160}} = 1.25$$

$$\text{[b]} \quad \mathcal{P}_1 = \frac{L_1}{N_1^2} = \frac{0.250}{(1000)^2} = 0.25 \times 10^{-6} \text{ Wb/A}$$

$$\mathcal{P}_2 = \frac{L_2}{N_2^2} = \frac{0.16}{(800)^2} = 0.25 \times 10^{-6} \text{ Wb/A}$$

$$\text{P 6.43} \quad \mathcal{P}_1 = \frac{L_1}{N_1^2} = \frac{400 \times 10^{-6}}{250^2} = 6.4 \text{ nWb/A}$$

$$\mathcal{P}_2 = \frac{L_2}{N_2^2} = \frac{900 \times 10^{-6}}{500^2} = 3.6 \text{ nWb/A}; \quad M = k\sqrt{L_1 L_2} = 450 \mu\text{H}$$

$$\mathcal{P}_{12} = \mathcal{P}_{21} = \frac{M}{N_1 N_2} = \frac{450 \times 10^{-6}}{(250)(500)} = 3.6 \text{ nWb/A}$$

$$\mathcal{P}_{11} = \mathcal{P}_1 - \mathcal{P}_{21} = 6.4 - 3.6 = 2.8 \text{ nWb/A}$$

$$\text{P 6.44 [a]} \quad k = \frac{M}{\sqrt{L_1 L_2}} = \frac{19.5}{\sqrt{676}} = 0.75$$

$$\text{[b]} \quad M_{\max} = \sqrt{676} = 26 \text{ mH}$$

$$\text{[c]} \quad \frac{L_1}{L_2} = \frac{N_1^2 \mathcal{P}_1}{N_2^2 \mathcal{P}_2} = \left(\frac{N_1}{N_2} \right)^2$$

$$\therefore \left(\frac{N_1}{N_2} \right)^2 = \frac{52}{13} = 4$$

$$\frac{N_1}{N_2} = \sqrt{4} = 2$$

$$\text{P 6.45 [a]} \quad L_1 = N_1^2 \mathcal{P}_1; \quad \mathcal{P}_1 = \frac{288 \times 10^{-3}}{10^6} = 288 \text{ nWb/A}$$

$$\frac{d\phi_{11}}{d\phi_{21}} = \frac{\mathcal{P}_{11}}{\mathcal{P}_{21}} = 0.5; \quad \mathcal{P}_{21} = 2\mathcal{P}_{11}$$

$$\therefore 288 \times 10^{-9} = \mathcal{P}_{11} + \mathcal{P}_{21} = 3\mathcal{P}_{11}$$

$$\mathcal{P}_{11} = 96 \text{ nWb/A}; \quad \mathcal{P}_{21} = 192 \text{ nWb/A}$$

$$M = k\sqrt{L_1 L_2} = (1/3)\sqrt{(0.288)(0.162)} = 72 \text{ mH}$$

$$N_2 = \frac{M}{N_1 \mathcal{P}_{21}} = \frac{72 \times 10^{-3}}{(1000)(192 \times 10^{-9})} = 375 \text{ turns}$$

$$[b] \mathcal{P}_2 = \frac{L_2}{N_2^2} = \frac{162 \times 10^{-3}}{(375)^2} = 1152 \text{ nWb/A}$$

$$[c] \mathcal{P}_{11} = 96 \text{ nWb/A [see part (a)]}$$

$$[d] \frac{\phi_{22}}{\phi_{12}} = \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}} = \frac{\mathcal{P}_2 - \mathcal{P}_{12}}{\mathcal{P}_{12}} = \frac{\mathcal{P}_2}{\mathcal{P}_{12}} - 1$$

$$\mathcal{P}_{21} = \mathcal{P}_{12} = 192 \text{ nWb/A}; \quad \mathcal{P}_2 = 1152 \text{ nWb/A}$$

$$\frac{\phi_{22}}{\phi_{12}} = \frac{1152}{192} - 1 = 5$$

$$P 6.46 \quad [a] \frac{1}{k^2} = \left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right) = \left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{21}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)$$

Therefore

$$k^2 = \frac{\mathcal{P}_{12}\mathcal{P}_{21}}{(\mathcal{P}_{21} + \mathcal{P}_{11})(\mathcal{P}_{12} + \mathcal{P}_{22})}$$

Now note that

$$\phi_1 = \phi_{11} + \phi_{21} = \mathcal{P}_{11}N_1i_1 + \mathcal{P}_{21}N_1i_1 = N_1i_1(\mathcal{P}_{11} + \mathcal{P}_{21})$$

and similarly

$$\phi_2 = N_2i_2(\mathcal{P}_{22} + \mathcal{P}_{12})$$

It follows that

$$(\mathcal{P}_{11} + \mathcal{P}_{21}) = \frac{\phi_1}{N_1i_1}$$

and

$$(\mathcal{P}_{22} + \mathcal{P}_{12}) = \left(\frac{\phi_2}{N_2i_2}\right)$$

Therefore

$$k^2 = \frac{(\phi_{12}/N_2i_2)(\phi_{21}/N_1i_1)}{(\phi_1/N_1i_1)(\phi_2/N_2i_2)} = \frac{\phi_{12}\phi_{21}}{\phi_1\phi_2}$$

or

$$k = \sqrt{\left(\frac{\phi_{21}}{\phi_1}\right) \left(\frac{\phi_{12}}{\phi_2}\right)}$$

[b] The fractions (ϕ_{21}/ϕ_1) and (ϕ_{12}/ϕ_2) are by definition less than 1.0, therefore $k < 1$.

$$P 6.47 \quad [a] W = (0.5)L_1i_1^2 + (0.5)L_2i_2^2 + Mi_1i_2$$

$$M = 0.8\sqrt{(0.025)(0.1)} = 40 \text{ mH}$$

$$W = (0.5)(0.025)(10)^2 + (0.5)(0.1)(15)^2 + (0.04)(10)(15) = 18.5 \text{ J}$$

[b] $W = (0.5)(0.025)(-10)^2 + (0.5)(0.1)(-15)^2 + (0.04)(-10)(-15) = 18.5 \text{ J}$

[c] $W = (0.5)(0.025)(-10)^2 + (0.5)(0.1)(15)^2 + (0.04)(-10)(15) = 6.5 \text{ J}$

[d] $W = (0.5)(0.025)(10)^2 + (0.5)(0.1)(-15)^2 + (0.04)(10)(-15) = 6.5 \text{ J}$

P 6.48 [a] $M = 1.0\sqrt{(0.025)(0.1)} = 50 \text{ mH}, \quad i_1 = 10 \text{ A}$


Therefore $50i_2^2 + 500i_2 + 1250 = 0, \quad i_2^2 + 10i_2 + 25 = 0$

Therefore $i_2 = -\left(\frac{10}{2}\right) \pm \sqrt{\left(\frac{10}{2}\right)^2 - 25} = -5 \pm \sqrt{0}$

Therefore $i_2 = -5 \text{ A}$

[b] No, setting W equal to a negative value will make the quantity under the square root sign negative.

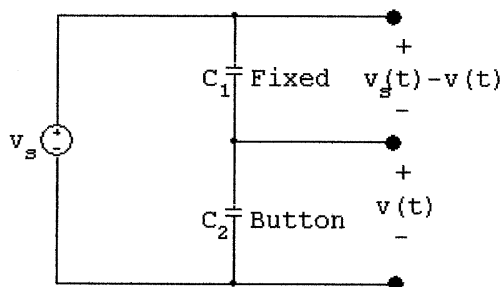P 6.49 When the button is not pressed we have



$$C_2 \frac{dv}{dt} = C_1 \frac{d}{dt}(v_s - v)$$

or

$$(C_1 + C_2) \frac{dv}{dt} = C_1 \frac{dv_s}{dt}$$

$$\frac{dv}{dt} = \frac{C_1}{(C_1 + C_2)} \frac{dv_s}{dt}$$


Assuming $C_1 = C_2 = C$

$$\frac{dv}{dt} = 0.5 \frac{dv_s}{dt}$$

or

$$v = 0.5v_s(t) + v(0)$$

When the button is pressed we have

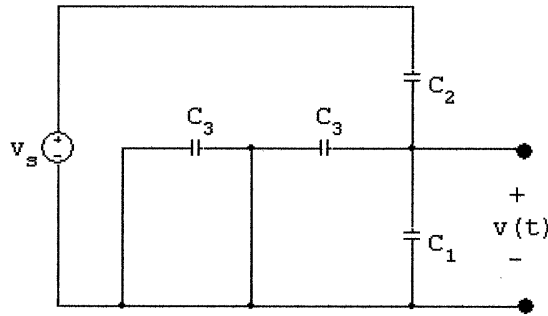

$$C_1 \frac{dv}{dt} + C_3 \frac{dv}{dt} + C_2 \frac{d(v - v_s)}{dt} = 0$$

$$\therefore \frac{dv}{dt} = \frac{C_2}{C_1 + C_2 + C_3} \frac{dv_s}{dt}$$

Assuming $C_1 = C_2 = C_3 = C$

$$\frac{dv}{dt} = \frac{1}{3} \frac{dv_s}{dt}$$

$$v = \frac{1}{3} v_s(t) + v(0)$$

Therefore interchanging the fixed capacitor and the button has no effect on the change in $v(t)$.

P 6.50 With no finger touching and equal 10 pF capacitors

$$v(t) = \frac{10}{20} (v_s(t)) + 0 = 0.5 v_s(t)$$

With a finger touching

Let C_e = equivalent capacitance of person touching lamp


$$C_e = \frac{(10)(100)}{110} = 9.091 \text{ pF}$$

Then $C + C_e = 10 + 9.091 = 19.091 \text{ pF}$

$$\therefore v(t) = \frac{10}{29.091} v_s = 0.344 v_s$$

$$\therefore \Delta v(t) = (0.5 - 0.344) v_s = 0.156 v_s$$

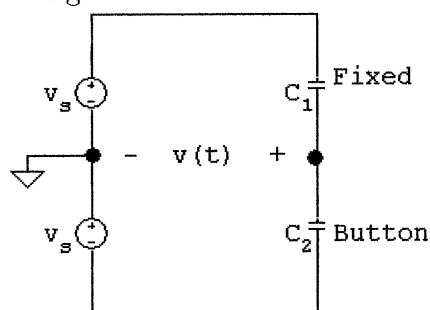
P 6.51 With no finger on the button the circuit is



$$C_1 \frac{d}{dt}(v - v_s) + C_2 \frac{d}{dt}(v + v_s) = 0$$

$$\text{when } C_1 = C_2 = C \quad (2C) \frac{dv}{dt} = 0$$

With a finger on the button

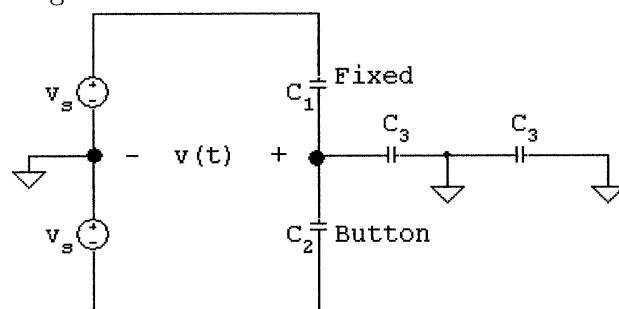

$$C_1 \frac{d(v - v_s)}{dt} + C_2 \frac{d(v + v_s)}{dt} + C_3 \frac{dv}{dt} = 0$$

$$(C_1 + C_2 + C_3) \frac{dv}{dt} + C_2 \frac{dv_s}{dt} - C_1 \frac{dv_s}{dt} = 0$$

$$\text{when } C_1 = C_2 = C_3 = C \quad (3C) \frac{dv}{dt} = 0$$

\therefore there is no change in the output voltage of this circuit.